



SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



DIGITAL PRINCIPLES AND SYSTEM DESIGN



Guess Today's Topic????



Master-Slave Flipflops

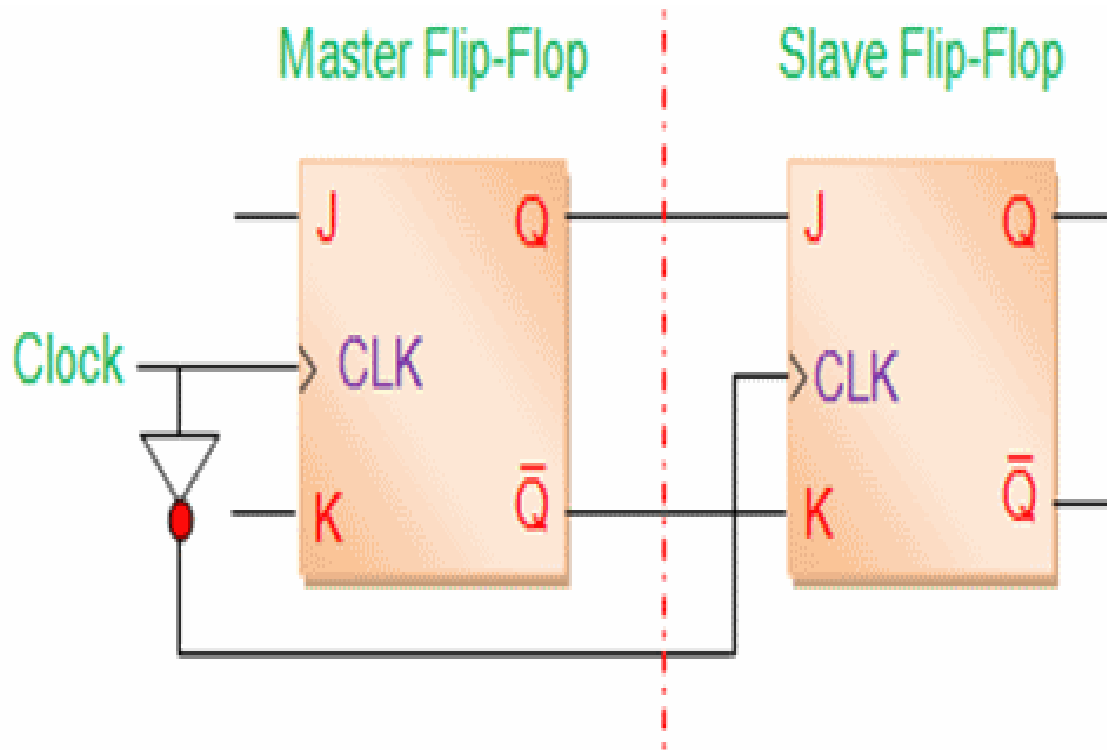


Fig 1 : Logic Diagram Master Slave Flip Flop




Master slave Flip Flop

- A master-slave flip-flop is constructed from two flip-flops.
- One circuit serves as a master and the other as a slave, and the overall circuit is referred to as a master-slave flip-flop.

SR Master-Slave Flip-Flop

 
- Read input at first half of clock cycle
- Output only changed at second half of clock cycle




SR Master-Slave Flip-Flop

- An RS Master-Slave Flip-Flop is pulse-triggered.
- This means:
 - Data are entered on the rising edge of the clock pulse
 - But, output is only changed on the falling edge of the clock pulse

SR Flip-Flop (master-slave)

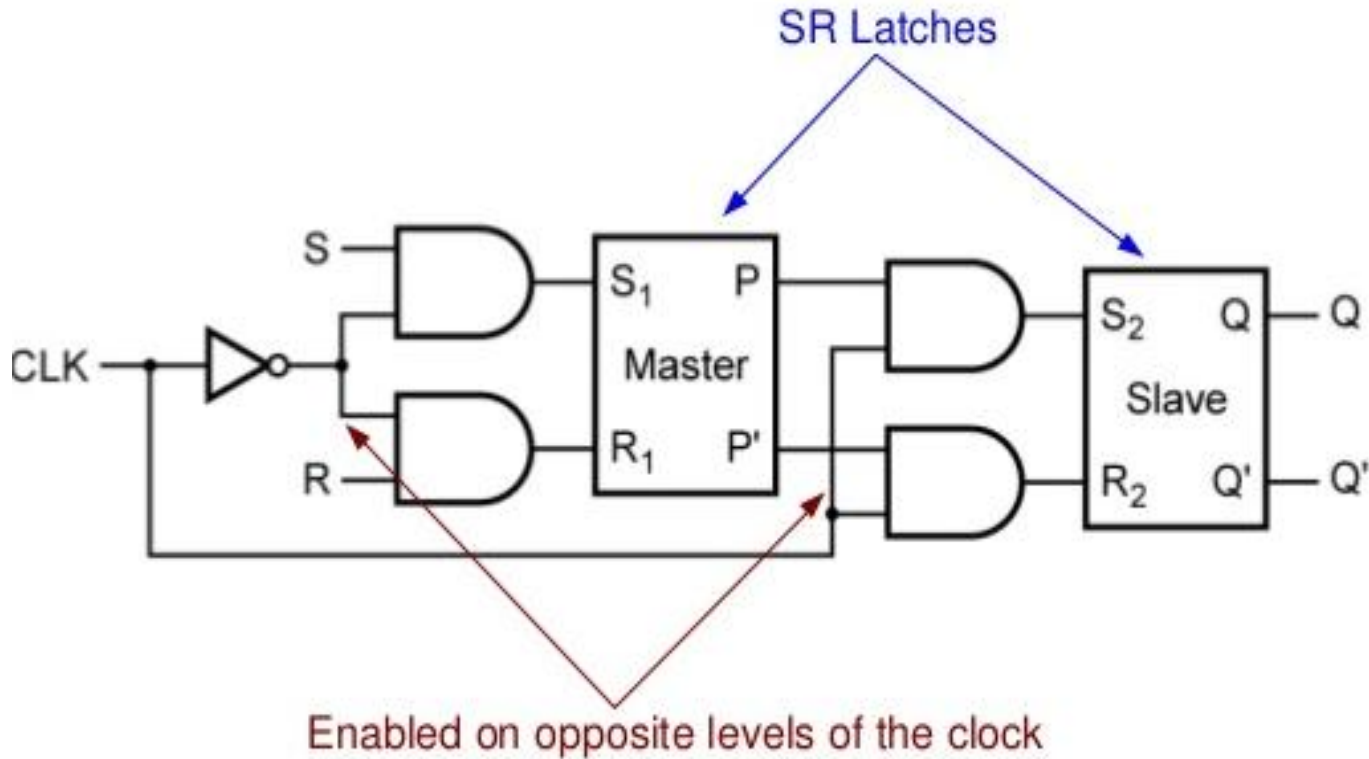

Master-Slave JK Flip-Flop

 

(a)


J	K	Next State of Q
0	0	Q
0	1	0
1	0	1
1	1	\bar{Q}

Master-Slave J-K Flip-Flop



A master-slave flip-flop contains two flip-flops/latches:

Master S-C latch (S-C Flip-Flop) - receives data while the input trigger clock is HIGH.

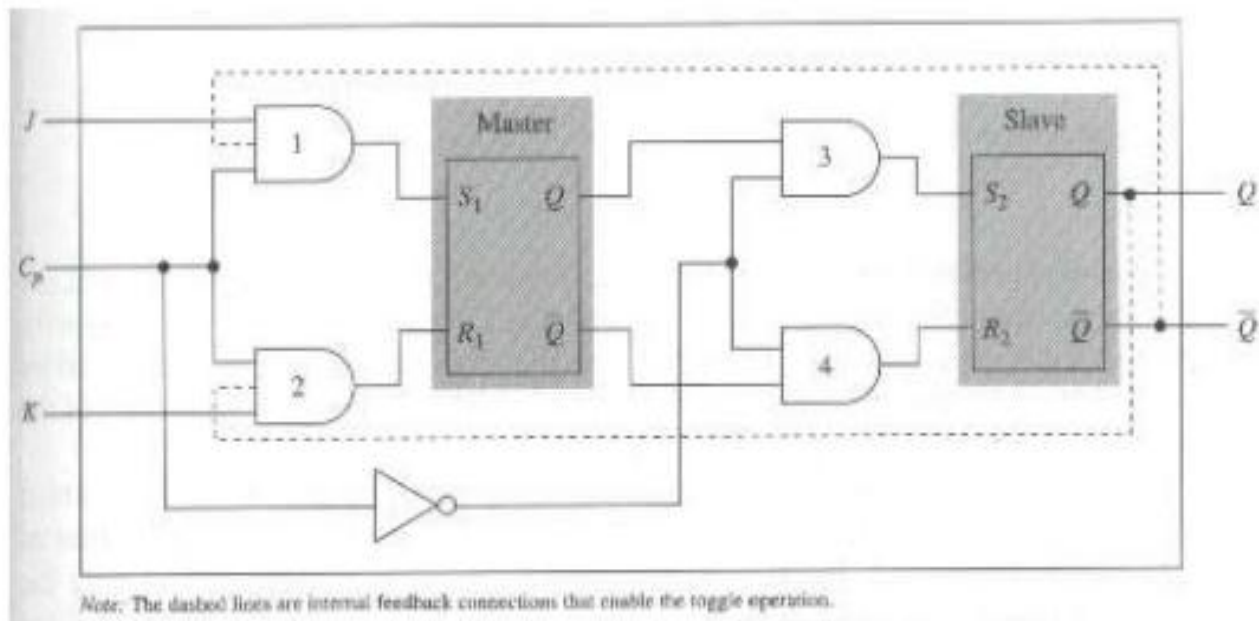Slave S-C latch (S-C Flip-Flop) - receives data from the master and output it when the clock goes LOW.



Master-Slave D Flip-Flop

 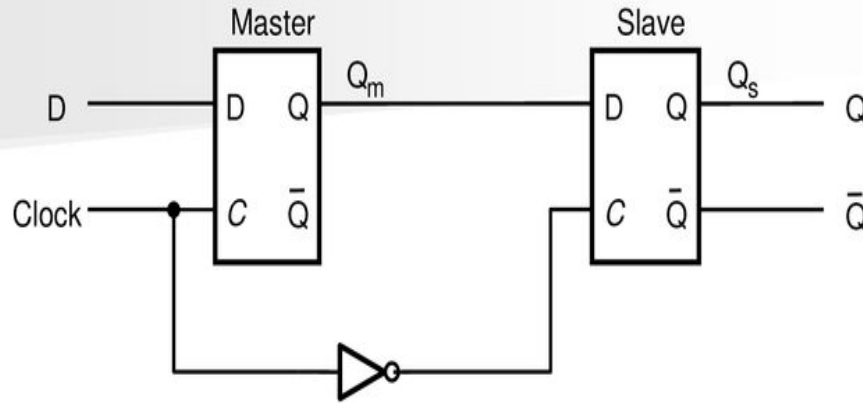

E.DIVYA , AP/ECE /Digital Circuits/Master-Slave FF



Assessment

**Draw the Logic diagram and
Circuit diagram for Master-Slave
D Flip Flop**





Thank
you

