



SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



Sequential Circuits

Flip-Flops



Flip-Flops


- Latches are “transparent” (= any change on the inputs is seen at the outputs immediately when $C=1$).
- This causes synchronization problems.

Solution: use latches to create flip-flops that can respond (update) only on specific times (instead of any time).

- Types: RS flip-flop and D flip-flop



 Master-Slave FF configuration using SR latches






Master-Slave FF configuration using SR latches (cont.)




S	R	CLK	Q	Q'	
0	0	1	Q_0	Q_0'	Store
0	1	1	0	1	Reset
1	0	1	1	0	Set
1	1	1	1	1	Disallowed
X	X	0	Q_0	Q_0'	Store

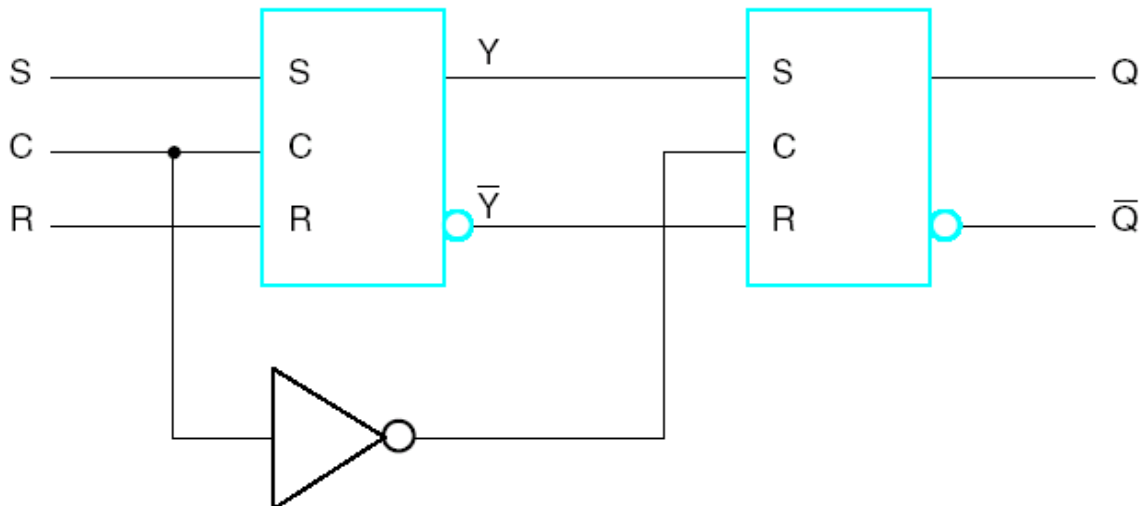- When $C=1$, master is enabled and stores *new* data, slave stores *old* data.
- When $C=0$, master's state passes to enabled slave, master not sensitive to new data (disabled).





D Flip-Flop

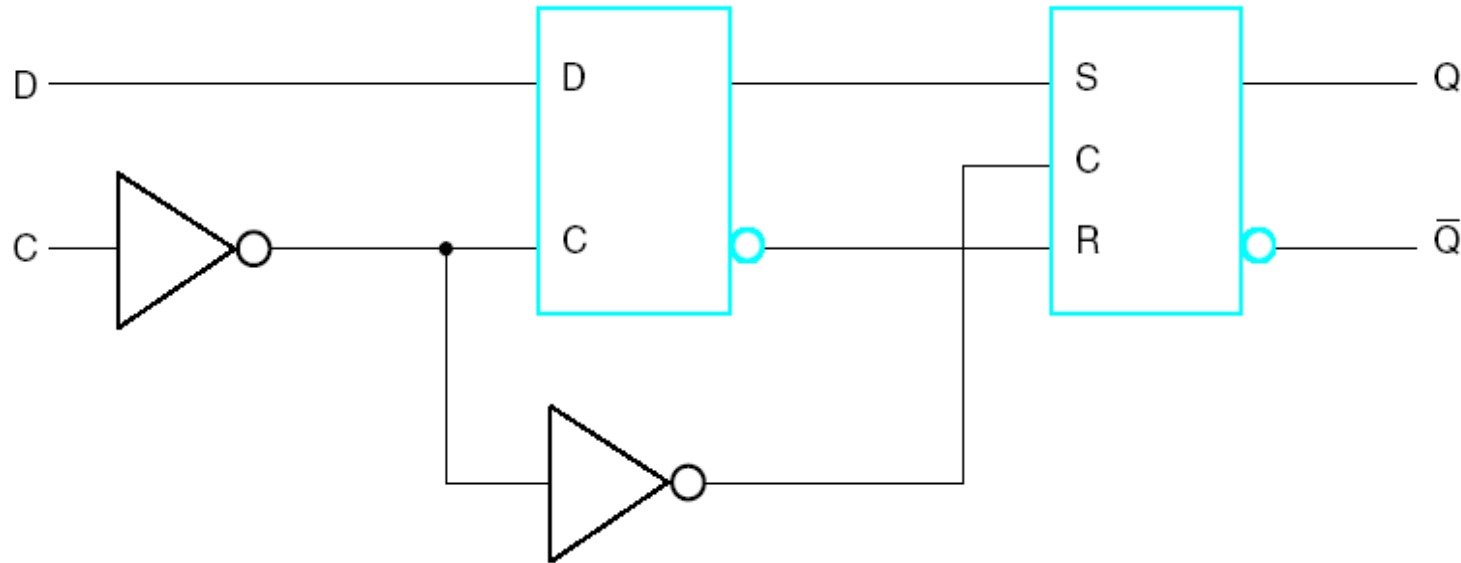



Characteristic Tables

- Defines the logical properties of a flip-flop (such as a truth table does for a logic gate).
- $Q(t)$ – present state at time t
- $Q(t+1)$ – next state at time $t+1$



Characteristic Tables (cont.)



SR Flip-Flop

S	R	Q(t+1)	Operation
0	0	Q(t)	No change/Hold
0	1	0	Reset
1	0	1	Set
1	1	?	Undefined/Invalid





Characteristic Tables (cont.)

D Flip-Flop		
D	Q(t+1)	Operation
0	0	Set
1	1	Reset

Characteristic Equation: $Q(t+1) = D(t)$



D Flip-Flop Timing Parameters

  

Setup time



Sequential Circuit Analysis

- **Analysis:** Consists of obtaining a suitable description that demonstrates the time sequence of inputs, outputs, and states.
- Logic diagram: Boolean gates, flip-flops (of any kind), and appropriate interconnections.
- The logic diagram is derived from any of the following:
 - Boolean Equations (FF-Inputs, Outputs)
 - State Table
 - State Diagram




Example




- Input: $x(t)$
- Output: $y(t)$
- State: $(A(t), B(t))$
- What is the Output

What is the Next State

 

 Example (continued)

- Boolean equations for the functions:
 - $A(t+1) = A(t)x(t) + B(t)x(t)$
 - $B(t+1) = A'(t)x(t)$
 - $y(t) = x'(t)(B(t) + A(t))$





State Table Characteristics

- *State table* – a multiple variable table with the following four sections:
 - *Present State* – the values of the state variables for each allowed state.
 - *Input* – the input combinations allowed.
 - *Next-state* – the value of the state at time (t+1) based on the present state and the input.
 - *Output* – the value of the output as a function of the present state and (sometimes) the input.

From the viewpoint of a truth table:

- the inputs are Input, Present State
- and the outputs are Output, Next State



Example: State Table



- The state table can be filled in using the next state and output equations:
 - $A(t+1) = A(t)x(t) + B(t)x(t)$
 - $B(t+1) = \bar{A}(t)x(t)$;
 - $y(t) = \bar{x}(t)(B(t) + A(t))$

Present State		Input	Next State		Output
A(t)	B(t)	x(t)	A(t+1)	B(t+1)	y(t)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0




State Diagrams

- The sequential circuit function can be represented in graphical form as a state diagram with the following components:
 - A circle with the state name in it for each state
 - A directed arc from the Present State to the Next State for each state transition
 - A label on each directed arc with the Input values which causes the state transition, and
 - A label:
 - On each circle with the output value produced, or
 - On each directed arc with the output value produced.

 Example: State Diagram

- Diagram gets confusing for large circuits
- For small circuits, usually easier to understand than the state table





THANK YOU

