



SNS COLLEGE OF ENGINEERING



(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING




DIGITAL CIRCUITS

Guess Today's Topic????

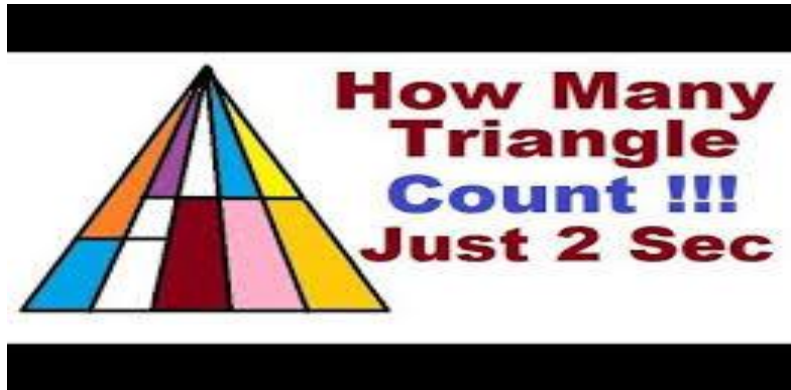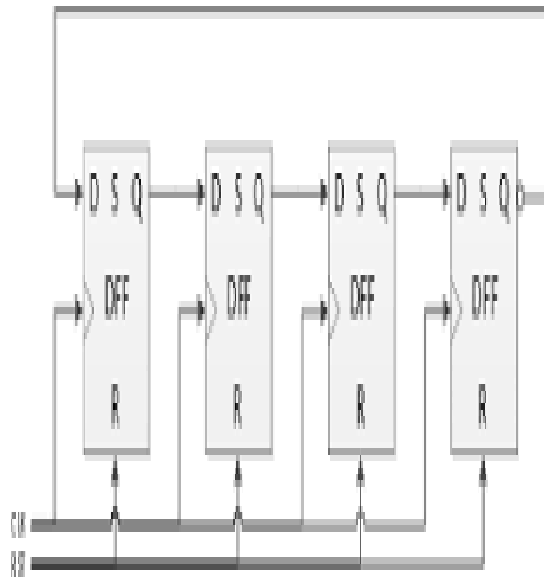


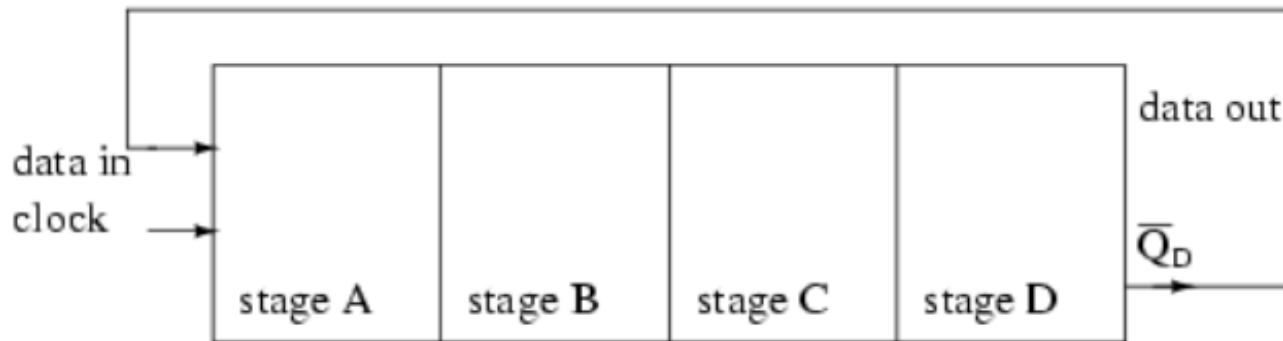If the output of a shift register is fed back to the input, a ring counter results.



Ring Counter; shift register output fed back to input

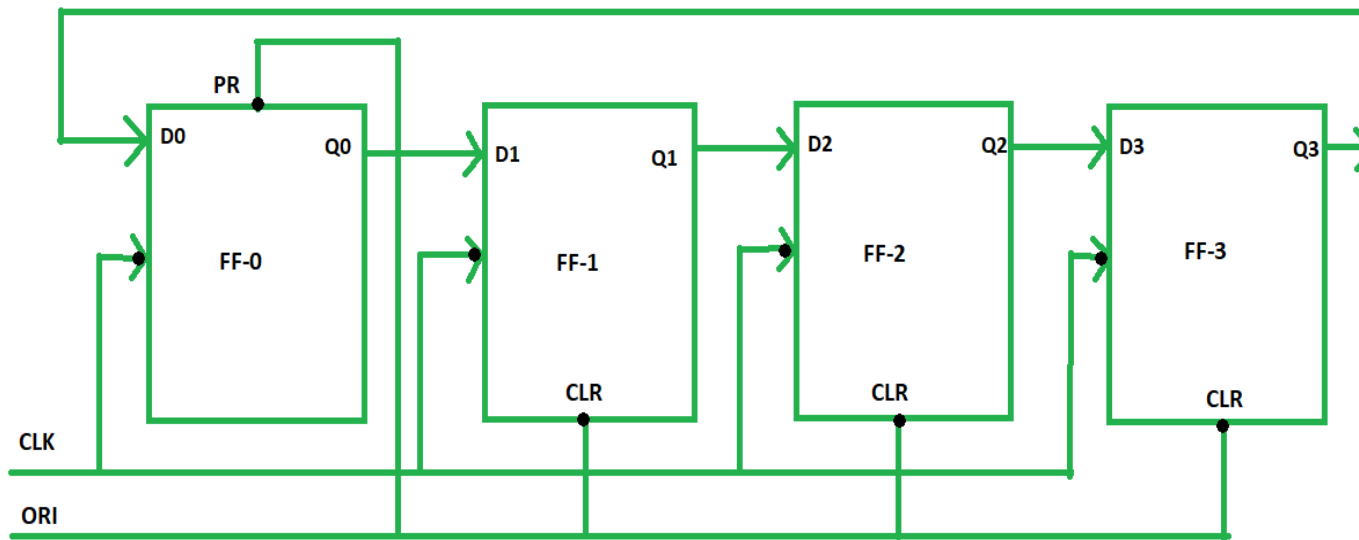- Ring counter is a typical application of Shift register
- No. of states in Ring counter = No. of flip-flop used




Ring Counter

Working

ORI	CLK	Q0	Q1	Q2	Q3
low	X	1	0	0	0
high	low	0	1	0	0
high	low	0	0	1	0
high	low	0	0	0	1
high	low	1	0	0	0

PRESETED 1





Working (Contd...)



- These two values are always fixed
 $PR = 0, Q = 1$
 $CLR = 0, Q = 0$

Also, here we use Overriding input (ORI) to each flip-flop. Preset (PR) and Clear (CLR) are used as ORI.

4 states are:

1 0 0 0

0 1 0 0


0 0 1 0

0 0 0 1




Types of Ring Counter

1. Straight Ring Counter

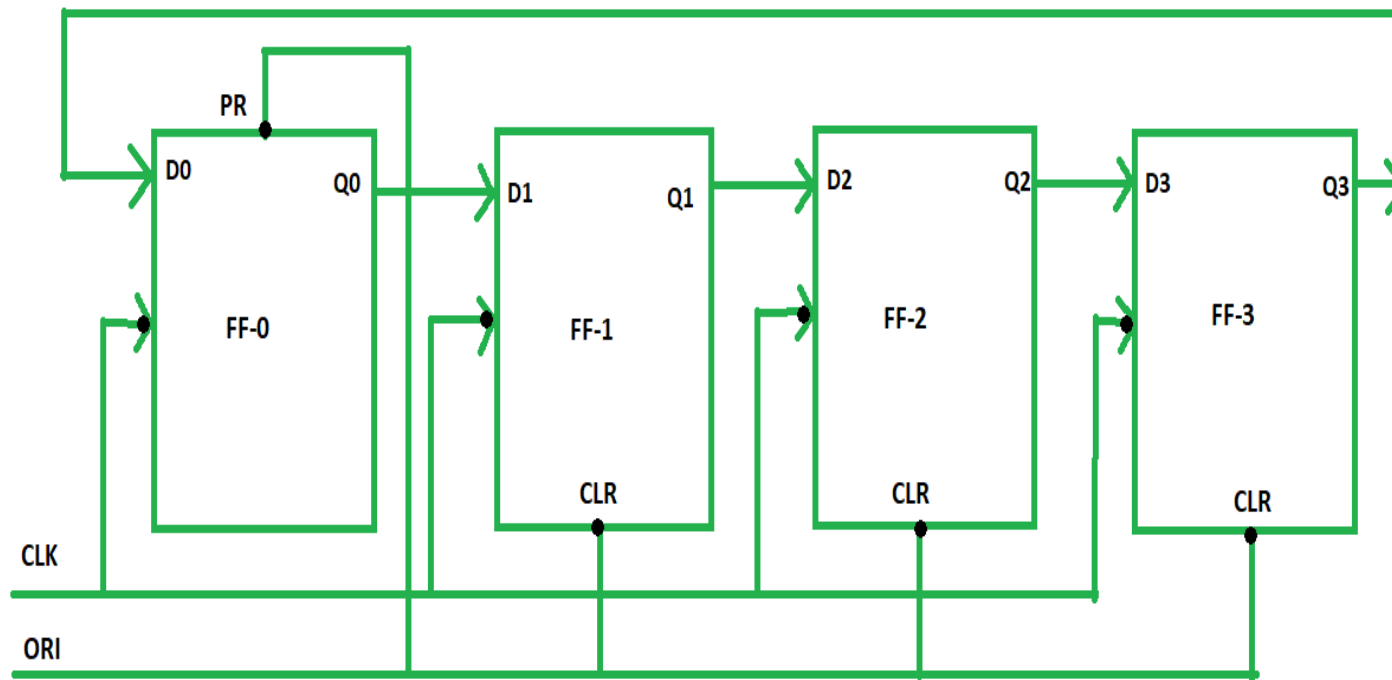

Straight Ring Counter

2. Twisted Ring Counter

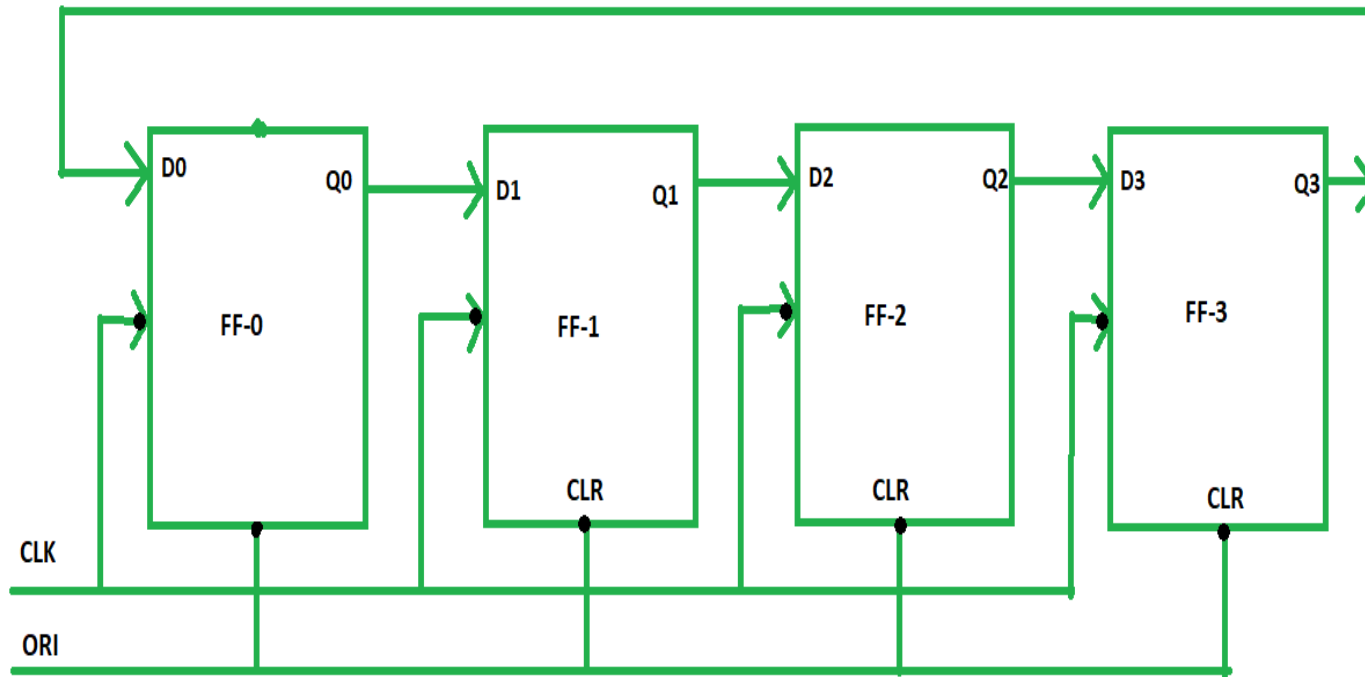

Twisted Ring Counter



Assessment

Design a 4-bit Ring Counter using four D flip-flops.





Thank
you

