



# **SNS COLLEGE OF ENGINEERING**

Kurumbapalayam (Po), Coimbatore – 641 107

**An Autonomous Institution**


Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

**DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING**

**COURSE NAME : 19EE201 CIRCUIT THEORY**

I YEAR /I SEMESTER EEE


Unit 1 – Basic Circuit Analysis

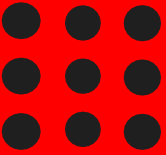




# Techniques of Circuit Analysis

## Mesh Analysis

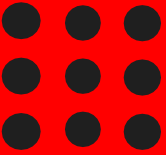



# Mesh Analysis

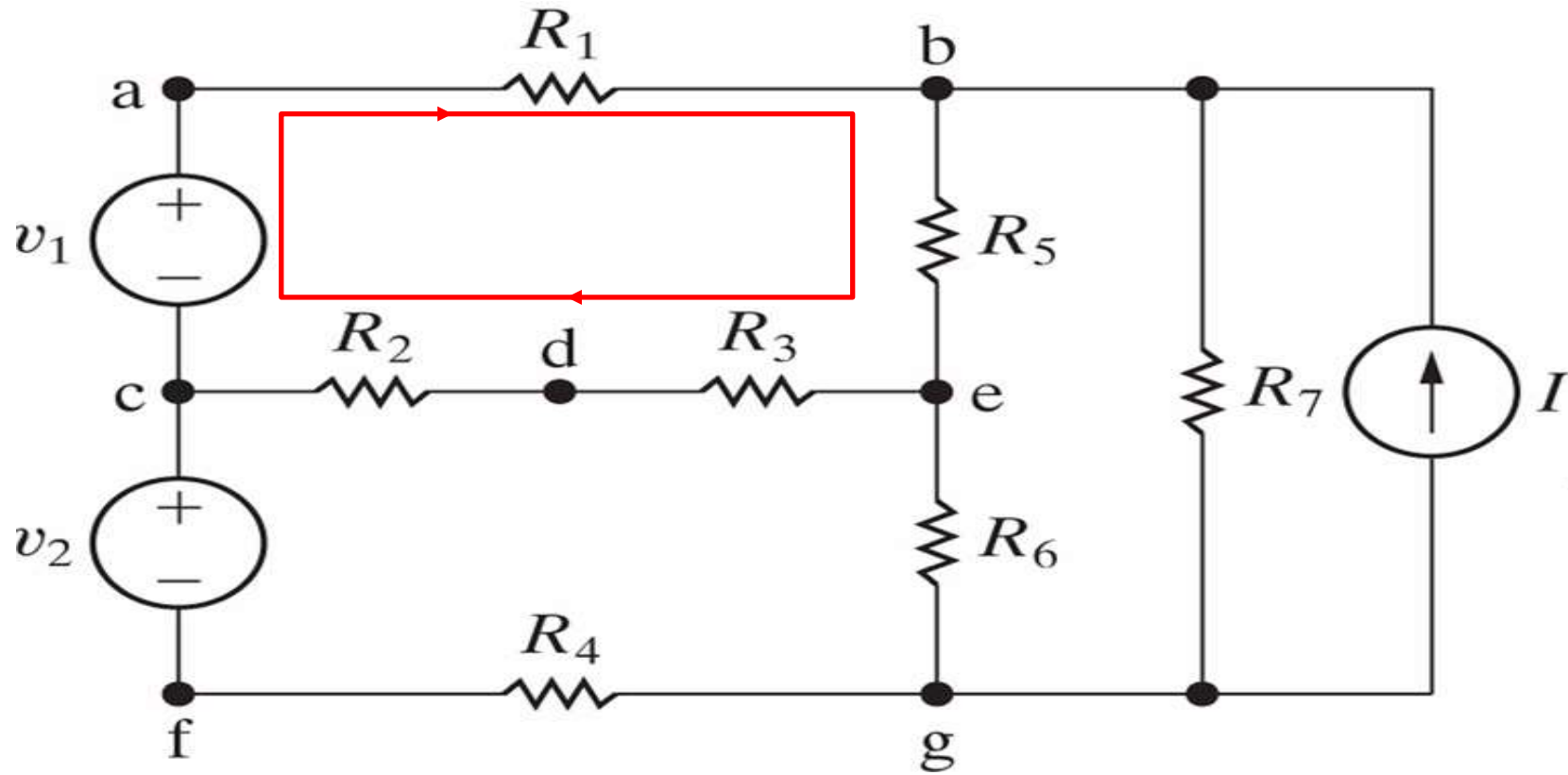

Mesh: a loop that does not enclose any other loops



## Mesh Analysis: Basic Concepts:

- In formulating mesh analysis we assign a mesh current to each mesh.

$$i_{R_3} = i_a - i_b$$

$$-v_1 + i_a R_1 + (i_a - i_b) R_3 = 0$$



$$i_b R_2 + v_2 - (i_a - i_b) R_3 = 0$$

$$i_b R_2 + v_2 + (i_b - i_a) R_3 = 0$$

Collecting the coefficients of  $i_a$  and  $i_b$

$$v_1 = i_a(R_1 + R_3) - i_b R_3 = 0$$

$$-v_2 = -i_a R_3 + i_b(R_2 + R_3) = 0$$

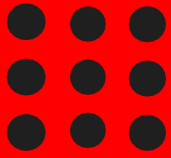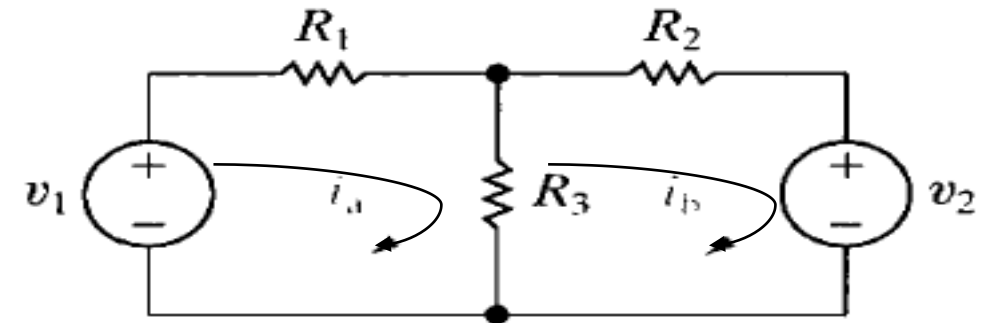



# Problem 1:

*Use the mesh – current method to find  $i_a$ ,  $i_b$  and  $i_c$*

$$-60 + 4i_1 + 10(i_1 - i_2) + 1i_1 = 0$$

$$15i_1 - 10i_2 = 60 \dots \dots \dots (1)$$

$$2i_2 + 20 + 3i_2 + 10(i_2 - i_1) = 0$$



$$-10i_1 + 15i_2 = -20 \dots \dots \dots (2)$$

*Solving,  $i_1 = 5.6A$ ,  $i_2 = 2.4A$*

$$i_a = i_1 = 5.6 \text{ A}$$

$$i_b = i_1 - i_2 = 3.2 \text{ A}$$


$$i_c = -i_2 = -2.4 \text{ A}$$

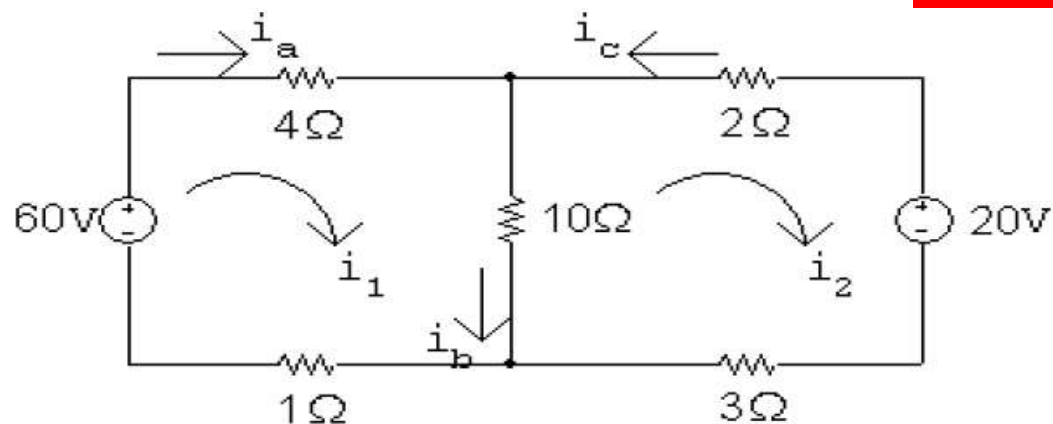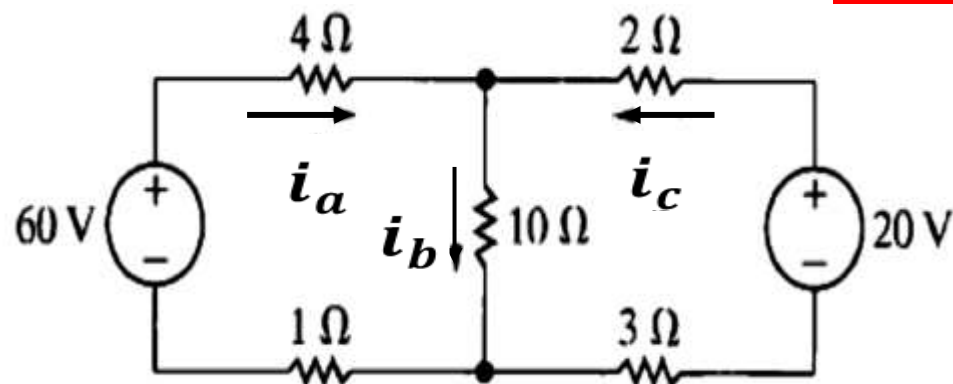


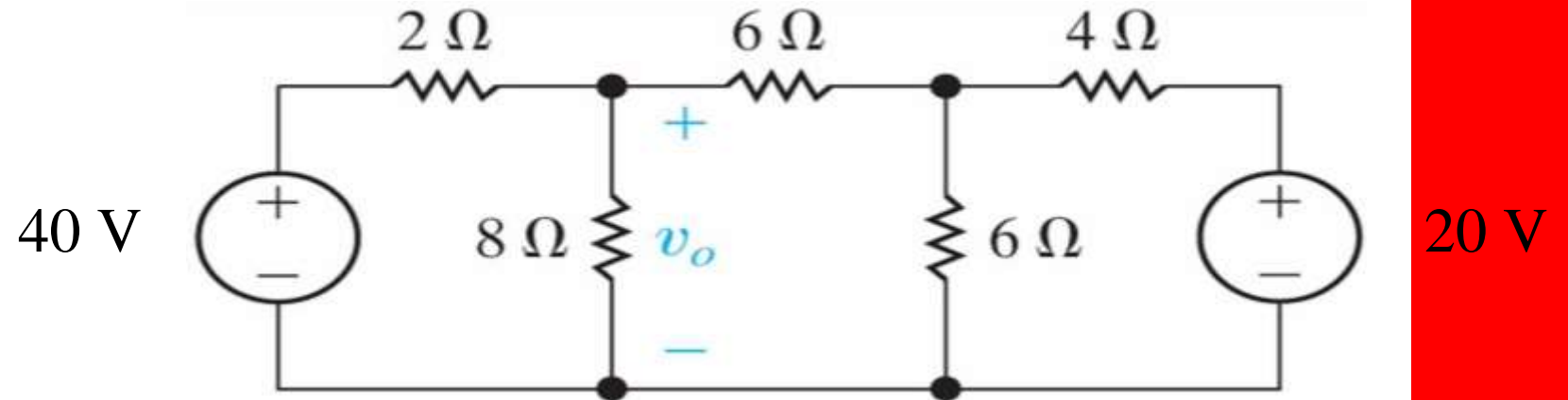
## Example 2 Using Mesh-Current Method

Use the mesh-current method to determine the power associated with each voltage source in the circuit shown



$$-40 + 2i_a + 8(i_a - i_b) = 0$$

$$8(i_b - i_a) + 6i_b + 6(i_b - i_c) = 0$$

$$6(i_c - i_b) + 4i_c + 20 = 0$$



$$-40 + 2i_a + 8(i_a - i_b) = 0$$

$$8(i_b - i_a) + 6i_b + 6(i_b - i_c) = 0$$

$$6(i_c - i_b) + 4i_c + 20 = 0$$


$$10i_a - 8i_b + 0i_c = 40; \quad i_a = 5.6 \text{ A,}$$

$$-8i_a + 20i_b - 6i_c = 0; \quad i_b = 2.0 \text{ A,}$$

$$0i_a - 6i_b + 10i_c = -20. \quad i_c = -0.80 \text{ A.}$$

$$p_{40\text{V}} = -40i_a = -224 \text{ W.} \quad p_{20\text{V}} = 20i_c = -16 \text{ W.}$$
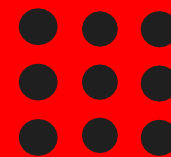
$$v_o = 8(i_a - i_b) = 8(3.6) = 28.8 \text{ V.}$$






# Mesh Analysis: Basic Concepts:

## ✓ ASSESSMENT PROBLEM

Objective 2—Understand and be able to use the mesh-current method

4.7 Use the mesh-current method to find (a) the power delivered by the 80 V source to the circuit shown and (b) the power dissipated in the 8  $\Omega$  resistor.

Answer: (a) 400 W;  
(b) 50 W.

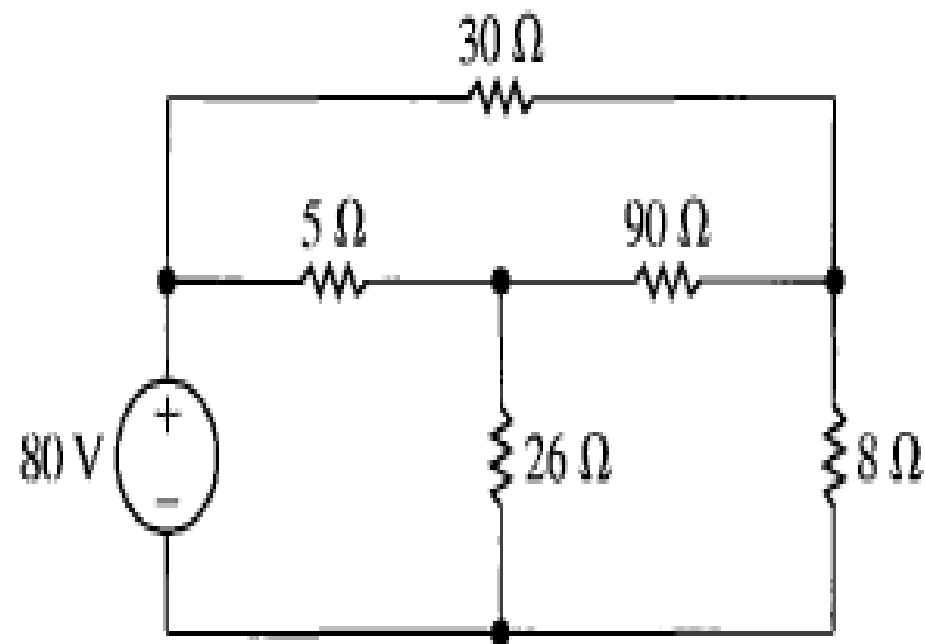






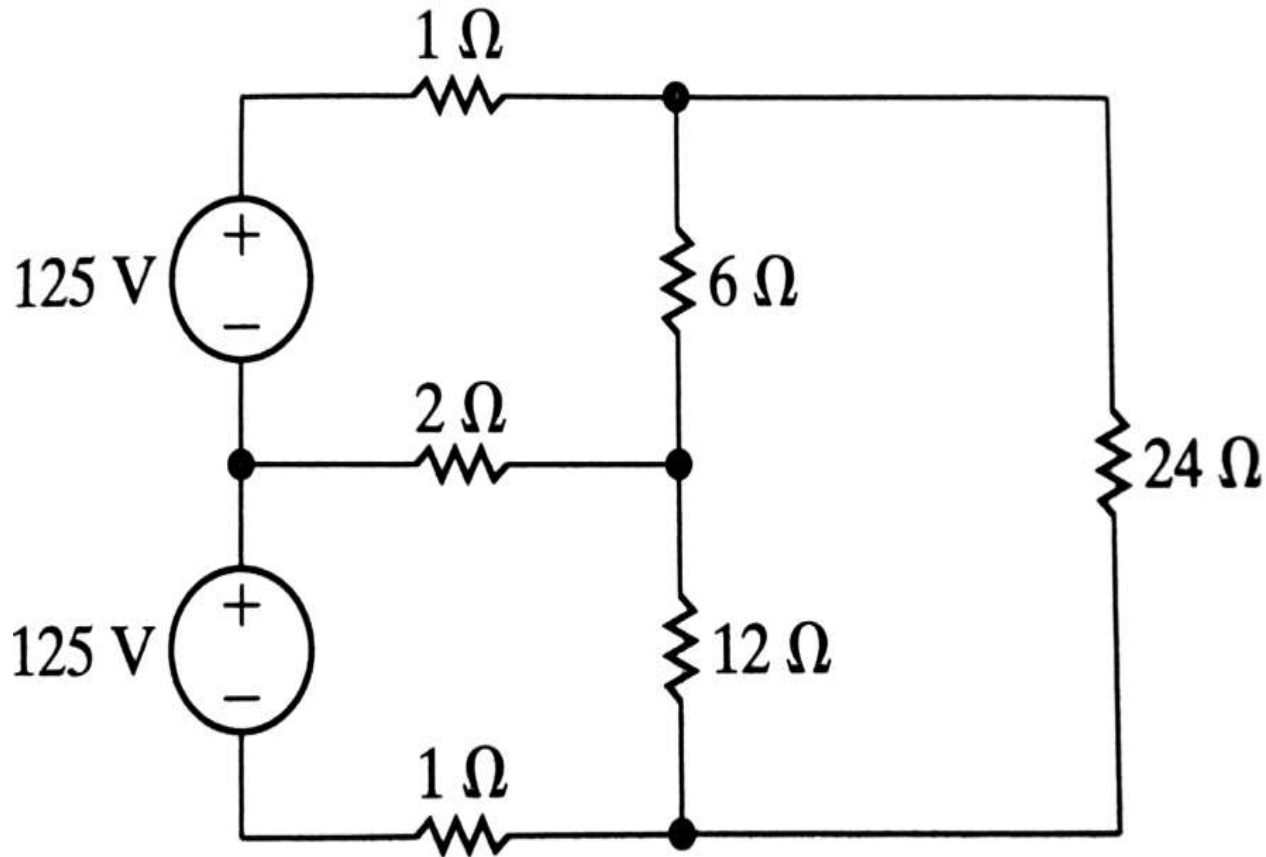
## Problem 3

Using Mesh-Current method, find all the mesh currents.



23.76 A,  
18.43 A,  
8.66 A

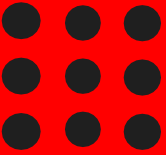



# REFERENCES

1. Muthusubramanian R, Salivahanan S, “Basic Electrical and Electronics Engineering”, Tata McGraw Hill Publishers, (2009) - UNIT I – V
2. Bhattacharya. S.K, “Basic Electrical and Electronics Engineering”, Pearson Education , (2017) – UNIT I – IV
3. Mehta V K, Mehta Rohit, “Principles of Electrical Engineering and Electronics”, S.Chand & Company Ltd, (2010)- UNIT I and II
4. Mehta V K, Mehta Rohit, “Principles of Electronics”, S.Chand & Company Ltd, (2005)- UNIT IV and V
5. <https://happho.com/install-concealed-conduit-electrical-wiring-system-properly/>

**THANK YOU**