

1.3 OHM'S LAW

Ohm's law states that in a linear network, at constant temperature the voltage across the conducting material is directly proportional to the current flowing through the material,

$$\text{i.e., } V \propto I$$

$$\text{or, } V = RI$$

where the constant of proportionality, R , is called *resistance*; its unit is ohm.

When the temperature changes, the resistivity (ρ) and the physical dimension (length/ or area A) of the resistance material also vary. As $R = \rho \frac{L}{A}$, any change in the value of resistivity or physical dimension would affect the value of the resistance, R . Therefore, Ohm's law is only valid at constant temperatures.

For illustration purpose, let us assume that a resistor, R , is connected between the nodes 1 and 2, with potentials V_1 and V_2 as shown in Fig. 1.8.

If $V_1 > V_2$, then the potential difference between these nodes 1 and 2 is given by

$$V_1 - V_2$$

If the current I flows because of this potential difference, then according to Ohm's law

$$V_1 - V_2 = IR$$

or simply, $V = IR$, where $V = V_1 - V_2$.

The V - I relationship for a linear resistor is shown in Fig. 1.9.

From this relationship, the unknown voltage across a resistor can be calculated by the known current and resistance values. Similarly, if the values of R and V are known, the value of I can be calculated using the relationship,

$$I = \frac{V}{R}$$

If the values of I and V are known, R can be calculated by using the relationship,

$$R = \frac{V}{I}$$

Limitations of Ohm's Law

1. Ohm's law is applicable only for metallic conductors maintained at a constant temperature. The law is not applicable if the temperature changes.
2. Ohm's law is not applicable to all non-metallic conductors.

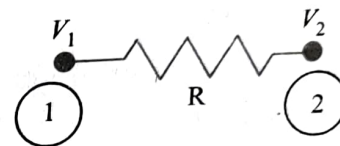


FIG. 1.8 An illustration for Ohm's law

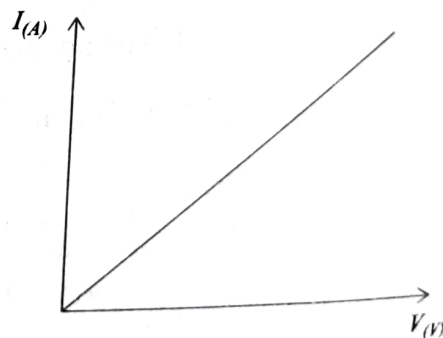


FIG. 1.9 V-I relationship for a linear resistor

3. It is also not applicable to non-linear devices such as diodes, transistors, and other semiconductor devices.

Example 1.1 Find the voltage drop across a $10\text{ k}\Omega$ resistor if the current flowing through it is 1 mA .

Solution

Given: $R = 10\text{ k}\Omega$ and $I = 1\text{ mA}$

According to Ohm's law, the voltage across the resistor is

$$V = IR = 1 \times 10^{-3} \times 10 \times 10^3 = 10\text{ V}$$

Example 1.2 Find the current in the circuit shown in Fig. E1.2.

Solution

Given: $V = 20\text{ V}$ and $R = 20\text{ k}\Omega$

According to Ohm's law, the current flowing through a $20\text{ k}\Omega$ resistor is

$$I = \frac{V}{R} = \frac{20}{20 \times 10^3} = 1\text{ mA}$$

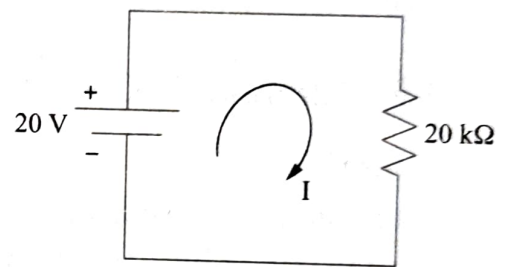


FIG. E1.2

Example 1.3 Find the value of resistance, R , in the circuit shown in Fig. E1.3, if the ammeter measures 1 mA and voltmeter measures 2 V .

Solution

Given the ammeter measures $I = 1\text{ mA}$ and the voltmeter measures $V_R = 2\text{ V}$.

Applying Ohm's law, the unknown resistance R is calculated as

$$R = \frac{V_R}{I} = \frac{2}{1 \times 10^{-3}} = 2\text{ k}\Omega$$

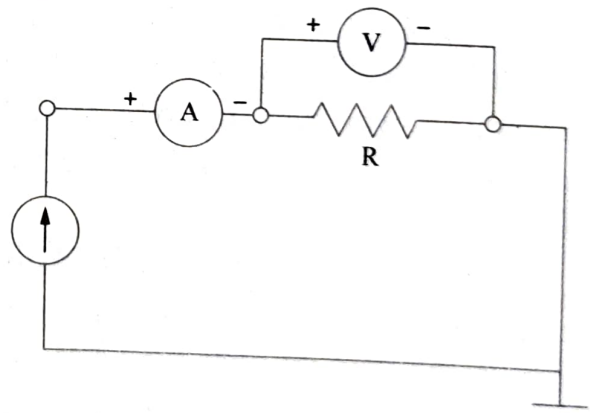


FIG. E1.3

Example 1.4 A conductivity meter measures the conductance of a material as 5 S . If the current flowing through that material is determined as 2 mA , find the applied voltage.

Solution

Given the conductance, $G = 5\text{ S}$

As resistance is the inverse of conductance, $R = \frac{1}{G} = \frac{1}{5} = 0.2\ \Omega$

The ammeter measures $I = 2\text{ mA}$

Therefore, the applied voltage, $V = IR = 2 \times 10^{-3} \times 0.2 = 0.4\text{ mV}$