

## 1.8 NODAL ANALYSIS METHOD

A junction point in an electrical circuit is called a node. A potential drop can be measured with respect to this point and another node acting as a reference point. Generally, grounded node is taken as a reference point. If  $n$  is the number of nodes, then the number of independent KCL equations in nodal analysis is  $(n-1)$  because one node acts as a reference node.

Consider the sample circuit shown in Fig. 1.18(a).

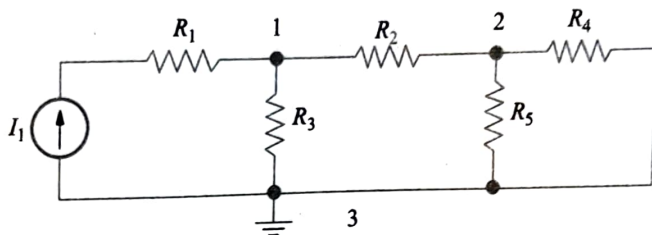


FIG. 1.18(a)

The branch currents entering and leaving node 1 can be marked as shown in Fig. 1.18(b).

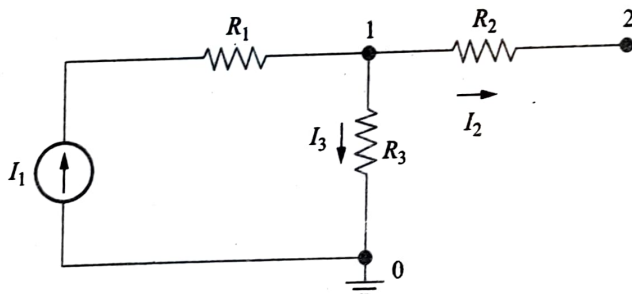


FIG. 1.18(b)

According to KCL, the currents entering the node 1 is equal to the current leaving that node. Thus,

$$I_1 = I_2 + I_3$$

According to Ohm's law,  $I_2 = \frac{V_1 - V_2}{R_2}$  and  $I_3 = \frac{V_1 - V_0}{R_3}$

Therefore,  $I_1 = \frac{V_1 - V_2}{R_2} + \frac{V_1 - V_0}{R_3}$  and since node 0 is grounded,  $V_0 = 0$ .

$$\begin{aligned} I_1 &= \frac{V_1 - V_2}{R_2} + \frac{V_1 - 0}{R_3} \\ &= \frac{V_1 - V_2}{R_2} + \frac{V_1}{R_3} \end{aligned}$$

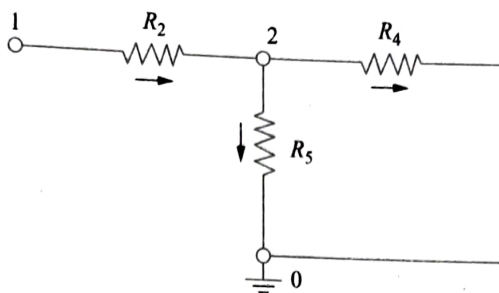


FIG. 1.18(c)

Similarly, with reference to node 2 in Fig. 1.18(c), we have

$$\frac{V_2 - V_1}{R_2} + \frac{V_2 - 0}{R_5} + \frac{V_2 - 0}{R_4} = 0$$

$$\frac{V_2 - V_1}{R_2} + V_2 \left( \frac{1}{R_4} + \frac{1}{R_5} \right) = 0$$

The above nodal equations for nodes 1 and 2 are used to find the voltages at each node.

### Steps involved in the nodal analysis method

**Step 1:** Identify all independent nodes wherever the current branches out and select a reference node.

**Step 2:** Write the nodal equation using KCL for all nodes except the reference node.

**Step 3:** Nodal equations are then solved to find nodal voltages and branch currents.

**Example 1.44** Using nodal analysis, determine nodal voltages for the circuit shown in Fig. E1.44(a)

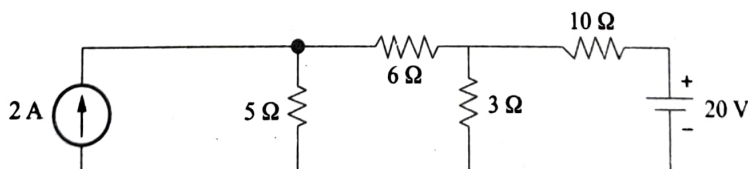


FIG. E1.44(a)

### Solution

**Step 1:** Identify all nodes and assign a reference node as shown in Fig. E1.44(b).

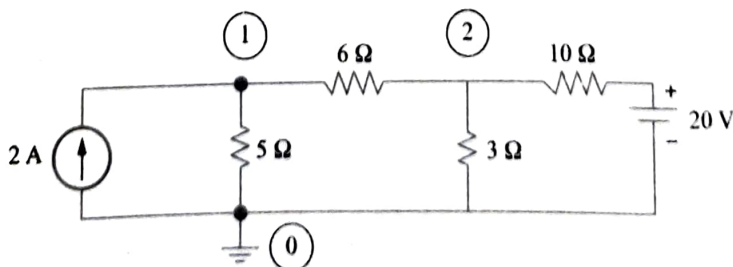


FIG. E1.44(b)

**Step 2** Write the nodal equation using KCL.

At node 1,

$$2 = \frac{V_1}{5} + \frac{V_1 - V_2}{6}$$

$$V_1 \left[ \frac{1}{5} + \frac{1}{6} \right] - V_2 \left[ \frac{1}{6} \right] = 2$$

$$0.367V_1 - 0.167V_2 = 2 \quad (1)$$

At node 2,

$$\frac{V_2 - V_1}{6} + \frac{V_2}{3} + \frac{V_2 - 20}{10} = 0$$

$$\frac{-V_1}{6} + V_2 \left[ \frac{1}{3} + \frac{1}{6} + \frac{1}{10} \right] - 2 = 0$$

$$-V_1 \left[ \frac{1}{6} \right] + V_2 \left[ \frac{1}{3} + \frac{1}{6} + \frac{1}{10} \right] = 2$$

$$-0.167V_1 + 0.597V_2 = 2 \quad (2)$$

**Step 3:** Upon solving the nodal Eqn. (1) and (2), we get

$$V_1 = 7.991 \text{ V and } V_2 = 5.585 \text{ V}$$

**Example 1.45** Find the unknown voltage  $V_x$  in the circuit shown in Fig. E1.45. Assume that  $V_1 = 16 \text{ V}$ .

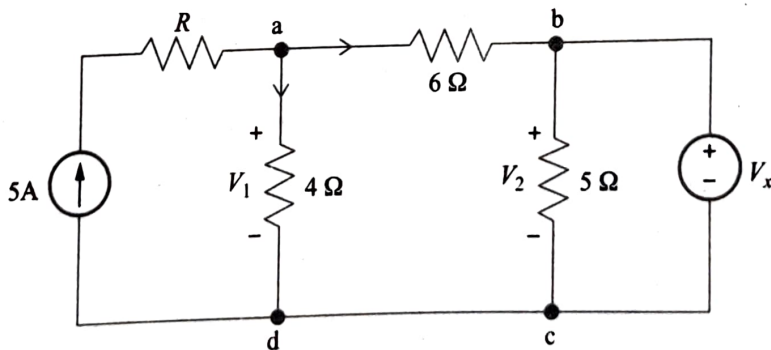


FIG. 1.45

**Solution**

Given  $V_1 = 16 \text{ V}$ , inspecting the circuit shown in Fig. E1.45, the current through the  $4\Omega$  resistor is  $V_1/4$ ,

i.e., 
$$I_{4\Omega} = \frac{16\text{V}}{4} = 4\text{A}$$

Applying KCL at node 'a', we get

$$5 = I_{4\Omega} + I_{6\Omega} = 4 + I_{6\Omega}$$

or, 
$$I_{6\Omega} = 5 - 4 = 1\text{ A}$$

Therefore, the voltage drop across the  $6\Omega$  resistor,  $V_{ab} = 1 \times 6 = 6\text{ V}$ .

Applying KVL to the loop 'abcd', we get

$$V_2 = V_1 - V_{ab} = 16 - 6 = 10\text{ V}.$$

Inspecting the circuit, it is noticed that  $V_x = V_2$ .

Hence,  $V_x = 10\text{ V}$

**Example 1.46** In the circuit shown in Fig. E1.46(a), determine: (a) the open circuit voltage  $V_{a-b}$ , (b) the short-circuit current through terminals a-b, and (c) the voltage drop across 3 A current source when a-b is open-circuited.

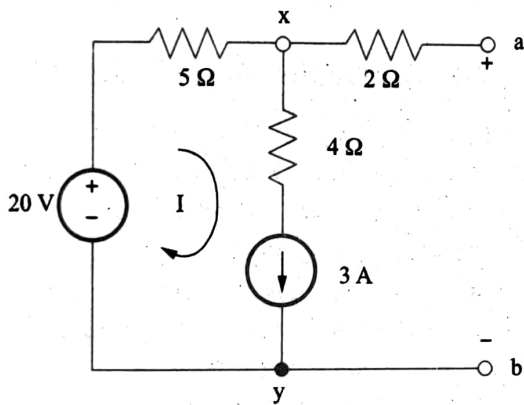


FIG. E1.46(a)

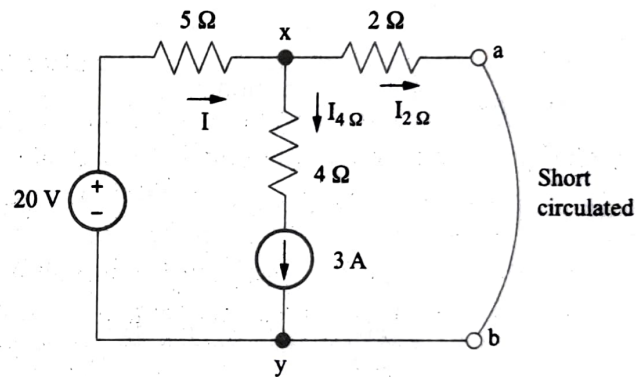


FIG. E1.46(b)

### Solution

(a) Inspecting the circuit shown in Fig. E1.46(a),  $I = 3\text{ A}$

Hence, the voltage drop across  $5\Omega$  resistor is  $V_{5\Omega} = 3 \times 5 = 15\text{ V}$

and the open-circuit voltage  $V_{a-b} = V_{xy} = 20 - V_{5\Omega} = 20 - 15 = 5\text{ V}$

(b) Short-circuiting the terminals a-b and applying KCL at node 'x', we get

$$I = I_{2\Omega} + I_{4\Omega}$$

An inspection of the circuit shown in Fig. E1.46(b) reveals that  $I = \frac{20 - V_{xy}}{5}$ ,  $I_{4\Omega} = 3\text{ A}$

and since 'a' and 'b' are shorted the nodes 'a', 'b' and 'y' merge with the node 'y', so

that 
$$I_{2\Omega} = \frac{V_{xy}}{2}\text{ A}$$

Therefore, 
$$\frac{20 - V_{xy}}{5} = 3 + \frac{V_{xy}}{2}$$

$$\frac{20 - V_{xy}}{5} = \frac{6 + V_{xy}}{2}$$

or,  $V_{xy} = \frac{10}{7} \text{ V}$

Hence, the short-circuit current through a-b is

$$I_{2\Omega} = \frac{V_{xy}}{2} = \frac{10}{2 \times 7} = \frac{5}{7} \text{ A}$$

(c) When the a-b terminal is open-circuited as shown in Fig. E1.46(a), assuming the voltage drop across 3 A source is  $V_{3\Omega}$  and applying KVL to the circuit, we get

$$-20 + 5I + 4I - V_{3\Omega} = 0$$

Since  $I = 3 \text{ A}$ ,  $-20 + 15 + 12 - V_{3\Omega} = 0$

Therefore,  $V_{3\Omega} = 7 \text{ V}$

**Example 1.47** Write the nodal equations for the circuit shown in Fig. E1.47.

**Solution**

Applying nodal analysis, we get

For node 1,

$$\frac{V_1 - 10}{4} + \frac{V_1 - V_2}{8} + \frac{V_1 - 4}{3} = 7$$

For node 2,

$$\frac{V_2 - V_1}{8} + \frac{V_2 - 4}{5} = 2$$

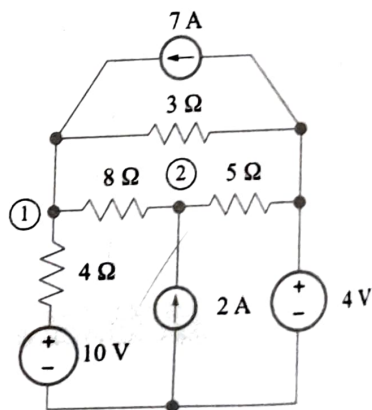


FIG. E1.47

**Example 1.48** For the circuit shown in Fig. E1.48, using Kirchoff's current law, find the values of the currents,  $I_1$  and  $I_2$ .

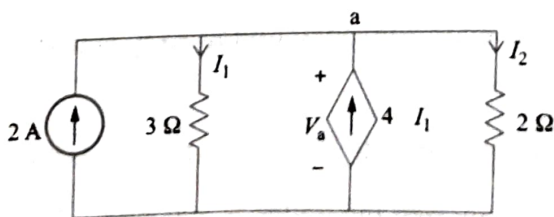


FIG. E1.48

**Solution**

We know that in a parallel circuit, the voltage remains the same across all the parallel branches. According to Ohm's law,  $I_1 = \frac{V_a}{3}$



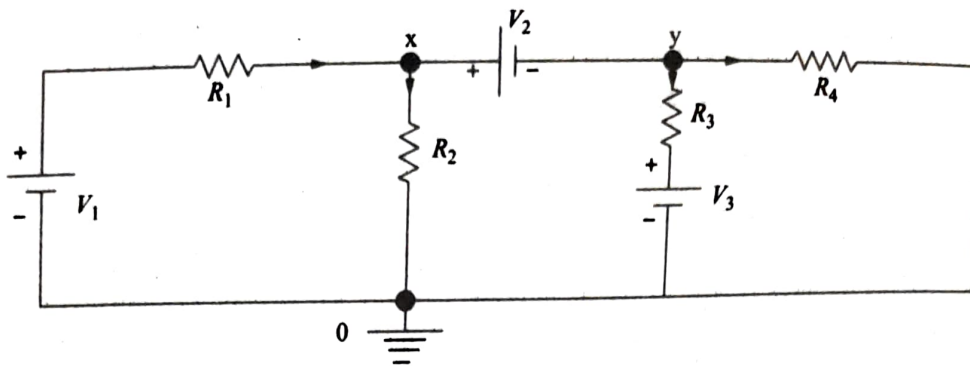


FIG. 1.19

**Example 1.50** Find the current through  $1\ \Omega$  resistor by using analysis method for the circuit shown in Fig. E1.50.

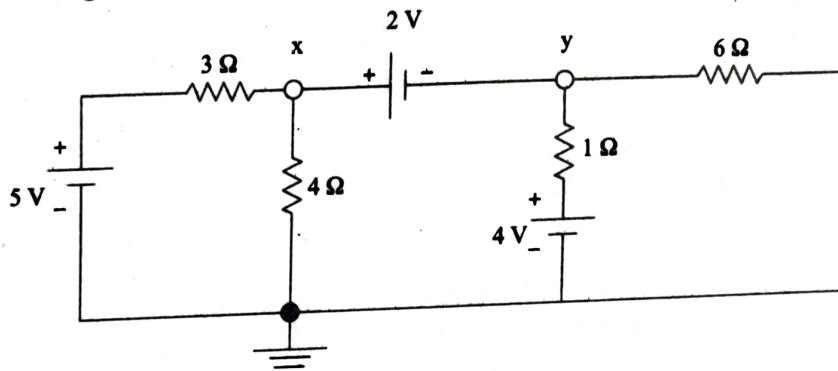


FIG. E1.50

**Solution**

Inspecting the circuit reveals that a voltage source is connected between two nodes 'x' and 'y'. Hence, the combined super node equation for the nodes 'x' and 'y' can be written as

$$\frac{V_x - 5}{3} + \frac{V_x}{4} + \frac{V_y - 4}{1} + \frac{V_y}{6} = 0$$

$$V_x \left[ \frac{1}{3} + \frac{1}{4} \right] + V_y \left[ 1 + \frac{1}{6} \right] - \frac{5}{3} - 4 = 0$$

$$0.583V_x + 1.666V_y = 5.666$$

We know that  $V_x - V_y = 2$

Solving the above equations, we get

$$V_x = 4\text{ V and } V_y = 2\text{ V}$$

The current through the  $1\ \Omega$  resistor,  $I_{1\Omega}$

$$I_{1\Omega} = \frac{V_y - 4}{1} = 2 - 4 = -2\text{ A}$$

Example and determ

Solution Applying

i.e., Applying

i.e., Solving th

According

and

Example  $V_o/V_p$  by n

**Example 1.51** For the given circuit shown in Fig. E1.51, write the node voltage equations and determine the currents in each branch for the given network.

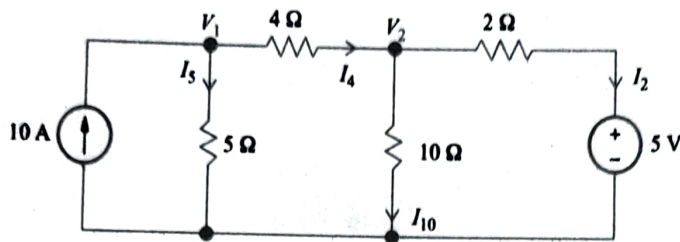


FIG. E1.51

**Solution**

Applying Kirchhoff's current law at node 1 we get

$$10 = \frac{V_1}{5} + \frac{V_1 - V_2}{4}$$

$$\text{i.e.,} \quad \frac{9}{20}V_1 - \frac{V_2}{4} = 10 \quad (1)$$

Applying KCL at node 2, we get

$$\frac{V_2 - V_1}{4} + \frac{V_2}{10} + \frac{V_2 - 5}{2} = 0$$

$$\text{i.e.,} \quad \frac{17}{20}V_2 - \frac{V_1}{4} = \frac{5}{2} \quad (2)$$

Solving the nodal Eqn. (1) and (2), we get

$$V_2 = 11.33 \text{ V}$$

$$V_1 = 28.5 \text{ V}$$

According to Ohm's law, the different branch currents are

$$I_5 = \frac{V_1}{5} = \frac{28.5}{5} = 5.7 \text{ A}$$

$$I_{10} = \frac{V_2}{10} = \frac{11.33}{10} = 1.133 \text{ A}$$

$$I_4 = \frac{V_1 - V_2}{4} = \frac{28.5 - 11.33}{4} = 4.2925 \text{ A}$$

and

$$I_2 = \frac{V_2 - 5}{2} = \frac{11.33 - 5}{2} = 3.165 \text{ A}$$

**Example 1.52** For the given circuit shown in Fig. E1.52, determine the voltage ratio,  $V_o/V_i$ , by nodal analysis.

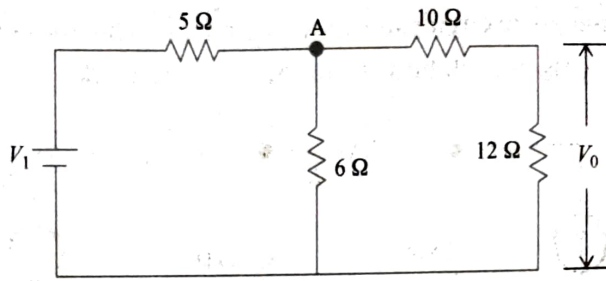


FIG. E1.52

**Solution**

Applying KCL at node A, we get

$$I_{5\Omega} + I_{6\Omega} + I_{22\Omega} = 0$$

$$\text{i.e., } \frac{V_A - V_I}{5} + \frac{V_A}{6} + \frac{V_A}{22} = 0$$

$$\text{i.e., } V_A \left( \frac{1}{5} + \frac{1}{6} + \frac{1}{22} \right) = \frac{V_I}{5}$$

$$\text{or, } V_A = 0.485 V_I \quad (1)$$

As the same current flows through both the resistors  $10\Omega$  and  $12\Omega$ , we have

$$I_{12\Omega} = I_{22\Omega}$$

$$\text{i.e., } \frac{V_A}{22} = \frac{V_o}{12}$$

$$V_A = 1.833 \times V_o \quad (2)$$

Substituting Eqn. (2) in Eqn. (1), we get

$$\frac{V_o}{V_I} = \frac{0.485}{1.833} = 0.264$$

**Example 1.53** For the circuit shown in Fig. E1.53, using nodal analysis find the voltage  $V_i$  which makes the current in  $10\Omega$  as zero.

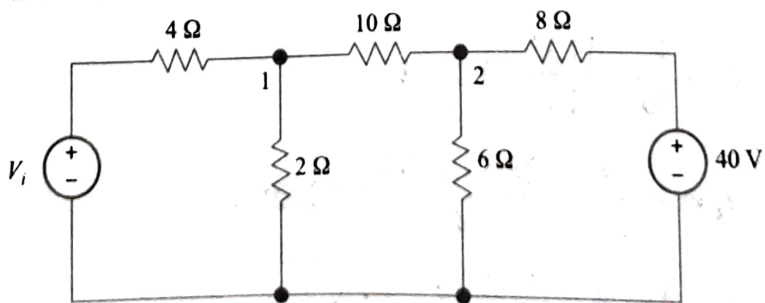


FIG. E1.53

**Solution**

Applying KCL at node 1, we get



$$\frac{V_1 - V}{4} + \frac{V_1}{2} + \frac{V_1 - V_2}{10} = 0$$

$$0.85V_1 - 0.1V_2 = \frac{V_i}{4} \quad (1)$$

Applying KCL at node 2, we get

$$\frac{V_2 - V_1}{10} + \frac{V_2}{6} + \frac{V_2 - 40}{8} = 0$$

$$0.39V_2 - 0.1V_1 = 5 \quad (2)$$

Since the current through  $10\Omega$  is zero, we have

$$V_1 - V_2 = 0$$

or,  $V_1 = V_2 \quad (3)$

Substituting Eqn. (3) in Eqn. (2), we get

$$V_2 = V_1 = 17.241 \text{ V}$$

Substituting these values in Eqn. (1), we get

$$V_i = 4 \times (0.85 - 0.1) \times 17.241 = 51.723 \text{ V}$$