

FIG. E2.39(d)

2.7 NORTON'S THEOREM

Norton's theorem states that "any two-terminal bilateral linear circuit consisting of energy sources and impedances can be replaced with a Norton's equivalent circuit with a simple Norton current source \bar{I}_N in parallel with a Norton's impedance Z_N connected to a load impedance Z_L ". Similar to Thevenin's theorem, Norton's theorem is also used to simplify the analysis of complex circuits.

The value of Norton's equivalent current \bar{I}_N can be calculated by shorting the load impedance Z_L . The Norton's equivalent impedance Z_N is obtained by the procedure similar to that of calculating Thevenin's equivalent impedance Z_{Th} .

Consider the circuit shown in Fig. 2.10(a) to illustrate the application of Norton's theorem.

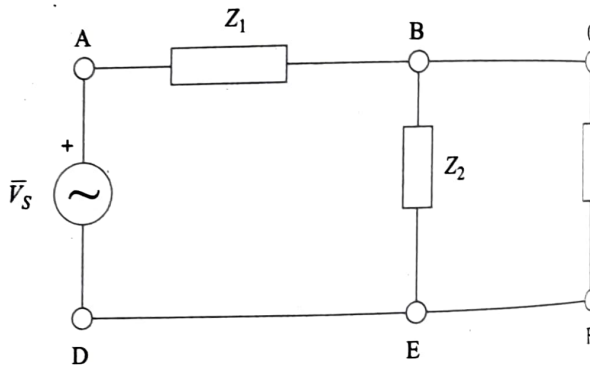


FIG. 2.10(a) A circuit with energy source and impedances

Step 1: To find Norton's current \bar{I}_N , short-circuit the load Z_L as shown in Fig. 2.10(b).

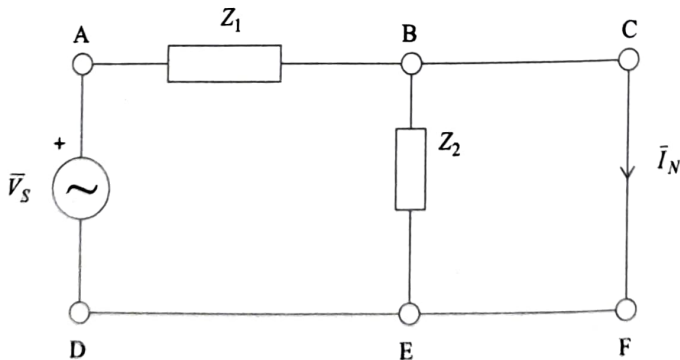


FIG. 2.10(b) Short-circuiting the load

As the entire current flows through the short-circuited terminals C and F and current flows through Z_2 , we have

$$\bar{I}_N = \frac{\bar{V}_S}{Z_1}$$

Step 2: To find Norton's equivalent impedance (Z_N)

$$Z_N = Z_{Th} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

Step 3: Norton's equivalent circuit with \bar{I}_N , Z_N and Z_L can be constructed as shown in Fig. 2.10(c).

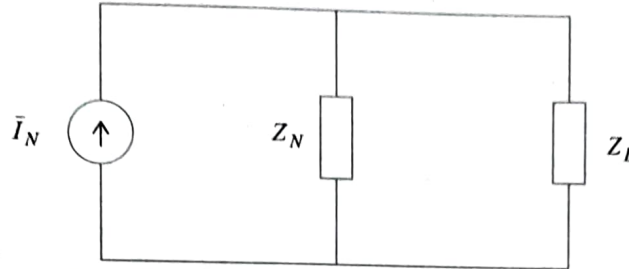


FIG. 2.10(c) Norton's equivalent circuit

It is important to note that using source transformation, Thevenin's equivalent circuit can be converted into Norton equivalent and vice versa as shown in Fig. 2.10(d).

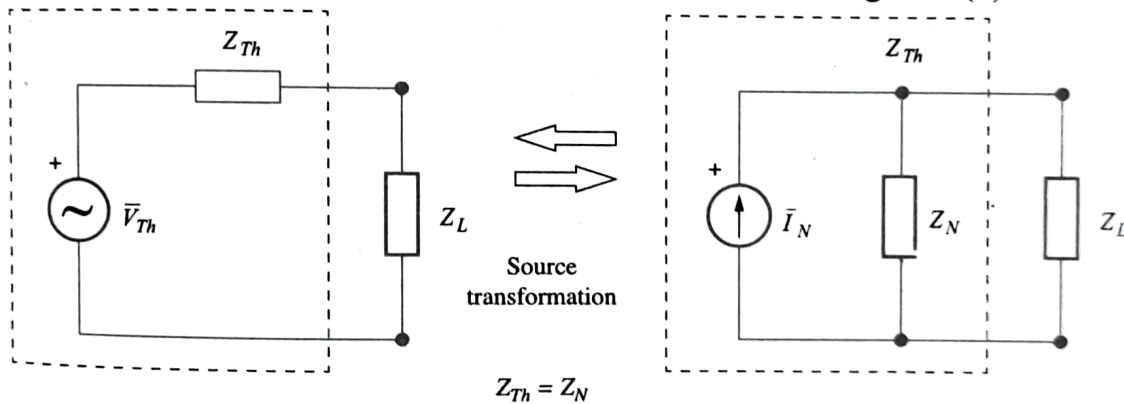


FIG. 2.10(d) Source transformation between Thevenin's equivalent circuit and Norton's equivalent circuit

If dependant sources are present in the circuit, the same procedure can be followed using Thevenin's theorem for solving problems.

Example 2.40 Find the voltage drop across the $12\ \Omega$ resistance using Norton's theorem for the circuit shown in Fig. E2.40(a).

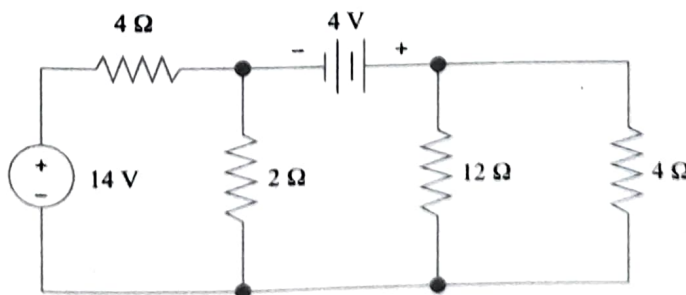


FIG. E2.40(a)

Solution

(a) To find Norton's current I_N :

Short the branch consisting of $12\ \Omega$ resistor as shown in Fig. E2.40(b).

Since the $4\ \Omega$ resistor is in parallel with a short-circuited terminal, it is removed from the circuit as shown in Fig. E2.40(c).

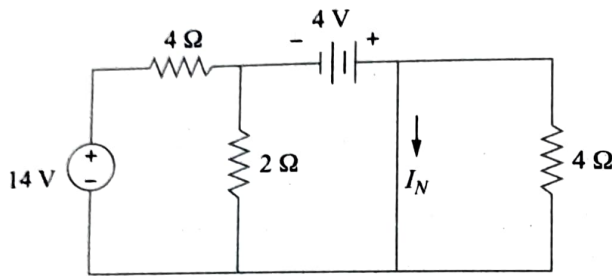


FIG. E2.40(b)

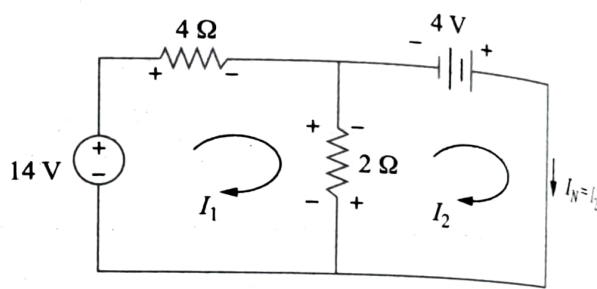


FIG. E2.40(c)

Applying KVL to the circuit shown in Fig. E2.40(c), we get

For loop 1, $4I_1 + 2(I_1 - I_2) = 14$

i.e., $6I_1 - 2I_2 = 14$

For loop 2, $2(I_2 - I_1) = 4$

i.e., $-2I_1 + 2I_2 = 4$

Upon solving Eqn.(1) and(2), we get

$$I_N = I_2 = 6.5\text{ A}$$

(b) To find R_N :

Open-circuit the $12\ \Omega$ resistor, and short-circuit the voltage source as shown in Fig. E2.40(d).

The circuit is further simplified as shown in Fig. E2.40(e).

Therefore, $R_N = \frac{4 \times 1.333}{4 + 1.333} \approx 1\ \Omega$

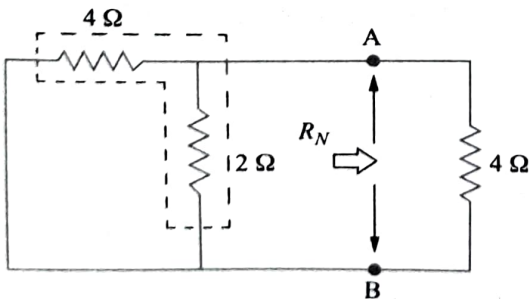


FIG. E2.40(d)

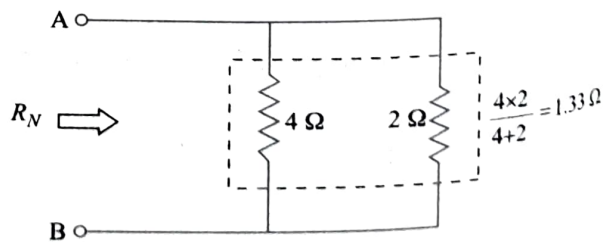


FIG. E2.40(e)

(c) The Norton's equivalent circuit is shown in Fig. E2.40(f).

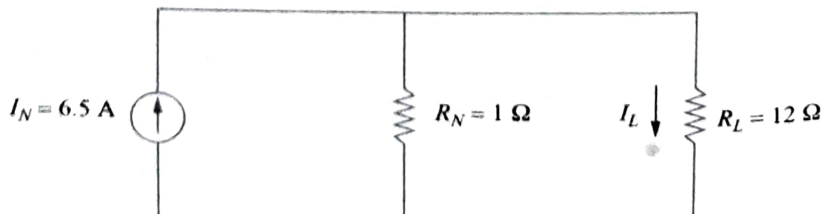


FIG. E2.40(f)

Therefore,

$$I_L = I_{12\Omega} = I_N \times \frac{R_N}{R_L + R_N}$$

$$= 6.5 \times \frac{1}{12 + 1} = 0.5 \text{ A}$$

Voltage drop across the 12Ω load resistor $V_L = I_L R_L = 0.5 \times 12 = 6 \text{ V}$.

Example 2.41 Obtain the Norton's Equivalent for the circuit shown in Fig. E2.41(a).

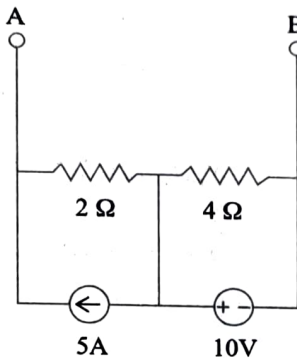


FIG. E2.41(a)

Solution

(a) To find I_N :

Short-circuit the branch AB as shown in Fig. E2.41(b).

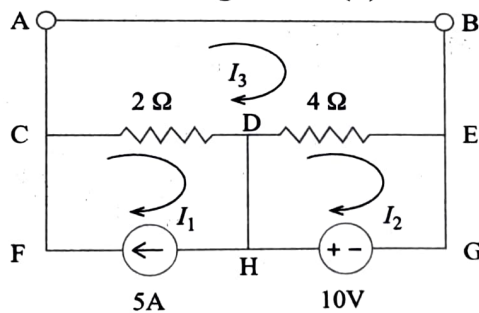


FIG. E2.41(b)

From Fig. E2.41(b), it is evident that

$$I_1 = 5 \text{ A}$$

Applying KVL to the remaining loops, we get

For the loop DEGHD,

$$4(I_2 - I_3) = 10$$

$$4I_2 - 4I_3 = 10 \quad (1)$$

For the loop ABEDCA

$$4(I_3 - I_2) + 2(I_3 - I_1) = 0$$

$$-2I_1 - 4I_2 + 6I_3 = 0$$

$$-4I_2 + 6I_3 = 2 \times 5 = 10 \quad (2)$$

Upon solving Eqn. (1) and (2), we get

$$I_2 = 12.5 \text{ A and } I_3 = 10 \text{ A}$$

Therefore, $I_N = I_3 = 10 \text{ A}$

(b) To calculate R_N :

Open-circuit the current source and short-circuit the voltage source as shown in Fig. E2.41(c)

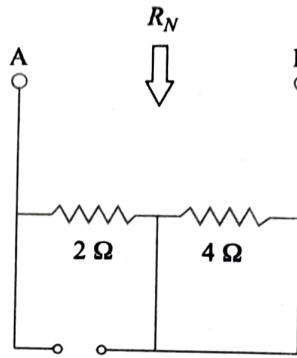


FIG. E2.41(c)

From the circuit shown in Fig. E2.41(c), it is evident that the 4Ω resistor is in parallel with the short circuit. Since the equivalent resistance of this parallel combination is zero, it can be removed.

Therefore, $R_N = 2 \Omega$

(c) The Norton's equivalent circuit is shown in Fig. E2.41(d).

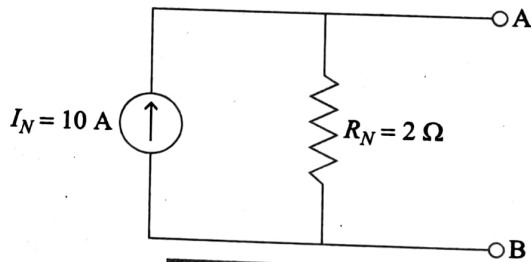


FIG. E2.41(d)

Example 2.42 Determine the current through the 2Ω resistor in the circuit shown in Fig. E2.42(a), using Norton's theorem.

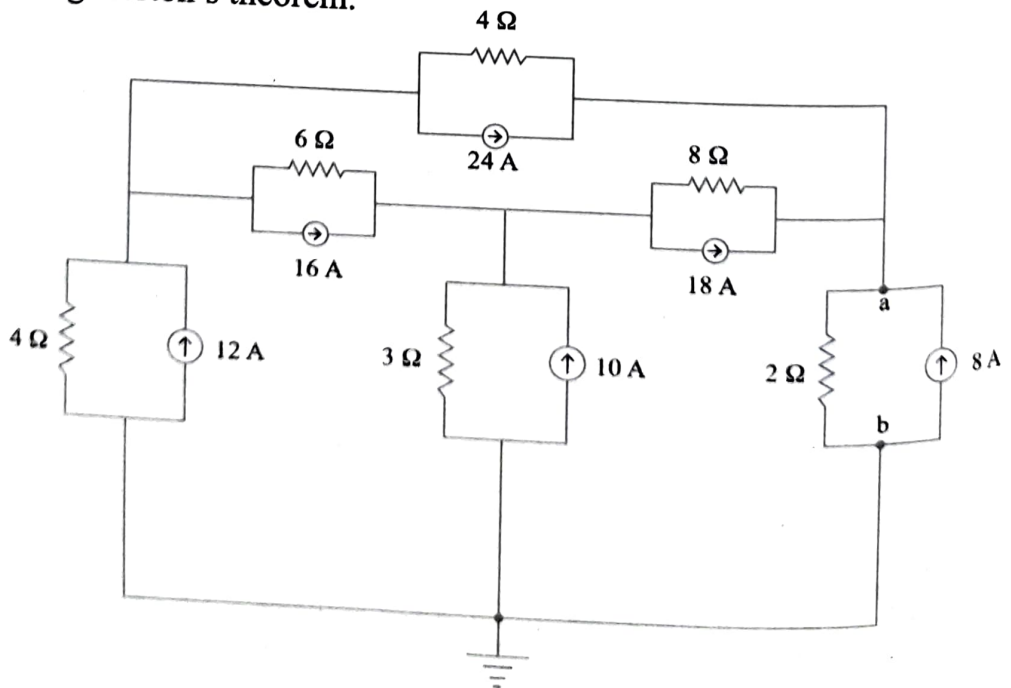


FIG. E2.42(a)

Solution
 Using source transformation, the current sources are converted into voltage sources as shown in Fig. E2.42(b).

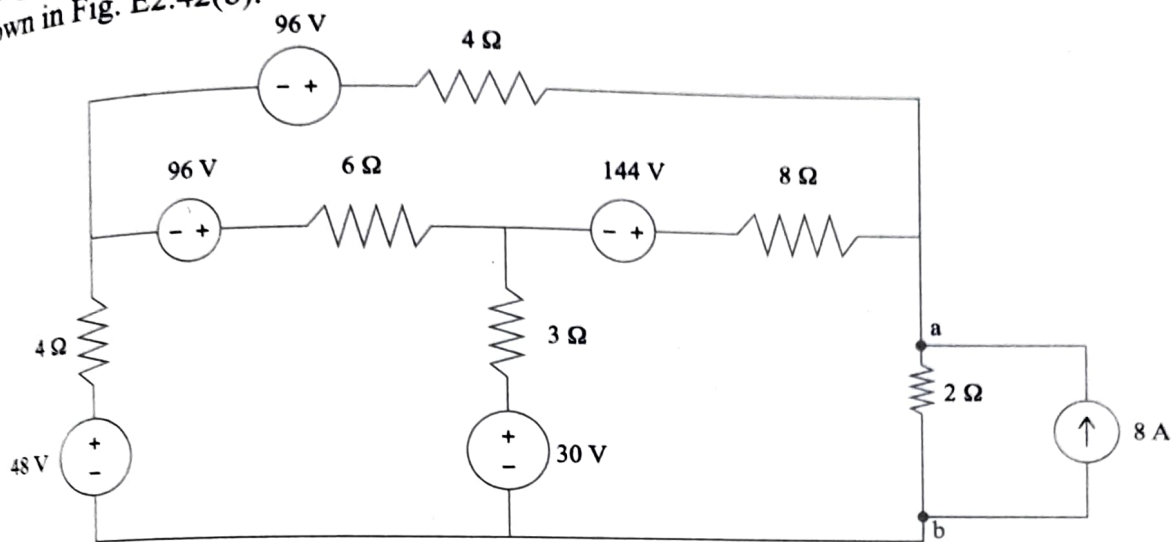


FIG. E2.42(b)

(a) To find I_N :

Short-circuit the load resistor $2\ \Omega$ as shown in Fig. E2.42(c).

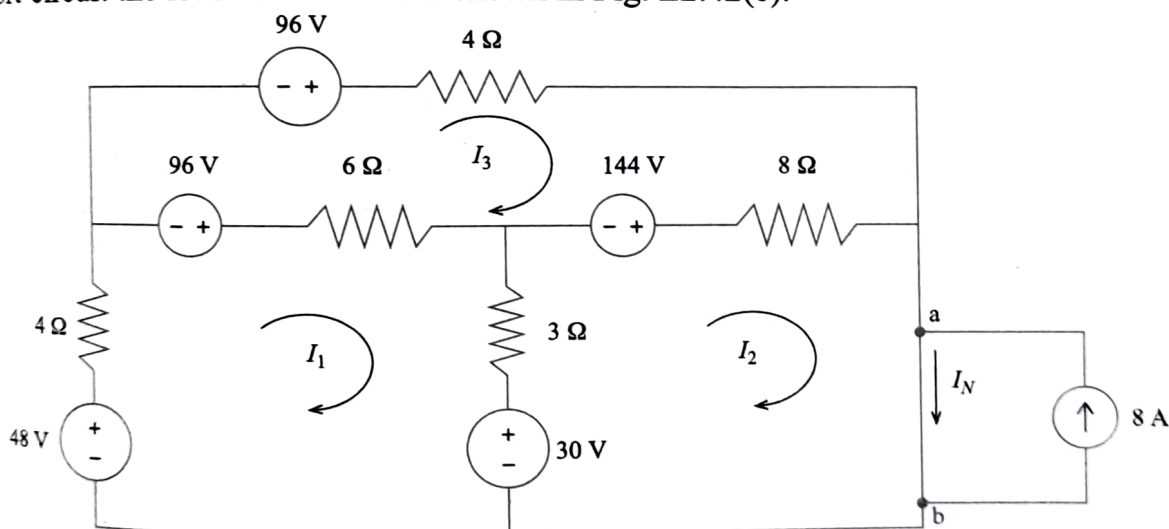


FIG. E2.42(c)

Applying KVL to this circuit, we get

For loop 1,

$$13I_1 - 3I_2 - 6I_3 = 96 - 30 + 48$$

For loop 2,

$$13I_1 - 3I_2 - 6I_3 = 114$$

$$-3I_1 + 11I_2 - 8I_3 = 144 + 30$$

For loop 3,

$$-3I_1 + 11I_2 - 8I_3 = 174$$

$$-6I_1 - 8I_2 + 18I_3 = 96 - 144 - 96$$

$$-6I_1 - 8I_2 + 18I_3 = -144$$

(1)

(2)

(3)

Writing Eqn. (1), (2) and (3) in matrix form, we have

$$\begin{bmatrix} 13 & -3 & -6 \\ -3 & 11 & -8 \\ -6 & -8 & 18 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 114 \\ 174 \\ -144 \end{bmatrix}$$

Applying Cramer's rule, we get

$$\Delta = \begin{vmatrix} 13 & -3 & -6 \\ -3 & 11 & -8 \\ -6 & -8 & 18 \end{vmatrix} = 896$$

$$\Delta_2 = \begin{vmatrix} 13 & 114 & -6 \\ -3 & 174 & -8 \\ -6 & -144 & 18 \end{vmatrix} = 28512$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{28512}{896} = 31.821 \text{ A}$$

From Fig. E2.42(c), It is evident that $I_N = I_2 + 8 = 31.821 + 8 = 39.821 \text{ A}$

(b) To find R_N :

Short-circuit the voltage sources and remove the load R_L as shown in Fig. E2.42(d)

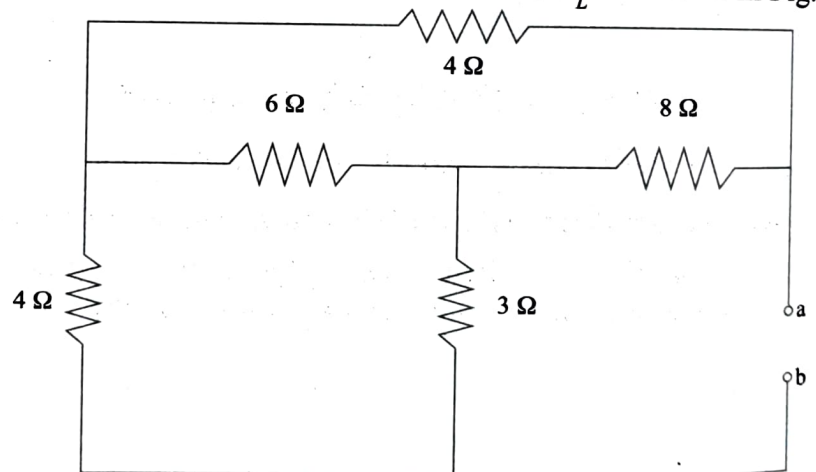


FIG. E2.42(d)

Apply delta-to-star transformation as shown in Fig. E2.42(e).

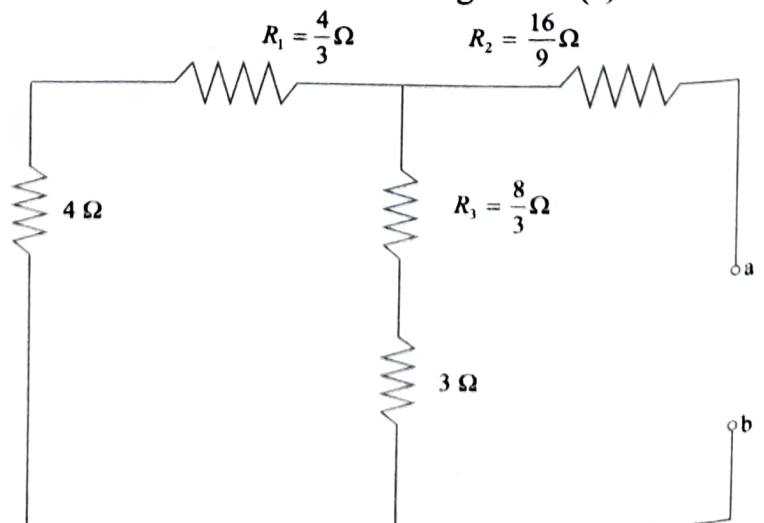


FIG. E2.42(e)

Here, $R_1 = \frac{6 \times 4}{6 + 4 + 8} = \frac{24}{18} = \frac{4}{3} \Omega$

$$R_2 = \frac{8 \times 4}{6 + 4 + 8} = \frac{32}{18} = \frac{16}{9} \Omega$$

and $R_3 = \frac{6 \times 8}{6 + 4 + 8} = \frac{48}{18} = \frac{8}{3} \Omega$

Therefore, $R_N = R_{ab} = \left[\left(4 + \frac{4}{3} \right) \parallel \left(\frac{8}{3} + 3 \right) \right] + \frac{16}{9}$
 $= \frac{5.333 \times 5.667}{5.333 + 5.667} + \frac{16}{9} = 4.525 \Omega$

(c) The Norton's equivalent circuit is shown in Fig. E2.42(f).

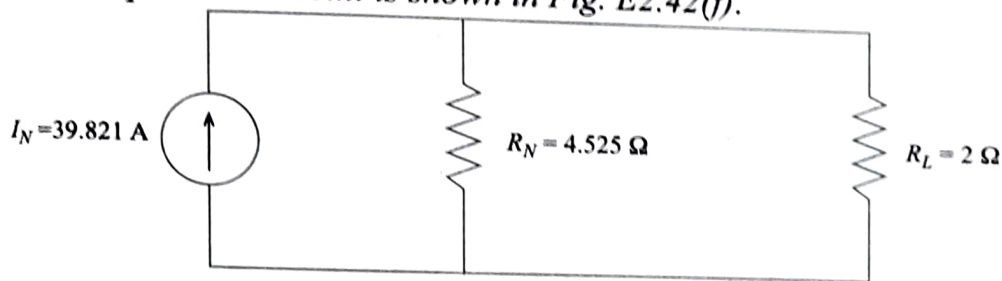


FIG. E2.42(f)

According to the current division rule,

$$I_{2\Omega} = \frac{39.821 \times 4.525}{4.525 + 2} = 27.6153 \text{ A}$$

Example 2.43 Obtain Norton's equivalent for the circuit shown in Fig. E2.43(a) across the terminal AB.

Solution

(a) To find I_N :

Short-circuit the load resistor R_x between the terminals AB, as shown in Fig. E2.43(b).

Let the current flowing through the 4Ω resistor be I_x in the direction as shown in Fig. E2.43(b).

Applying KCL at node 'c', we get

$$4I = I + I_x$$

or

$$I_x = 3I$$

Applying KVL to the super mesh ECABDFE, we get

$$-4I_x + 6I - 2I_x = 4$$

$$-6(3I) + 6I = 4$$

$$-12I = 4$$

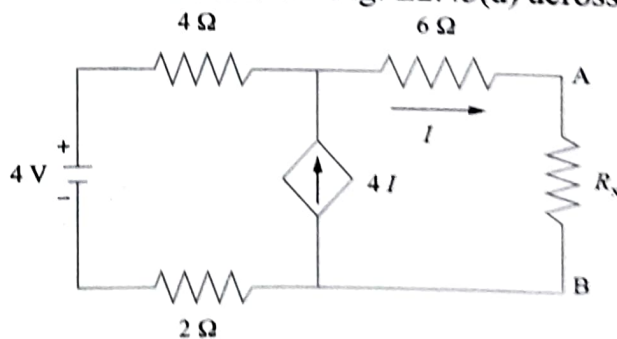


FIG. E2.43(a)

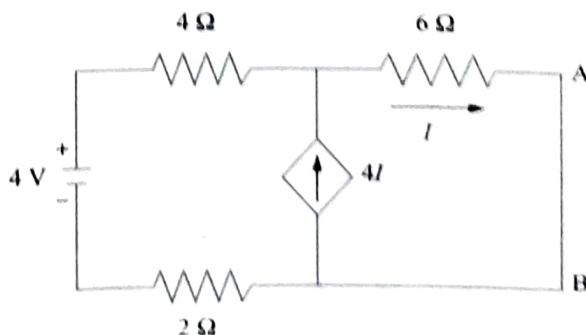


FIG. E2.43(b)