
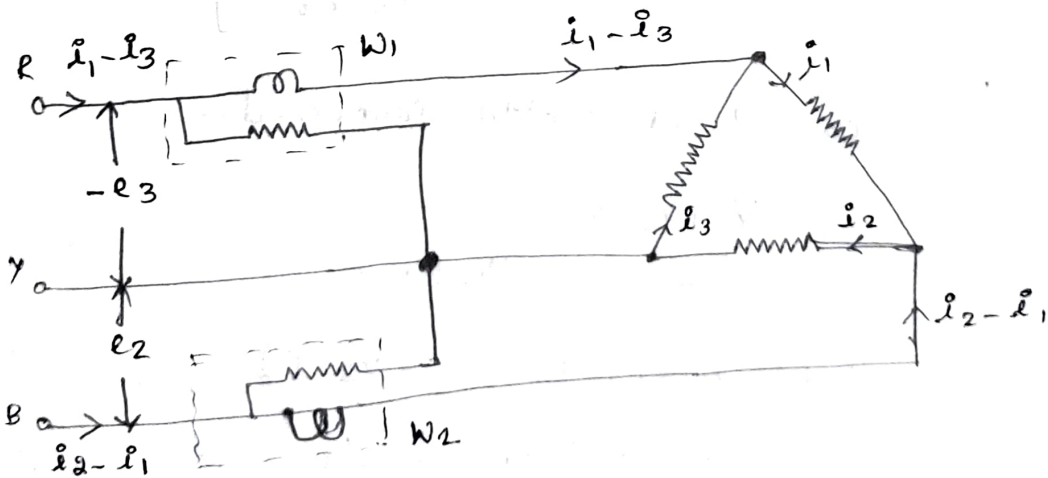


method :-

→ This method is applied usually for measuring the electrical power in 3-phase, 3-wire circuit. The load may be balanced or unbalanced. It may be connected either in delta or star

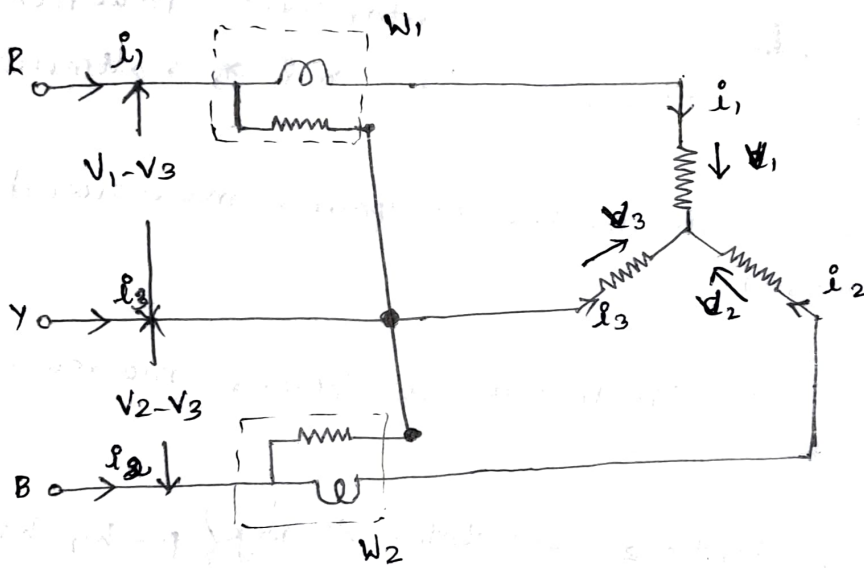→ The current coils of 2-wattmeters are inserted in two of the lines and voltage coil of each wattmeter is connected from its own current coil to the line in which no wattmeter has been connected. The connections of wattmeters in this method are shown below,



* The instantaneous power, $P = V_1 \cdot i_1 + V_2 \cdot i_2 + V_3 \cdot i_3$ (1)

$$\therefore i_1 + i_2 + i_3 = 0$$

$$\text{(or)} \quad i_3 = -(i_1 + i_2)$$

$$\text{Sub } i_3 = -(i_1 + i_2)$$

$$P = V_1 \cdot i_1 + V_2 \cdot i_2 - V_3 \cdot (i_1 + i_2)$$

$$P = i_1 (V_1 - V_3) + i_2 (V_2 - V_3)$$

i_1 = Instantaneous current flowing through the current coil of Wattmeter

$(V_1 - V_3)$ = the Instantaneous Potential difference across voltage coil of Wattmeter-1

$i_1 \cdot (V_1 - V_3)$ = Instantaneous power measured by Wattmeter-1

$i_2 (V_2 - V_3)$ = Instantaneous power measured by Wattmeter-2

$$\therefore P = W_1 + W_2 \quad \text{(or) total Average Power} \quad P = W_1 + W_2$$

Case (b) :- Load - Delta connected :-

$$V_1 + V_2 + V_3 = 0$$

$$\text{(or)} \quad V_1 = -(V_2 + V_3)$$

$$\therefore P = V_1 \cdot i_1 + V_2 \cdot i_2 + V_3 \cdot i_3$$

$$= -(V_2 + V_3) \cdot i_1 + V_2 \cdot i_2 + V_3 \cdot i_3$$

$$P = -V_3 (i_1 - i_3) + V_2 (i_2 - i_1)$$

$-V_3$ = Instantaneous potential difference across the voltage coil of Wattmeter-1

$$\therefore \frac{W_2 - W_1}{W_2 + W_1} = \frac{\cancel{\sqrt{3}} V_L \cdot I_L \cdot \sin \phi}{\sqrt{3} \cdot V_L \cdot I_L \cdot \cos \phi}$$

$$\sqrt{3} \cdot (W_2 - W_1) = V_L \cdot \sqrt{3} \cdot V_L \cdot I_L \cdot \sin \phi$$

$$\therefore \frac{\sqrt{3} (W_2 - W_1)}{(W_1 + W_2)} = \tan \phi$$

$$\tan \phi = \sqrt{3} \frac{(W_2 - W_1)}{(W_2 + W_1)}$$

$$W_1 + W_2 = \text{Total Active Power} = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos \phi$$

$$W_1 = V_L \cdot I_L \cdot \cos(30^\circ + \phi), \quad W_2 = V_L \cdot I_L \cdot \cos(30^\circ - \phi)$$

$$W_2 - W_1 = \text{Reactive Power} = \sqrt{3} \cdot V_L \cdot I_L \cdot \sin \phi$$

(i) $\phi = 0^\circ$, power factor is unity

$$W_1 = W_2 = V_L \cdot I_L \cdot \cos 30^\circ$$

Readings of both Wattmeters are equal

In magnitude

(ii) $\phi = 60^\circ$, power factor is 0.5 and $\phi < 60^\circ > 0.5$

$$W_1 = V_L \cdot I_L \cdot \cos(30^\circ + 60^\circ) = V_L \cdot I_L \cdot \cos 90^\circ = 0$$

$$W_2 = V_L \cdot I_L \cdot \cos(30^\circ - 60^\circ) = \frac{\sqrt{3}}{2} V_L \cdot I_L$$

(iii) $\phi = 90^\circ > \phi > 60^\circ$ | $W_1 = 0$
 $W_2 = \text{Read the total power}$

$$W_2 = +ve, \quad (W_1 = -ve)$$

Power factor < 0.5

(iv) $\phi = 90^\circ$,

$$W_1 = V_L \cdot I_L \cdot \sin 30^\circ$$

$$W_2 = -V_L \cdot I_L \cdot \sin 30^\circ$$

$$W_1 + W_2 = 0$$

* In 2-Wattmeter method, total Reactive power can also be found

$$\therefore \text{Total Reactive power} = \sqrt{3} V_L I_L \sin \phi$$

$$= \sqrt{3} (W_2 - W_1)$$

* power factor calculations:-

(a) $V = 277\sqrt{2} \sin(377t + 30^\circ) \text{ V}$

$i = 5.1\sqrt{2} \sin(377t - 10^\circ) \text{ A}$

$\theta = (30^\circ - (-10^\circ)) = 40^\circ$

$\text{P.F.} = \cos \phi = \cos 40^\circ = 0.766$; $P = 277 \times \cos \phi$

(b) $V = 679 \cdot \sin(377t + 50^\circ) \text{ V}$

$i = 13 \cdot \cos(377t + 10^\circ) \text{ A}$

$\cos x = \sin(x + 90^\circ)$

$i = 13 \cdot \sin(377t + 90^\circ + 10^\circ)$

$i = 13 \cdot \sin(377t + 100^\circ) \text{ A}$ [$\because \cos x = \sin(x + 90^\circ)$]

$\theta = (50^\circ - 100^\circ) = -50^\circ$

$\text{P.F.} = \cos(-50^\circ) = 0.643$

$P = \frac{679}{\sqrt{2}} \times \frac{13}{\sqrt{2}} \times 0.643 = 2.84 \text{ kW}$

(c) $V = -170 \cdot \sin(377t - 30^\circ) \text{ V}$ [$\because -\sin x = \sin(x \pm 180^\circ)$]

$i = 8.1 \cdot \cos(377t + 30^\circ) \text{ A}$ $V = +170 \cdot \sin(377t + 150^\circ)$

$\cos x = \sin(x + 90^\circ)$

$i = 8.1 \sin(377t + 120^\circ) \text{ A}$

$\therefore \theta = (+150^\circ - (-120^\circ)) = (270^\circ)$

$\cos \phi = \cos 270^\circ =$

(d) $V = V_m \cdot \sin \omega t$, $I = I_m \cdot \sin(\omega t - 45^\circ)$

$\theta = (0 - (+45^\circ))$

$\theta = -45^\circ$

$\cos \phi = \cos 45^\circ = \frac{1}{\sqrt{2}} = 0.707$ (lagging)

Problem-1:- The two Wattmeter method is used to measure a power in a three-phase load. The Wattmeters readings are 400W and -35W. Calculate

- (i) Total active power, (ii) power factor, and (iii) Reactive power

$$W_2 = 400W$$

$$W_1 = -35$$

1. Total Active power = $W_1 + W_2 = 400 + (-35) = 365W$

$$2. \tan \phi = \frac{\sqrt{3} [W_2 - W_1]}{W_2 + W_1} = \frac{\sqrt{3} [400 - (-35)]}{400 + (-35)}$$

$$\tan \phi = 2.064$$

$$\phi = 64.15^\circ$$

$$\cos \phi = 0.4359$$

3. Reactive power: $\sqrt{3}(W_2 - W_1) = \sqrt{3} \cdot V_L \cdot I_L \cdot \sin \phi$

$$W_2 - W_1 = V_L \cdot I_L \cdot \sin \phi$$

$$\therefore W_2 - W_1 = 435$$

$$\therefore \text{Reactive power} = \sqrt{3} \times 435 = 753.44 \text{ VAR}$$

Problem-2:- The input power to a three-phase load is 10KW at 0.8 p.f. Two Wattmeters are connected to measure the power, find the individual readings of the Wattmeters

$$W_1 + W_2 = 10 \times 10^3 = 10000 \quad \text{--- (1)}$$

$$\phi = \cos^{-1}(0.8) = 36.87^\circ$$

$$\tan \phi = 0.75 = \frac{\sqrt{3} [W_2 - W_1]}{[W_2 + W_1]}$$

$$0.75 [W_2 + W_1] = \sqrt{3} W_2 - \sqrt{3} W_1$$

$$\frac{0.75}{\sqrt{3}} [W_2 + W_1] = W_2 - W_1$$

$$0.433 W_2 + 0.433 W_1 = W_2 - W_1$$

$$0.57 \quad 4300 = W_2 - W_1 \quad \text{--- (2)}$$

$$W_2 = 7.165 \text{ kW}$$

$$W_1 = 2.835 \text{ kW}$$

problem-3:- The readings are -3000W and 8000W, load capacitive

$$(1) \text{ Input power} = W_1 + W_2 = -3000 + 8000 = 5000 \text{ W}$$

$$(2) \tan \phi = \frac{\sqrt{3} [W_2 - W_1]}{[W_1 + W_2]} = \frac{\sqrt{3} [8000 - (-3000)]}{[8000 + (-3000)]} = 3.81$$

$$(3) \phi = 75.29^\circ (\text{lead}); \cos \phi = 0.25$$

problem-4:- $I_L = 17 \text{ A}$, $V_L = 440$, Wattmeter reading = 4488 VAR

$$\cos \phi = 0.8$$


✓ problem-5:- The power consumed in a three phase balanced star connected load is 2kW at a power factor of 0.8 lagging. The supply voltage is 400V, 50 Hz. calculate the resistance and reactance of each phase

∴ Power consumed = 2 kW

$$W_1 + W_2 = 2 \times 10^3 = \sqrt{3} V_L \cdot I_L \cdot \cos \phi$$

$$I_L = \frac{2000}{\sqrt{3} \times 400 \times 0.8} = 3.6 \text{ A}$$
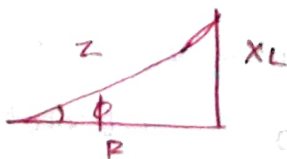
$$\therefore Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{400}{\frac{\sqrt{3}}{3.6}} = 64.15 \text{ A}$$



$$\therefore \cos \phi = \frac{R}{Z}; \quad R = Z \cdot \cos \phi$$
$$= 64.15 \times 0.8 = 51.32 \text{ } \Omega$$

$$\sin \phi = \frac{X_L}{Z}; \quad X_{ph} = Z \cdot \sin \phi$$
$$= 64.15 \times 0.6 = 38.5 \text{ } \Omega$$

Problem-6:- Two wattmeters to measure power 5 kW, P.f - unity. If the p.f - changed to 0.707 lagging, calculate total input power, calculate the readings of two wattmeters

$$W_1 + W_2 = 10 \text{ kW} \quad \text{--- (1)}$$

$$\tan \theta = \frac{\sqrt{3} [W_2 - W_1]}{[W_1 + W_2]} \quad \cos \phi = 0.707$$

$$\phi = 45^\circ$$

$$W_2 - W_1 = \frac{10}{\sqrt{3}} = 5.773 \text{ kW} \quad \text{--- (2)}$$

$$W_2 = 7.886 \text{ kW}$$

$$W_1 = 2.113 \text{ kW}$$

Problem-7:- The input power to a 1.6 kV, 50 Hz three-phase motor is measured by using two wattmeters method. The motor is running at full-load and full-load efficiency is 86%. The readings are 255 kW and 85 kW, respectively. Determine, (1) Input power, (2) power factor, (3) ^{line} current and (4) output power

$$(1) \text{ Input power} = W_1 + W_2 = 340 \text{ kW}$$

$$(2) \tan \theta = \frac{\sqrt{3} [W_2 - W_1]}{[W_2 + W_1]} = 0.866$$

$$\cos \phi = 0.756 \text{ (lag)}$$

(3) Line current:-

$$1.6 \times 10^3 = V_L \cdot I_L \cdot \cos \phi = W_1 + W_2$$

$$I_L = \frac{1.6 \times 10^3 (W_1 + W_2)}{\sqrt{3} \cdot V_L \cdot \cos \phi}$$

$$= 162.28 \text{ A}$$

(4) Output power:-

$$\text{Output} = \text{Input} \times \text{Efficiency}$$

$$= 340 \times 0.86 = 292.4 \text{ kW}$$