

Problem-3; $R = 15 \Omega$, $L = 0.2 \text{ H}$, $C = 3 \mu\text{F}$, $V = 400 \text{ V}$, $\omega = 50 \text{ rad/s}$

UNIT-V

Analysing Three-Phase circuits


* Generation of 3-phase voltage :-

→ The equations for the instantaneous voltages of 3-phases are given below,

$$e_{RR'} = E_m \sin \omega t \quad \text{--- (1)}$$


$$e_{YY'} = E_m \sin(\omega t - 120^\circ) \quad \text{--- (2)}$$
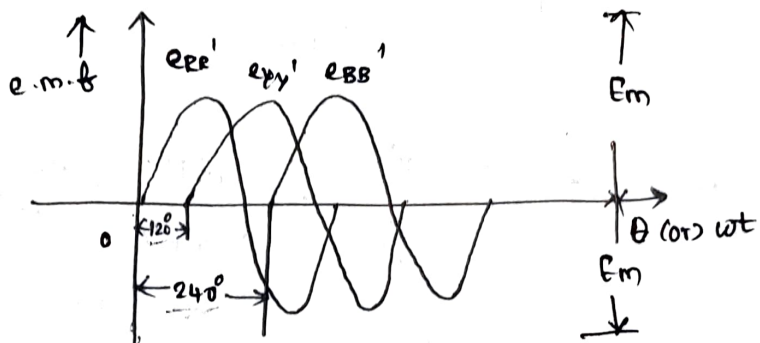
$$e_{BB'} = E_m \sin(\omega t - 240^\circ) \quad \text{--- (3)}$$



$$\therefore E_{r.m.s} = \frac{E_m}{\sqrt{2}}$$

Voltage	Polar form	Rectangular form
E_R	$E \angle 0^\circ$	$E(1 + j0)$
E_Y	$E \angle -120^\circ$	$E(-0.5 - j0.866)$
E_B	$E \angle 120^\circ$	$E(-0.5 + j0.866)$

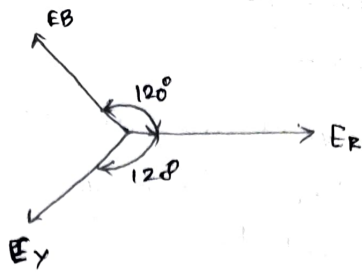

$$\therefore E_R + E_Y + E_B = 0$$

* phase Sequence:-

* The order in which the Alternating quantities attain their maximum values is called the "phase sequence"

→ RYB - Positive Sequence

→ RBY - Negative Sequence

* Interconnection of the phases:-

* The three phases are interconnected to

(i) Achieve the economy

(ii) Reduce the number of conductors and space

(iii) reduce the complexity of the circuit


* There are two types of interconnection.

They are,

(i) star (or) Wye (Y) connection

(ii) Delta (or) (Δ) mesh connection

(i) star (or) Wye (Y) connection:-

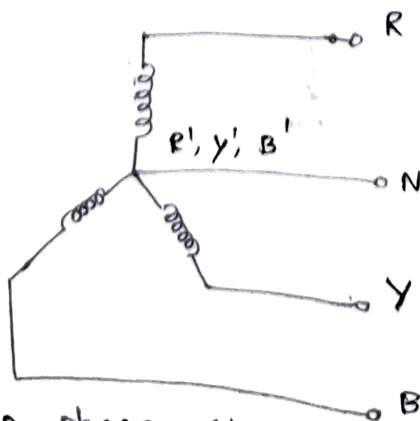

(a) 3-phase star connection

(a) Line voltage and phase voltage in Star-system:-

* The voltage across each coil is called "phase voltage" and it is denoted by E_p ^{(or) E_ϕ} . It is also the voltage between each line and neutral



$$|E_{RN}| = |E_{YN}| = |E_{BN}| = |E_\phi|$$

$$E_{RN} = E_\phi \angle 0^\circ$$

$$E_{YN} = E_\phi \angle 120^\circ$$

$$E_{BN} = E_\phi \angle 240^\circ$$

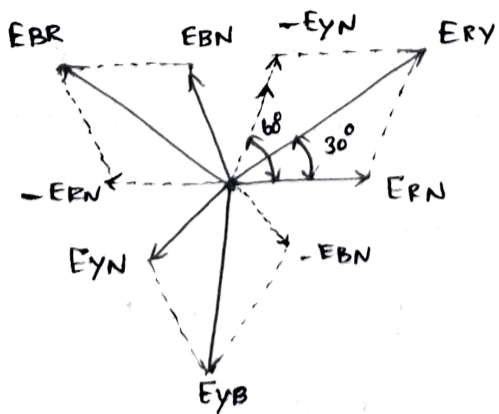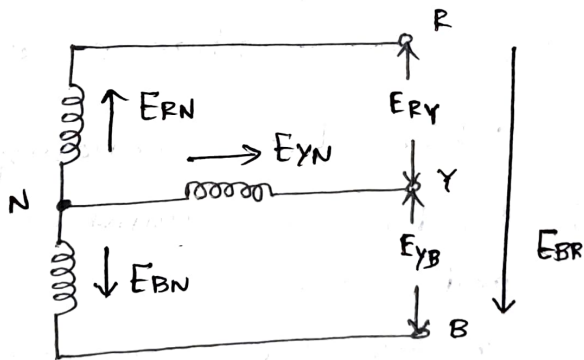* The phase and line voltage in star-connection is given by,



(b) Relation between E_L and E_ϕ in balanced 3-phase system:

1. $E_{RY} = E_{RN} - E_{YN}$

$$= E_\phi \angle 0^\circ - E_\phi \angle -120^\circ$$

$$= \sqrt{3} \cdot E_\phi$$

$$E_{RY} = 440 \angle 30^\circ (V)$$

$$E_{YB} = 440 \angle -90^\circ (V)$$

$$E_{BR} = 440 \angle 150^\circ (V)$$

2. $E_{YB} = E_{YN} - E_{BN} = E_\phi \angle -120^\circ - E_\phi \angle 120^\circ$

$$= \sqrt{3} E_\phi \angle -90^\circ$$

3. $E_{BR} = E_{BN} - E_{RN}$

$$= E_\phi \angle 120^\circ - E_\phi \angle 0^\circ$$

$$= \sqrt{3} E_\phi \angle 150^\circ$$

$\therefore E_L = \sqrt{3} E_\phi$

$I_L = I_{ph}$



* Three-phase power, $P = \sqrt{3} V_L \cdot I_L \cdot \cos\phi$

$$E_{RY} = E_R - E_Y$$

$$E_{YB} = E_Y - E_B$$

$$E_{BR} = E_B - E_R$$

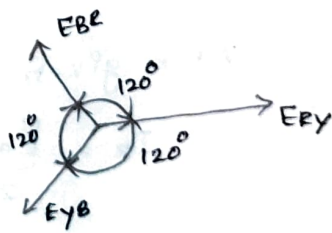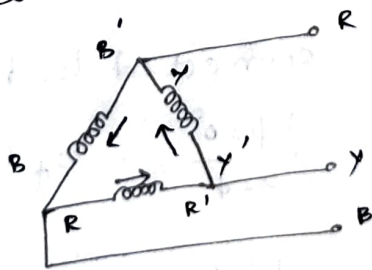(19) Delta connection: - (or) mesh-connection:



$$|E_{RY}| = |E_{YB}| = |E_{BR}| = E_L = E_\phi \quad \text{--- (1)}$$

$$E_{RY} = E_\phi \angle 0^\circ = E_\phi [1 + j0]$$


$$E_{YB} = E_\phi \angle -120^\circ = E_\phi \left[-0.5 - j \frac{\sqrt{3}}{2} \right]$$

$$E_{BR} = E_\phi \angle 120^\circ = E_\phi \left[-0.5 + j \frac{\sqrt{3}}{2} \right]$$

* The phasor sum of line voltages,

$$= E_{RY} + E_{YB} + E_{BR} = 0$$

* Balanced star-connected load:

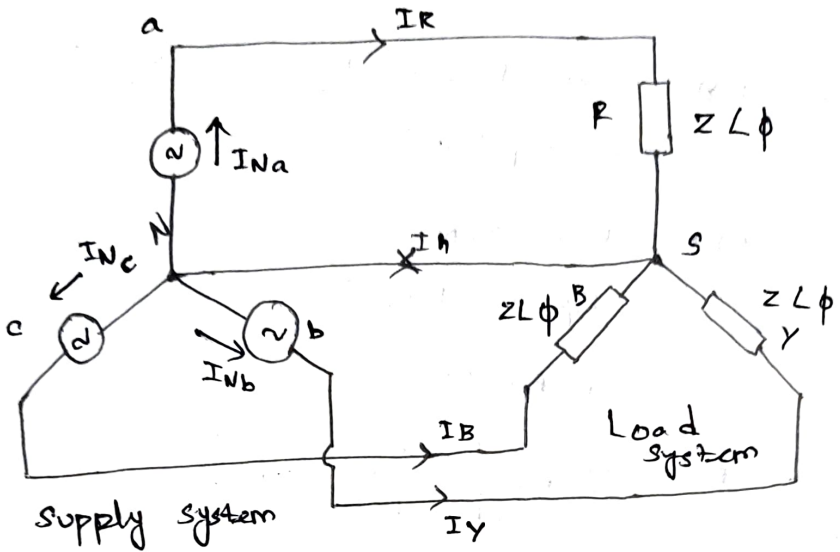

* In 3-phase, 4-wire system, the neutral point-N of the supply is connected.

$$I_{Na} = I_R = I_{RS}$$

$$I_{Nb} = I_Y = I_{YS}$$

$$I_{Nc} = I_B = I_{BS}$$

For star-connection, $I_L = I_\phi$

* For given star-connected load,

$$I_R = \frac{E_{aN}}{Z} = \frac{E_\phi \angle 0^\circ}{Z \angle \phi} = I_\phi \angle \phi$$

$$I_Y = \frac{E_{bN}}{Z} = \frac{E_\phi \angle -120^\circ}{Z \angle \phi} = I_\phi \angle -\phi - 120^\circ$$


$$I_B = \frac{E_{cN}}{Z} = \frac{E_\phi \angle 120^\circ}{Z \angle \phi} = I_\phi \angle -\phi + 120^\circ$$

* By applying, -KCL at star point-S,

$$I_N = I_R + I_Y + I_B$$


In a balanced system, $I_N = 0$

$$\therefore I_R + I_Y + I_B = 0$$

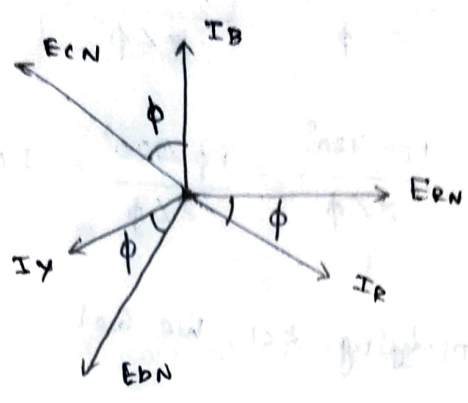


Phasor diagram

* Balanced Delta connected load:-

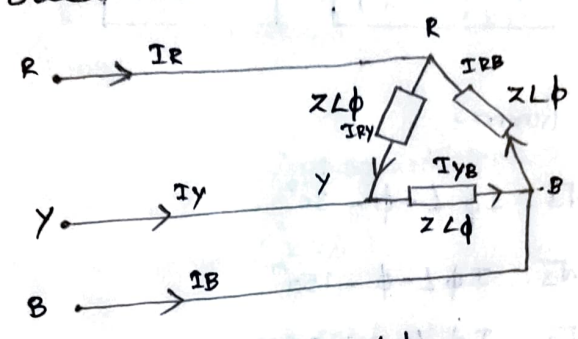

\therefore Load, $Z = ZL\phi$

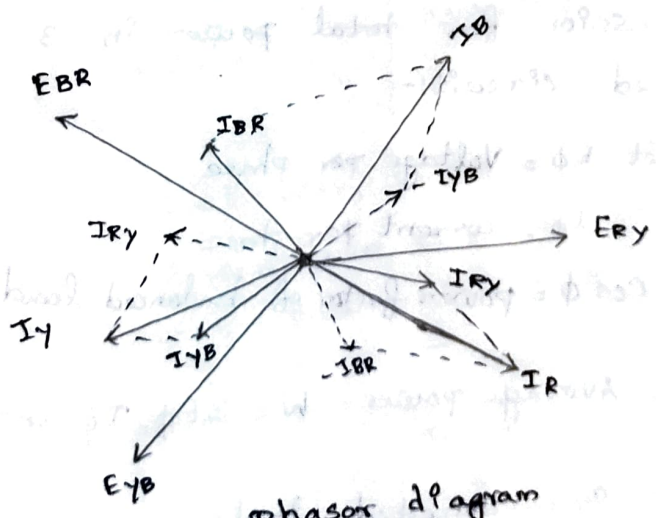

Phasor diagram

* Assume the phase sequence to be RYB.
Taking E_{RY} as reference

$$I_{RY} = \frac{E_{RY} \angle 0^\circ}{Z \angle \phi} = \frac{E \phi \angle -\phi}{Z} = I \phi \angle -\phi$$

neutral

$\phi - 120^\circ$

$\phi + 120^\circ$

t - S,

PAPER LID.

$$\therefore I_{YB} = \frac{E_{YB} \angle -120^\circ}{Z \angle \phi} = \frac{E \phi \angle -120^\circ}{Z \angle \phi} = I \phi \angle -\phi - 120^\circ$$

$$I_{BR} = \frac{E_{BR} \angle 120^\circ}{Z \angle \phi} = \frac{E \phi \angle 120^\circ}{Z \angle \phi} = I \phi \angle -\phi + 120^\circ$$

\therefore By Applying - KCL, We Get,

$$I_R = I_{RY} - I_{BR} = I_{RY} + (-I_{BR})$$

$$\boxed{\therefore I_L = \sqrt{3} I \phi}$$

$$\boxed{V_L = V_{ph}}$$

\therefore In polar form,

$$I_R = \sqrt{3} \cdot I \phi \angle -\phi - 30^\circ$$

$$I_Y = \sqrt{3} \cdot I \phi \angle -\phi - 150^\circ$$

$$I_B = \sqrt{3} \cdot I \phi \angle -\phi + 90^\circ$$

* Expression for total power in 3-phase Balanced circuit:-

Let $E \phi$ = Voltage per phase

$I \phi$ = current per phase

$\cos \phi$ = power factor of balanced load

$$\therefore \text{Total Average Power} = W = 3 \cdot E \phi \cdot I \phi \cdot \cos \phi$$

Case - 1:- Star-connected load:-

$$\text{Let, } \boxed{E_L = \frac{E \phi}{\sqrt{3}}}$$

$$\rightarrow E \phi = \frac{E_L}{\sqrt{3}}$$

$$\boxed{I_L = I \phi}$$

$$\therefore W = 3 \cdot \frac{E_L}{\sqrt{3}} \cdot I_L \cdot \cos \phi = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos \phi$$

Case-2:- Delta-connected load:-

Let, $E_L = E_\phi$ $I_L = \sqrt{3} \cdot I_\phi$

$\therefore W = 3 \cdot E_\phi \cdot I_\phi \cdot \cos \phi$


$W = 3 \cdot E_L \cdot \frac{I_L}{\sqrt{3}} \cdot \cos \phi$

$\therefore W = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos \phi$

$\frac{W}{1000}; \quad \frac{W}{1000} = \frac{\sqrt{3} \cdot V_L \cdot I_L \cdot \cos \phi}{1000}$

$\frac{W}{1000}$ - denoted in ("kW")

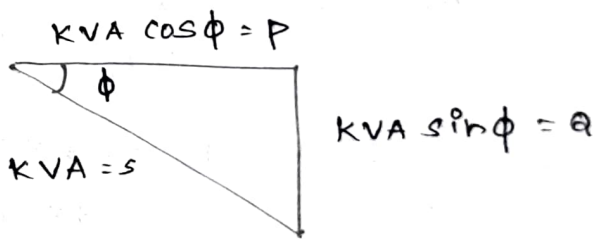$\frac{\sqrt{3} \cdot V_L \cdot I_L}{1000}$ - Apparent power and measured in -
 -kV amperes ("kVA")



\therefore Real power, $P = V \cdot I \cdot \cos \phi$ (kW)

Apparent power, $S = V \cdot I$ (kVA)

Reactive power = $V \cdot I \cdot \sin \phi$

Sequence - ABC:-



$V_{AB} = V_L \angle 120^\circ$

$V_{BC} = V_L \angle 0^\circ$

$V_{CA} = V_L \angle 240^\circ$

$V_{AN} = \frac{V_L}{\sqrt{3}} \angle 90^\circ$

$V_{BN} = \frac{V_L}{\sqrt{3}} \angle -30^\circ$

$V_{CN} = \frac{V_L}{\sqrt{3}} \angle -150^\circ$



$-30^\circ \angle 120^\circ$

$V_{AB} = V_L \angle 240^\circ$

$V_{BC} = V_L \angle 0^\circ$

$V_{CA} = V_L \angle 120^\circ$

$V_{AN} = \frac{V_L}{\sqrt{3}} \angle -90^\circ$

$V_{BN} = \frac{V_L}{\sqrt{3}} \angle 30^\circ$

$V_{CN} = \frac{V_L}{\sqrt{3}} \angle 150^\circ$

Problem-1:- A balanced star-connected load of $(8+j6) \Omega$ per phase is connected to a 3-phase, 50 Hz supply. Find the line current, power factor, power, reactive volt Amperes and total volt Amperes

$$V_L = 230 \text{ V}$$

$$\therefore V_\phi = \frac{V_L}{\sqrt{3}} = \frac{230}{\sqrt{3}} = 133 \text{ V}$$

$$\text{Impedance, } Z = 8 + j6 \\ = 10 \angle 36.9^\circ$$

$$|Z_\phi| = 10, \quad \phi = 36.9^\circ$$

$$(i) \text{ for star, } I_L = I_\phi = \frac{|V_\phi|}{|Z_\phi|} = \frac{133}{10} = 13.3 \text{ A}$$

$$(ii) \text{ power factor} = \cos \phi = \cos 36.9^\circ = 0.8 \text{ lag}$$

$$\text{or } \cos \phi = \frac{|R_\phi|}{|Z_\phi|} = \frac{8}{10} = 0.8$$

$$(iii) \text{ Apparent power} = \sqrt{3} \cdot V_L \cdot I_L = \sqrt{3} \times \sqrt{3} \cdot V_\phi \times I_\phi \\ = 3 \times V_\phi \times I_\phi \\ = \sqrt{3} \times 230 \times 13.3 = 5298 \text{ VA}$$

$$(iv) \text{ Real power} = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos \phi = 5298 \times 0.8 = 4239 \text{ W}$$

$$(v) \text{ Reactive power} = \sqrt{3} \times V_L \times I_L \times \sin \phi \\ = 5298 \times 0.6 = 3179 \text{ VAR}$$

Problem-2:- A three-phase, four-wire, ^{CBA}ABC-system, with effective line voltage of 120V, has three impedance of $20 \angle -30^\circ \Omega$ in Y-connection. Determine the line currents

$$V_L = 120V, \quad Z_\phi = 20 \angle -30^\circ$$


$$V_\phi = \frac{V_L}{\sqrt{3}} = \frac{120}{\sqrt{3}} = 69.28V$$

$$\therefore I_L = I_\phi = \frac{V_\phi}{Z_\phi}$$

\therefore Effective line voltage, = 120V

$$\therefore V_L \text{ Maximum line voltage} = 120 \times \sqrt{2} = 169.70V$$
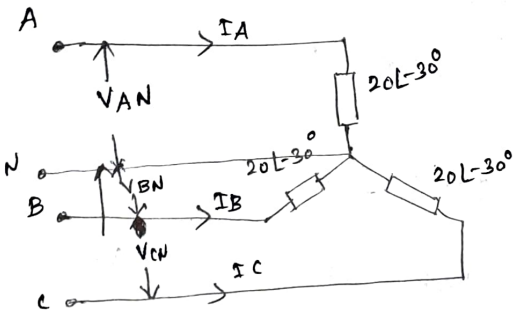
$$\therefore V_\phi = \frac{V_L}{\sqrt{3}} = \frac{169.70}{\sqrt{3}} = 97.97V \approx 98.0V$$



$$\therefore V_{AN} = 98.0 \angle -90^\circ, \quad V_{BN} = 98.0 \angle 30^\circ, \quad V_{CN} = 98.0 \angle 150^\circ$$


$$\therefore I_A = \frac{V_{AN}}{Z} = \frac{98.0 \angle -90^\circ}{20 \angle -30^\circ} = 4.90 \angle -60^\circ \text{ A}$$

$$I_B = \frac{V_{BN}}{Z} = \frac{98.0 \angle 30^\circ}{20 \angle -30^\circ} = 4.90 \angle 60^\circ \text{ A}$$

$$I_C = \frac{V_{CN}}{Z} = \frac{98.0 \angle 150^\circ}{20 \angle -30^\circ} = 4.90 \angle 180^\circ \text{ A}$$

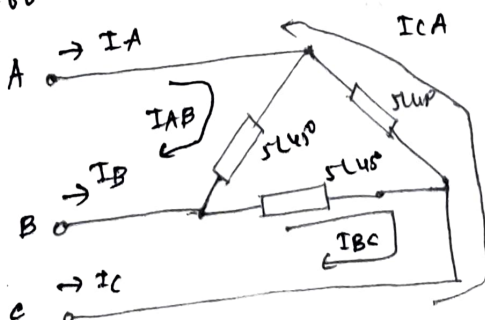Problem-2:- A three-phase, three-wire ABC system, with an effective line voltage of 120V, has three impedances $5.0 \angle 45^\circ$. Determine line currents

$$V_L = V_{\text{eff}} \times \sqrt{2} = 169.70V; \quad V_L = V_\phi = 169.70V$$



$$I_A = I_{AB} + I_{BC}$$

$$= \frac{169.70 \angle 0^\circ}{5 \angle 45^\circ} + \frac{169.70 \angle -120^\circ}{5 \angle 45^\circ}$$

$$= 33.94 \angle -45^\circ + 33.94 \angle -165^\circ$$

$$= 58.7 \angle 45^\circ (A)$$

$$V_{BC} = 169.70 \angle 0^\circ$$

$$V_{AB} = 169.70 \angle 120^\circ$$

$$V_{BA} = 169.70 \angle 240^\circ$$

$$I_B = I_{BC} + I_{CA}$$

$$= 58.7 \angle -75^\circ (A)$$

$$I_C = I_{AB} + I_{BC}$$

$$= 58.7 \angle 165^\circ (A)$$

$$I_A = I_{AB} - I_{CA}$$

$$I_B = I_{AB} - I_{BC} \quad I_{BC} - I_{AB}$$

$$I_C = I_{CA} - I_{BC}$$

$$I_{AB} = \frac{169.70 \angle 0^\circ}{5 \angle 45^\circ} = 33.94 \angle -45^\circ$$

$$I_{BC} = \frac{169.70 \angle -120^\circ}{5 \angle 45^\circ} = 33.94 \angle -165^\circ$$


$$I_{CA} = \frac{169.70 \angle -240^\circ}{5 \angle 45^\circ} = 33.94 \angle -285^\circ$$

$$I_A = 58.785 \angle -75^\circ$$

$$I_B = 58.785 \angle 165^\circ$$

$$I_C = 58.785 \angle 45^\circ$$

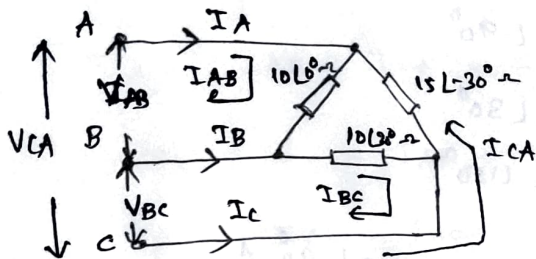Problem-3:- A three-phase, 4-wire, ~~CBA~~ ABC system, with effective line voltage of ^{339.4} 120V, has impedances $Z_{AB} = 10 \angle 0^\circ \Omega$, $Z_{BC} = 10 \angle 30^\circ \Omega$, $Z_{CA} = 15 \angle -30^\circ \Omega$. Obtain phase and line currents.



$$V_{AB} = 339.4 \angle 120^\circ$$

$$V_{BC} = 339.4 \angle 0^\circ$$

$$V_{CA} = 339.4 \angle 240^\circ$$

$$\therefore V_L = V_\phi = 339.4 \text{ V}$$

$$I_{AB} = \frac{339.4 \angle 120^\circ}{10 \angle 0^\circ} = 33.94 \angle 120^\circ \text{ A}$$

$$I_{BC} = \frac{339.4 \angle 0^\circ}{10 \angle 30^\circ} = 33.94 \angle -30^\circ \text{ A}$$


$$I_{CA} = \frac{339.4 \angle 240^\circ}{15 \angle -30^\circ} = 22.63 \angle 270^\circ \text{ A}$$

$$\therefore I_A = I_{AB} - I_{CA} = 54.72 \angle 108.1^\circ \text{ A}$$

$$I_B = I_{BC} - I_{AB} = 65.56 \angle -45^\circ \text{ A}$$

$$I_C = I_{CA} - I_{BC} = 29.93 \angle -169.1^\circ \text{ A}$$

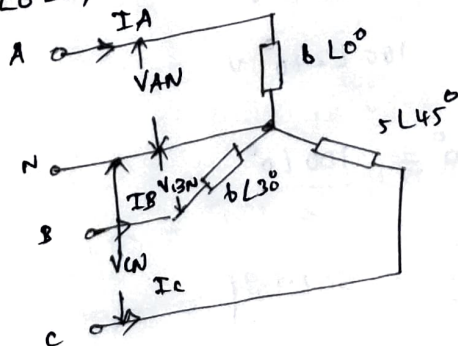Problem-4:- A three-phase, four-wire, 150V, CBA-system has Y-connected, with impedances $Z_A = 6 \angle 0^\circ \Omega$, $Z_B = 6 \angle 30^\circ \Omega$, $Z_C = 5 \angle 45^\circ \Omega$. Obtain all line currents.



$$V_{AB} = 120 \angle 240^\circ \text{ V}$$

$$V_{BC} = 120 \angle 0^\circ \text{ V}$$

$$V_{CA} = 120 \angle 120^\circ \text{ V}$$

$$V_{AN} = 86.6 \angle -90^\circ$$

$$V_{BN} = 86.6 \angle 30^\circ$$

$$V_{CN} = 86.6 \angle 150^\circ$$

$$\therefore I_A = \frac{V_{AN}}{Z_A} = 14.43 \angle -90^\circ \text{ A}$$

$$I_B = \frac{V_{BN}}{Z_B} = 14.43 \angle 0^\circ \text{ A}$$

$$I_C = \frac{V_{CN}}{Z_C} = 17.32 \angle 105^\circ \text{ A}$$

Problem-4:- A balanced Δ -connected load has one phase current $I_{BC} = 2 \angle -90^\circ \text{ A}$. Find the other phase currents and the three line currents if the system is an ABC system. If the line voltage is 100V, what is the load impedance.

$$I_{BC} = 2 \angle -90^\circ$$

$$\therefore I_{BC} = \frac{V_{BC}}{Z}$$

$$V_{AB} = 100 \angle 120^\circ \text{ V}$$

$$V_{BC} = 100 \angle 0^\circ \text{ V}$$

$$V_{CA} = 100 \angle 240^\circ \text{ V}$$

$$2 \angle -90^\circ = \frac{100 \angle 0^\circ}{Z}$$

$$\boxed{Z = 50 \angle 90^\circ}$$

$$\therefore I_{AB} = \frac{V_{AB}}{Z} = \frac{100 \angle 120^\circ}{50 \angle 90^\circ} = 2 \angle 30^\circ$$


$$\therefore I_{CA} = \frac{V_{CA}}{Z} = \frac{100 \angle 240^\circ}{50 \angle 90^\circ} = 2 \angle 150^\circ$$

$$\therefore I_A = I_{AB} - I_{CA} = 2 \angle 30^\circ - 2 \angle 150^\circ = 2\sqrt{3} \text{ A}$$

$$I_B = I_{BC} - I_{AB} = 2 \angle -90^\circ - 2 \angle 30^\circ = 2\sqrt{3} \angle -120^\circ \text{ A}$$

$$I_C = I_{CA} - I_{BC} = 2 \angle 150^\circ - 2 \angle -90^\circ = 2\sqrt{3} \angle +120^\circ \text{ A}$$

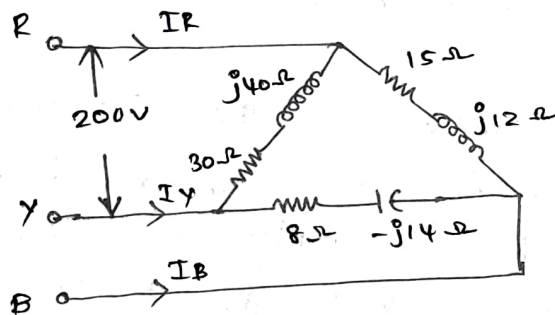Problem-5:- Determine the line currents for the unbalanced delta connected load shown below. Phase Sequence - RYB



$$V_{RY} = 200 \angle 120^\circ \text{ V}$$

$$V_{YB} = 200 \angle 0^\circ \text{ V}$$

$$V_{RB} = 200 \angle 240^\circ \text{ V}$$

$$I_{RY} = \frac{V_{RY}}{Z} = \frac{200 \angle 120^\circ}{30 + j40} = 4 \angle 66.866^\circ \text{ A}$$

$$I_{YB} = \frac{V_{YB}}{Z} = \frac{200 \angle 0^\circ}{8 - j14} = 12.40 \angle 60.25^\circ \text{ A}$$


$$I_{RB} = \frac{V_{RB}}{Z} = \frac{200 \angle 240^\circ}{15 + j12} = 10.41 \angle -158.65^\circ \text{ A}$$

$$\therefore I_R = I_{RY} - I_{RB} = 14.07 \angle 35.01^\circ \text{ A}$$

$$I_Y = I_{YB} - I_{RY} = 8.43 \angle 57.12^\circ \text{ A}$$

$$I_B = I_{BA} - I_{YB} = 21.51 \angle -137.43^\circ \text{ A}$$

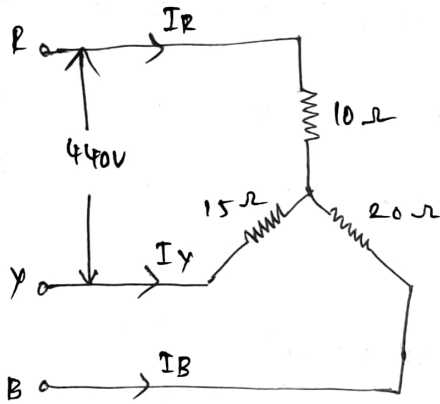Problem-6:- A unbalanced, star-connected load is supplied from a 3 ϕ , 440V, symmetrical system. Determine the line currents and power input to the circuit. Assume -RYB sequence. Take V_{Rn} as reference.



$$P = I^2 R = 13418 \text{ W}$$

Problem-7:- Determine the line currents and the total power for the unbalanced- Δ connected load. A 3-phase supply, with effective line voltage of 240V is given to the circuit

