

#### 4.1.6 Quality factor ( $Q$ ) and its effect on bandwidth

The Quality factor  $Q$  is the ratio of the reactive power in the inductor or capacitor to the true power in the resistance in series with the coil or capacitor.

$$\text{The quality factor } Q = 2\pi \times \frac{\text{maximum energy stored}}{\text{energy dissipated per cycle}}$$

In an inductor, the maximum energy stored is given by

$$= \frac{1}{2} LI^2$$

$$\begin{aligned} \text{Energy dissipated per cycle} &= \left( \frac{I}{\sqrt{2}} \right)^2 R \times T \\ &= \frac{I^2 RT}{2} \end{aligned}$$

$$\text{Quality factor of the coil } Q = 2\pi \times \frac{\frac{1}{2} LI^2}{\frac{I^2 R}{2} \times \frac{1}{f}}$$

$$Q = \frac{2\pi fL}{R} = \frac{\omega L}{R}$$

In a capacitor, the maximum energy stored is given by  $= \frac{1}{2} CV^2$

$$\text{The energy dissipated per cycle} = \left( \frac{I}{\sqrt{2}} \right)^2 RT$$

Quality factor of the capacitor is

$$\frac{2\pi \times \frac{1}{2} C \left( \frac{I}{\omega C} \right)^2}{\frac{I^2}{2} R \times \frac{1}{f}} = \frac{1}{\omega CR}$$

$\therefore$  In a series circuit Quality factor

$$Q = \frac{\omega L}{R} = \frac{1}{\omega CR}$$

#### 4.1.7 Magnification in resonance

If in a series  $RLC$  circuit, the voltage applied is  $V$ , and the current at resonance is  $I$ , then the voltage across inductor  $L$  is  $V_L = IX_L = \left( \frac{V}{R} \right) \omega_r L$

Similarly, the voltage across capacitor  $C$

$$V_c = IX_c = \frac{V}{R\omega_r C}$$

$$Q = \frac{1}{\omega_r CR} = \frac{\omega_r L}{R}$$

where  $\omega_r$  is the frequency at resonance.


Therefore  $V_L = VQ$

$V_C = VQ$

The ratio of voltage across either  $L$  or  $C$  to the voltage applied at resonance is defined as magnification.

Magnification  $Q = \frac{V_L}{V}$  (or)  $\frac{V_c}{V}$

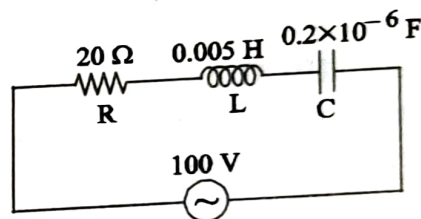**EXAMPLE 12:** A series RLC circuit has  $R = 20 \Omega$ ,  $L = 0.005 H$  and  $C = 0.2 \times 10^{-6} F$ . It is fed from a 100 V variable frequency source. Find (i) frequency at which current is maximum (ii) impedance at this frequency and (iii) voltage across inductor at this frequency.



(AU/EEE - Dec 2005)

**HOTS**

**Solution :**

(i) Maximum current

$$I_{\max} = \frac{V}{R} = \frac{100}{20} = 5 A$$

Frequency at which current is maximum

$$f_r = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{0.005 \times 0.2 \times 10^{-6}}} = 5033 \text{ Hz}$$

$f_r = 5033 \text{ Hz}$

(ii) Impedance at this frequency

$Z = R = 20 \Omega$

(iii) Voltage across inductor at this frequency  $V_L = IX_L$

$$X_L = 2\pi fL = 2 \times \pi \times 5033 \times 0.005 = 158.11 \Omega$$

$$V_L = 5 \times 158.11 = 790.55 \text{ V}$$

$$V_L = 790.55 \text{ V}$$

**EXAMPLE 13:** A series RLC circuit consists of  $R = 100 \Omega$ ,  $L = 0.02 \text{ H}$  and  $C = 0.02 \mu\text{F}$ . Calculate the frequency of resonance.


**LOTS**

(AU/EEE - Dec 2005)

**Solution :**

$$\text{Resonant frequency } f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.02 \times 0.02 \times 10^{-6}}}$$

$$f_r = 7957.74 \text{ Hz}$$

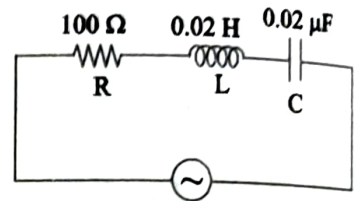

**EXAMPLE 14:** A series RLC circuit has  $R = 50 \Omega$ ,  $L = 0.01 \text{ H}$  and  $C = 0.04 \mu\text{F}$ . Find resonant frequency, circuit impedance and current under resonance condition, voltage across inductor under resonance when system voltage is 100 V.

**LOTS**

(AU/ECE - Dec 2005)

**Solution :**

$$\text{Resonant frequency } f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.01 \times 0.04 \times 10^{-6}}}$$

$$f_r = 7957.74 \text{ Hz}$$

Current under resonance condition


$$I_{\max} = \frac{V}{R} = \frac{100}{50} = 2 \text{ A}$$

Voltage across inductor  $V_L = IX_L$


$$\begin{aligned} X_L &= 2\pi f_r L = 2\pi \times 7957.74 \times 0.01 \\ &= 500 \Omega \end{aligned}$$

$$V_L = 2 \times 500 = 1000 \text{ V}$$

$$V_L = 1000 \text{ V}$$

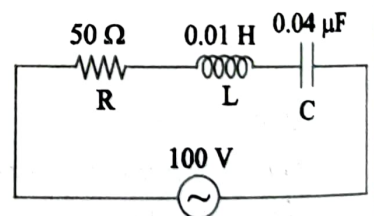

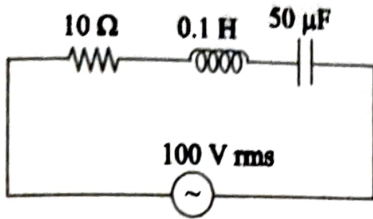**EXAMPLE 15:** For the circuit shown in figure, determine the frequency at which the circuit resonates? Also, find the voltage across the inductor at resonance and the Q-factor of the circuit.



(AU/EEE - Dec 2007)

**HOTS**

**Solution :**

$$\text{Resonant frequency } f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 50 \times 10^{-6}}}$$

$$f_r = 71.18 \text{ Hz}$$

At resonance, the current  $I = \frac{V}{R} = \frac{100}{10} = 10 \text{ A}$

Inductive reactance  $X_L = 2\pi fL = 2\pi \times 71.18 \times 0.1 = 44.72 \Omega$

Voltage across inductor  $V_L = IX_L = 10 \times 44.72$

$$V_L = 447.2 \text{ V}$$

$$Q \text{ factor} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{10} \sqrt{\frac{0.1}{50 \times 10^{-6}}}$$

$$Q = 4.472$$

**EXAMPLE 16:** A series RLC circuit with  $R = 5 \Omega$ ,  $L = 40 \text{ mH}$  and  $C = 1 \mu\text{F}$ . Calculate the Q of the circuit, the separation between half power frequencies, the resonant frequency and the half power frequencies.


(AU/EEE - Dec 2007)

**HOTS**

**Solution :**

$$Q \text{ - factor} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{5} \sqrt{\frac{40 \times 10^{-3}}{1 \times 10^{-6}}}$$

$$Q = 40$$

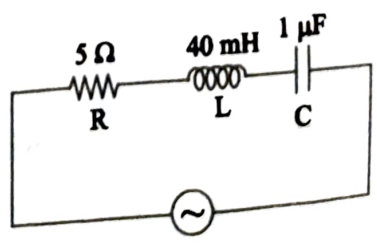



The separation between half power frequencies

$$f_2 - f_1 = \frac{R}{2\pi L} = \frac{5}{2\pi \times 40 \times 10^{-3}} = 20 \text{ Hz}$$

$$f_2 - f_1 = 20 \text{ Hz}$$

Resonant frequency

$$f_r = Q (f_2 - f_1) = 40 \times 20 = 800 \text{ Hz}$$

$$f_r = 800 \text{ Hz}$$

Half power frequencies

$$f_1 = f_r - \frac{R}{4\pi L} = 800 - \frac{5}{4\pi \times 40 \times 10^{-3}}$$


$$= 800 - 9.95 = 790.05 \text{ Hz}$$

$$f_1 = 790.05 \text{ Hz}$$

$$f_2 = f_r + \frac{R}{4\pi L} = 800 + \frac{5}{4\pi \times 40 \times 10^{-3}} = 809.95$$

$$f_2 = 809.95 \text{ Hz}$$

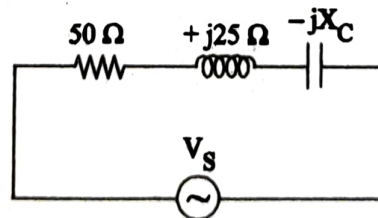**EXAMPLE 17:** For the circuit shown in figure, determine the value of capacitive reactance and impedance at resonance.



(AU/ECE - Dec 2006)

LOTS

**Solution :**

At resonance condition, inductive reactance is equal to capacitive reactance i.e.,

$$X_L = X_C = 25 \Omega$$

$$X_C = 25 \Omega$$

Impedance at resonance

$$Z = R = 50 \Omega$$

**EXAMPLE 18:** A 240 V, 100 Hz ac source supplies a series RLC circuit consisting of a capacitor and a coil. If the coil has 55 m Ω resistance and 7 mH inductance, calculate the value of the capacitor at 100 Hz resonance frequency, the Q - factor and the half power frequencies of the circuit.

**HOTS**

(AU/EEE - Dec 2008)

**Solution :**

$$f_r = 100 \text{ Hz}$$


$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$f_r^2 = \frac{1}{(2\pi)^2 LC}$$

$$C = \frac{1}{f_r^2 L (2\pi)^2}$$

$$= \frac{1}{100^2 \times 7 \times 10^{-3} \times (2\pi)^2} = 3.6186 \times 10^{-4} \text{ F}$$

**C = 361.86 μ F**

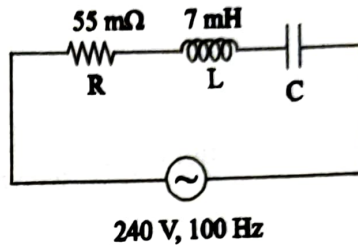

$$Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{55 \times 10^{-3}} \sqrt{\frac{7 \times 10^{-3}}{361.86 \times 10^{-6}}}$$

**Q = 80**

Half power frequencies

$$f_1 = f_r - \frac{R}{4\pi L} = 100 - \frac{55 \times 10^{-3}}{4\pi \times 7 \times 10^{-3}}$$

**f<sub>1</sub> = 99.374 Hz**

$$f_2 = f_r + \frac{R}{4\pi L} = 100 + \frac{55 \times 10^{-3}}{4\pi \times 7 \times 10^{-3}}$$

**f<sub>2</sub> = 100.625 Hz**

**EXAMPLE 19:** An inductive coil having a resistance of  $20 \Omega$  and an inductance of  $0.02 \text{ H}$  is connected in series with  $0.01 \mu\text{F}$  capacitor. Calculate: (a)  $Q$  of the coil (b) Resonant frequency of the circuit.

**LOTS**

(AU/ECE - May 2006)


**Solution :**

$$(a) \quad Q - \text{factor} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{20} \sqrt{\frac{0.02}{0.01 \times 10^{-6}}}$$


$$Q = 70.71$$

$$(b) \quad \text{Resonant frequency } f_r = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{0.02 \times 0.01 \times 10^{-6}}}$$

$$f_r = 11254 \text{ Hz}$$

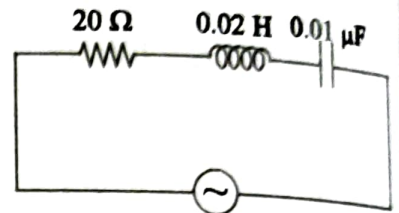

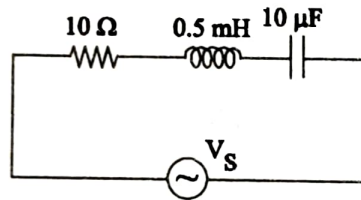**EXAMPLE 20:** Determine the resonant frequency for the circuit.



**LOTS**

(AU/EEE - May 2004)

**Solution :**

$$\text{Resonant frequency } f_r = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{0.5 \times 10^{-3} \times 10 \times 10^{-6}}}$$

$$f_r = 2250 \text{ Hz}$$

**EXAMPLE 21:** A series RLC circuit consists of  $50 \Omega$  resistance,  $0.2 \text{ H}$  inductance and  $10 \mu\text{F}$  capacitance with the applied voltage of  $20 \text{ V}$ . Determine the resonant frequency. Find the  $Q$  factor of the circuit. Compute the lower and upper frequency limits and also find the bandwidth of the circuit.


**HOTS**

(AU, Coimbatore/EEE - Dec. 2010) (AU/EEE - May 2004)

**Solution :**

$$Q - \text{factor} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{50} \sqrt{\frac{0.2}{10 \times 10^{-6}}} = 2.82$$

$$Q = 2.82$$

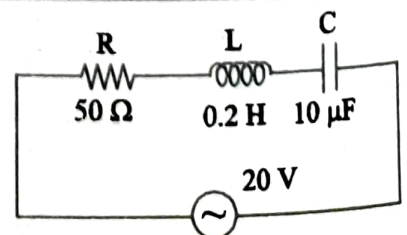

$$\text{Resonant frequency } f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.2 \times 10 \times 10^{-6}}}$$

$$f_r = 112.54 \text{ Hz}$$

$$\text{Lower frequency limit } f_1 = f_r - \frac{R}{4\pi L} = 112.54 - \frac{50}{4\pi \times 0.2}$$

$$f_1 = 92.64 \text{ Hz}$$

$$\text{Upper frequency limit } f_2 = f_r + \frac{R}{4\pi L} = 112.54 + \frac{50}{4\pi \times 0.2}$$

$$f_2 = 132.43 \text{ Hz}$$

$$\text{Bandwidth } BW = f_2 - f_1 = 132.43 - 92.64$$

$$BW = 39.79 \text{ Hz}$$

**EXAMPLE 22:** A coil of inductance 0.75 H and a resistance 40 Ω is a part of a series resonant circuit having a resonant frequency of 160 Hz. If the supply voltage is 230 V, 50 Hz, find (i) current (ii) power factor (iii) voltage across the coil

**HOTS**

(AU/ECE - Dec 2004)

**Solution :**

First find the capacitor value.

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$


$$C = \frac{1}{(2\pi f_r)^2 L} = \frac{1}{(2\pi \times 160)^2 \times 0.75}$$

$$C = 1.32 \mu\text{F}$$

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.75 = 235.62 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 1.32 \times 10^{-6}} = 2411.43 \Omega$$
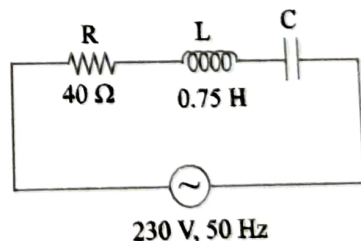
$$\begin{aligned} \text{Impedance } Z &= \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{40^2 + (235.62 - 2411.43)^2} \\ &= 2176.17 \Omega \text{ (capacitive)} \end{aligned}$$





(i) Current

$$I = \frac{V}{Z} = \frac{230}{2176.17}$$

$$I = 0.1056 \text{ A}$$

(ii) Power factor

$$\cos \phi = \frac{R}{Z} = \frac{40}{2176.17}$$

$$\cos \phi = 0.0183 \text{ (leading)}$$

(iii) Impedance of the coil

$$Z_{\text{coil}} = \sqrt{R^2 + X_L^2} = \sqrt{40^2 + 235.62^2} = 239 \Omega$$

Voltage across the coil

$$V_{\text{coil}} = I Z_{\text{coil}} = 0.1056 \times 239$$

$$V_{\text{coil}} = 25.23 \text{ V}$$

**EXAMPLE 23:** A series RLC circuit has  $Q = 75$  and a pass band (between half power frequencies) of 160 Hz. Calculate the resonant frequency and the upper and lower frequencies of the pass band.

**HOTS****(AU/EEE - May 2007)****Solution :**

$$Q = 75$$

$$BW = f_2 - f_1 = 160 \text{ Hz} \quad \dots (i)$$

$$f_r = Q (f_2 - f_1) = 75 \times 160 = 12000 \text{ Hz}$$

$$f_r = 12000 \text{ Hz}$$

We know that  $f_1 f_2 = f_r^2 = (12000)^2$

$$f_1 + f_2 = \sqrt{(f_2 - f_1)^2 + 4 f_1 f_2} = \sqrt{(160)^2 + 4 \times (12000)^2} = 24000 \quad \dots (ii)$$

From equations (i) and (ii)

$$f_2 - f_1 = 160$$

$$f_2 + f_1 = 24000$$

$$2 f_2 = 24160$$

$$f_2 = \frac{24160}{2} = 12080 \text{ Hz}$$

$$f_2 = 12080 \text{ Hz}$$


$$f_2 - f_1 = 160$$

$$\therefore f_1 = 12080 - 160 = 11920 \text{ Hz}$$

$$f_1 = 11920 \text{ Hz}$$

**EXAMPLE 24:** In the circuit shown in figure, a maximum current of 0.1 A flows through the circuit when the capacitor is at  $5 \mu\text{F}$  with a fixed frequency and a voltage of 5V. Determine the frequency at which the circuit resonates, the bandwidth, the quality factor  $Q$  and the value of resistance of resonance frequency.

**HOTS**

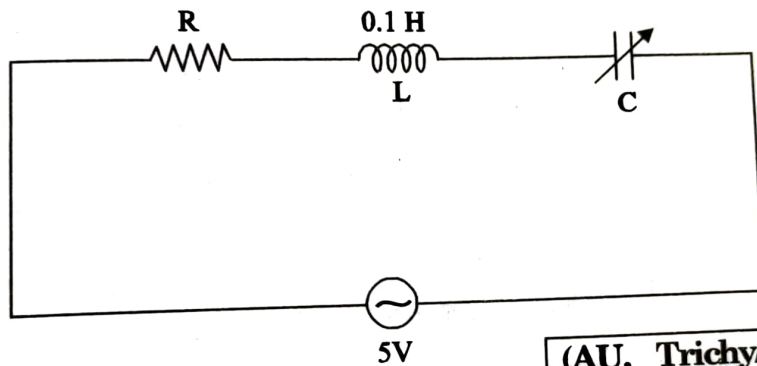

(AU, Trichy/EEE - June 2009)

**Solution :**

At resonance condition,  $Z = R$

$$R = \frac{V}{I_{\max}} = \frac{5}{0.1} = 50 \Omega$$

$$\text{Resonant frequency } f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 5 \times 10^{-6}}} = 225.08 \text{ Hz}$$

$$f_r = 225.08 \text{ Hz}$$

$$\text{Quality factor } Q = \frac{\omega_r L}{R} = \frac{2\pi f_r L}{R} = \frac{2\pi \times 225.08 \times 0.1}{50} = 2.828$$

$$Q = 2.828$$

$$\text{Bandwidth } BW = \frac{f_r}{Q} = \frac{225.08}{2.828} = 79.62 \text{ Hz}$$

$$BW = 79.59 \text{ Hz}$$