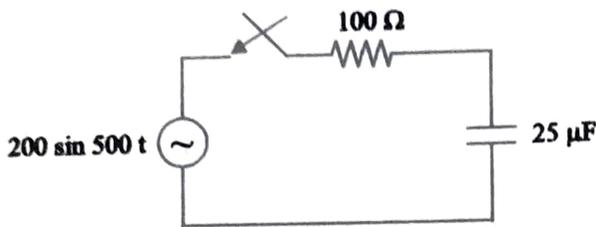


EXAMPLE 31: In the circuit of figure, find the current $i(t)$. Assume initial charge in the capacitor is zero.

HOTS



(AU/EEE - Dec 2007)

Solution :

Applying KVL,

$$100 i + \frac{1}{25 \times 10^{-6}} \int i dt = 200 \sin 500 t$$

Taking Laplace transform on both sides,

$$100 I(s) + 40000 \frac{I(s)}{s} = 200 \frac{500}{s^2 + 500^2}$$

$$I(s) \left[100 + \frac{40000}{s} \right] = \frac{100000}{s^2 + 500^2}$$

$$I(s) = \frac{100000}{\left(100 + \frac{40000}{s} \right) (s^2 + 500^2)}$$

$$I(s) = \frac{1000 s}{(s + 400) (s^2 + 500^2)}$$

$$\frac{1000 s}{(s + 400) (s^2 + 500^2)} = \frac{K_1}{s + 400} + \frac{K_2}{s + j500} + \frac{K_3}{s - j500}$$

$$K_1 = \frac{-400}{41} = -9.76$$

$$K_2 = \frac{5(4 + j5)}{41}$$

$$K_3 = \frac{5(4 - j5)}{41}$$

$$i(t) = -9.76 e^{-400t} + \frac{5}{41} \left[(4 + j5) e^{-j500t} + (4 - j5) e^{j500t} \right]$$

$$i(t) = -9.76 e^{-400t} + \frac{10}{\sqrt{41}} \left[\frac{4}{\sqrt{41}} \cos 500t - \frac{5}{\sqrt{41}} \sin 500t \right]$$

$$i(t) = -9.76 e^{-400t} + 1.562 \sin(500t + 38.7^\circ)$$


$$\text{or } I(s) + \frac{400 I(s)}{s} = \frac{10^3}{s^2 + 500^2}$$

$$(s + 400) I(s) = \frac{10^3 s}{s^2 + 500^2}$$

$$\text{or } I(s) = \frac{10^3 s}{(s + 400) (s^2 + 500^2)}$$

EXAMPLE 32: Determine the current when the switch is closed at a time corresponding to $\phi = 0$ in the circuit shown in figure. The initial charge on the capacitor is 2 coulombs with polarity as shown.

HOTS

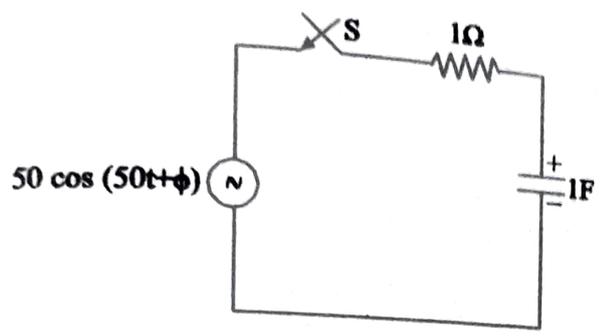

(AU, Trichy/EEE - Dec 2008)

Solution :

Applying Kirchhoff's voltage law,

$$i(t) + \frac{1}{1} \int_{-\infty}^t i dt = 50 \cos(50t)$$

$$i(t) + \int_{-\infty}^0 \frac{dq}{dt} dt + \int_0^t i dt = 50 \cos(50t)$$

Taking Laplace transforms on both sides, we have

$$I(s) + \frac{I(s)}{s} + \frac{q_0}{s} = \frac{50s}{s^2 + 50^2}$$

$$I(s) \left[1 + \frac{1}{s} \right] + \frac{2}{s} = \frac{50s}{s^2 + 50^2}$$

$$I(s) = \left[\frac{50s}{s^2 + 50^2} - \frac{2}{s} \right] \frac{s}{s+1}$$

$$I(s) = \frac{[50s^2 - 2s^2 - 2(50)^2]}{(s^2 + (50)^2)(s+1)}$$

$$I(s) = \frac{48s^2 - 2(50)^2}{(s^2 + (50)^2)(s+1)}$$

By partial fractions,

$$I(s) = \frac{K_1}{(s+j50)} + \frac{K_2}{(s-j50)} + \frac{K_3}{(s+1)}$$

$$K_1 = I(s)(s + j50) \Big|_{s = -j50}$$

$$K_1 = \frac{48s^2 - 2(50)^2}{(s - j50)(s + 1)} \Big|_{s = -j50} \quad K_1 = \frac{1250}{50 + j}$$

$$K_2 = I(s)(s - j50) \Big|_{s = j50}$$

$$K_2 = \frac{48s^2 - 2(50)^2}{(s + j50)(s + 1)} \Big|_{s = j50} \quad K_2 = \frac{1250}{50 - j}$$

$$K_3 = I(s)(s + 1) \Big|_{s = -1}$$

$$= \frac{48s^2 - 2(50)^2}{s^2 + (50)^2} \Big|_{s = -1} \quad K_3 = -1.98$$

Substituting the values of K_1 , K_2 and K_3 we get

$$I(s) = \frac{1250}{(50 + j)(s + j50)} + \frac{1250}{(50 - j)(s - j50)} - \frac{1.98}{(s + 1)}$$

Taking inverse Laplace transform,


$$i(t) = \frac{1250}{(50 + j)} e^{-j50t} = \frac{1250}{(50 - j)} e^{j50t} - 1.98 e^{-t} \text{ A}$$

EXAMPLE 33: A sinusoidal voltage of $10 \sin 100t$ is connected in series with a switch and $R = 10 \Omega$ and $L = 0.1 \text{ H}$. If the switch is closed at $t = 0$, determine the transient current $i(t)$.

HOTS

(AU/EEE - Nov. 2011)

Solution :

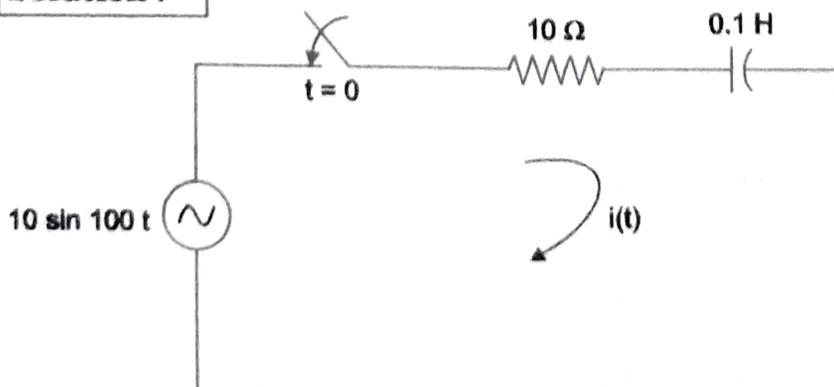

$$R = 10 \Omega \quad L = 0.1 H \quad v = 10 \sin 100 t$$

$$10 i(t) + 0.1 \frac{di(t)}{dt} = 10 \sin 100 t$$

Taking Laplace transform on both sides, assuming zero initial conditions.

$$10 I(s) + 0.1 s I(s) = 10 \times \frac{100}{s^2 + 100^2}$$

$$I(s) [10 + 0.1 s] = \frac{1000}{s^2 + 100^2}$$

$$I(s) 0.1 \left[s + \frac{10}{0.1} \right] = \frac{1000}{s^2 + 100^2}$$

$$I(s) [s + 100] = \frac{1000}{0.1 (s^2 + 1000^2)}$$

$$I(s) [s + 100] = \frac{10000}{s^2 + 100^2}$$

$$I(s) = \frac{10000}{(s + 100)(s^2 + 100^2)}$$

$$I(s) = \frac{10000}{(s + j 100)(s - j 100)(s + 100)}$$

$$\frac{10000}{(s + j 100)(s - j 100)(s + 100)} = \frac{A}{(s + j 100)} + \frac{B}{(s - j 100)} + \frac{C}{(s + 100)}$$

$$10000 = A(s - j 100)(s + 100) + B(s + j 100)(s + 100) + C(s + j 100)(s - j 100)$$

Put $s = -j 100$

$$10000 = A(-j 100 - j 100)(-j 100 + 100)$$

$$10000 = A(-j 200)(-j 100 + 100)$$

$$10000 = A(j^2 20000 - j 20000)$$

$$10000 = 10000 A(-2 - j 2)$$

$$A = \frac{1}{(-2 - j 2)} \times \frac{(-2 + j 2)}{(-2 + j 2)} = -0.25 + j 0.25$$

Put $s = j 100$

$$10000 = B(j 100 + j 100)(j 100 + 100)$$

$$10000 = B(j 200)(j 100 + 100)$$

$$10000 = B (-20000 + j20000)$$

$$10000 = 10000 B (-2 + j2)$$

$$B = \frac{1}{-2 + j2} \times \frac{(-2 - j2)}{(-2 - j2)}$$

$$B = -0.25 - j0.25$$

Put $S = -100$

$$10000 = C (-100 + j100) (-100 - j100)$$

$$10000 = C (10000 + 10000)$$

$$C = \frac{10000}{20000} = \frac{1}{2} = 0.5$$

$$I(s) = \frac{-0.25 + j0.25}{s + j100} + \frac{-0.25 - j0.25}{s - j100} + \frac{0.5}{s + 100}$$

Taking inverse Laplace transform

$$i(t) = (-0.25 + j0.25)e^{-j100t} + (-0.25 - j0.25)e^{j100t} + 0.5e^{-100t}$$

$$i(t) = -0.25e^{-j100t} + j0.25e^{-j100t} - 0.25e^{j100t} - j0.25e^{j100t} + 0.5e^{-100t}$$

$$i(t) = -0.25(e^{j100t} + e^{-j100t}) + (-j0.25)(e^{j100t} - e^{-j100t}) + 0.5e^{-100t}$$


$$i(t) = (-0.25)2\cos 100t + (-j0.25)(2j)\sin 100t + 0.5e^{-100t}$$

$$i(t) = -0.5\cos 100t + 0.5\sin 100t + 0.5e^{-100t}$$

$$i(t) = 0.5[-\cos 100t + \sin 100t + e^{-100t}] \text{ A}$$

EXAMPLE 34: A sinusoidally varying voltage of $V = 50 \sin 10t$ is applied to a series RC circuit shown in figure, is at time $t = 0$, $R = 2 \Omega$ and $C = 0.25 \text{ F}$. Find the equation for the current in the circuit assuming initial charge on capacitor to be zero.

HOTS

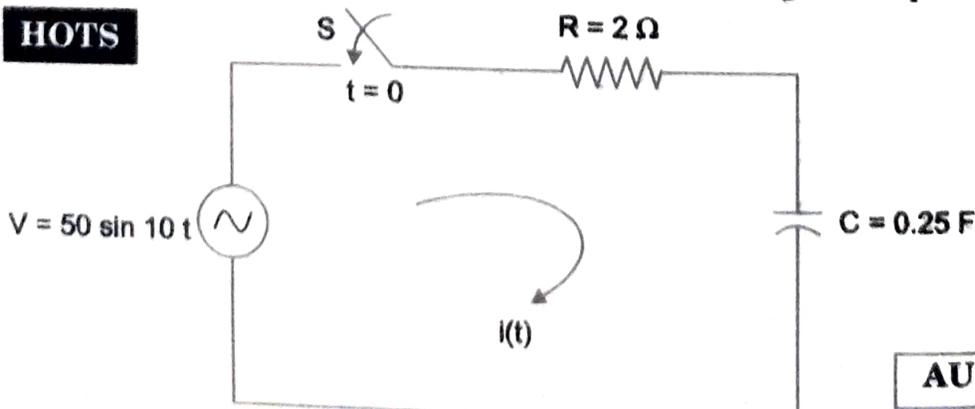

olution :

$$2i(t) + \frac{1}{0.25} \int i(t) dt = 50 \sin 10t$$

Taken Laplace transform on both sides, with zero initial condition

$$2I(s) + 4 \frac{I(s)}{s} = 50 \frac{10}{s^2 + 10^2}$$

$$I(s) \left[2 + \frac{4}{s} \right] = \frac{500}{s^2 + 10^2}$$

$$I(s) \left[\frac{2s + 4}{s} \right] = \frac{500}{s^2 + 10^2}$$

$$I(s) [2s + 4] = \frac{500s}{s^2 + 10^2}$$

$$I(s) 2(s + 2) = \frac{500s}{s^2 + 10^2}$$

$$I(s) = \frac{500s}{2(s^2 + 10^2)}$$

$$I(s) = \frac{250s}{(s + j10)(s - j10)(s + 2)}$$

$$\frac{250s}{(s + j10)(s - j10)(s + 2)} = \frac{A}{(s + j10)} + \frac{B}{(s - j10)} + \frac{C}{(s + 2)}$$

$$250s = A(s - j10)(s + 2) + B(s + j10)(s + 2) + C(s + j10)(s - j10)$$

Put $s = j10$

$$250(j10) = B(j10 + j10)(j10 + 2)$$

$$j2500 = B(j20)(j10 + 2)$$

$$125 = B(j10 + 2)$$

$$B = \frac{125(2 - j10)}{(2 + j10)(2 - j10)} = 2.4 - j12.02$$

Put $s = -j10$

$$250(-j10) = A(-j10 - j10)(-j10 + 2)$$

$$-j2500 = A(-j20)(2 - j10)$$

$$125 = A (2 - j 10)$$

$$A = \frac{125 (2 + j10)}{(2 - j10) (2 + j10)}$$

$$A = 2.4 + j 12.02$$

Put $s = -2$

$$250 (-2) = C (-2 + j10) (-2 - j10)$$

$$-500 = C (4 + 100)$$

$$-500 = C 104$$

$$C = \frac{-500}{104} = -4.81$$

$$I(s) = \frac{2.4 + j 12.02}{s + j10} + \frac{2.4 - j 12.02}{s - j10} - \frac{4.81}{s + 2}$$

Taking inverse Laplace transform

$$i(t) = (2.4 + j 12.02) e^{-j10t} + (2.4 - j12.02) e^{j10t} - 4.81 e^{-2t}$$

$$i(t) = 2.4 e^{-j10t} + j12.02 e^{-j10t} + 2.4 e^{j10t} - j12.02 e^{j10t} - 4.81 e^{-2t}$$

$$i(t) = 2.4 (e^{j10t} + e^{-j10t}) - j1.202 (e^{j10t} - e^{-j10t}) - 4.81 e^{-2t}$$

$$i(t) = 2.4 (2 \cos 10t) - j12.02 (2j \sin 10t) - 4.81 e^{-2t}$$

$$i(t) = 4.8 \cos 10t + 24.04 \sin 10t - 4.81 e^{-2t} \text{ A}$$

3.4.3 Transient response for RLC circuit

3.4.3.1 Step input

Applying KVL to the series RLC circuit (Figure 3.15)

$$iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = E$$

Assume no initial charge on the capacitor.

Taking Laplace transform on both sides,

$$RI(s) + L [sI(s) - i(0)] + \frac{1}{C} \frac{I(s)}{s} = \frac{E}{s}$$

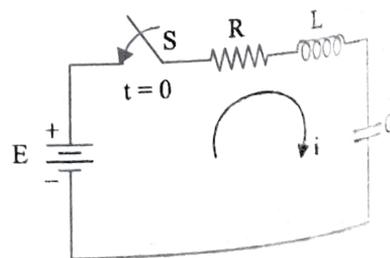


Fig. 3.15