



# SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



## 19EC502 – TRANSMISSION LINES AND ANTENNAS

III YEAR/ V SEMESTER


1

### UNIT 1 – TRANSMISSION LINE THEORY

### TOPIC – IMPEDANCE MATCHING & QUARTER WAVE LINE



# WHAT DO YOU INFER FROM THE DIAGRAM ?

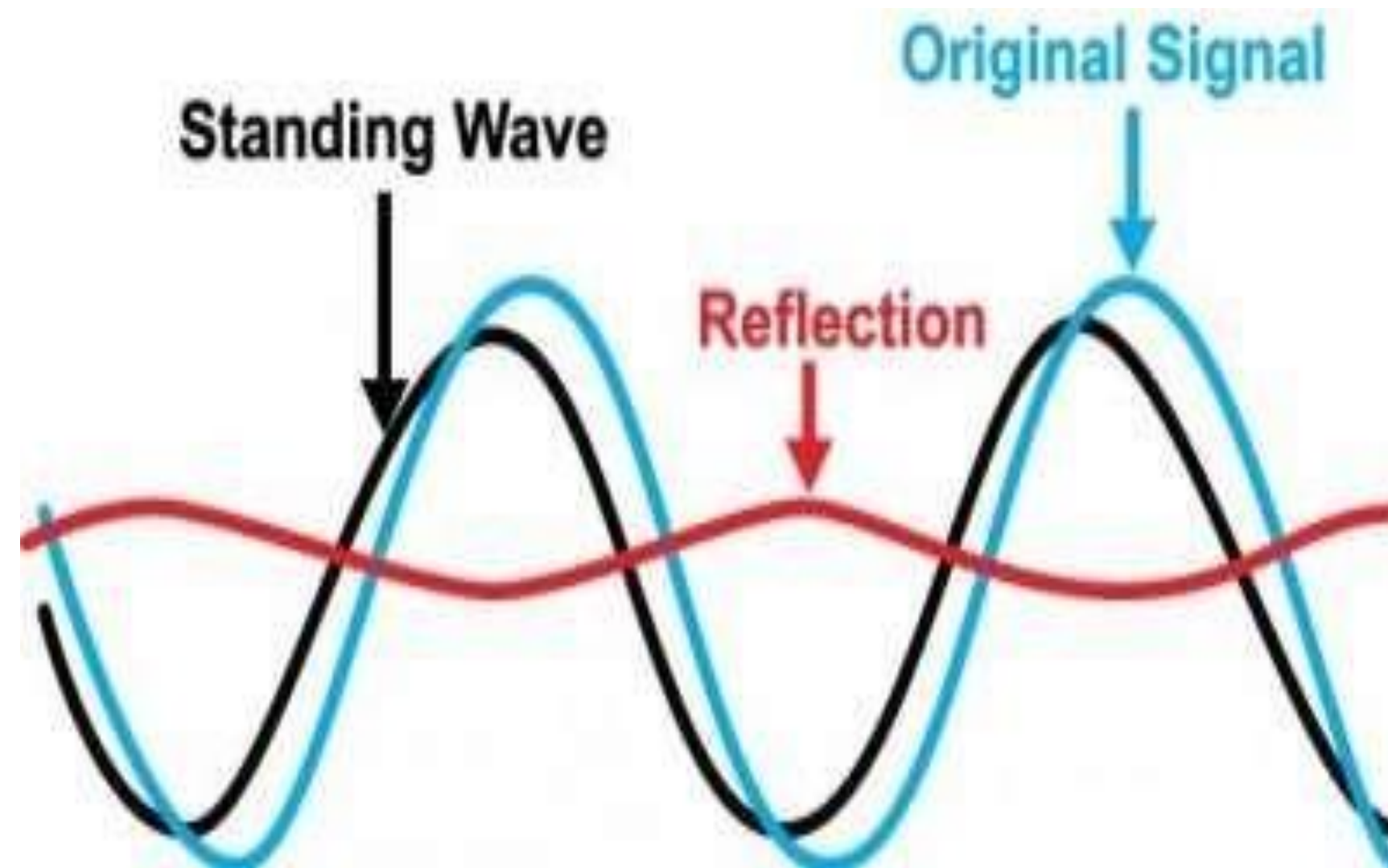



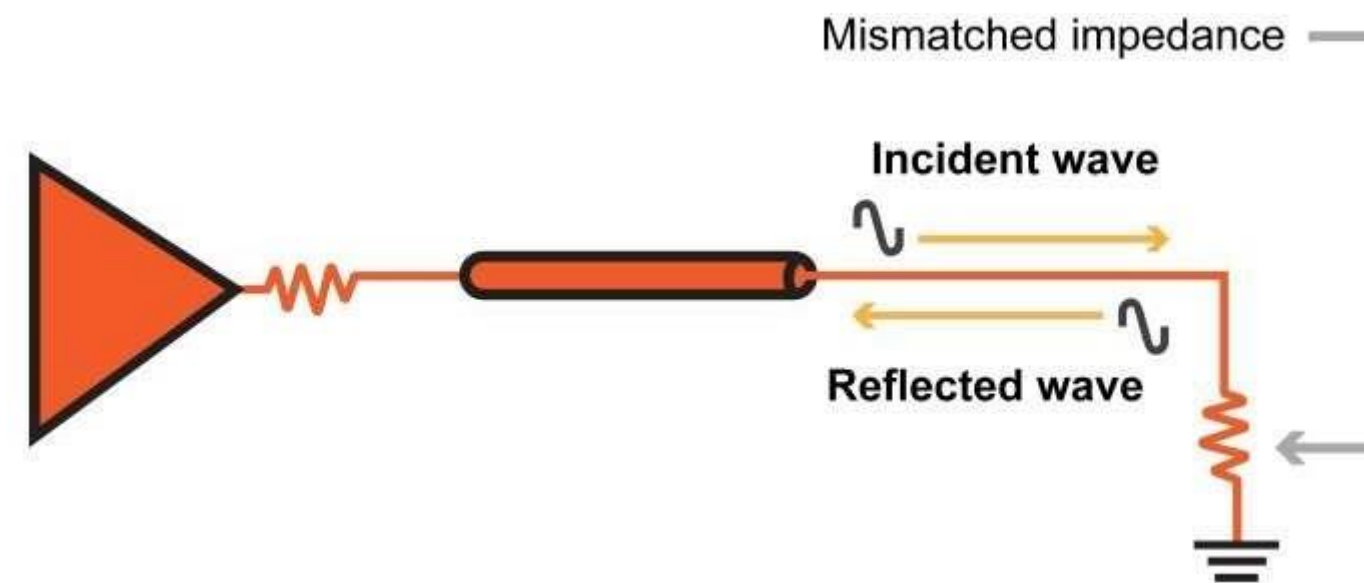
# IMPEDANCE MISMATCH AND EFFECTS



- Load impedance is not matched with the characteristic impedance of the transmission line, reflections occur
- This allows the load to absorb the wave energy resulting in power loss





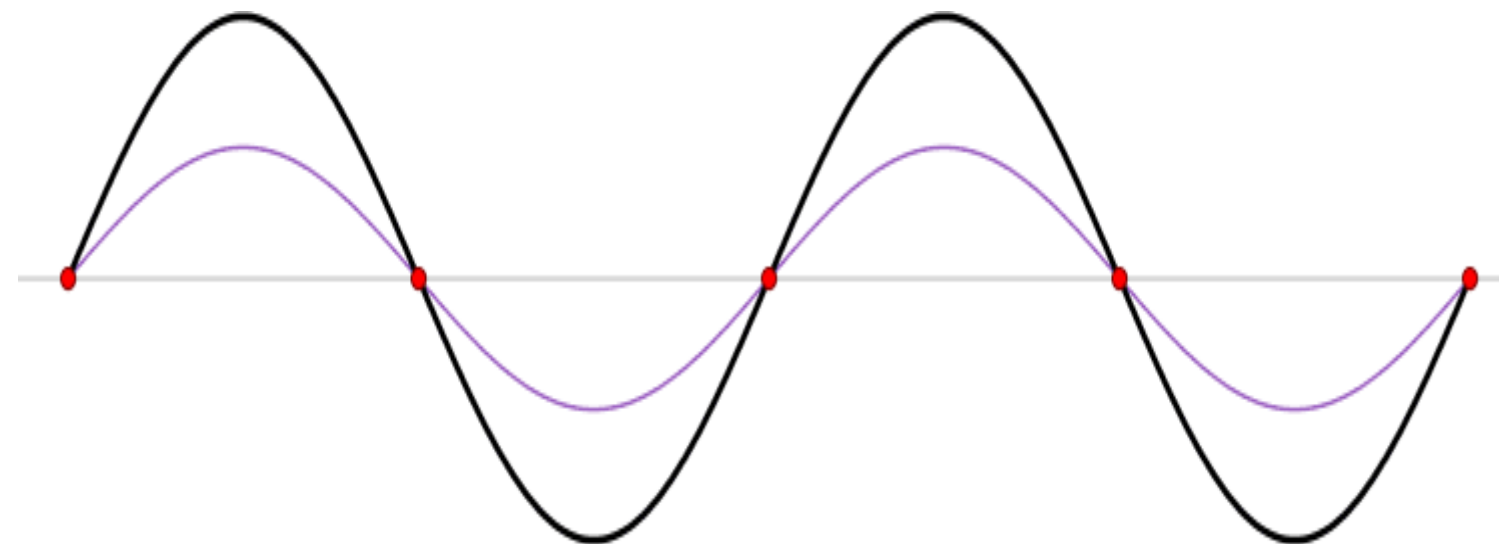
# IMPEDANCE MISMATCH AND EFFECTS



- Reflections are problematic because they reduce the amount of power that can be transferred from source to load
- Reflections also lead to standing waves
- The high-amplitude portions of a standing wave can damage components or cables





# IMPEDANCE MISMATCH AND EFFECTS



- In applications like TV picture transmission, reflection make impairment of picture quality due to ghost images.






# IMPEDANCE MISMATCH AND EFFECTS



- In applications like transmission of pulses, pulse shape distortion occurs
- Problem of frequency stability
- Signal strength get reduced which reduces signal-to-noise ratio

## Example of Pulse Distortion

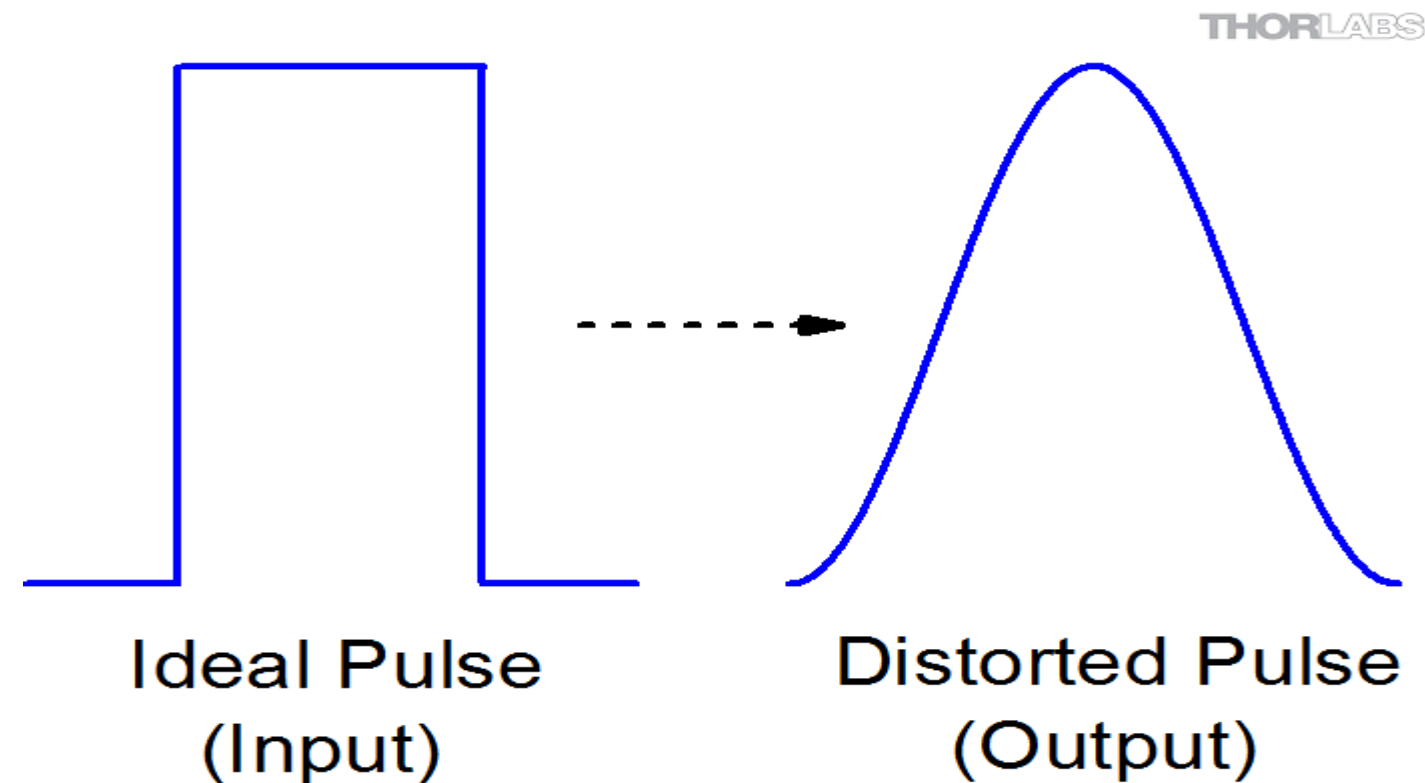



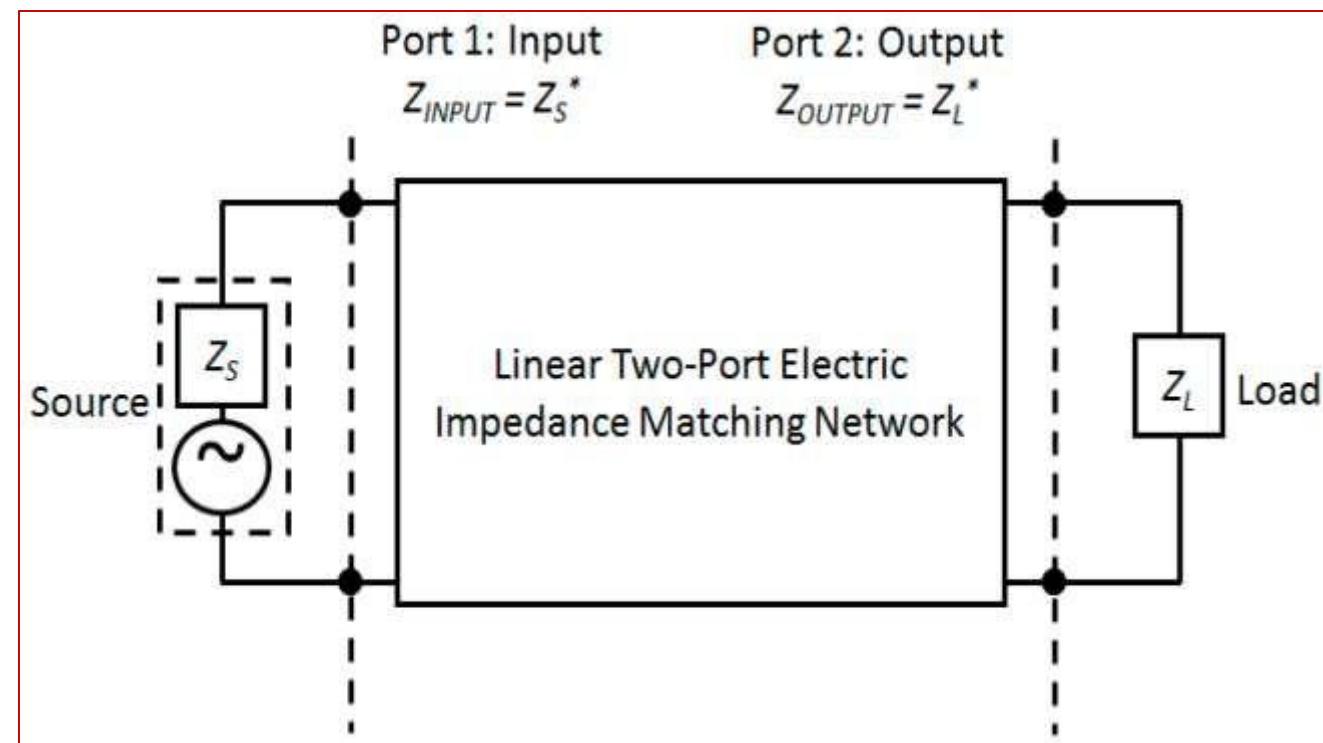
# IMPEDANCE MATCHING NETWORKS



- Impedance matching networks are impedance transformers
- They transform the load impedance to the characteristic impedance of the line or
- To transform the line impedance to equal source impedance to provide impedance matching





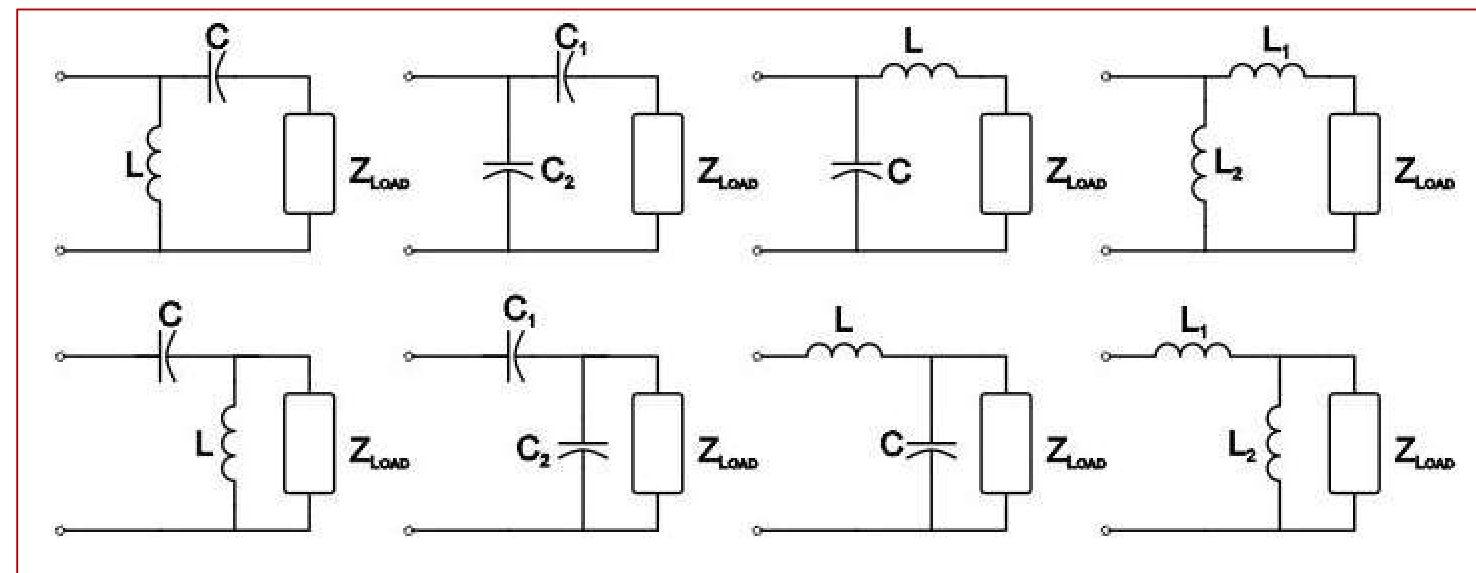
# IMPEDANCE MATCHING NETWORKS - TYPES



- Using inductance or capacitance and a section of transmission line
- Using L-C combination
- Using quarter wave transformers
- Using half wave line and eighth wave lines
- Using short circuited stubs







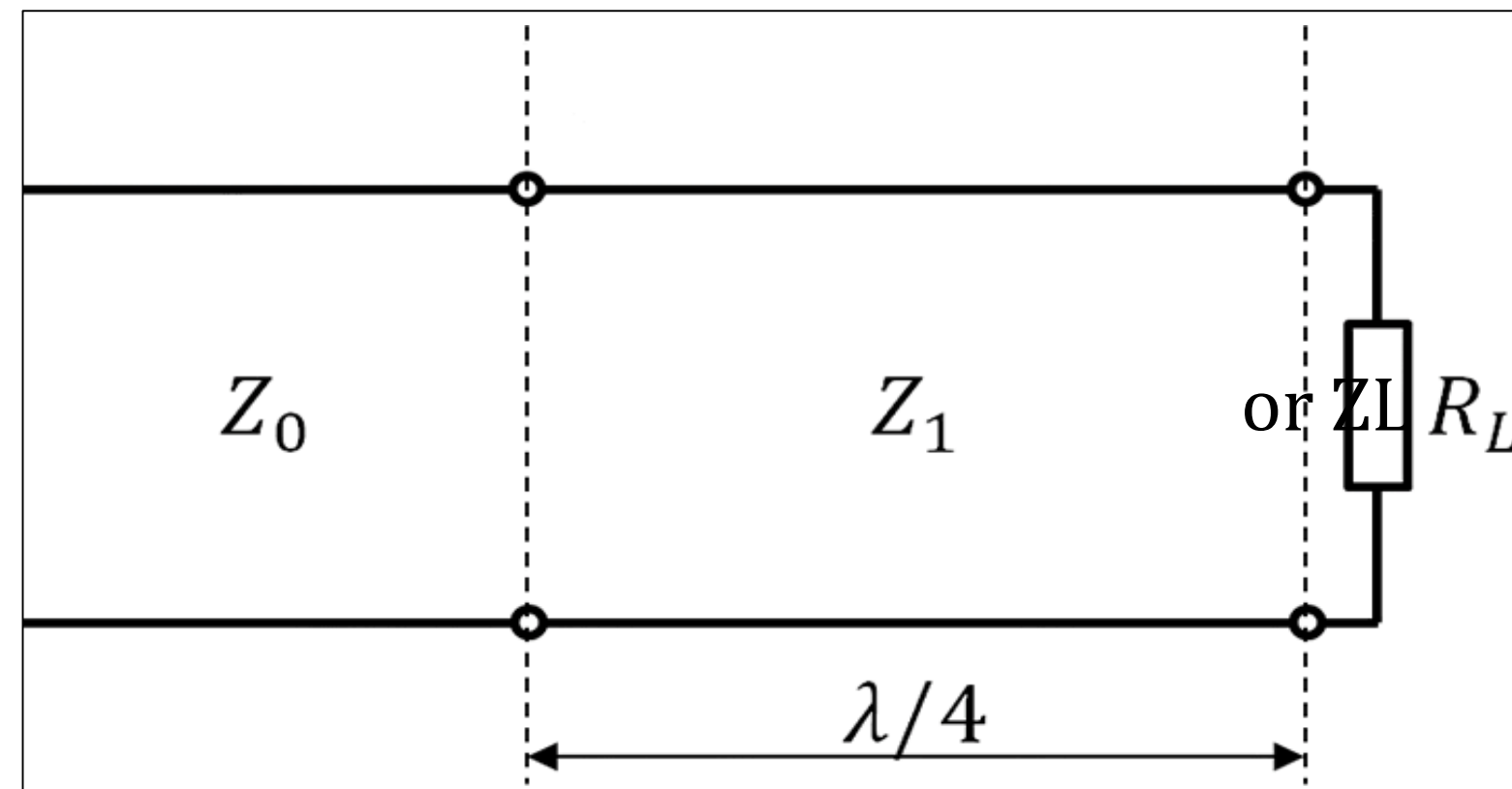
# IMPEDANCE MATCHING NETWORKS – QUARTER WAVE TRANSFORMER



- Fig shows a lossless transmission line with characteristic impedance  $Z_0$  connected to load  $Z_L$
- Since  $Z_0 \neq Z_L$ , a quarter wave transformer is inserted for impedance matching.
- Length of quarter wave transformer is  $\lambda/4$
- Input impedance of the transformer is  $Z_S = R_{02}/Z_R$





# IMPEDANCE MATCHING NETWORKS - QUARTER WAVE TRANSFORMER



$$Z_s = Z_0 \left[ \frac{Z_R + j R_0 \tan \beta s}{R_0 + j Z_R \tan \beta s} \right]$$

Dividing by  $\tan \beta s$

$$Z_s = R_0 \left[ \frac{\frac{Z_R}{\tan \beta s} + j R_0}{\frac{R_0}{\tan \beta s} + j Z_R} \right]$$

$$\beta s = \cancel{\beta} \frac{2\pi}{\lambda} \times \frac{\lambda}{4} = \pi/2$$

$$\therefore Z_s = R_0 \left[ \frac{\frac{Z_R}{\tan \pi/2} + j R_0}{\frac{R_0}{\tan \pi/2} + j Z_R} \right]$$

$$\tan \pi/2 = \infty$$

$$Z_s = R_0 \left[ \frac{j R_0}{j Z_R} \right] = \frac{R_0^2}{Z_R}$$

$$\boxed{Z_s = \frac{R_0^2}{Z_R}}$$



# QUARTER WAVE TRANSFORMER - APPLICATIONS



- Used as a transformer
- Used as an impedance inverter
- Used to couple a transmission line to a resistive load
- Used if the load is not pure resistance
- Used as an insulator

