



SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING




19EC502 – TRANSMISSION LINES AND ANTENNAS

III YEAR/ V SEMESTER

UNIT 1– TRANSMISSION LINE THEORY

TOPIC – SINGLE STUB MATCHING

MATCHING NETWORKS

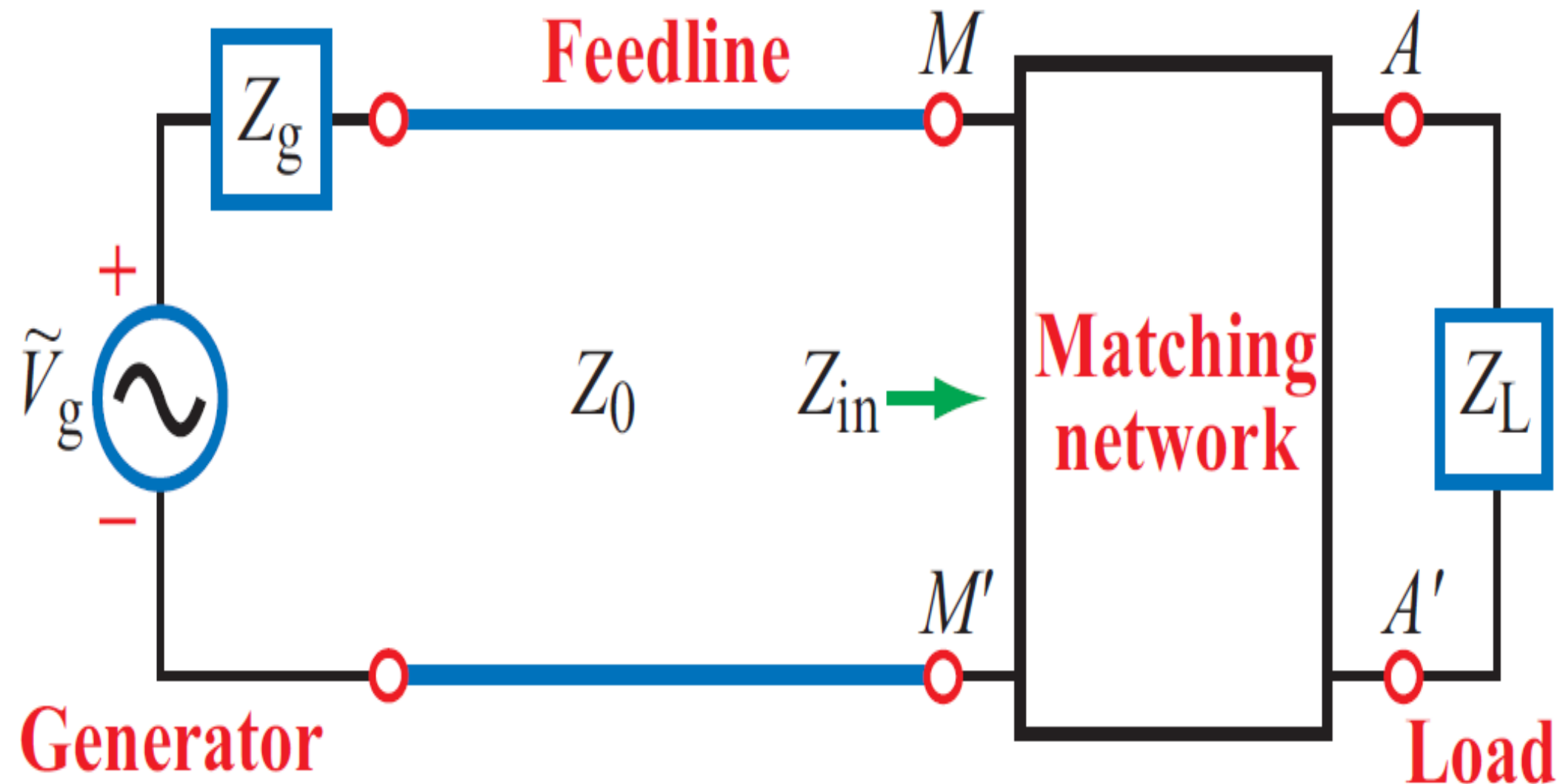

What is the purpose of matching networks of a transmission line?



MATCHING NETWORKS


- When a high frequency line is terminated in its characteristic impedance R_0 , it is operated as a smooth line
- Under such conditions,
 - there will be no reflections
 - maximum power delivered to the load
 - increased efficiency
- But in practice the loads such as antennas do not provide resistances equal to R_0 of the line
- So it is necessary to add some of the impedance matching networks between the line and load



STUB MATCHING





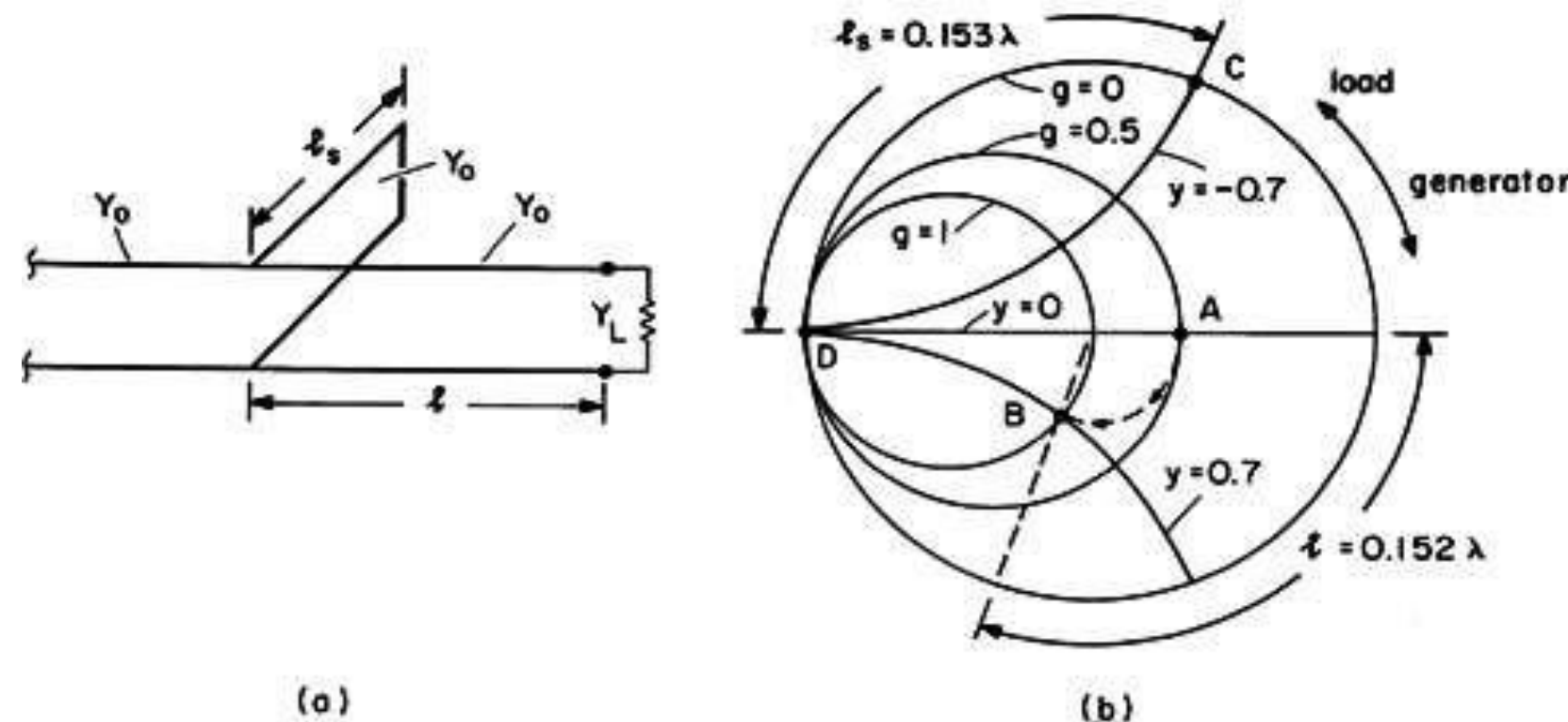- One of the impedance matching is to use open or short circuited stubs
- A stub of suitable length is connected in parallel with the line at a certain distance from the load
- Because of parallel connection of stub, it is convenient to work with admittances



STUB MATCHING - TYPES

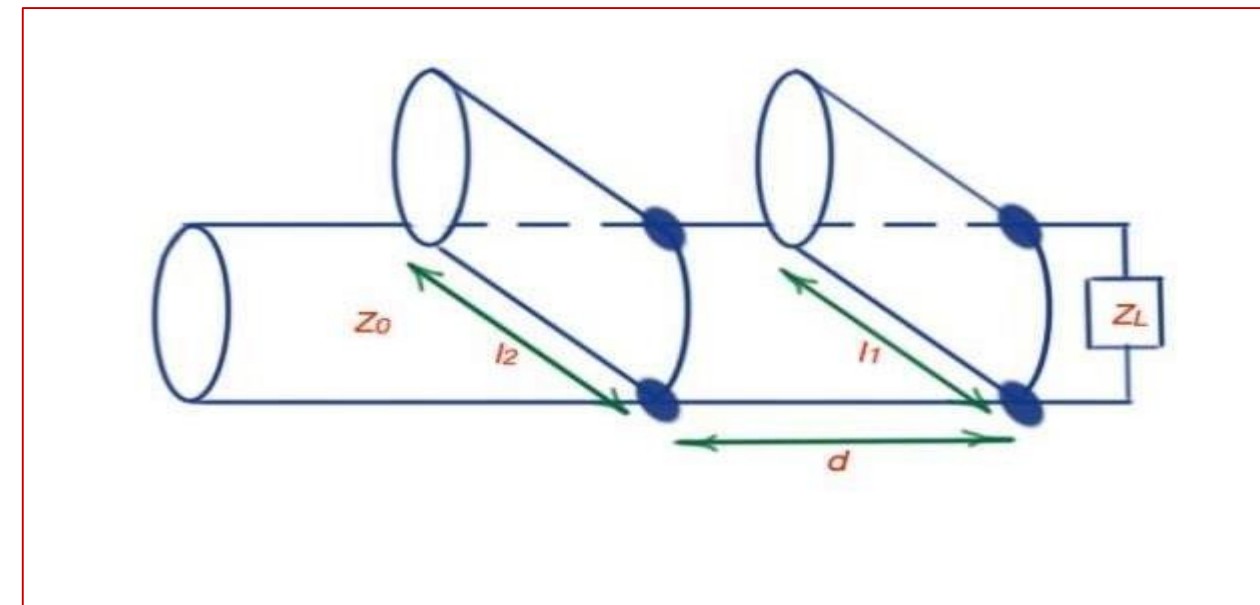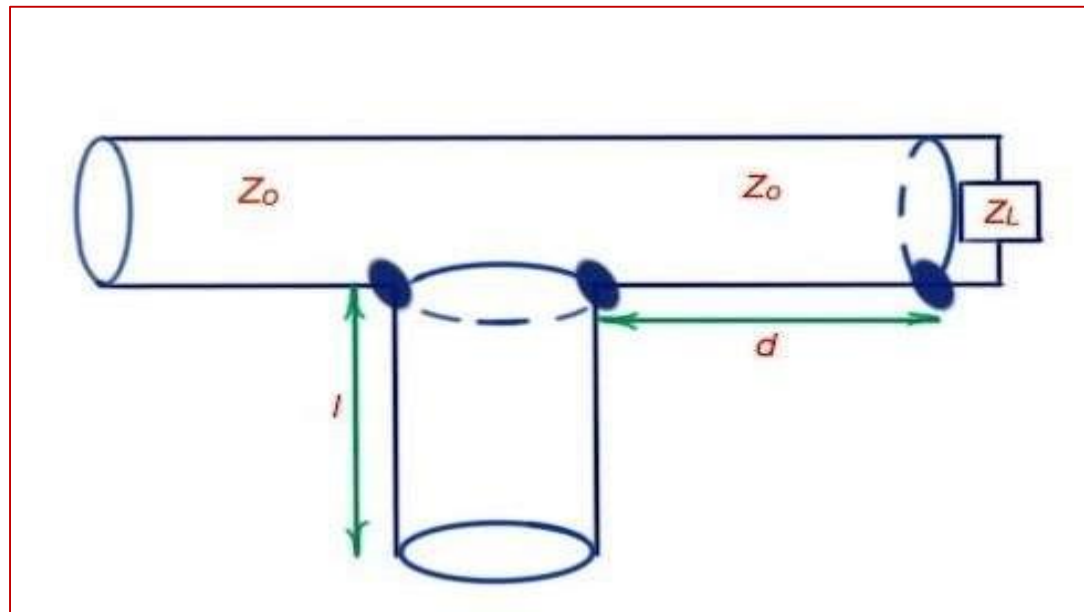- 1. Single stub matching** - A stub is connected in parallel to the transmission line at a fixed distance from load
- 2. Double stub matching** - A type of matching where two stubs are shunted to main transmission line on a fixed distance






SINGLE STUB MATCHING - PRINCIPLE



- The input impedance at any point on a line is given by
$$Z_S = R_0 \pm jX$$
- The input admittance is
$$Y_S = G_0 \pm jB$$
- Then the short circuited stub of $+jB$ is connected at that point across the transmission line
- Then the total admittance is given by,
$$Y_S = G_0 \pm jB \mp jB = G_0$$
$$Z_S = R_0$$
- Thus the line from the source to the point is then terminated in R_0 . It act as a smooth line


SINGLE STUB MATCHING – DESIGN PARAMETERS

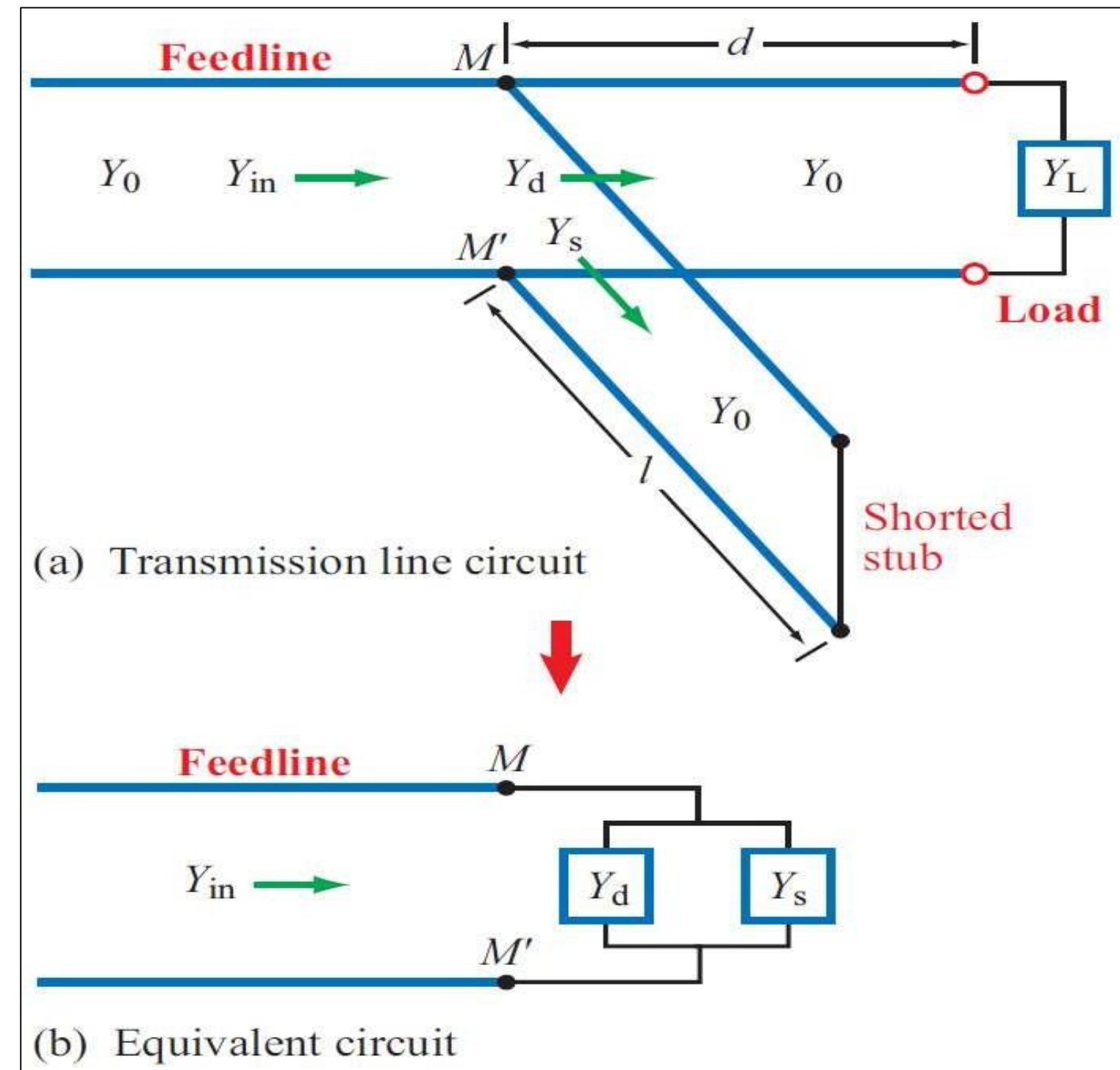- **Design parameters**
 - The point of stub connection
 - Length of the stub





SINGLE STUB MATCHING - DIAGRAM

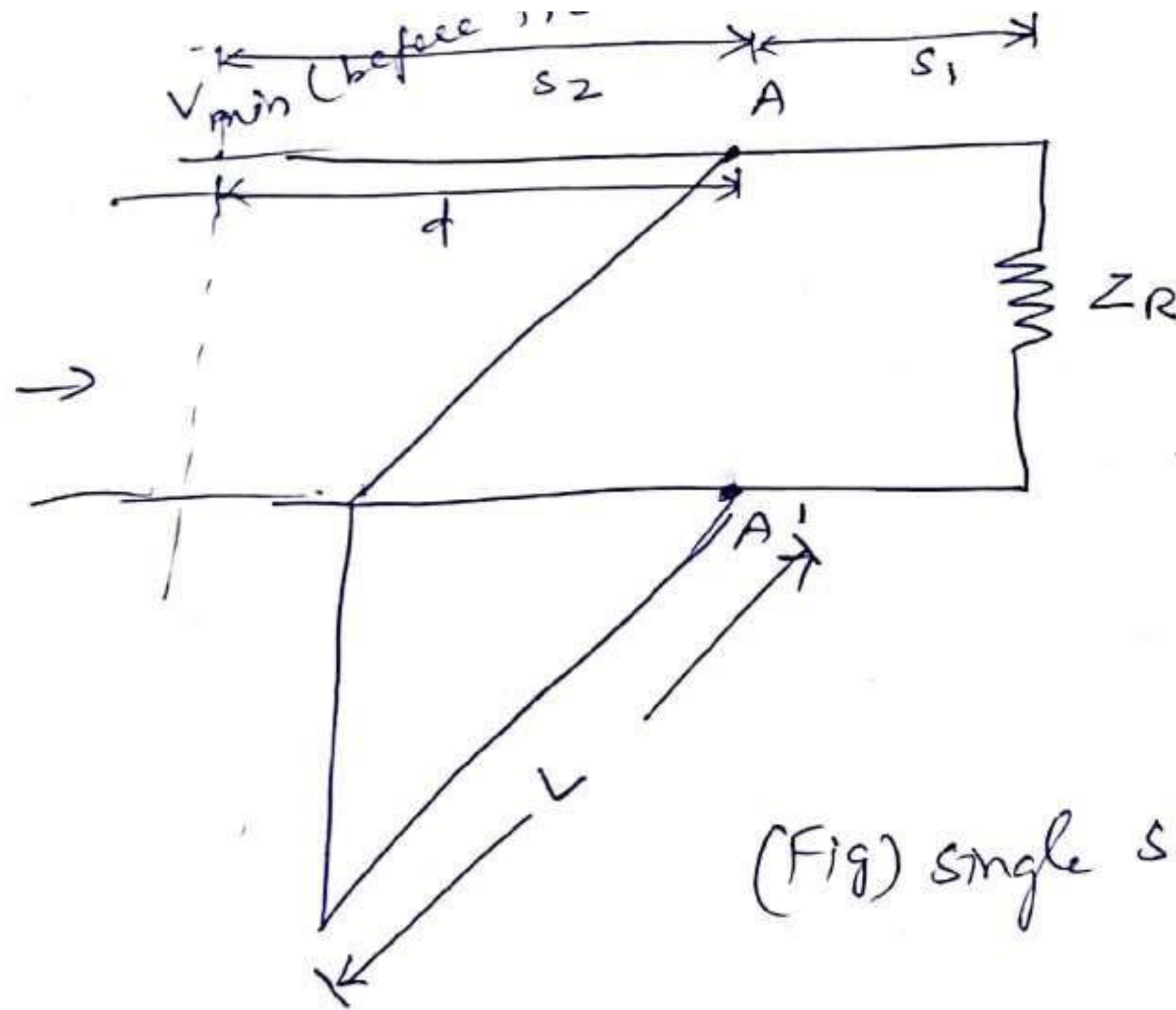

(Fig) single stub matching.



LENGTH OF THE STUB



$$L = \frac{\lambda}{2\pi} \tan^{-1} \left(\frac{\sqrt{1-|k|^2}}{2|k|} \right)$$

(or)

$$L = \frac{\lambda}{2\pi} \tan^{-1} \frac{\sqrt{S}}{S-1}$$

This is the length of the stub to be placed d meters towards the load from a point at which a V_{\min} existed before the attachment of the stub



DISTANCE OF THE STUB



$$d = \pm \frac{\cos^{-1} \left(\frac{S-1}{S+1} \right) \frac{\lambda}{4}}{\pi}$$

The stub should be connected at this distance from d measured from either direction from a V_{\min} nearest to the load



SINGLE STUB MATCHING - PROBLEM



A 75 Ohm lossless line is to be matched to a $100-j80$ Ohms load with a shorted stub. Calculate the distance from the load, the stub length, and the necessary stub admittance.

Answer: Change z_L to admittance: Find d =distance to circle with $\text{real}=1$ as:

$$d = .4338 - .3393 = 0.094l \text{ or}$$

$$.0662 - .1607 = 0.094l \text{ (both yield same } d)$$

$$[\text{or next intersection i.e. } 1-jb : d = 0.272l,]$$

$$\text{Short stub: } .25l - .124l = 0.126l$$


$$\text{Or } 0.376l - .25l = 0.126l \text{ (both yield same distance)}$$

$$\text{With } y_{\text{stub}} = -j.96/75 = -j.0128 \text{ mhos}$$



SINGLE STUB MATCHING - STEPS

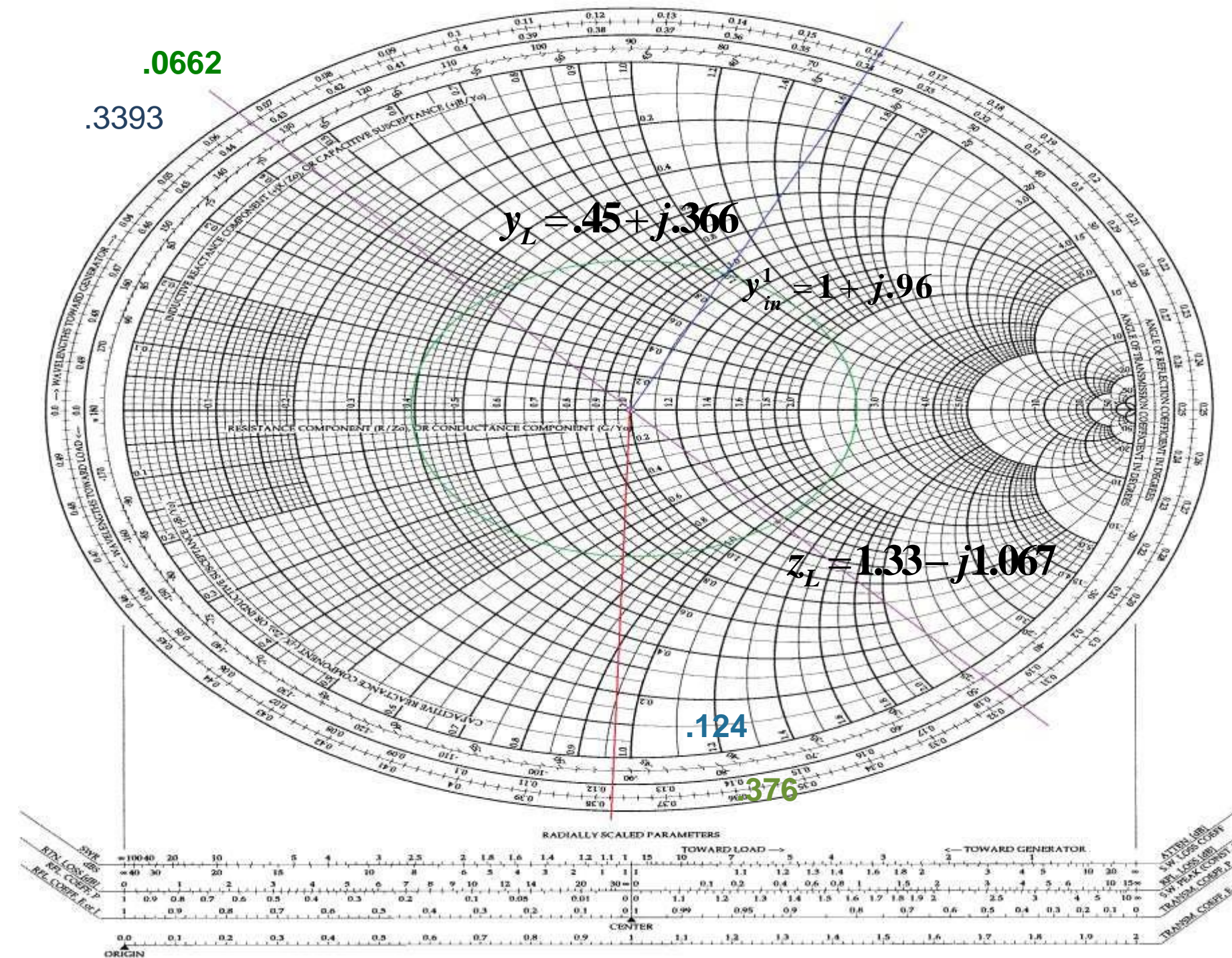The Complete Smith Chart
Black Magic Design





SINGLE STUB MATCHING – ASSIGNMENT PROBLEM



A load impedance $Z_L = 25 - j50$ Ohms is connected to a 50 Ohm transmission line. Insert a shunt element to eliminate reflections towards the sending end of the line. Insert a shunt element to eliminate reflections towards the sending end of the line.

Specify the insert location d (in wavelengths), the type of element, and its value, given that $f = 100$ MHz



ADVANTAGES OF SHORT CIRCUITED STUB OVER OPEN CIRCUITED STUB



- The length of short circuited stub can be easily changed but it is not easy in an open circuited stub
- Because of the shorting plate at the end mechanical rigidity of a short circuited stub is better than an open circuited stub
- The open circuit in the open circuited stubs do not behave like a true open circuit
- Poses fabrication problem



THANK YOU