



SNS COLLEGE OF ENGINEERING

(Autonomous)

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



19EC502 – TRANSMISSION LINES AND ANTENNAS

III YEAR/ V SEMESTER

1


UNIT 1 – TRANSMISSION LINE THEORY

TOPIC – DOUBLE STUB MATCHING



DISADVANTAGES OF SINGLE STUB MATCHING

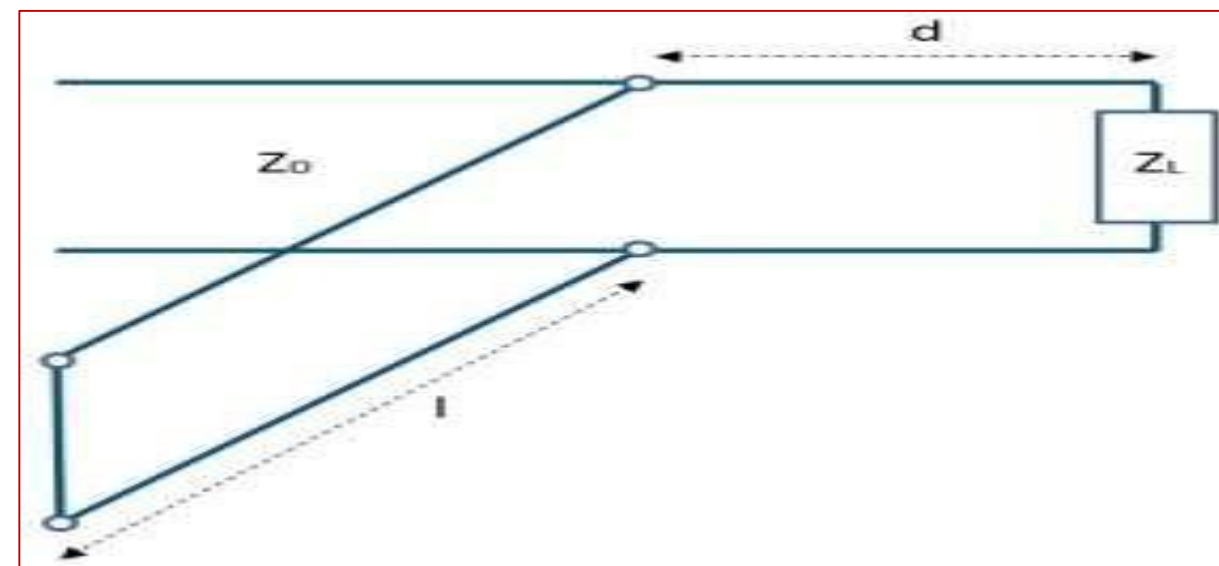
- Single stub matching is applicable for single frequency
- For final adjustment the stub has to be moved along the line.
- It is possible for open wire line and it is difficult for coaxial line
- To overcome the drawbacks of the single-stub matching technique, the DOUBLE STUB MATCHING double-stub matching technique is employed





DOUBLE STUB MATCHING

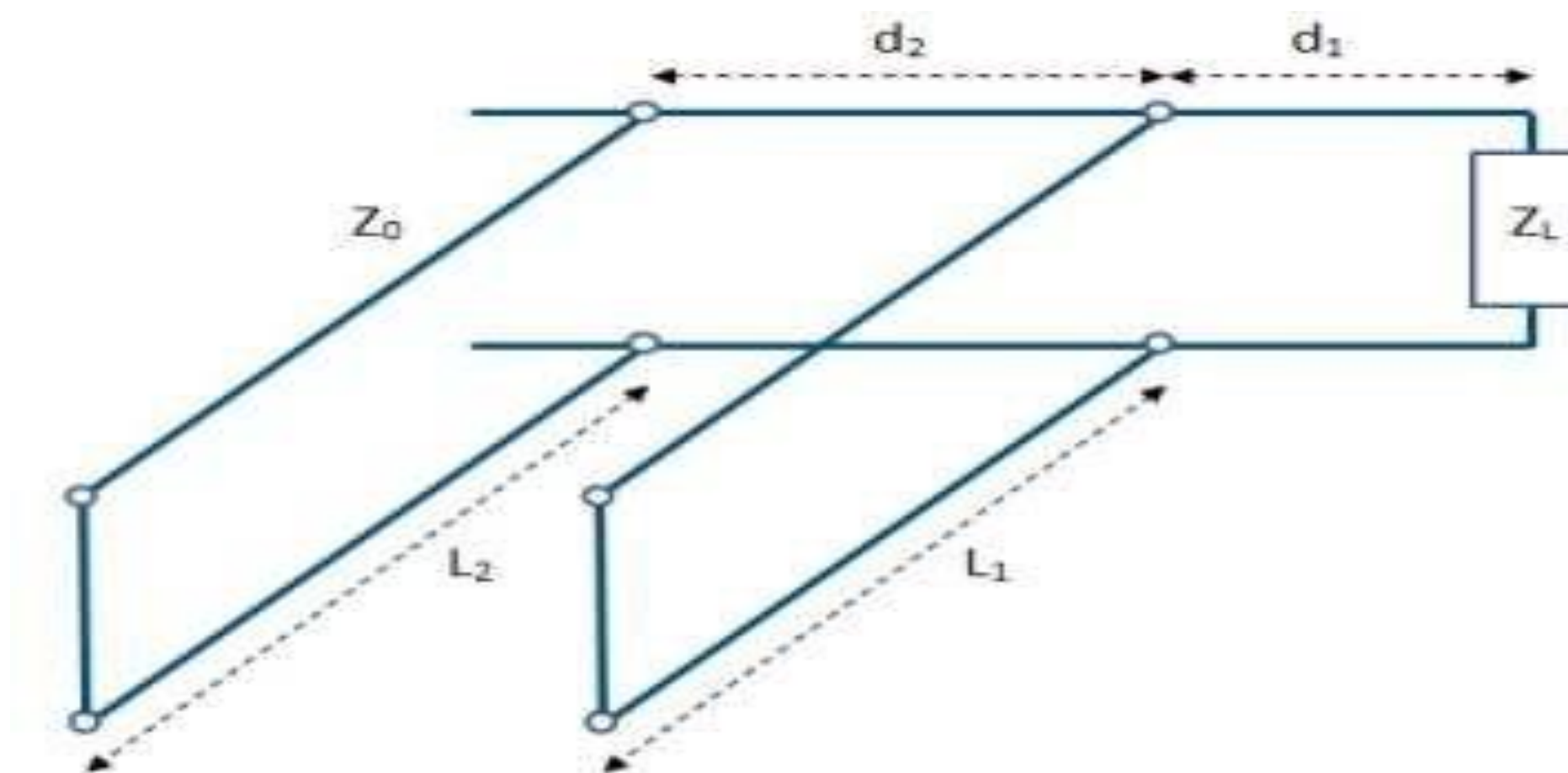- Two short circuited stubs of length l_1 and l_2 are used
- Stub 1 of length l_1 is located at a distance d_1 from the load
- Similarly stub 2 of length l_2 is located at a distance d_2 from stub 1





DOUBLE STUB MATCHING - PRINCIPLE

The input impedance of a dissipationless line at any point, distance 's' away from the load is given by,

$$Z_s = Z_0 \left[\frac{Z_R + j Z_0 \tan \beta s}{Z_0 + j Z_R \tan \beta s} \right] \rightarrow \textcircled{1}$$

In terms of admittances, subs.

$$Z_s = \frac{1}{Y_s}, \quad Z_0 = \frac{1}{Y_0} \quad \& \quad Z_R = \frac{1}{Y_R} \quad \text{in eq } \textcircled{1}$$

$$\frac{1}{Y_s} = \frac{1}{Y_0} \left[\frac{\frac{1}{Y_R} + j \frac{1}{Y_0} \tan \beta s}{\frac{1}{Y_0} + j \frac{1}{Y_R} \tan \beta s} \right] \rightarrow \textcircled{2}$$



DOUBLE STUB MATCHING - PRINCIPLE

Multiply by Y_R in both NR & DR of R.H.S

$$\frac{Y_0}{Y_S} = \left[\frac{1 + \frac{Y_R}{Y_0} \tan \beta s}{\frac{Y_R}{Y_0} + j \tan \beta s} \right] \rightarrow \textcircled{3}$$

Inverting eq $\textcircled{3}$,

$$\frac{Y_S}{Y_0} = \frac{\frac{Y_R}{Y_0} + j \tan \beta s}{1 + \frac{Y_R}{Y_0} \tan \beta s} \rightarrow \textcircled{4}$$

sub $\frac{Y_S}{Y_0} = Y_S \rightarrow$ Normalized input

impedance & $\frac{Y_R}{Y_0} = Y_R \rightarrow$ Normalized load
impedance

in eq $\textcircled{4}$



DOUBLE STUB MATCHING - PRINCIPLE

$$Y_S = \frac{Y_R + j \tan \beta L}{1 + j Y_R \tan \beta L} \rightarrow (5)$$

Rationalizing eq (5)

$$Y_S = \frac{Y_R + j \tan \beta L}{1 + j Y_R \tan \beta L} \times \frac{1 - j Y_R \tan \beta L}{1 - j Y_R \tan \beta L}$$

$$= \frac{Y_R - j Y_R^2 \tan \beta L + j \tan \beta L + Y_R \tan^2 \beta L}{1 + Y_R^2 \tan^2 \beta L}$$

$$\therefore Y_S = \frac{Y_R (1 + \tan^2 \beta L) + j (1 - Y_R^2) \tan \beta L}{1 + Y_R^2 \tan^2 \beta L} \rightarrow (6)$$



DOUBLE STUB MATCHING - PRINCIPLE

Stub 1 is located at point A-A' at a distance $s = d_1$ from the load.

\therefore Subs $s = d_1$ in eq (6),

$$Y_s = \frac{Y_R (1 + \tan^2 \beta d_1)}{1 + Y_R^2 \tan^2 \beta d_1} + \frac{j (1 - Y_R^2) \tan \beta d_1}{1 + Y_R^2 \tan^2 \beta d_1}$$

$$Y_s = g_i + j b_i \quad \rightarrow (7)$$

Now a stub 1 having susceptance $\pm j b_1$ is added at this point, the new admittance will be

$$Y_s' = g_i + j b_i'$$

$$\text{where } b_i' = b_i \pm b_1$$



DOUBLE STUB MATCHING - PRINCIPLE

At B-B', the normalized admittance is given by,

$$Y_S' = \frac{Y_S}{G_0} = 1 \pm j b_2$$

The stub 2 is adjusted such that the susceptance of stub 2 is $\mp j b_2$.
So the new admittance at B-B' is

$$Y_S' = 1 \pm j b_2 \mp j b_2$$

$$Y_S' = \frac{Y_S}{G_0} = 1$$

$$\therefore Y_S = G_0$$

$$\boxed{Z_S = R_0}$$

This is the required condition.



DOUBLE STUB MATCHING - PRINCIPLE

The spacing between the stubs should not be more than or equal to $\lambda/2$.

It may be,

$$\lambda/16, \lambda/8, 3\lambda/16, \dots, \frac{3\lambda}{8}$$

The most common separations are

$$\lambda/4 \text{ \& } 3\lambda/8$$



DOUBLE STUB MATCHING - PROBLEM

- For a load of $Z_R/Z_0 = 0.8 + j 1.2$. Design a double stub tuner making the distance between the two stubs $3\lambda/8$. Specify the stub length and distance from the load to the first stub. The stubs are short circuited. Verify using Smith Chart



DOUBLE STUB MATCHING - PROBLEM

- **Step 1 :**

Finding normalized admittance from the given normalized impedance

$$Z_R/Z_0 = 0.8 + j 1.2$$

Rationalizing

$$\begin{aligned} Y_R/G_0 &= 0.8 - j 1.2 / 2.08 \\ &= 0.4 - j 0.6 \end{aligned}$$

Mark the point on the chart



DOUBLE STUB MATCHING - PROBLEM

Step 2 :

Trace the unity circle on the chart (the circle passes through real value 1 of the horizontal axis)

Step 3:

Draw a circle which lies between point 1 on the horizontal axis and the reactance value 0.375λ . ($3 \lambda/8$ circle)

Step 4 :

Move the line from normalized admittance without changing the real value. It cuts the $3 \lambda/8$ circle at a point $0.4-j0.2$. This is the point where stub 1 is connected



DOUBLE STUB MATCHING - PROBLEM

Step 5 :

Find the difference between the susceptance. The new susceptance is $j0.6 - j0.2 = j0.4$. Draw a line which passes through $j0.4$. From the short circuit end to the point of stub connection 1 is the distance $d1$

Step 6:

Find the susceptance value at a point where unity circle cut with another circle has radius of centre point to stub 1 connection point

Step 7 :

The susceptance value at that point is $+j1$. Find the opposite susceptance $-j1$. This is the point where stub 2 is connected. The distance between stub 1 connection point and stub 2 connection point is the distance $d2$

