



**SNS COLLEGE OF ENGINEERING**  
**(Autonomous)**  
**DEPARTMENT OF CSE - IoT**

**COURSE NAME:19EC306 / DIGITAL CIRCUITS**  
**II YEAR/III SEMESTER**

**UNIT:1- MINIMIZATION TECHNIQUES AND LOGIC GATES**

**TOPIC:NOR IMPLEMENTATION**




# NAND & NOR IMPLEMENTATION


- Digital circuits are more frequently constructed with NAND or NOR gates than with AND and OR gates.
  - easier to fabricate with electronic components.
  - They are the basic gates used in all IC.
- Rules and procedures have been developed for the conversion from Boolean functions given in terms of AND, OR, and NOT into equivalent NAND or NOR logic diagrams.




# NAND & NOR IMPLEMENTATION

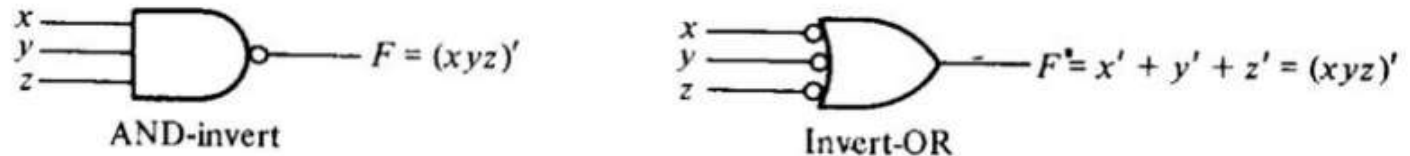

(a) Two graphic symbols for NAND gate.

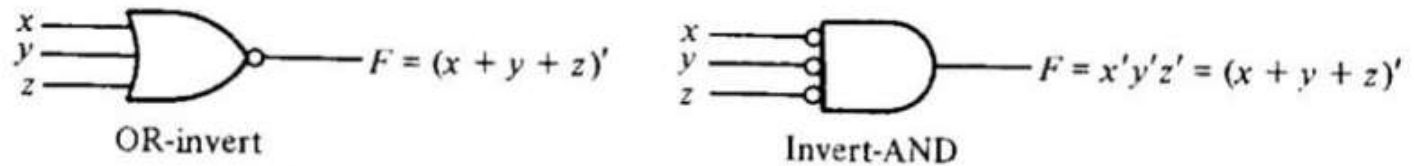

(b) Two graphic symbols for NOR gate.

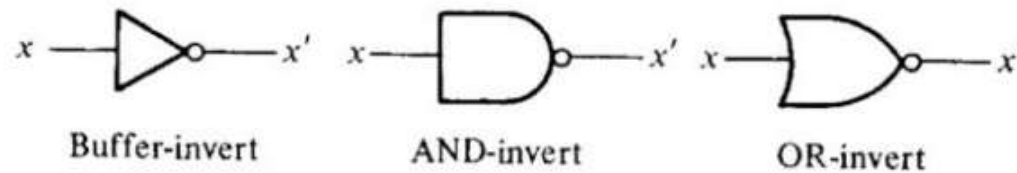

(c) Three graphic symbols for inverter.




# NOR IMPLEMENTATION


- The NOR function is the dual of the NAND function.
  - All procedures and rules for NOR logic are the dual of the corresponding procedures and rules developed for NAND logic.
- implementation of a Boolean function with NOR gates requires that the function be simplified in product of sums form.
  - To obtain the simplified product of sums from a map, it is necessary to combine 0's in the map and then complement the function.



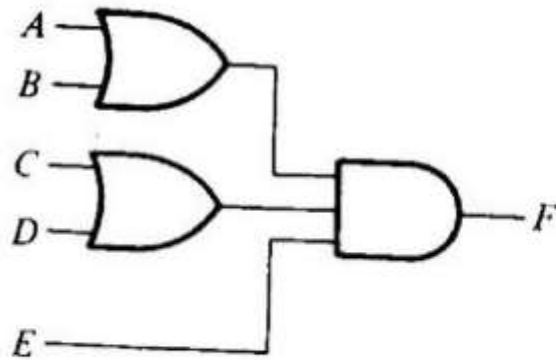
# Three ways to implement $F = (A + B)(C + D)E$



(a)

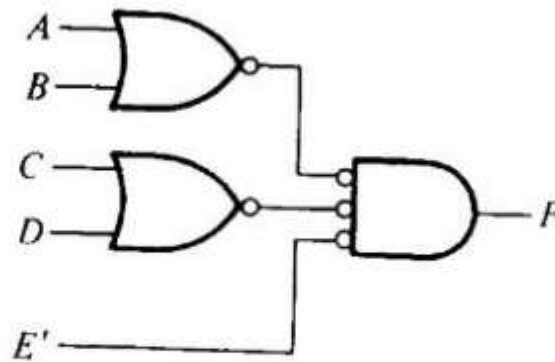


(b)

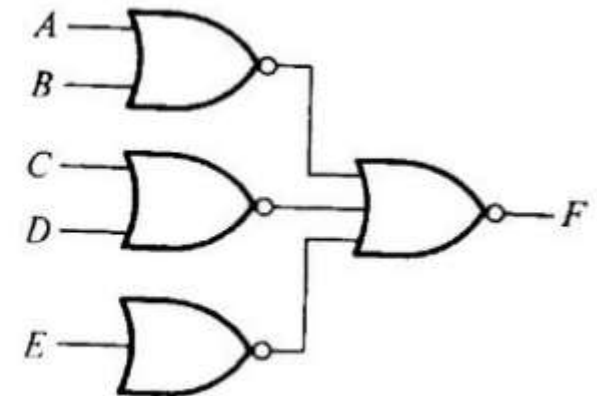

(c)



# NOR as an OR GATE

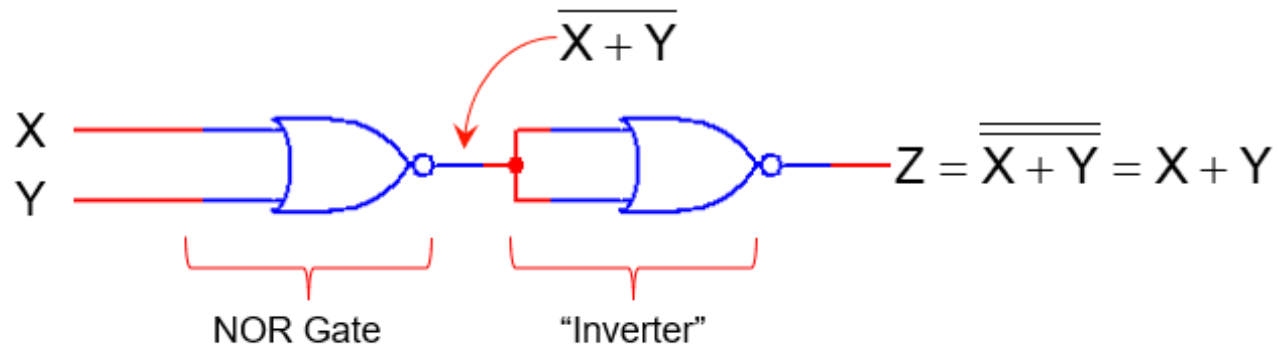


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

Equivalent to OR Gate



# NOR as an AND GATE

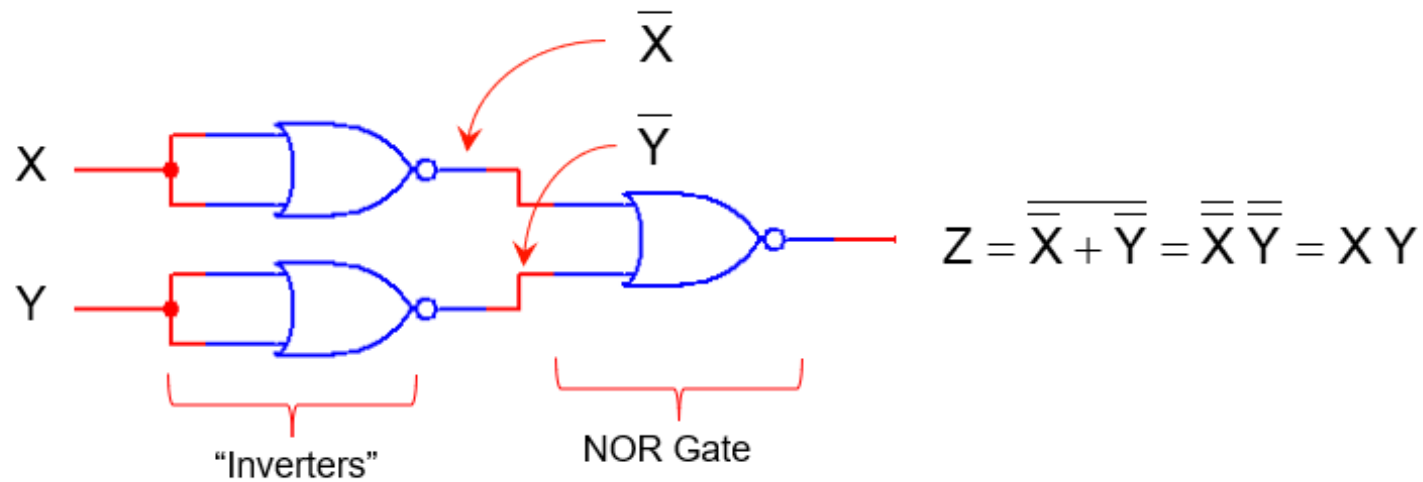


X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

Equivalent to AND Gate


# NOR GATE EQUIVALENT OF AOI GATES





AND

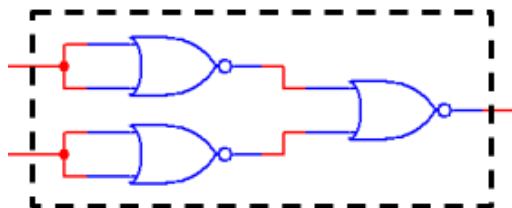

OR

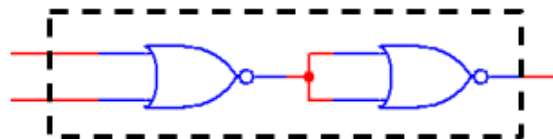

INVERTER

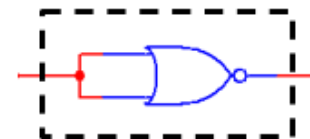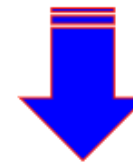






# Process for NOR implementation

1. If starting from a logic expression, implement the design with AOI logic.
2. In the AOI implementation, identify and replace every AND, OR, and INVERTER gate with its NOR equivalent.
3. Redraw the circuit.
4. Identify and eliminate any double inversions. (i.e. back-to-back inverters)
5. Redraw the final circuit.


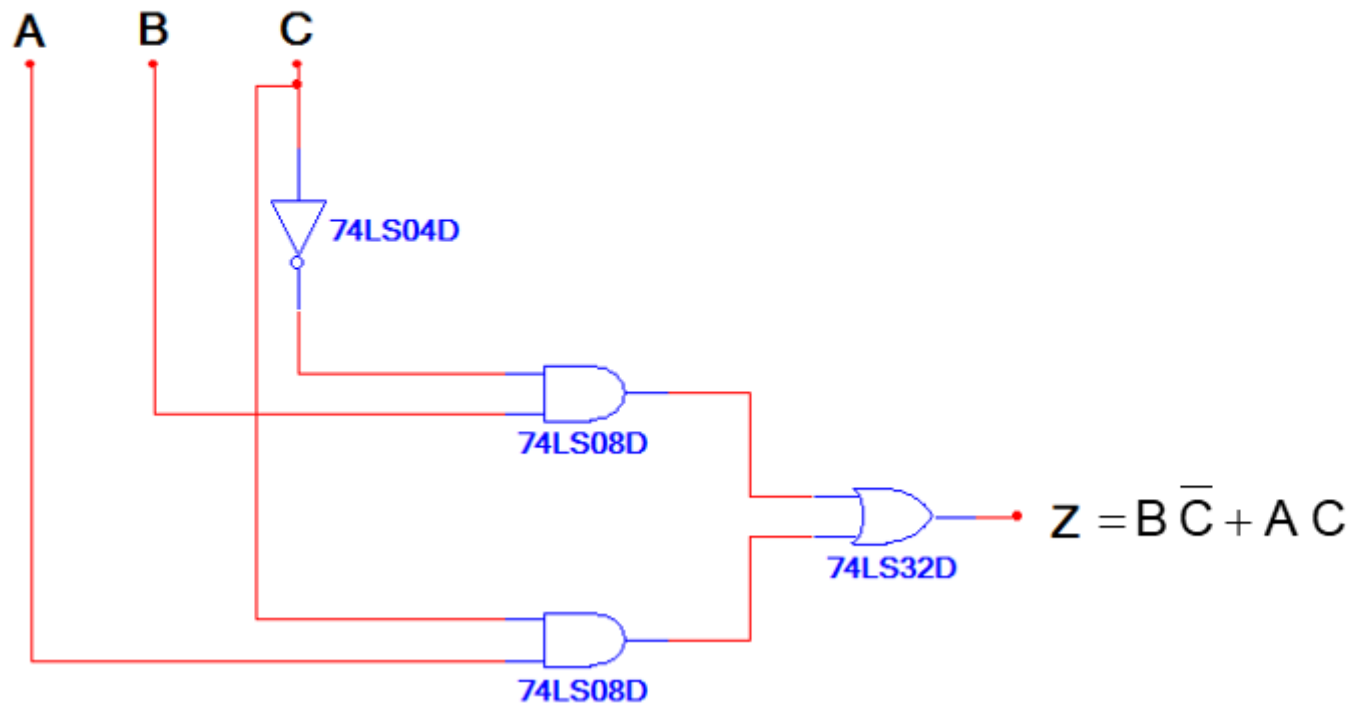
# Example

Design a NOR Logic Circuit that is equivalent to the AOI circuit shown below.






# NOR Implementation
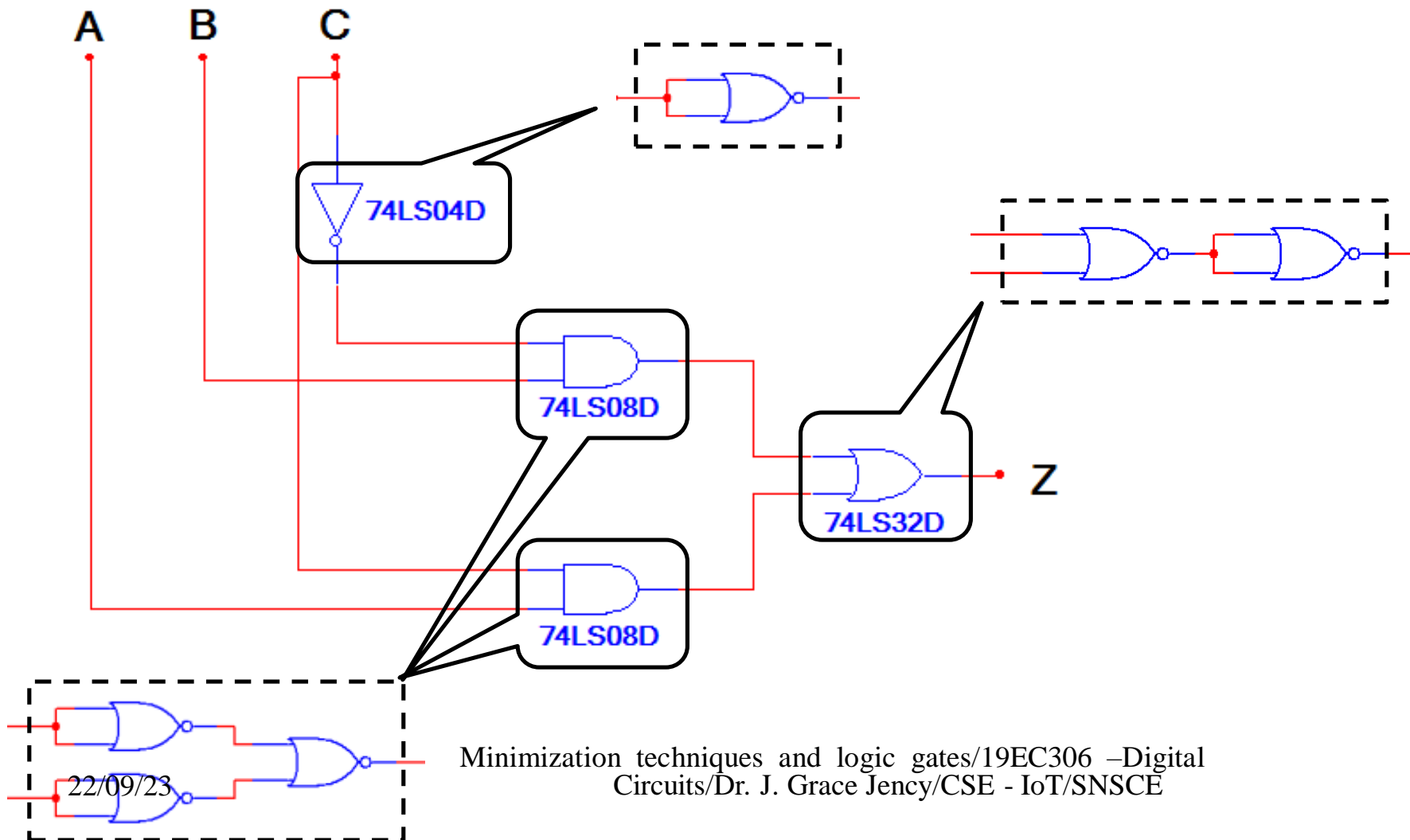
## Solution – Step 2

Identify and replace every AND, OR, and INVERTER gate with its NAND equivalent.






# NOR Implementation

## Solution – Step 3



Redraw Circuit.

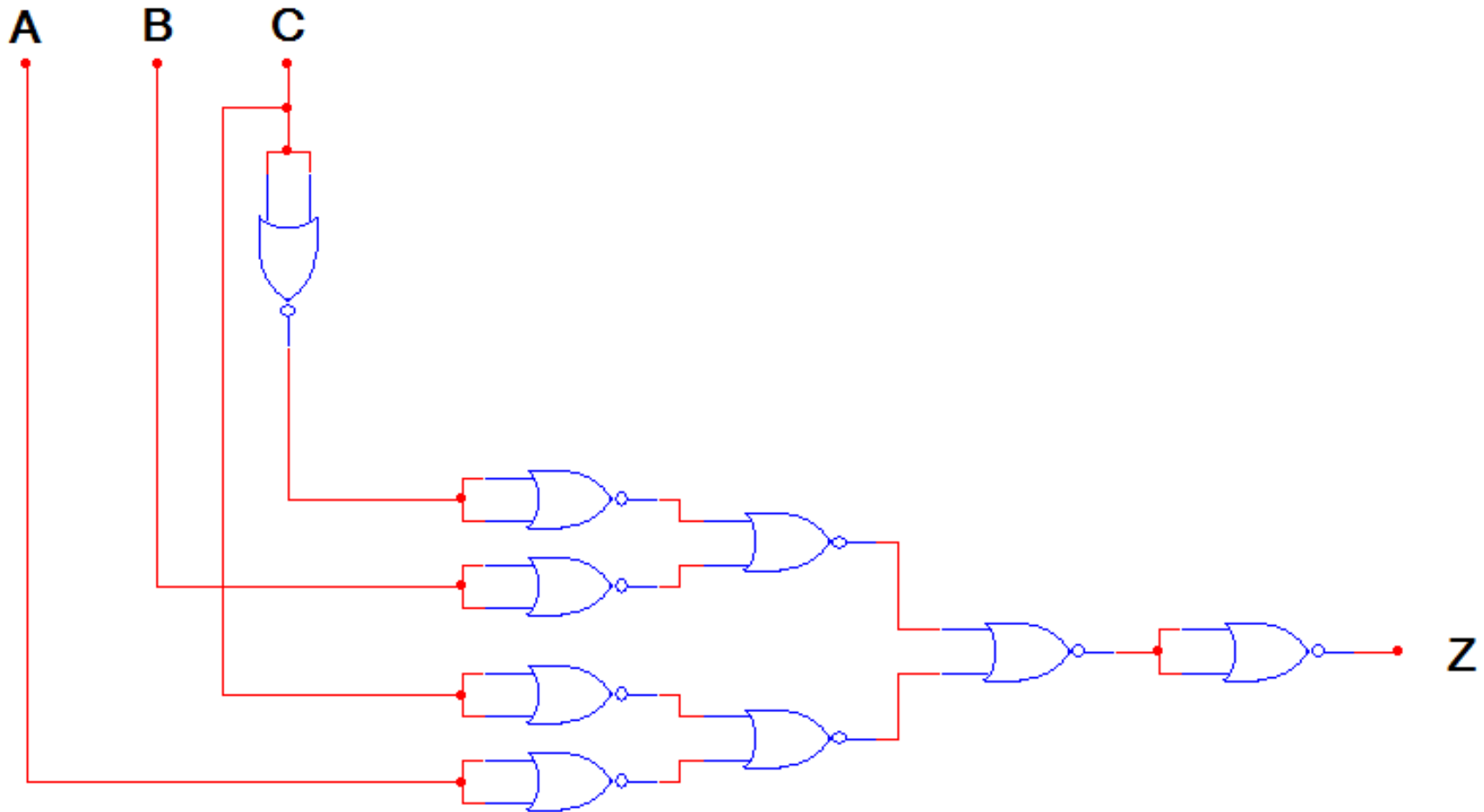




# NOR Implementation
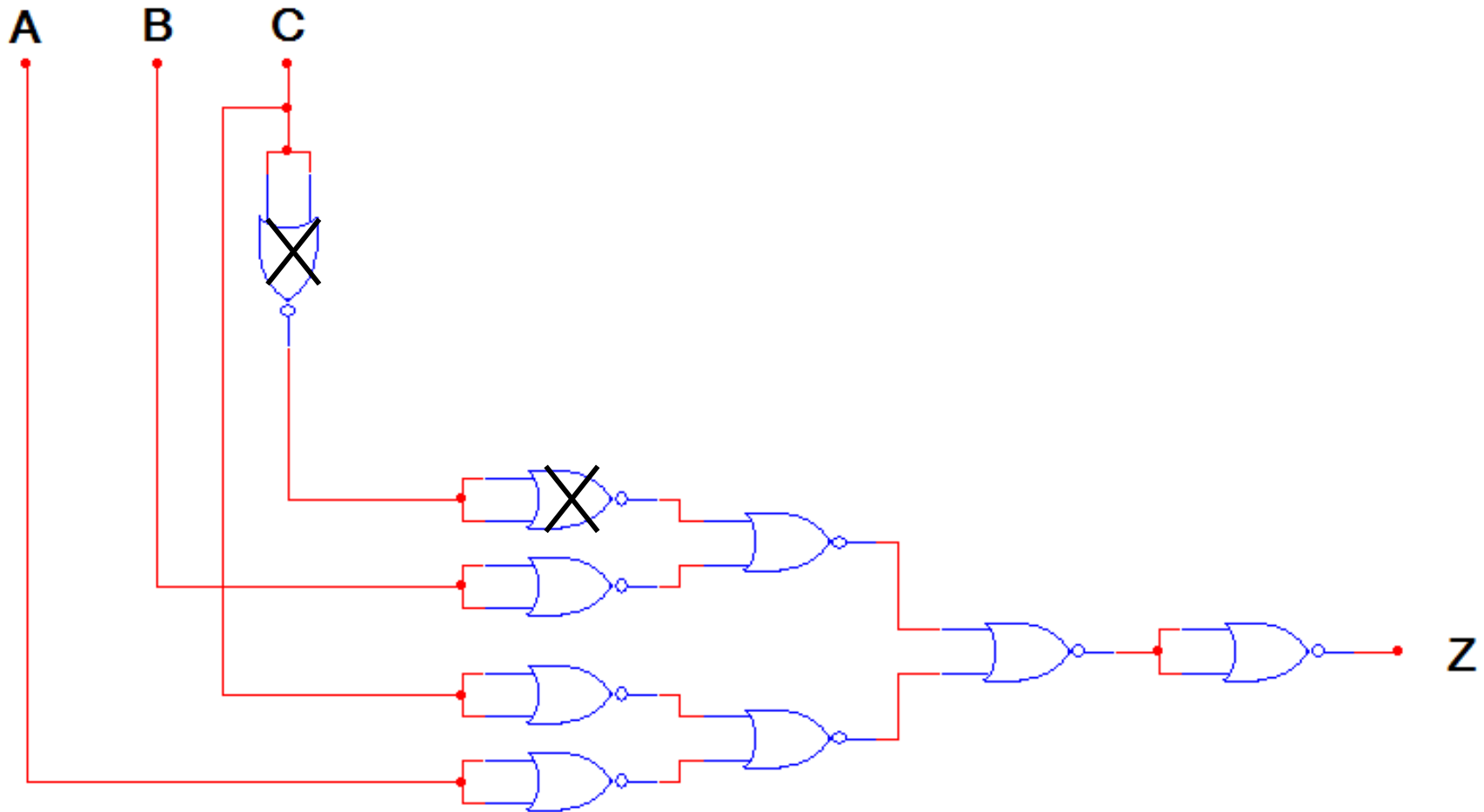
## Solution – Step 4



Identify and eliminate any double inversions.






# NOR Implementation

## Solution – Step 5




Redraw Circuit.

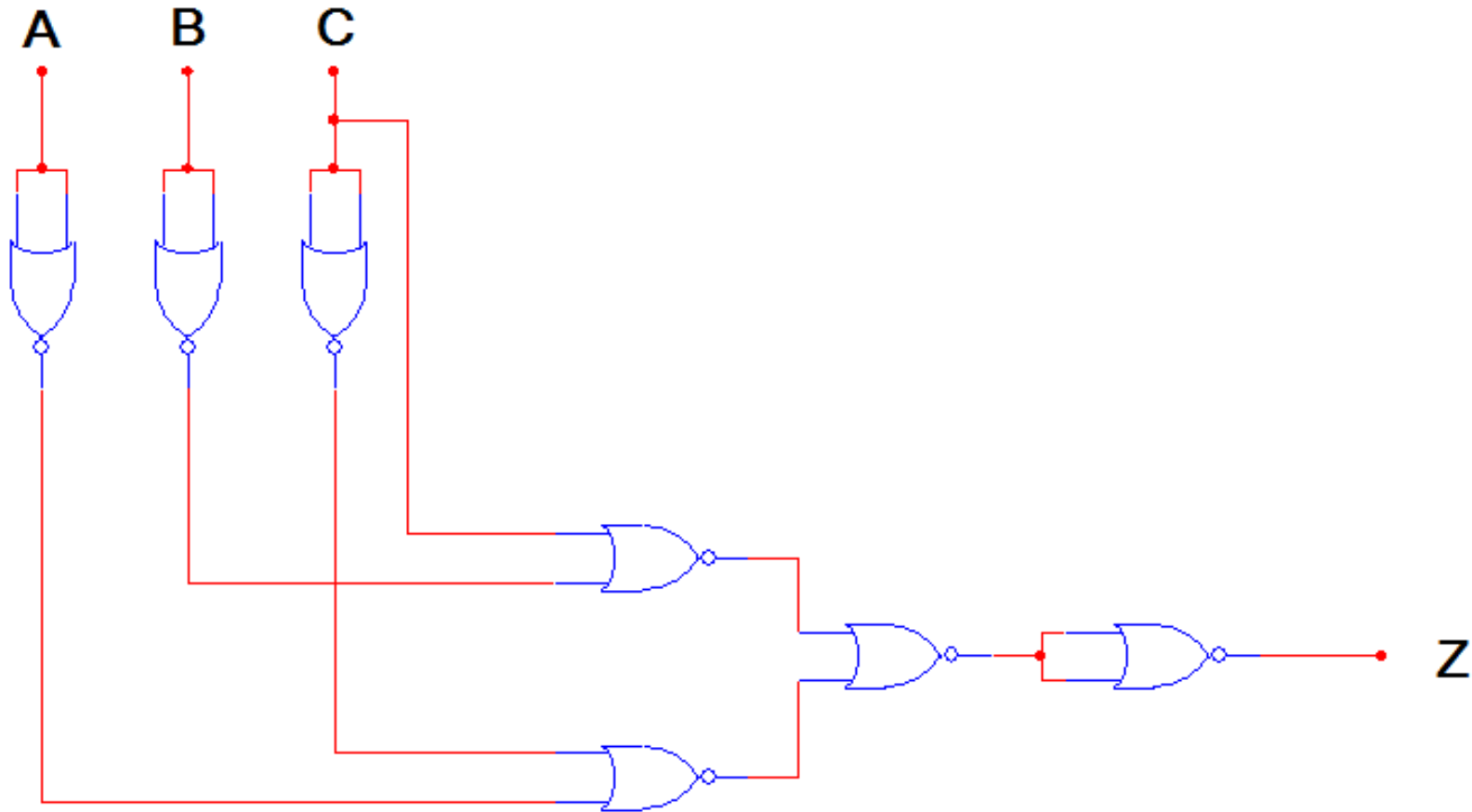



# Proof of Equivalence

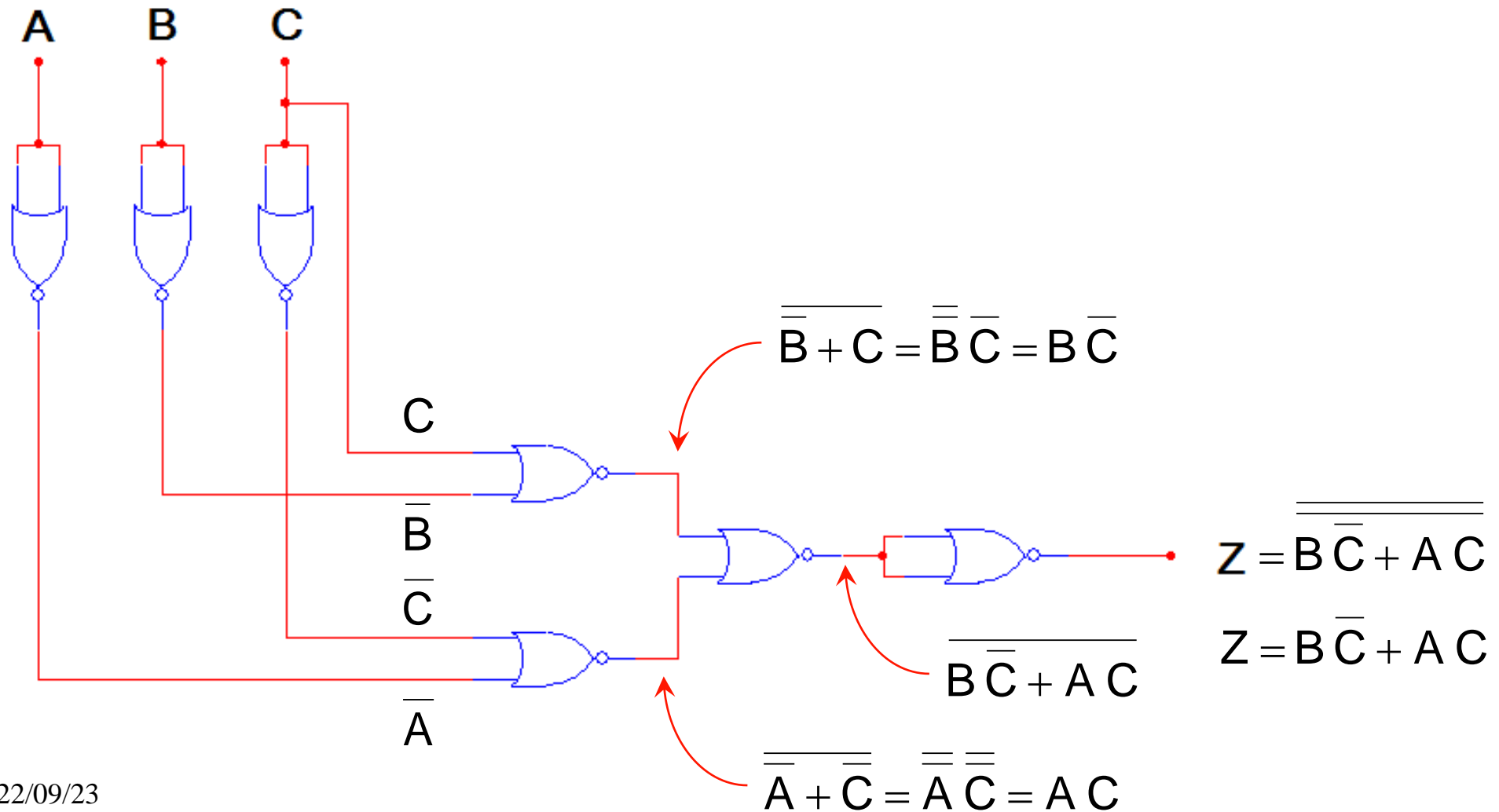

22/09/23



*Thank  
you*