

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech.(ECE)/(EE/EEE)/(EIE) (Sem.-4)

DIGITAL ELECTRONICS

Subject Code : EC-204

Paper ID : [A0307]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A

1. Write briefly :

1. Subtract (23-17) using 2's and 1's complement.
2. Explain term Resolution and accuracy of D/A converter.
3. What is difference between synchronous and ripple counter.
4. What is race around condition and how it is improved?
5. Give the characteristics table of RS and D Flip-flop.
6. Explain difference between combinational and sequential circuits.
7. What are the advantages of CMOS over DTL?
8. Add two BCD numbers 435+375.
9. Explain difference between static and dynamic memory.
10. Explain the function of PRESET and CLEAR in Flip-flop.

SECTION-B

2. Design a BCD to Grey code converter circuit.
3. Explain the working of simultaneous and counter type A/D converter in detail.
4. Explain the totem pole TTL NAND logic families in detail.
5. Explain 3 bit Asynchronous counter using wave form and design MOD-14 Ripple Counter.
6. Solve using K map and implement with the help of NAND gates only

$$F_{(v, w, x, y)} = \prod m(0,1,2,3,8,10,11) + d(13,14,15)$$

SECTION-C

7. Solve using K-map and Q-M methods and implement using NAND gates only.
$$F_{(v, w, x, y, z)} = \sum m(0,1,2,3,9,10,12,16,18,19,29,31) + d(13,14,26).$$
8. Design a MOD-6 up-down counter using JK Flip-flop by avoiding lockout conditions.
9. Write a short note on **any two** :
 - a. Ring counter and Johnson counter.
 - b. Voltage of frequency conversion
 - c. PLA