

Roll No.

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech.(ECE)/(EE/EEE)/(EIE)

(Sem.-4)

**DIGITAL ELECTRONICS**

Subject Code : EC-204

Paper ID : [A0307]

Time : 3 Hrs.

Max. Marks : 60

**INSTRUCTIONS TO CANDIDATES :**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

**SECTION-A**

**1. Write briefly :**

- a) What is a weighted code, give two examples?
- b) Perform the BCD addition of 67 and 58.
- c) Compare a canonical and slandered form.
- d) What is a parity checker?
- e) Write excitation table of a J-K and D flip-flop.
- f) Compare a synchronous and asynchronous counter.
- g) Define resolution and accuracy of D/A converter.
- h) Compare a PLA and PAL.
- i) Define tri-state logic.
- j) What is wired AND gate?

### SECTION-B

2. In a new number system X and Y are successive digits such that  $(XY)_r = (25)_{10}$  and  $(XY)_r = (31)_{10}$  find X, Y, r.
3. Reduce to its minimum sum of products form using theorems only  
 $X = A'B'C'D' + A'B'CD' + AB'C'D' + A'CD + AB'CD'$
4. Implement the following function using  $4 \times 1$  multiplexer  $y = \sum m(0, 2, 6, 8, 9, 11, 13, 15)$
5. What is a dual slope A/D converter? Draw its circuit and explain its working.
6. A ripple counter uses flip-flops having  $t_{pd} = 12$  ns. What can be the largest mode counter constructed from flip-flops and operated at 10 MHz?

### SECTION-C

7. Explain the reading and writing process in a typical Bipolar RAM cell.
8. Give the classification of TTL. Explain working of a totem pole TTL.
9. Design a BCD synchronous up/down counter using J-K flip-flop.