

Roll No. 

|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

Total No. of Questions: 09

Total No. of Pages: 02

**B. Tech. ECE/(EE/EEE)/EIE (Sem. 4)**

**DIGITAL ELECTRONICS**

**Subject Code: EC-204**

**Paper ID: A0307**

Time: 3 Hrs.

Max. Marks: 60

**INSTRUCTIONS TO CANDIDATES:**

1. Section A is **COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. Section B contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. Section C contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

**SECTION A**

1. Explain briefly:
  - a) Convert to BNS to grey code (11110001101).
  - b)  $(213)_8 - (145)_8 = (\text{-----})_8$  and  $(2FC)_{16} + (1CD)_{16} = (\text{-----})_{16}$
  - c) What is race around condition and how it is improved.
  - d) Subtract using 2's and 1's complement (34-14).
  - e) Solve  $(185)_8 = (\text{-----})_{10}$  and  $(ADF)_{16} = (\text{-----})_2$
  - f) What is the difference between combinational and sequential circuits.
  - g) What are the advantages of TTL over DTL
  - h) What are the applications of ring counter.
  - i) Explain terms fan-in, fan-out and Resolution AD Converter.
  - j) What are the applications of Multiplexer?

### SECTION B

2. Solve using K-map and implement using NAND gates only.  
$$F(v,w,x,y) = \prod m(0,1,2, 7,9,11,14,15) + d(4,5)$$
3. Design full adder using 4:1 Multiplexer and 8:1 MUX.
4. Design four bit binary number system to grey code converter.
5. Explain-working of CMOS NAND gate in detail.
6. Explain the working of voltage to time conversion circuit.

### SECTION C

7. Solve using Q-M method and verify the result with K-map. Also implement using NOR gates only.  
$$F(v,w,x,y,z) = \sum m(0,1,2,4,5, 14,15,19,23,25,27,29,31) + d(7,8,9,11)$$
8. (a) Explain the working single slope AID converter.  
(b) Design MOD-5 counter using JK Flip-flops.
9. Design MOD-6 up-down counter using D flip-flops.