



**SNS COLLEGE OF ENGINEERING**  
**(Autonomous)**  
**DEPARTMENT OF CSE - IoT**



**COURSE NAME:19EC306 / DIGITAL CIRCUITS**  
**II YEAR/III SEMESTER**

**UNIT:1- MINIMIZATION TECHNIQUES AND LOGIC GATES**

**TOPIC:SUM OF PRODUCTS & PRODUCTS OF SUM**



# Karnaugh map - Outline

- Feel a little difficult using Boolean algebra laws, rules, and theorems to simplify logic?
- A K-map provides a systematic method for simplifying Boolean expressions and, if properly used, will produce the simplest SOP or POS expression possible, known as the minimum expression.

# K – Map – SOP Reduction



- After an SOP expression has been mapped, we can do the process of *minimization*:
  - Grouping the 1s
  - Determining the minimum SOP expression from the map
- You can group 1s on the K-map according to the following rules by enclosing those adjacent cells containing 1s.
- **The goal** is to maximize the size of the groups and to minimize the number of groups.


# K – Map – SOP Reduction



Minimize the following boolean function-

$$F(A, B, C, D) = \Sigma m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$$

Then, we have-

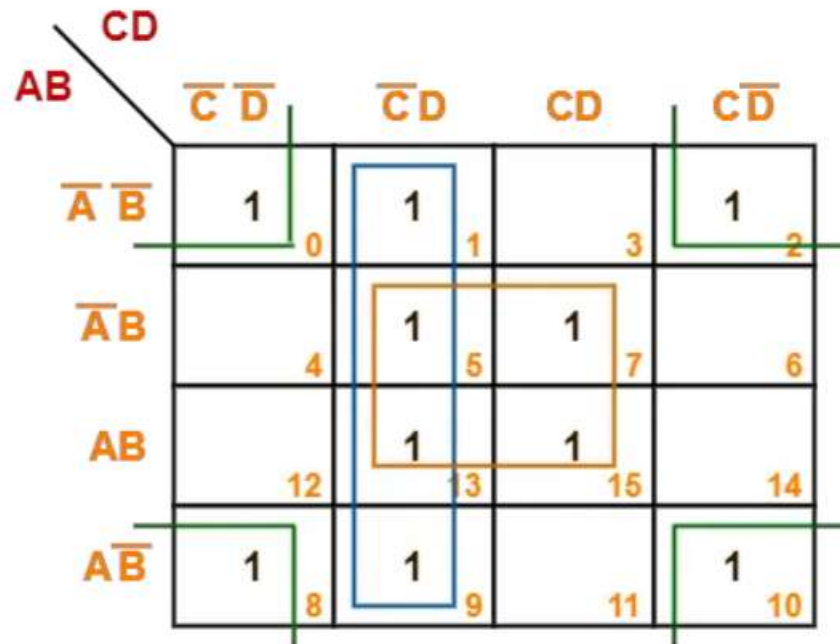

Thus, minimized boolean expression is-

$$F(A, B, C, D) = BD + C'D + B'D'$$



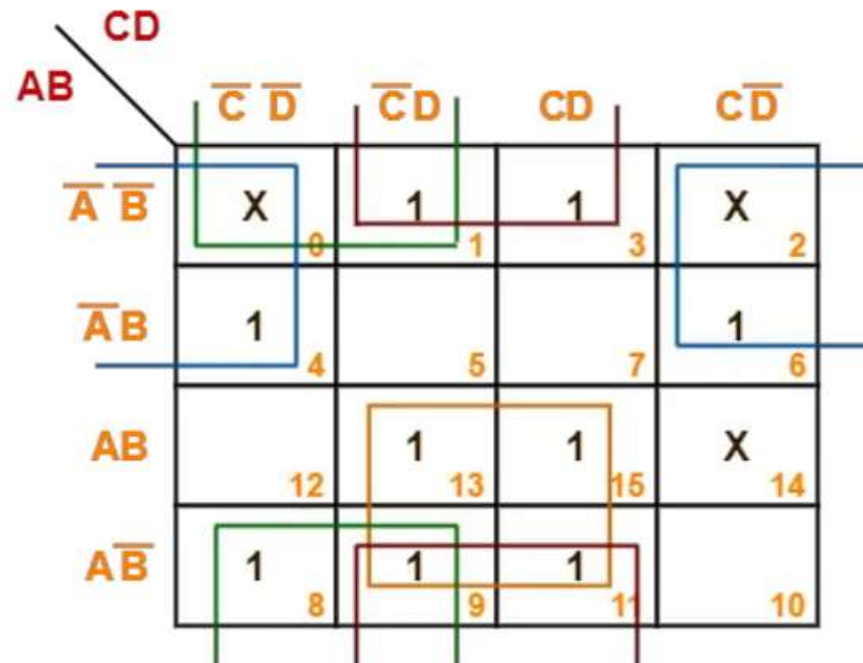
# K- Map Examples



Minimize the following boolean function-

$$F(A, B, C, D) = \Sigma m(1, 3, 4, 6, 8, 9, 11, 13, 15) + \Sigma d(0, 2, 14)$$



Thus, minimized boolean expression is-

$$F(A, B, C, D) = AD + B'D + B'C' + A'D'$$



# K – Map – POS Reduction



- The approaches are much the same (as SOP) except that with POS expression, 0s representing the standard sum terms are placed on the K-map instead of 1s.

The expression:

$$(A+B+C)(A+\bar{B}+C)(\bar{A}+\bar{B}+C)(\bar{A}+B+\bar{C})$$


000    010    110    101

		C	
		0	1
AB	00	0	
	01	0	
	11	0	
	10		0
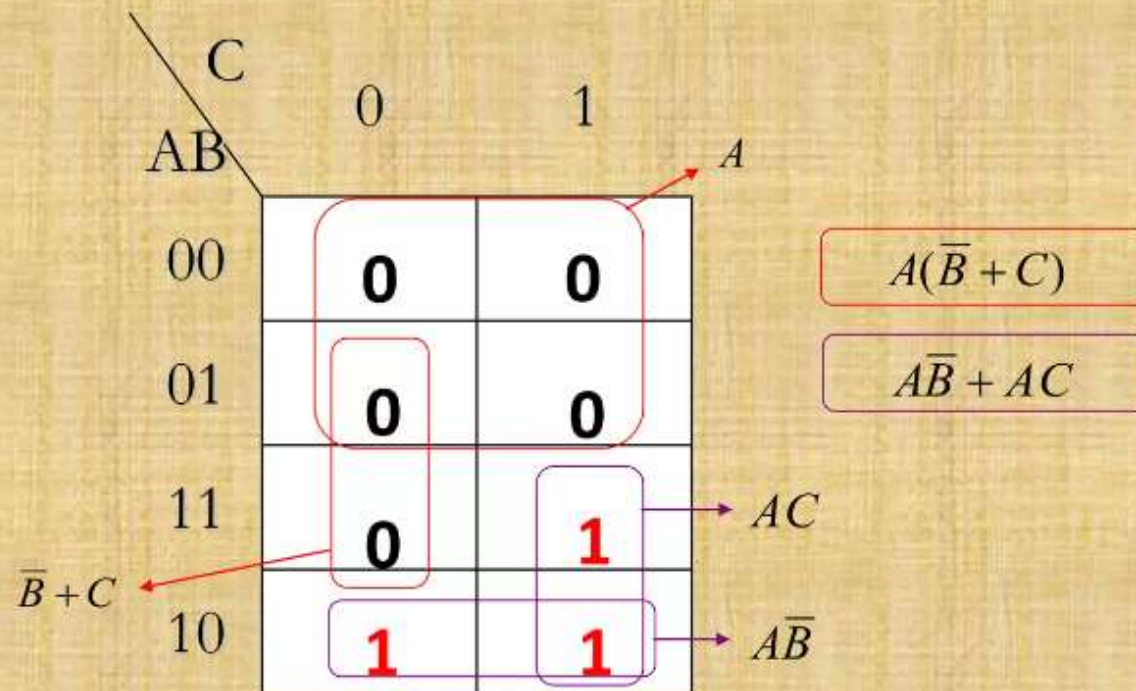
# Contd....



$$\underline{(A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+C)}$$





# Design of combinational digital circuit



- From the problem statement derive the truth table
- From the truth table derive the unsimplified logic expression
- Simplify the logic expression
- From the simplified expression draw the logic circuit





*Thank  
you*