



SNS COLLEGE OF TECHNOLOGY

**Coimbatore-35
An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

16EC303–VLSI DESIGN

III YEAR/ V SEMESTER

UNIT III-SEQUENTIAL LOGIC CIRCUITS

TOPIC 1-STATIC LATCHES AND DYNAMIC REGISTERS



OUTLINE



- **LATCH VERSUS REGISTER**
- **LATCH-BASED DESIGN**
 - MUX,
 - MASTER SLAVE REGISTER
- **ACTIVITY**
- **TIME,CLK BASED LATCHES**
- **PULSE-TRIGGERED LATCHES**
- **SUMMARY**



Introduction – Latches and Registers



REGISTER

- Used to hold the system state. Clock pulse is applied to the registers. On the rising edge of the clock pulse, the next state bits are copied to the output of the registers .

Two Types

1. **Positive edge triggered** – input is copied on positive edge of clock.
2. **Negative edge triggered** - input is copied on negative edge of clock.

LATCH

- Level sensitive circuit which is used to pass the D input to the Q output when clock is high.

SET UP TIME

- Time during which the data input is valid before the transition of the clock pulse.

HOLD TIME

- Time during which the data input remains valid after the edge of the clock pulse.


CONTAMINATION DELAY – Minimum Delay




LATCH VERSUS REGISTER



- Latch
stores data when
clock is low

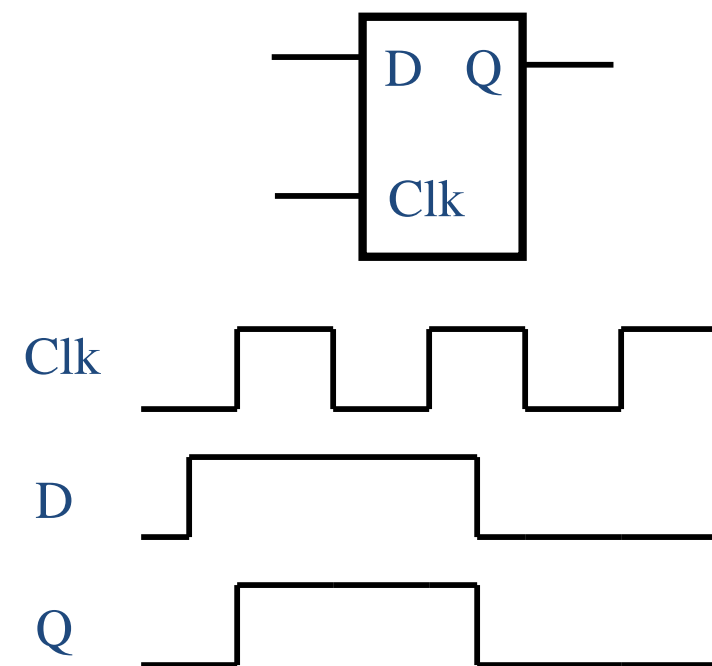

- Register
stores data when
clock rises

 





LATCHES



Positive Latch

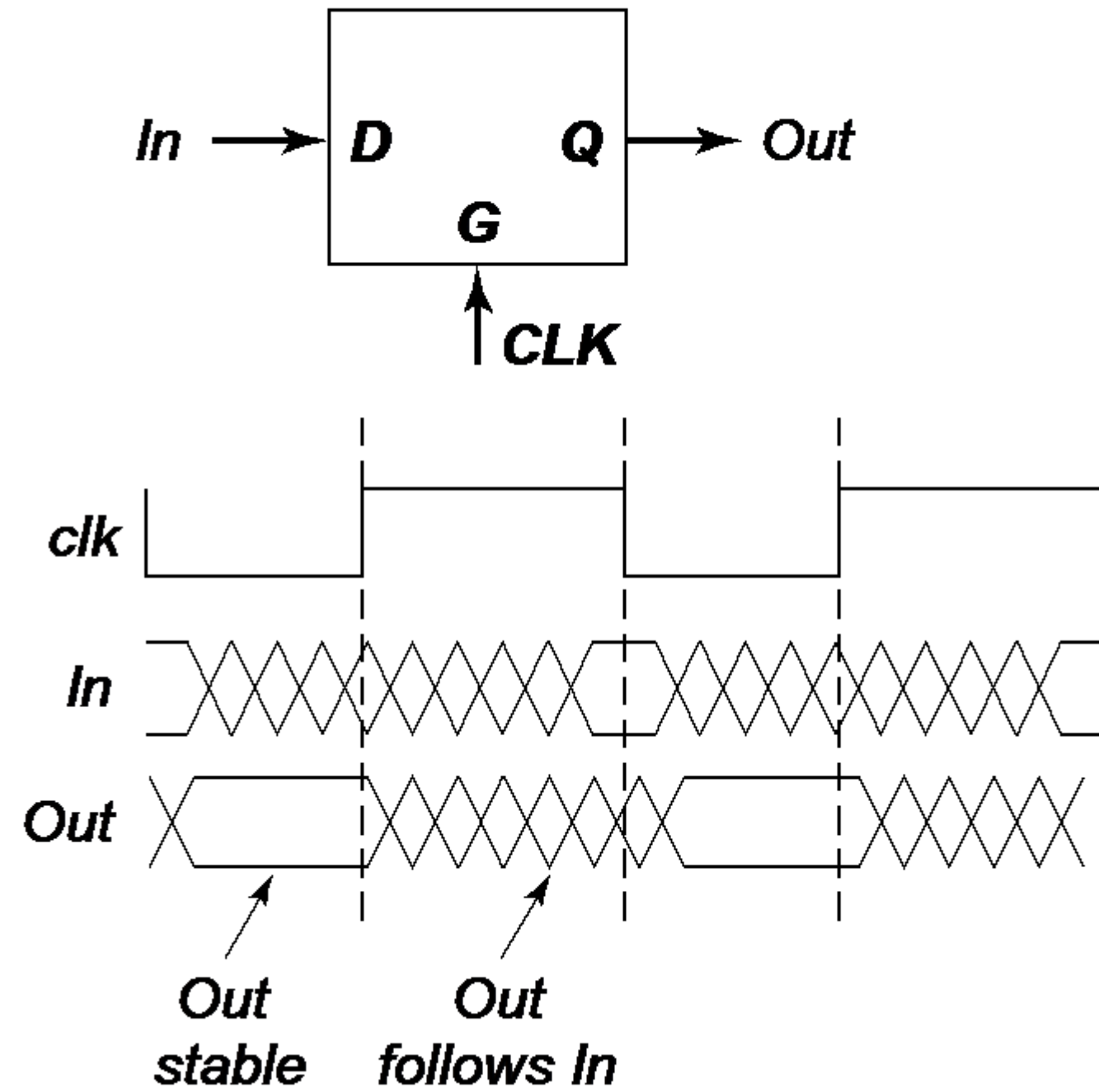

Negative Latch

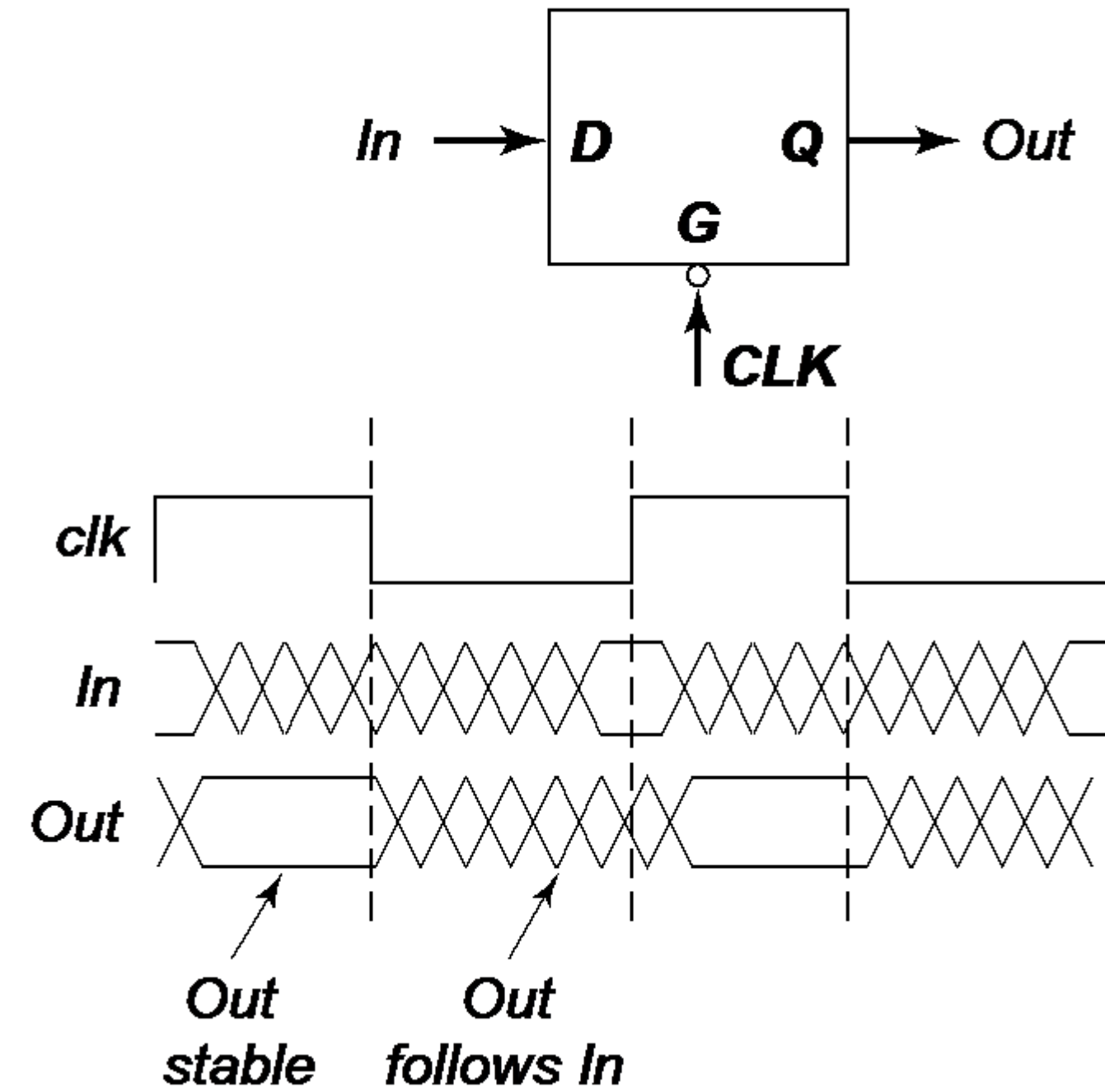




LATCH-BASED DESIGN




- N latch is transparent when $f = 0$

- P latch is transparent when $f = 1$

 





TIMING DEFINITIONS

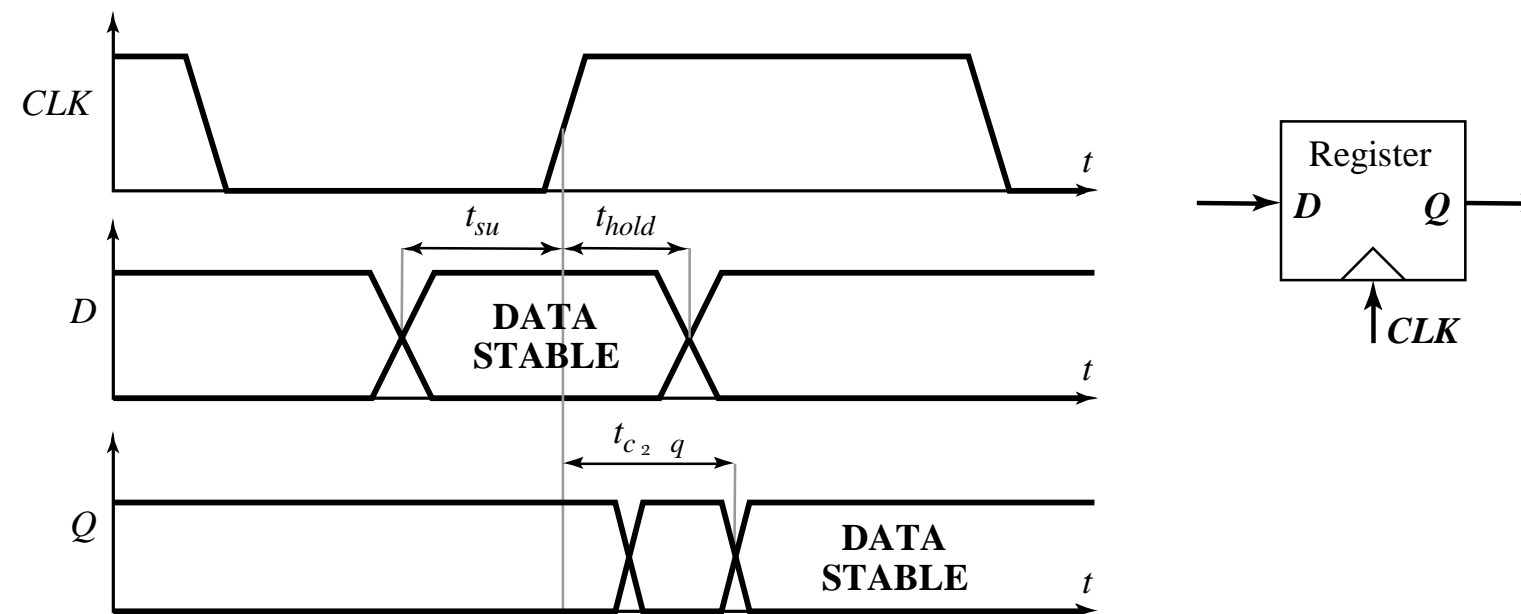




POSITIVE FEEDBACK: BI-STABILITY

  



META-STABILITY

 


Gain should be larger than 1 in the transition region




WRITING INTO A STATIC LATCH

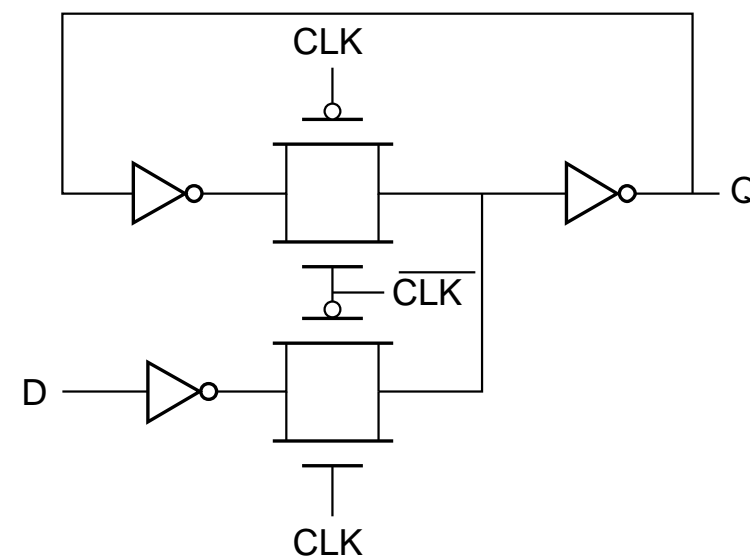Use the clock as a decoupling signal,
that distinguishes between the transparent and opaque states




Converting into a MUX

 

Forcing the state
(can implement as NMOS-only)



MUX-BASED LATCH

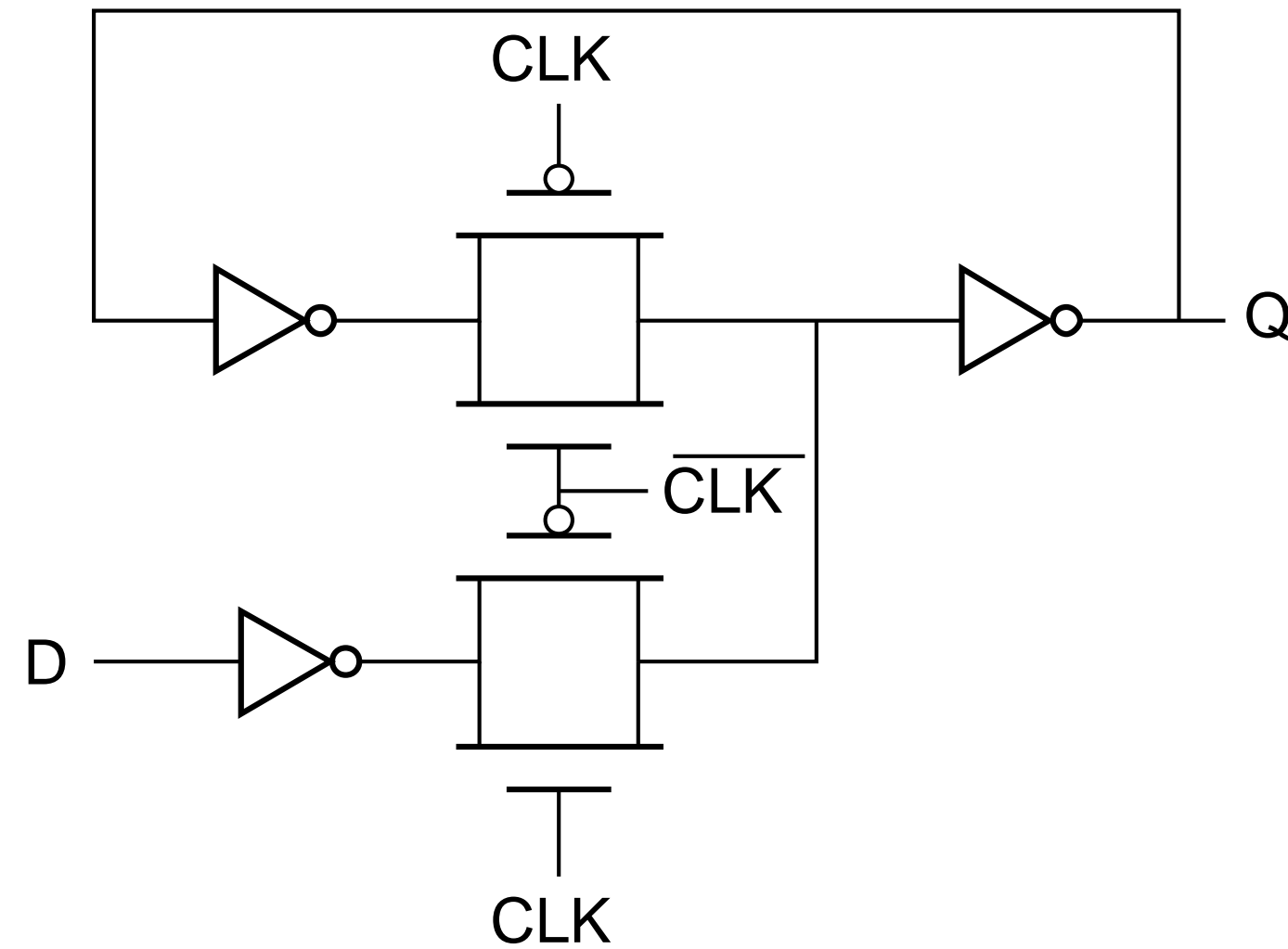




MUX-BASED LATCHES




Negative latch
(transparent when CLK= 0)

 

$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$



Positive latch
(transparent when CLK= 1)

 

$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$



MUX-BASED LATCH

 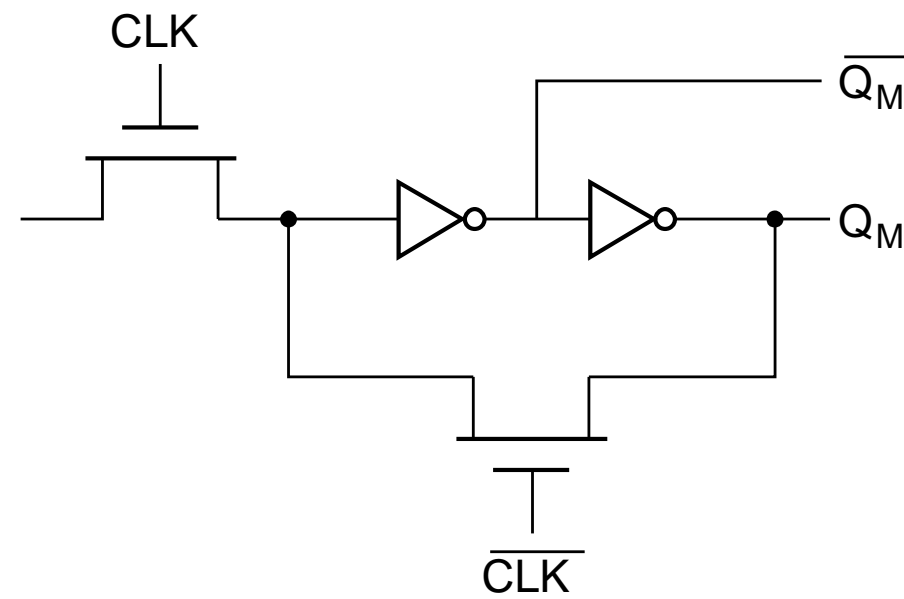


NMOS only

Non-overlapping clocks



MASTER-SLAVE (EDGE-TRIGGERED) REGISTER

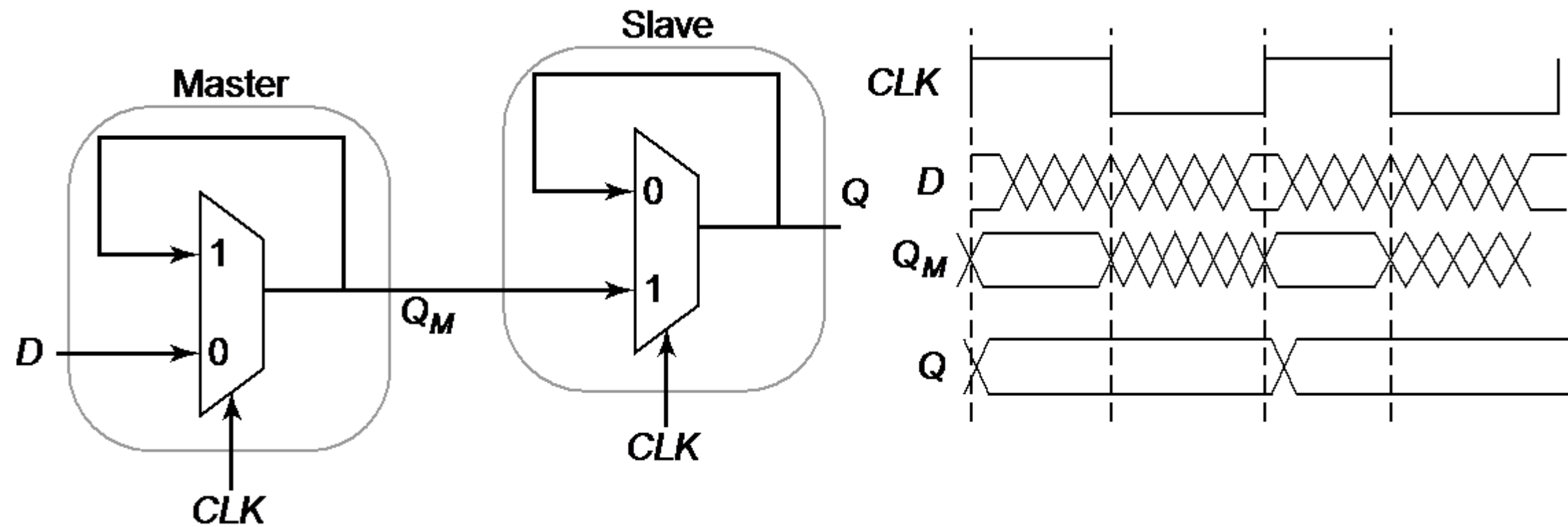


Two opposite latches trigger on edge
Also called master-slave latch pair



MASTER-SLAVE REGISTER




Multiplexer-based latch pair

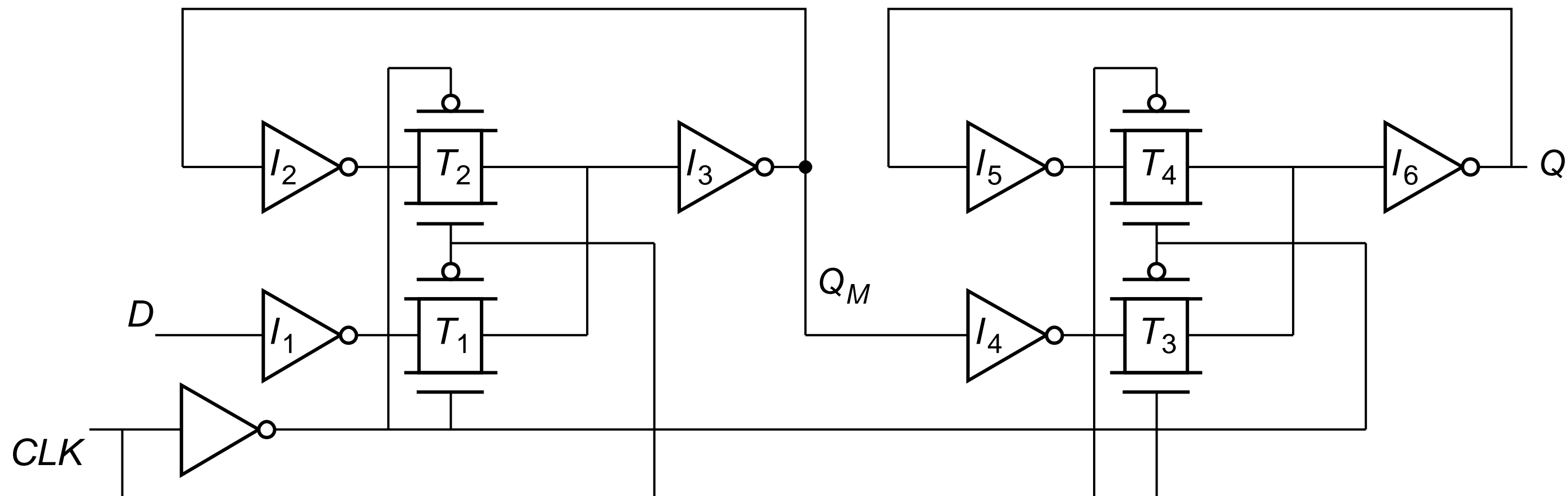




CLK-Q DELAY

 




SETUP TIME

 

 
(a) $T_{\text{setup}} = 0.21 \text{ nsec}$



(b) $T_{\text{setup}} = 0.20 \text{ nsec}$




REDUCED CLOCK LOAD MASTER-SLAVE REGISTER

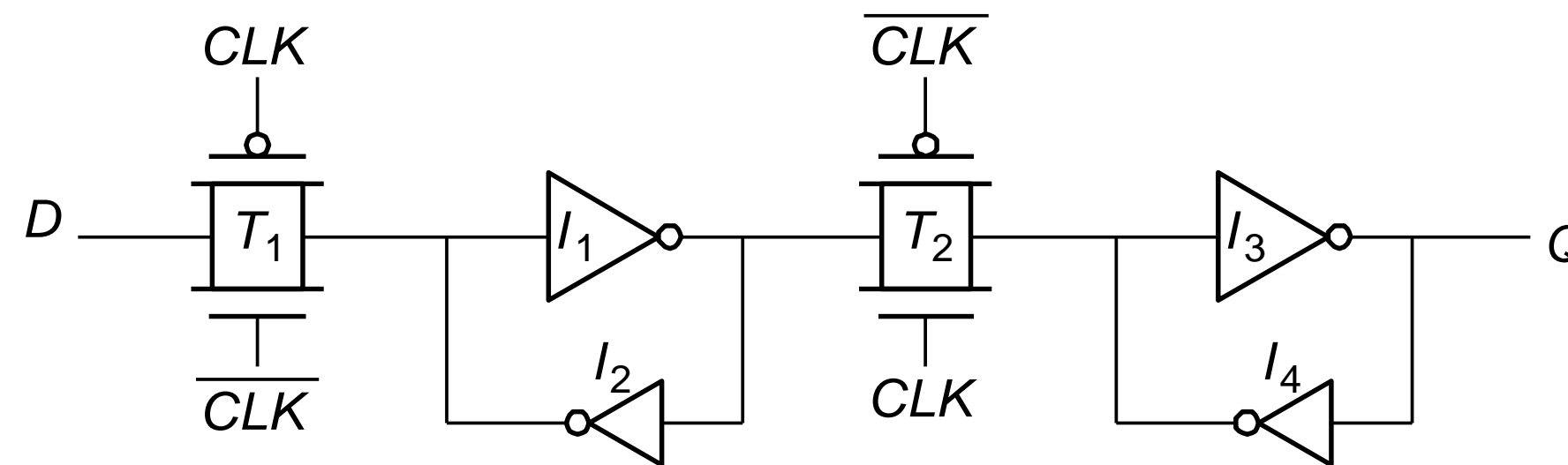




AVOIDING CLOCK OVERLAP

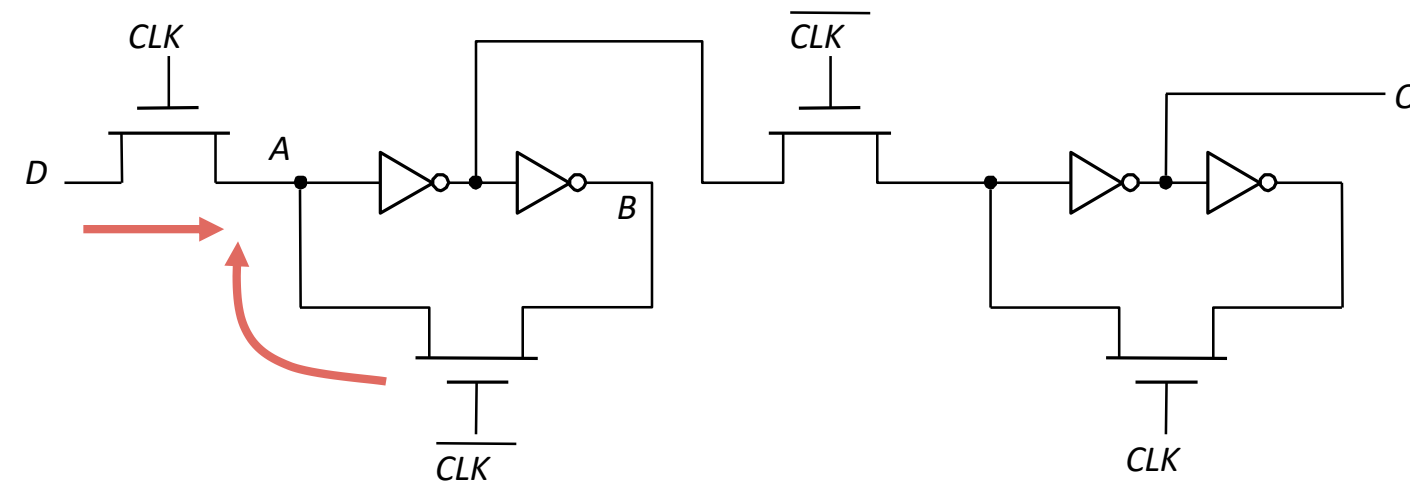


a) Schematic diagram

 

b) Overlapping clock pairs




OTHER LATCHES/REGISTERS: C²MOS

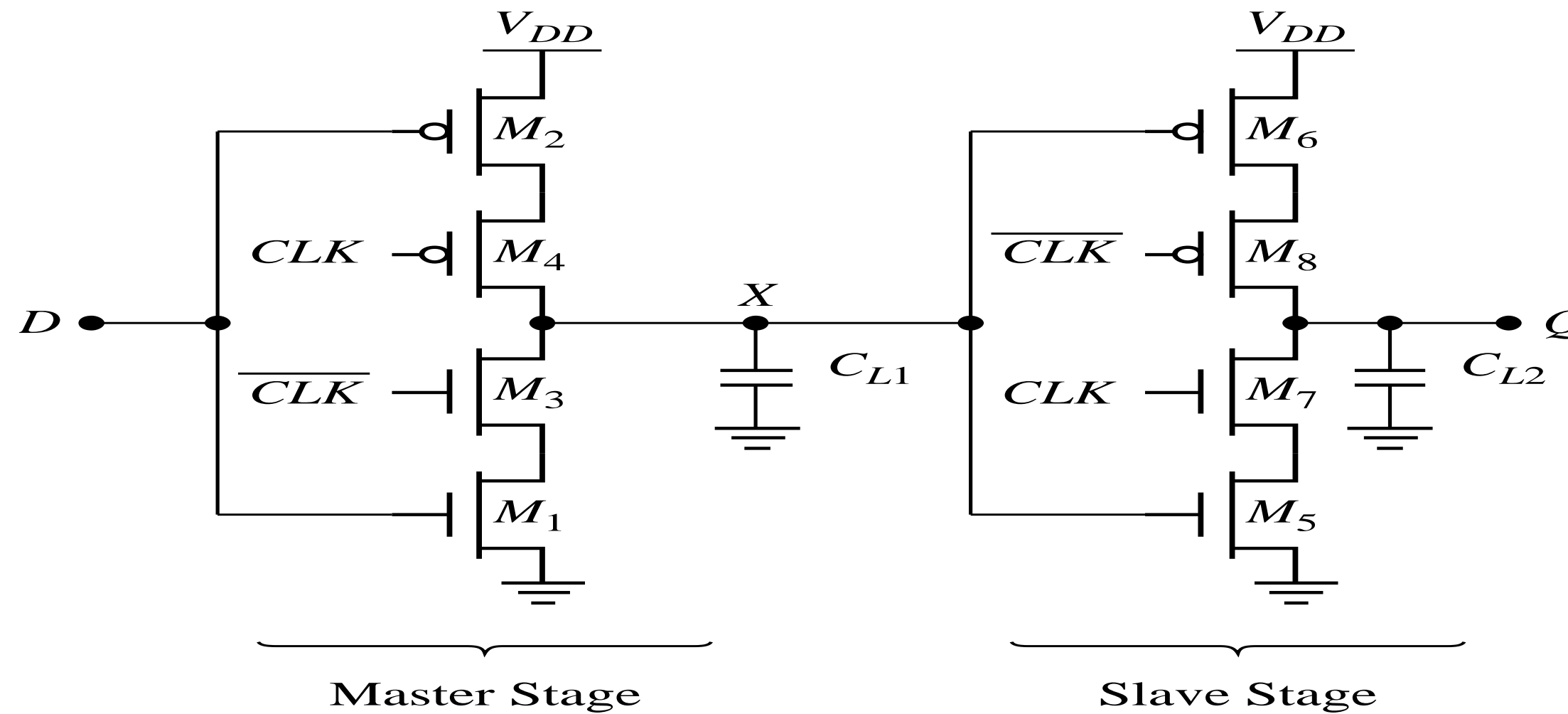

“Keepers” can be added to make circuit pseudo-static




INSENSITIVE TO CLOCK-OVERLAP

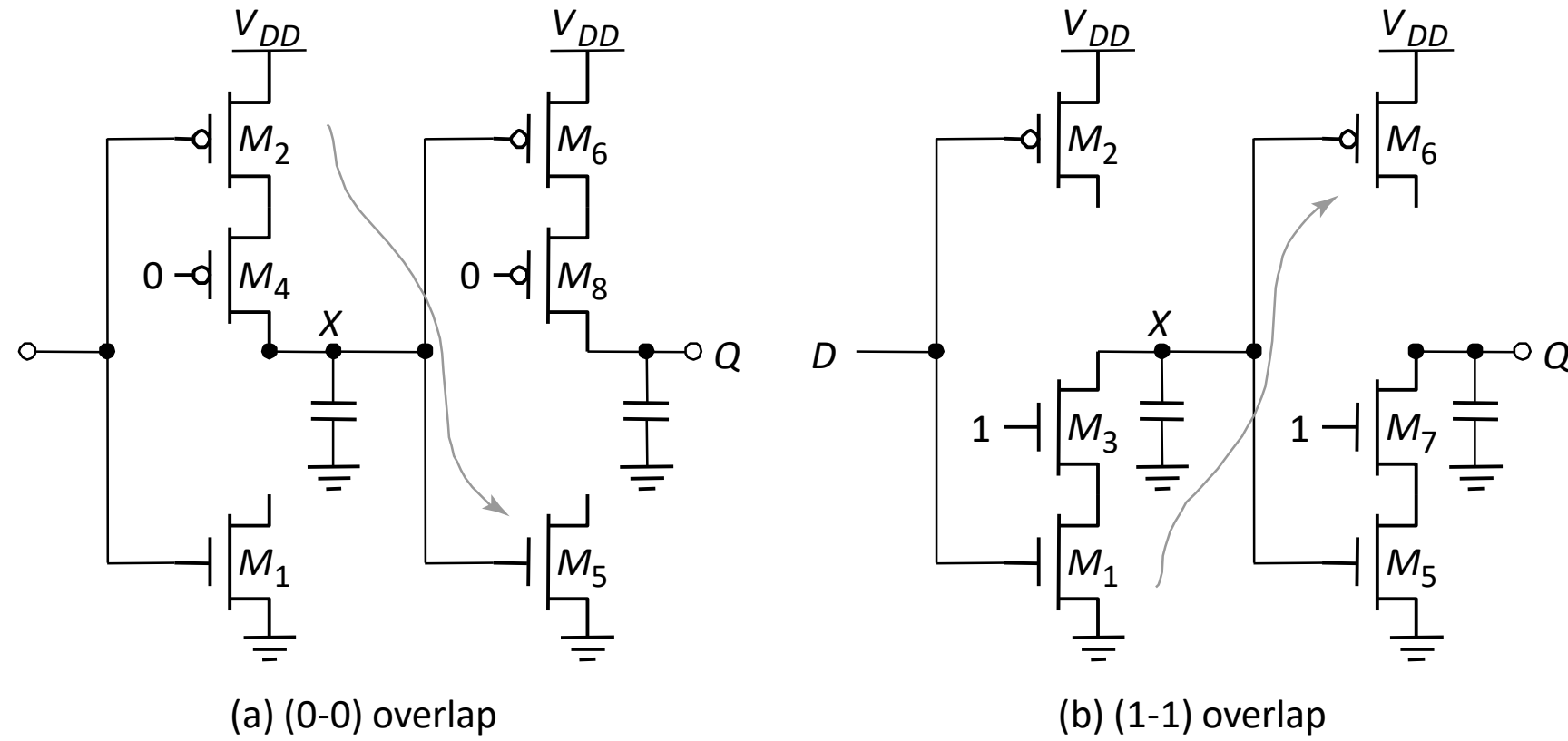



OTHER LATCHES/REGISTERS: TSPC

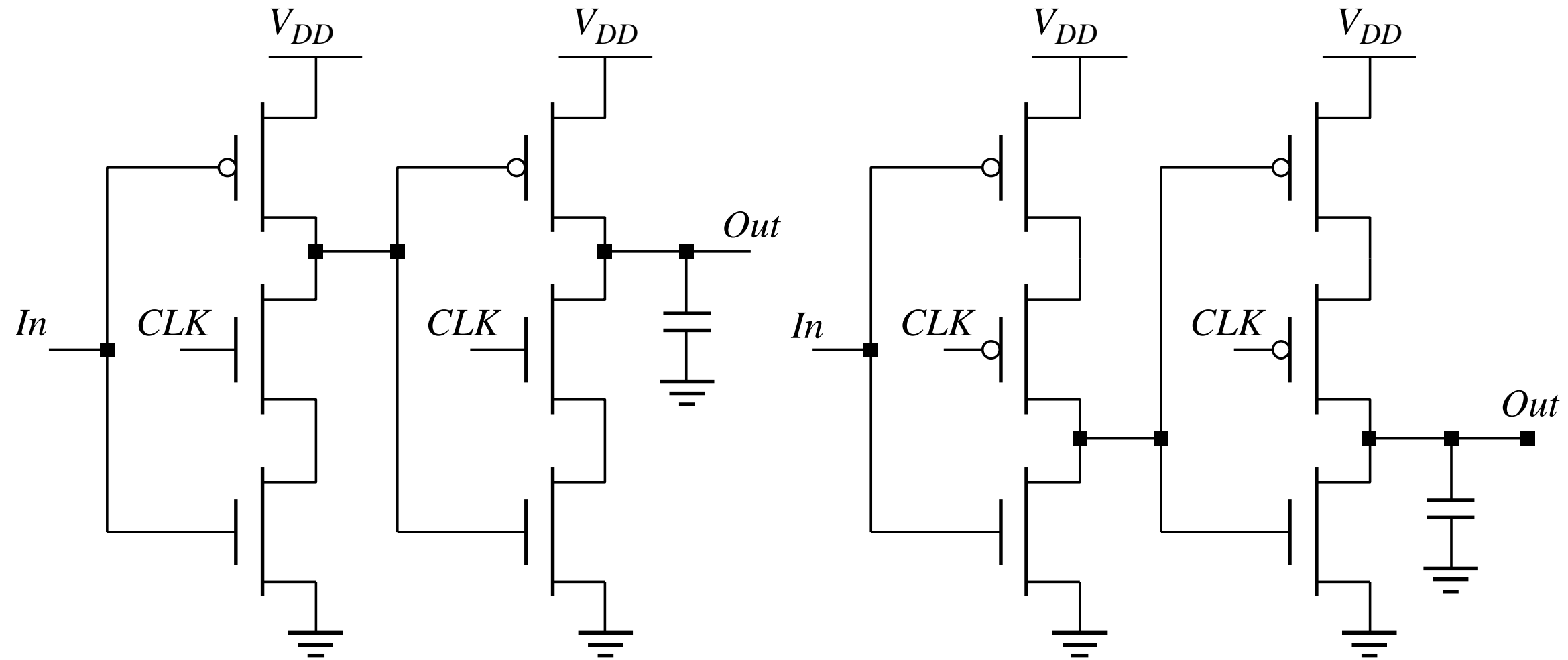


Positive latch
(transparent when CLK= 1)

Negative latch
(transparent when CLK= 0)






INCLUDING LOGIC IN TSPC

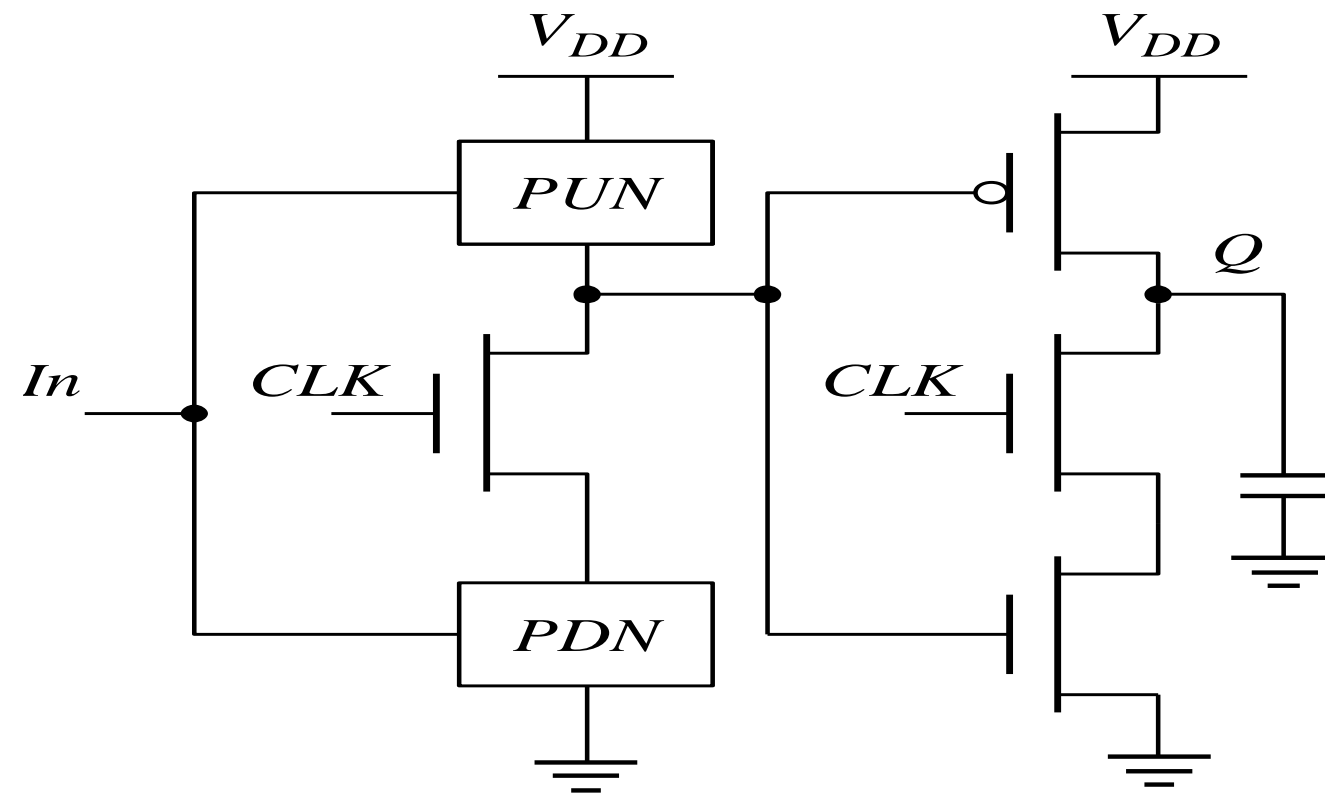

Example: logic inside the latch

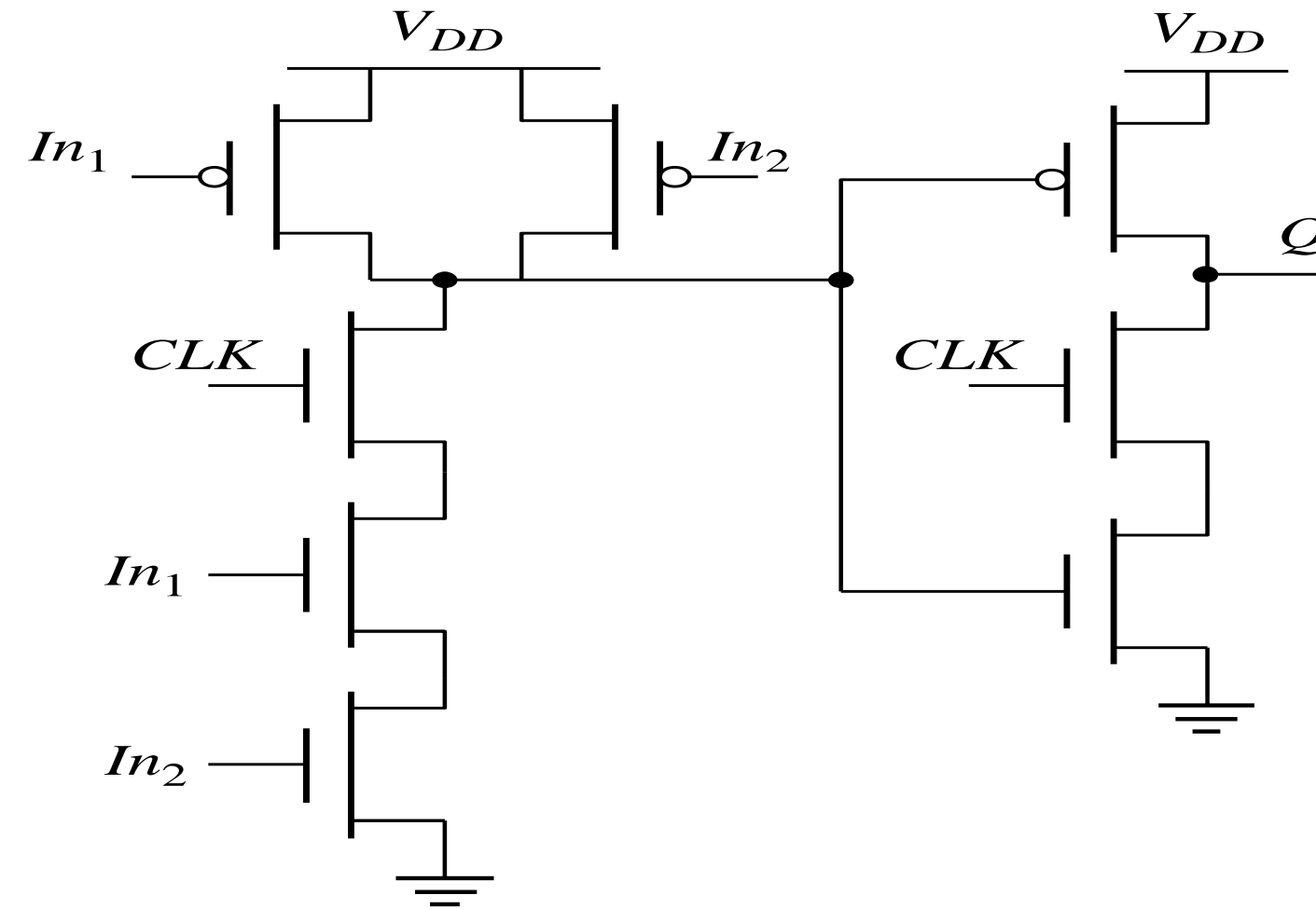


AND latch





TSPC REGISTER

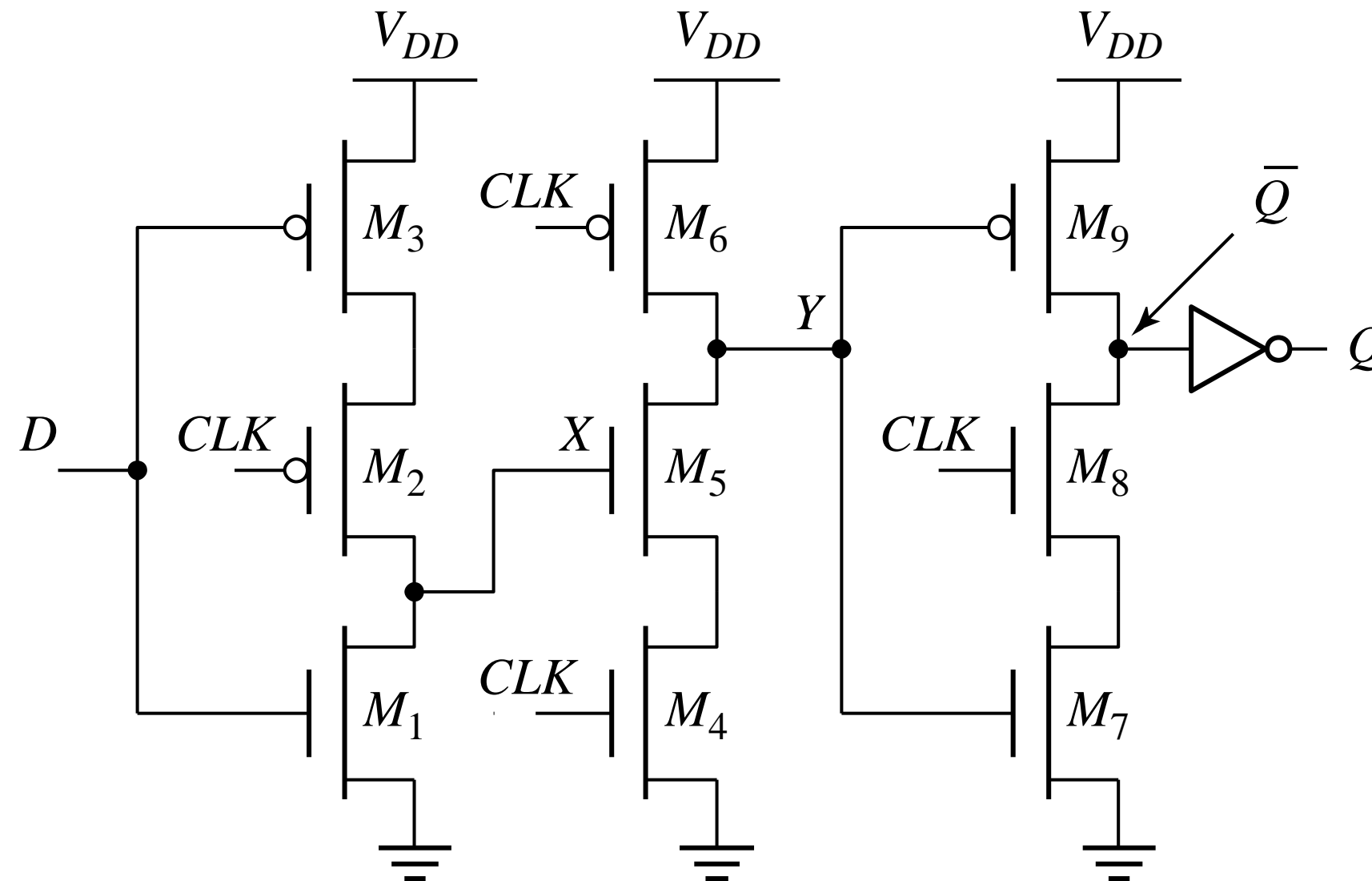




PULSE-TRIGGERED LATCHES AN ALTERNATIVE APPROACH




Ways to design an edge-triggered sequential cell:

Master-Slave Latches

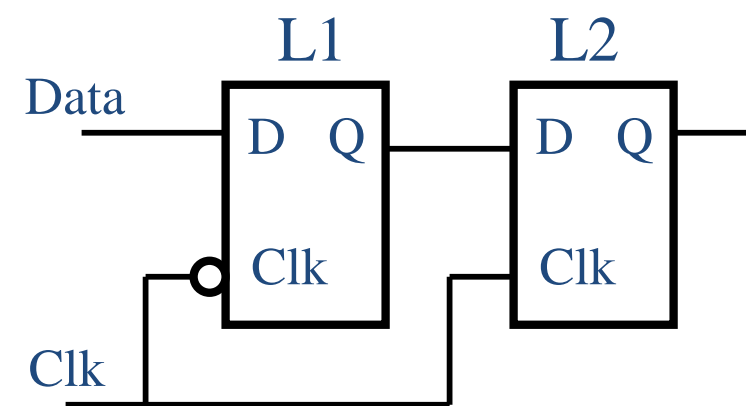

Pulse-Triggered Latch

 



ASSESSMENT



1. Compare Latch vs Register
2. Define Bi stability
3. Draw Master slave flip flop using latches





SUMMARY & THANK YOU