



# SNS COLLEGE OF TECHNOLOGY

Coimbatore-35  
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

### 19EC306 – DIGITAL CIRCUITS

II YEAR/ III SEMESTER


### UNIT 2 – COMBINATIONAL CIRCUITS

### TOPIC – DEMULTIPLEXER


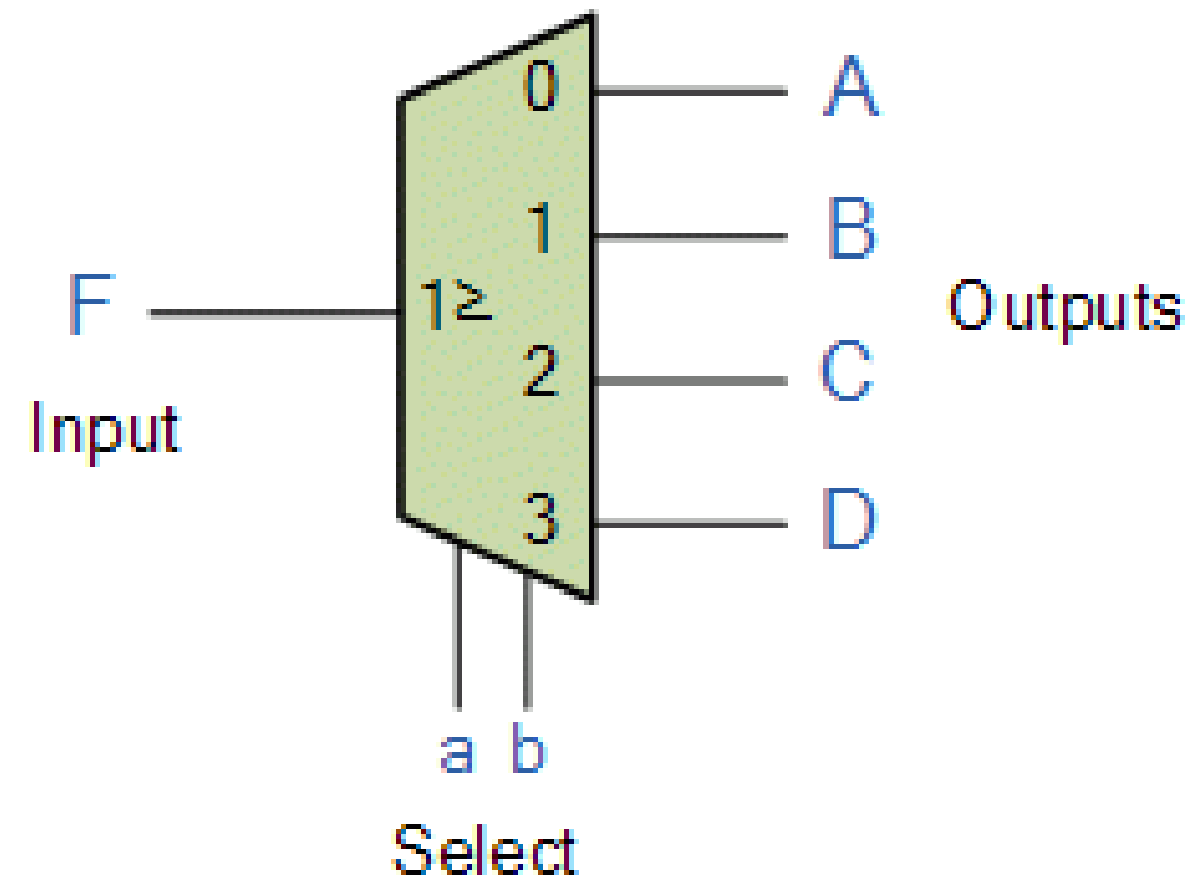
## What is De Multiplexer?

- De-Multiplexer is a combinational circuit that performs the reverse operation of Multiplexer. It has single input, 'n' selection lines and maximum of  $2^n$  outputs.
- One of these data inputs will be connected to the output based on the values of selection lines..





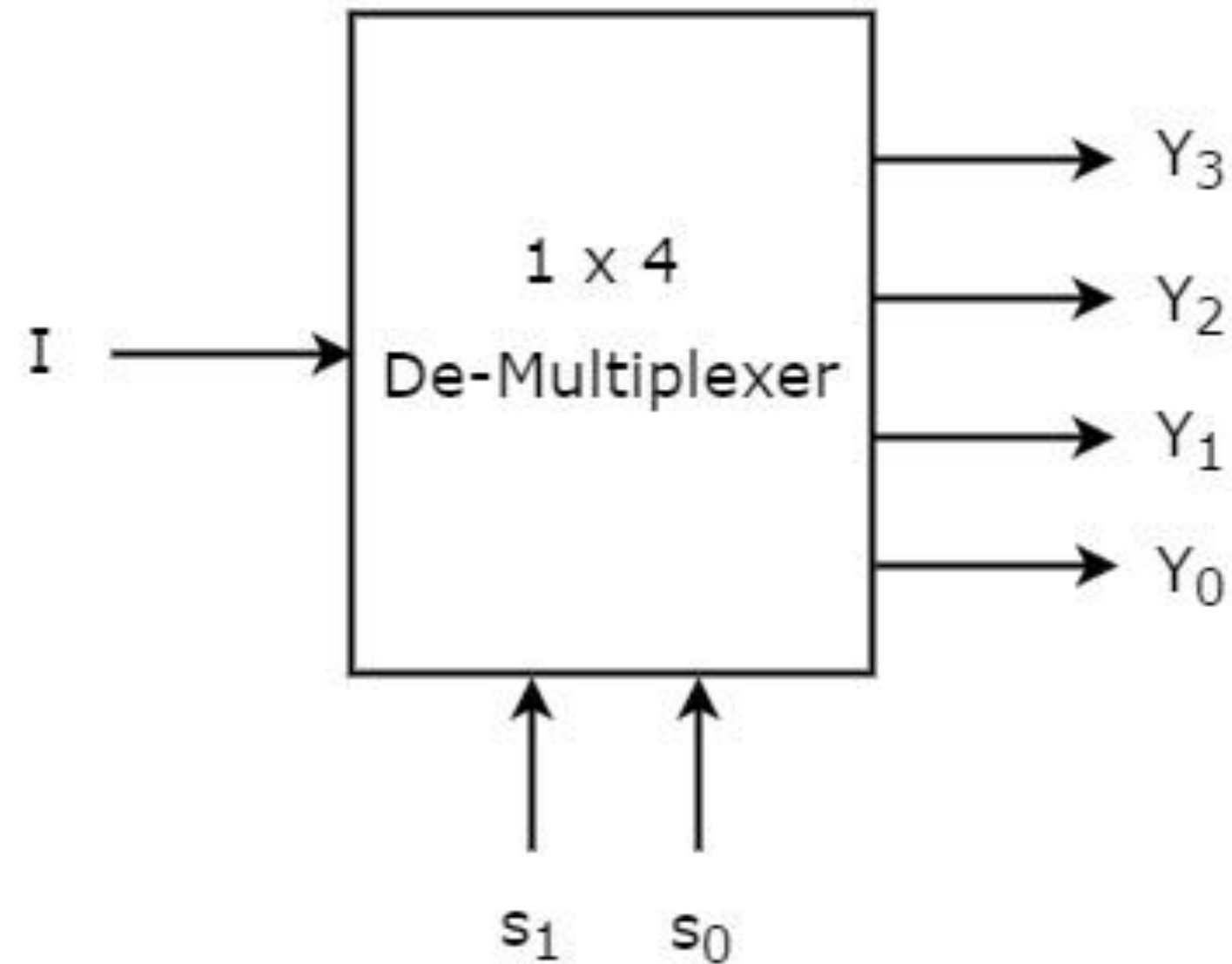
# 1x4 De-Multiplexer



- 1x4 De-Multiplexer has one input I, two selection lines, s1 & s0 and four outputs Y3, Y2, Y1 & Y0.






- The single input 'I' will be connected to one of the four outputs, Y3 to Y0 based on the values of selection lines s1 & s0. The Truth table of 1x4 De-Multiplexer is shown below.

Selection Inputs		Outputs			
S <sub>1</sub>	S <sub>0</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0



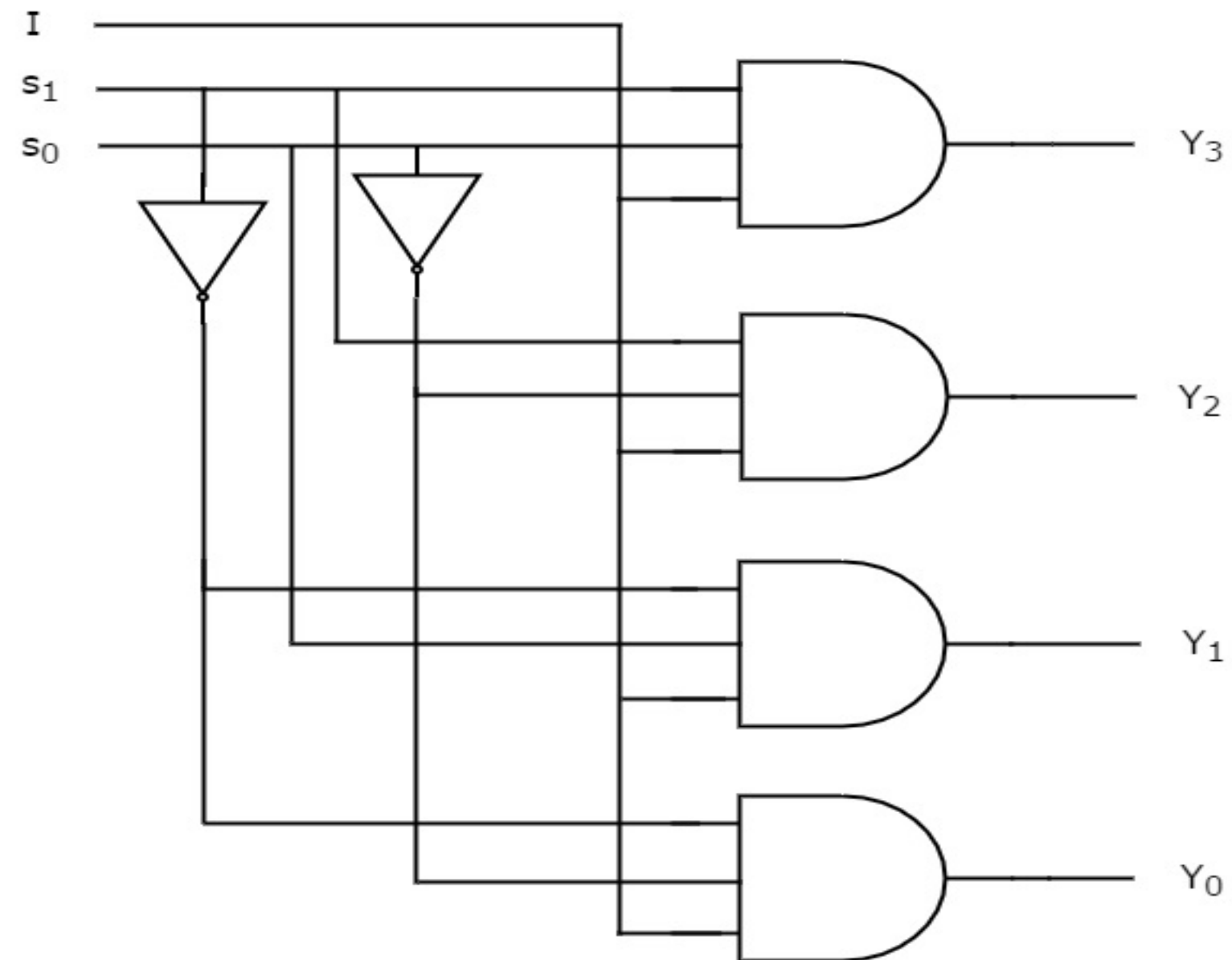We can implement these Boolean functions using Inverters & 3-input AND gates. The circuit diagram of 1x4 De-Multiplexer is shown in the following figure.





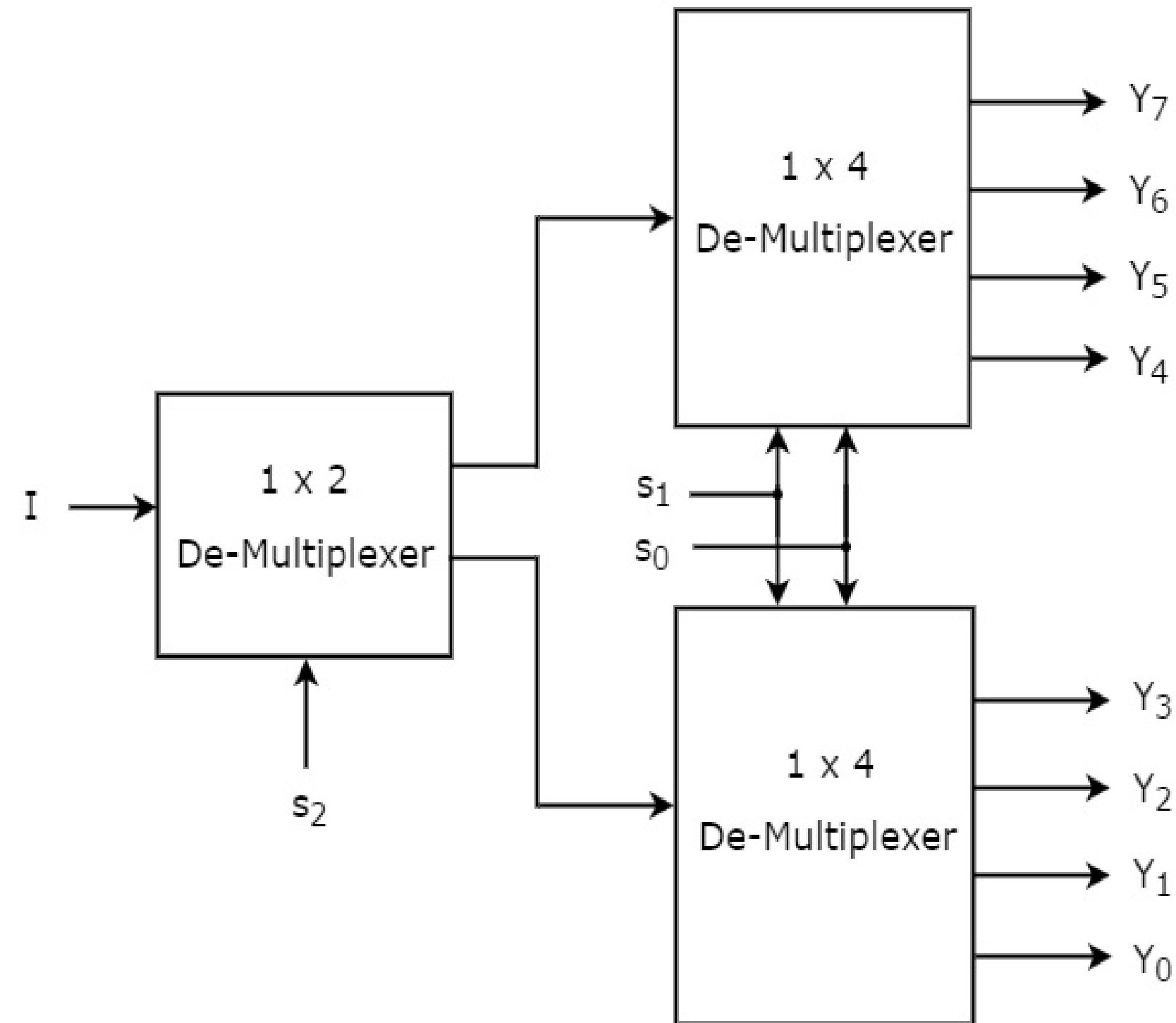
# 1x8 De-Multiplexer



1x8 De-Multiplexer has single input, three selection lines and eight outputs.






**1x8 De-Multiplexer has one input I, three selection lines s<sub>2</sub>, s<sub>1</sub> & s<sub>0</sub> and outputs Y<sub>7</sub> to Y<sub>0</sub>. The Truth table of 1x8 De-Multiplexer is shown below.**


Selection Inputs			Outputs							
s <sub>2</sub>	s <sub>1</sub>	s <sub>0</sub>	Y <sub>7</sub>	Y <sub>6</sub>	Y <sub>5</sub>	Y <sub>4</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	I
0	0	1	0	0	0	0	0	0	I	0
0	1	0	0	0	0	0	0	I	0	0
0	1	1	0	0	0	0	I	0	0	0
1	0	0	0	0	0	I	0	0	0	0
1	0	1	0	0	I	0	0	0	0	0
1	1	0	0	I	0	0	0	0	0	0
1	1	1	I	0	0	0	0	0	0	0
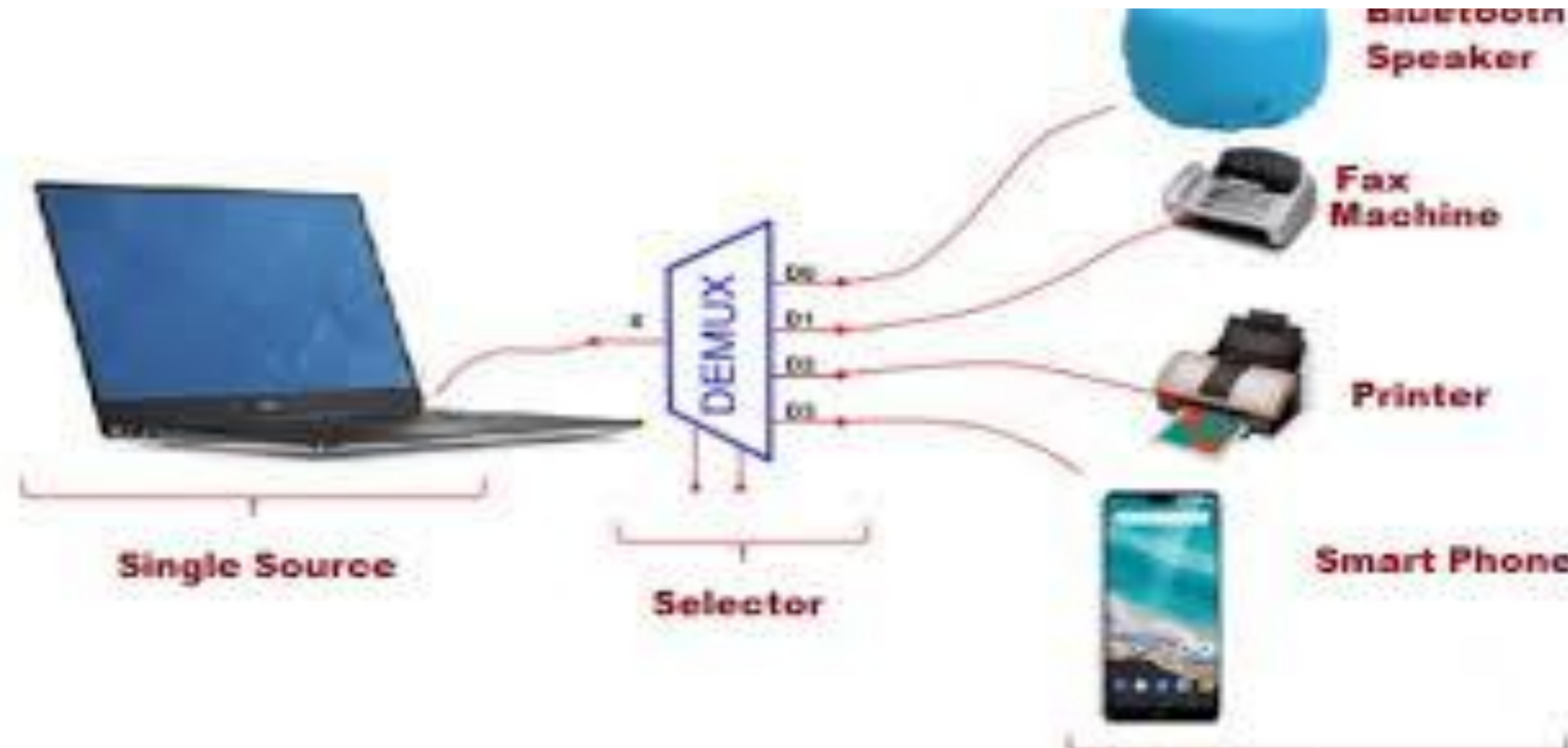
# Applications

Demultiplexer is used to connect a single source to multiple destinations. The main application area of demultiplexer is communication system where multiplexer are used.





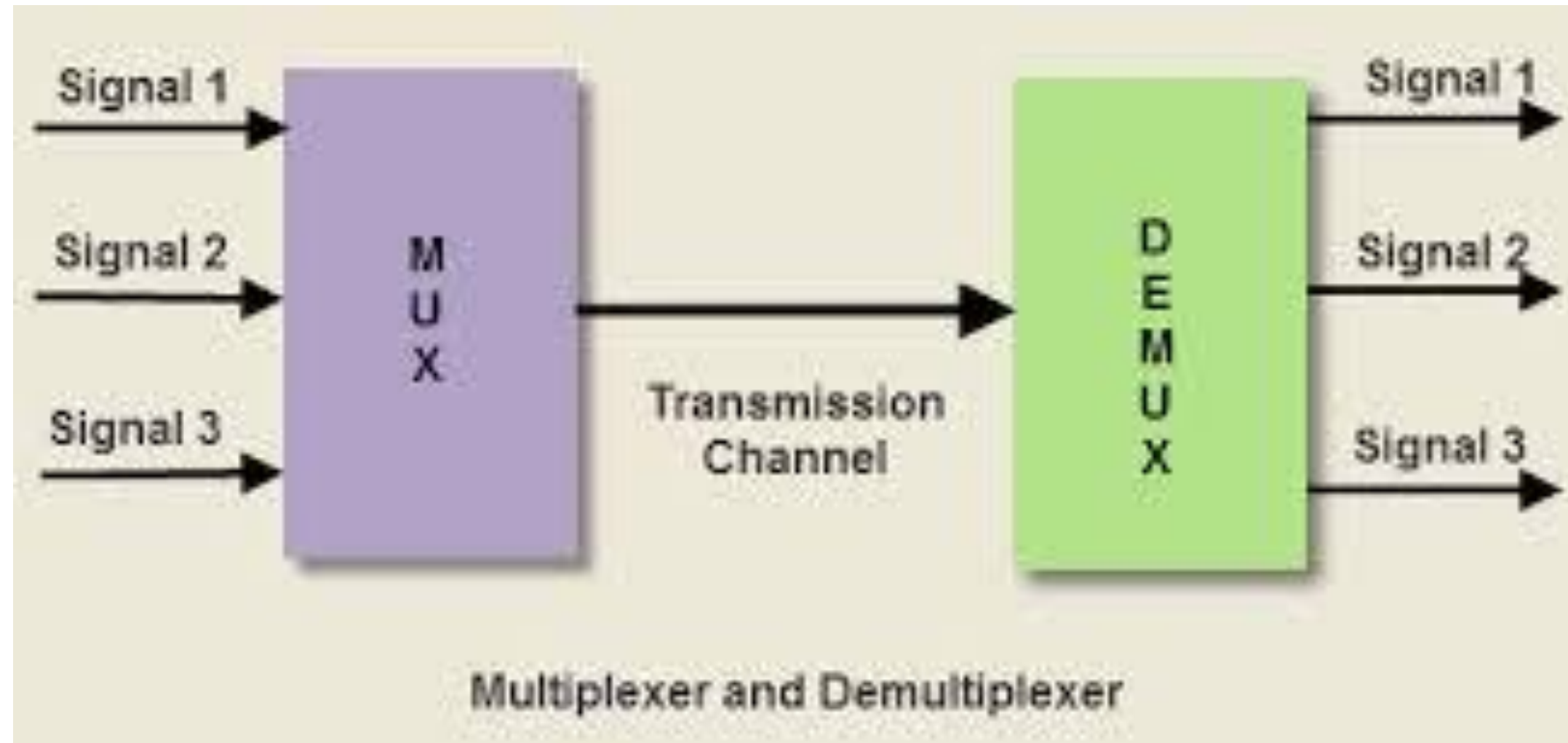

11/3/2023



**THANK YOU**

11/3/2023