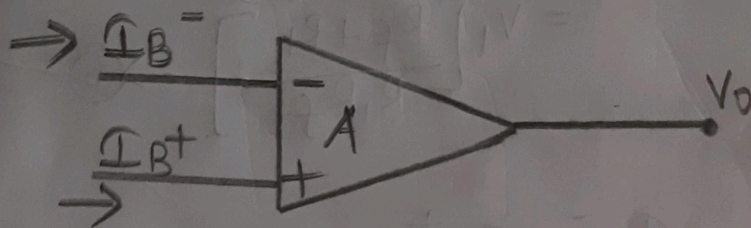


DC characteristics of op-Amp:


- * Input bias current
- * Input offset current
- * Input offset voltage
- * Thermal drift

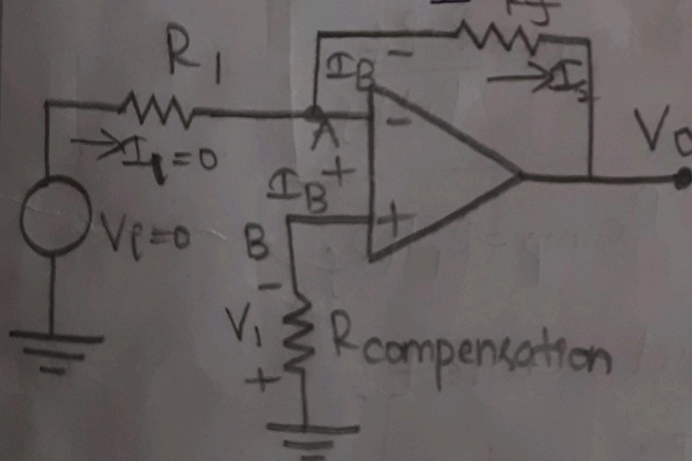(i) Input bias current:



$$I_p = 0, \quad o/p = 500 \text{ nA}$$

$$I_B = \frac{I_B^+ + I_B^-}{2} \rightarrow \textcircled{1}$$



$$V_o = I_B^- \cdot R_f \rightarrow \textcircled{2}$$

$$V_o = V_2 - V_1$$

Apply KVL to find R_{comp} ,

At $e/p = 0$

$$I_1 = \frac{V_1}{R_1}; \quad I_2 = \frac{V_2}{R_f}$$

$$V_o = V_2 - V_1 \rightarrow \textcircled{3}$$

$$V_1 = I_B^+ R_{comp} \rightarrow \textcircled{4}$$

$$I_B^+ = \frac{V_1}{R_{comp}}$$

Assume,

$$V_2 = V_1$$

$$I_2 = \frac{V_2}{R_f}$$

$$I_2 = \frac{V_1}{R_f} \rightarrow \textcircled{5}$$

KCL at node 'a',

$$I_B^- = I_1 + I_2$$

$$= \frac{V_1}{R_1} + \frac{V_1}{R_f}$$

$$I_B^- = V_1 \left[\frac{1}{R_1} + \frac{1}{R_f} \right]$$

$$= V_1 \left[\frac{R_f + R_1}{R_1 R_f} \right] \rightarrow \textcircled{6}$$

Assume

$$I_B^- = I_B^+$$

$$V_1 \left[\frac{R_1 + R_f}{R_1 R_f} \right] = \frac{V_1}{R_{comp}}$$

$$R_{comp} = \frac{R_1 R_f}{R_1 + R_f}$$

$$R_{comp} = R_1 \parallel R_f$$

(ii) Input Offset current:

We know,

$I_B^+ \Rightarrow$ Bias current at non-inverting terminal.

$I_B^- \Rightarrow$ Bias current at inverting terminal.

* $R_{comp} \Rightarrow$ To bring o/p practically zero when e/p is zero.

* Bias current \downarrow voltage

If e/p is zero, some current will be present in o/p.

* For making that o/p as zero a R_{comp} is connected.

* There is a small difference b/w I_B^+ & $I_B^- \Rightarrow$ offset current.

For compensation we are assuming

$$I_B^+ = I_B^-$$

Diff b/w I_B^+ & $I_B^- =$ offset current $[I_{OS}]$

$$|I_{OS}| = I_B^+ - I_B^-$$

We KVT,

$$V_1 = I_B^+ R_{comp} \rightarrow \text{⑦} \quad [\text{Refer eq ④}]$$

$$I_1 = \frac{V_1}{R_1}$$

At node 'a',

$$[I_1 + I_2 = I_B^-]$$

$$I_2 = I_B^- - I_1$$

$$= I_B^- - \frac{V_1}{R_1}$$

$$I_2 = I_B^- - \frac{I_B^+ R_{comp}}{R_1}$$

$$V_0 = V_2 - V_1$$

[Refer eq ③]

$$V_2 = I_2 \cdot R_f$$

$$V_0 = I_2 R_f - I_B^+ R_{comp}$$

$$V_0 = \left[I_B^- - \frac{I_B^+ R_{comp}}{R_1} \right] R_f - I_B^+ R_{comp}$$

Substitute $R_{comp} = \frac{R_1 R_f}{R_1 + R_f}$,

$$V_0 = \left[I_B^- - \frac{I_B^+ R_1 R_f}{R_1 (R_1 + R_f)} \right] R_f - I_B^+ \left(\frac{R_1 R_f}{R_1 + R_f} \right)$$

$$= \frac{I_B^- R_1 R_f (R_1 + R_f) - I_B^+ R_1 R_f^2 - I_B^+ R_1 R_f^2}{R_1 (R_1 + R_f)}$$

$$= \frac{R_1 [I_B^- R_f (R_1 + R_f) - I_B^+ R_f^2 - I_B^+ R_f R_1]}{R_1 (R_1 + R_f)}$$

$$V_0 = \frac{I_B^- R_f (R_1 + R_f) - I_B^+ R_f^2 - I_B^+ R_f R_1}{R_1 + R_f}$$

$$V_0 = R_f \left[\frac{I_B^- (R_1 + R_f) - I_B^+ R_f - I_B^+ R_1}{R_1 + R_f} \right]$$

$$V_0 = R_f \left[\frac{I_B^- (R_1 + R_f) - I_B^+ (R_f + R_1)}{R_1 + R_f} \right]$$


$$V_0 = R_f I_B^- - \frac{R_f I_B^+ (R_f + R_1)}{R_1 + R_f}$$

$$V_0 = R_f I_B^- - R_f I_B^+$$


$$V_0 = R_f [I_B^- - I_B^+]$$

$$V_0 = R_f [I_{OS}]$$

05/09/2023 (iii) Input offset voltage:

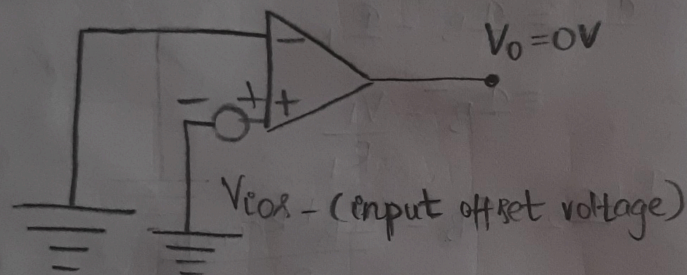

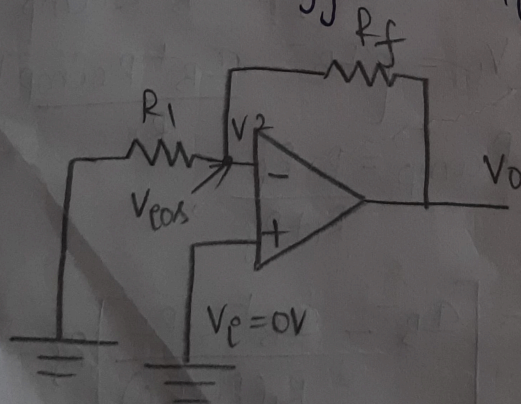The voltage should be given to op-Amp in order to nullify the o/p voltage.



$$V_0 = \left[1 + \frac{R_f}{R_1} \right] V_{icos}$$

$$V_{icos} = |V_e - V_2|$$

$$V_{icos} = |0 - V_2|$$

$$V_2 = \frac{\text{Voltage across the resistor}}{\text{Total component (resistors)}} \times \text{I/p voltage}$$

$$V_2 = \left(\frac{R_1}{R_1 + R_f} \right) V_0$$

$$V_0 = \left(\frac{R_1 + R_f}{R_1} \right) V_2$$

$$V_{eOS} = |V_c - V_2| \text{ \& } V_c = 0$$

$$V_0 = \left[1 + \frac{R_f}{R_1} \right] V_{eOS}$$

(iv) Thermal drift:

* Bias current, offset current and offset voltage may change with temperature.

* A circuit carefully nullified at 25°C may not remain same if temperature varies.

* The change due to temperature is referred as thermal drift.

$$\text{Thermal drift in i/p offset current} = \frac{\Delta I_{OS}}{\Delta T}$$

$$\text{Thermal drift in i/p bias current} = \frac{\Delta I_B}{\Delta T}$$

$$\text{Thermal drift in i/p offset voltage} = \frac{\Delta V_{eOS}}{\Delta T}$$

AC characteristics of Op-Amp:

* Frequency response

* Slew rate

* Stability of Op-Amp


* Frequency compensation of op-Amp.

(i) Frequency response:

* The variation in operating frequency will cause variations in gain and phase angle.



* The manner in which the gain of the Op-Amp respond to different frequencies is called frequency response.

09/2023

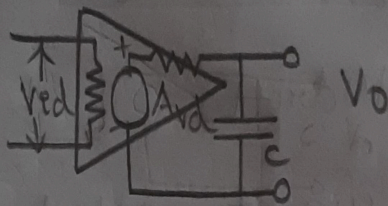

* Frequency response should be uniform.

It varies due to the capacitance effect.

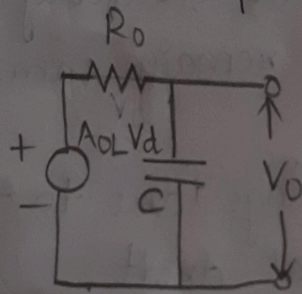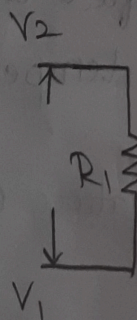

Open loop gain (A_{OL}) = 90 dB.

* If frequency \uparrow gain will be $\downarrow \Rightarrow$ this condition is known as roll off.

\downarrow

Gain = 20 dB.

* As per voltage divider rule,

$$= \frac{\text{Voltage across the component}}{\text{Total components}} \times \text{Input voltage.}$$

Voltage across 'c',

[Capacitor is defined by $-j\omega c$]

$$V_o = \frac{-j\omega c}{R_o - j\omega c} \times A_{oL} V_d$$

$$\frac{V_o}{V_d} = \frac{1}{\frac{R_o - j\omega c}{-j\omega c}} \times A_{oL} \quad \left[s = -\frac{1}{j} \right]$$

$$\frac{V_o}{V_d} = \frac{1}{R_o + \frac{1}{j\omega c}} \times A_{oL}$$

$$\boxed{\frac{V_o}{V_d} = A} \rightarrow \text{gain}$$

[$\therefore V_d =$ Difference b/w i/p voltage]

$$A = \frac{1}{\frac{[jR_o\omega c + 1]}{j\omega c}} \times A_{oL}$$

$$A = \frac{A_{oL}}{1 + jR_o\omega c}$$

$$A = \frac{A_{oL}}{1 + jR_o\omega c}$$

$$A = \frac{A_{oL}}{1 + jR_o(2\pi f c)}$$

$$A = \frac{A_{oL}}{1 + j f c \left(\frac{1}{f_1}\right)}$$

$$\boxed{A = \frac{A_{oL}}{1 + j(f/f_1)}}$$

$$\left[\begin{aligned} \omega &= 2\pi f c \\ 2\pi R_o &= \frac{1}{f_1} \\ \omega c &= \omega c \\ &= \frac{1}{f} \end{aligned} \right]$$

$f_1 =$ Corner frequency

Magnitude + phase angle,

$$|A| = \frac{A_{oL}}{\sqrt{1 + (f/f_1)^2}}$$

$$[a + jb = \sqrt{a^2 + b^2}]$$


$$\phi = -\tan^{-1}(f/f_1) = -\tan^{-1}(b/a) \quad \left[\begin{aligned} a &= 1 \\ b &= f/f_1 \end{aligned} \right]$$

* Op-Amp with three different corner frequencies

$$A = A_{OL} \times f_1 f_2 f_3$$

$$[1 + j(f/f_1)][1 + j(f/f_2)][1 + j(f/f_3)]$$

Output waveform:

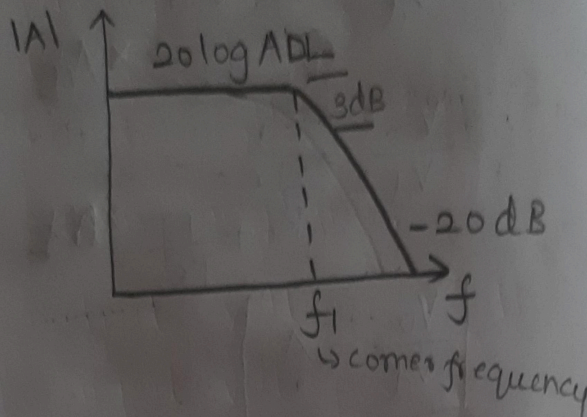


* $f < f_1 \Rightarrow$ Magnitude of gain $20 \log A_{OL}$

* $f = f_1 \Rightarrow$ 3dB down from A_{OL}
Gain

* $f > f_1 \Rightarrow$ Role off at -20 dB .

Phase characteristics:

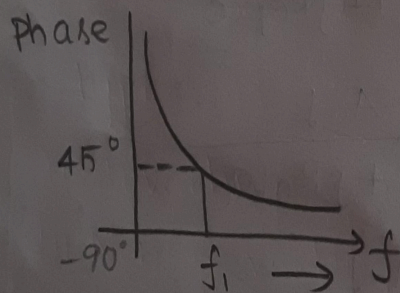

2023 (ii) Slew rate:



* Rate of change of an output voltage w.r.t time.

(or)

* Time the O/p takes to change from 10% to 90%.


$$SR = \left. \frac{dv_o}{dt} \right|_{\max} \quad (\text{or}) \quad S_n = \frac{I_{\max}}{C}$$

* Unit \Rightarrow Volts / μsec .

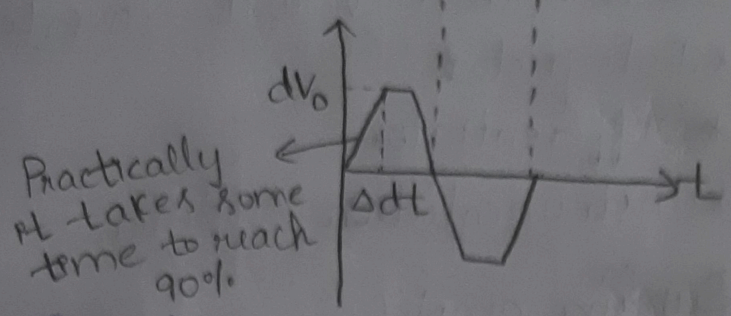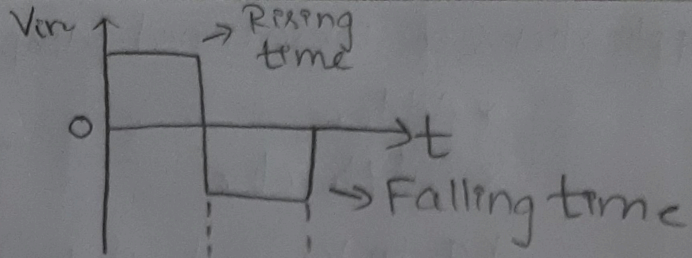

Practically it takes some time to reach 90%.

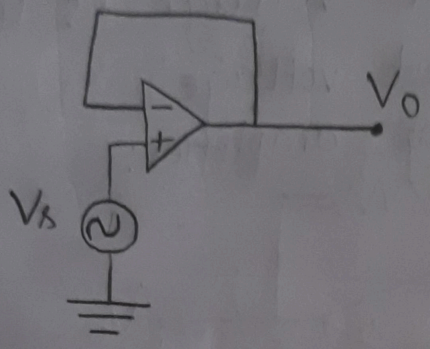Consider voltage follower → output follows the input voltage
 so, $V_s = V_o$



$$V_s = V_o$$

(source voltage) (output voltage)

$$V_s = V_m \sin \omega t$$

$$V_o = V_m \sin \omega t$$

$$\frac{dV_o}{dt} = V_m \frac{d}{dt} \sin \omega t$$

$$\frac{dV_o}{dt} = \omega V_m \cos \omega t$$

At max $\cos \omega t = 1$

$$SR = \omega V_m \quad [\because \omega = 2\pi f]$$

$$SR = 2\pi f V_m \quad \text{V/sec}$$

$$SR = 2\pi f_{max} V_m \times \frac{1}{10^6} \quad \text{V/}\mu\text{sec}$$

$$f_{max} = \frac{SR \times 10^6}{2\pi V_m}$$

[Full power bandwidth]

$$= \frac{SR \times 10^6}{6.28 V_m}$$