


Applications of Operational Amplifiers:

- * Adder
- * Subtractor
- * I to V and V to I converter
- * Integrator
- * Differentiator
- * Instrumentation Amplifier.

(i) Adder / Summing amplifier:

The output voltage is the sum of all the input voltage.

Inverting summing amplifiers:

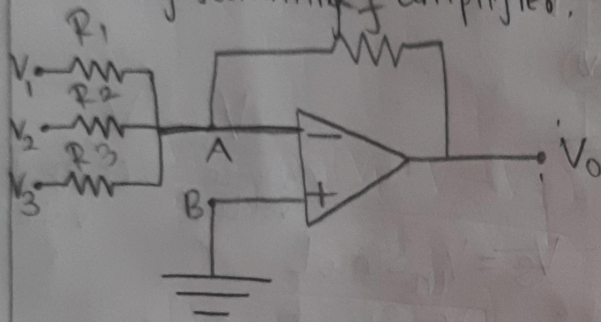

* Two types:

(i) Inverting summing amplifier.

(ii) Non-inverting summing amplifier.

Apply KCL at node A,

$$\frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_2} + \frac{V_3 - V_A}{R_3} + \frac{V_0 - V_A}{R_f} = 0$$

$V_d = 0$
 $V_A = V_B$
As $V_B = 0$ grounded
 $V_A = 0$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_0}{R_f} = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_0}{R_f}$$


$$-R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right] = V_0$$

Consider $R_1 = R_2 = R_3 = R_f$

$$V_0 = \ominus (V_1 + V_2 + V_3)$$

As it is connected to inverting terminal

Non-inverting summing amplifiers:

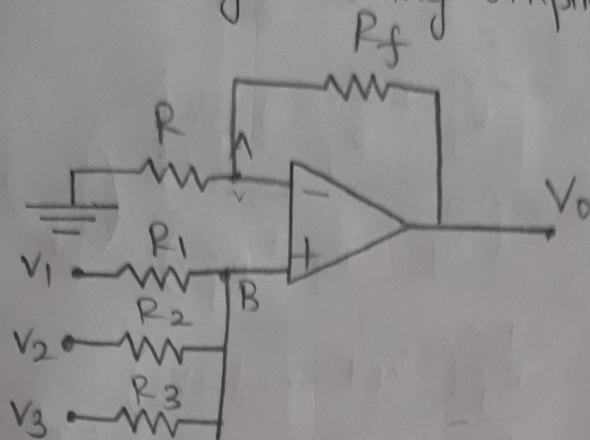

At node A,

$$\frac{0 - V_A}{R} + \frac{V_0 - V_A}{R_f} = 0$$

$$\frac{V_0 - V_A}{R_f} = \frac{V_A}{R} \Rightarrow \frac{V_A}{R} + \frac{V_A}{R_f} = \frac{V_0}{R_f}$$

$$V_0 = R_f V_A \left(\frac{1}{R} + \frac{1}{R_f} \right) \rightarrow \textcircled{1}$$

At node b,

$$\frac{V_1 - V_B}{R_1} + \frac{V_2 - V_B}{R_2} + \frac{V_3 - V_B}{R_3} = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = V_B \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = V_B \left(\frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_1 R_2 R_3} \right)$$

$$V_B = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \left(\frac{R_1 R_2 R_3}{R_2 R_3 + R_1 R_3 + R_1 R_2} \right)$$

$$V_B = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)} \rightarrow \textcircled{2}$$

Sub ② in ①, $[V_A = V_B]$

$$\frac{V_0}{R_f} = \frac{\left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}\right)}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)} \left[\frac{1}{R} + \frac{1}{R_f}\right]$$

Let $R_1 = R_2 = R_3 = R_f = \frac{R_f}{2}$


$$\frac{V_0}{R_f} = \frac{\frac{2V_1}{R_f} + \frac{2V_2}{R_f} + \frac{2V_3}{R_f}}{\left(\frac{2}{R_f} + \frac{2}{R_f} + \frac{2}{R_f}\right)} \left(\frac{2}{R_f} + \frac{1}{R_f}\right)$$

$$= \frac{\frac{1}{R_f} (2V_1 + 2V_2 + 2V_3)}{\frac{1}{R_f} (6)} \left(\frac{3}{R_f}\right)$$

$$\frac{V_0}{R_f} = \frac{2(V_1 + V_2 + V_3)}{2R_f}$$

$$V_0 = V_1 + V_2 + V_3$$

(ii) Subtractor / Difference amplifier:

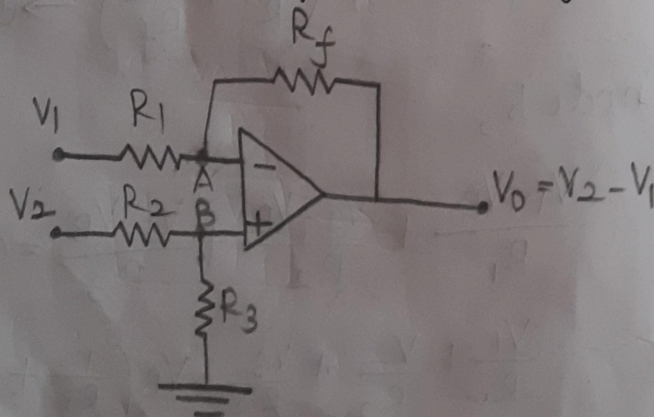

*A circuit that takes the difference b/w two signals is called subtractor.

Output = Difference of i/p.

Assume,

$$R = R_1 = R_2 = R_3 = R_f$$

At inverting terminal (or) A,

$$V_2 = 0, V_1 = \text{applied}$$

$$V_0 = -\left(\frac{R_f}{R_1}\right) V_1$$

$$\boxed{V_0 = -V_1}$$

At non-inverting terminal (or) at B,

$$V_1 = 0, V_2 = \text{applied}$$

$$V_0 = \left[1 + \frac{R_f}{R_1}\right] V_A \rightarrow \textcircled{1}$$

~~V₀ =~~

At node 'a',

$$V_A = V_2 \times \frac{R_3}{R_2 + R_3} \rightarrow \textcircled{2}$$

Sub $\textcircled{2}$ in $\textcircled{1}$,


$$V_0 = \left[1 + \frac{R_f}{R_1}\right] \left[V_2 \times \frac{R_3}{R_2 + R_3}\right]$$


$$V_0 = 2 \left(V_2 \times \frac{R_f}{2R_f}\right)$$

$$\boxed{V_0 = V_2}$$

Output voltage = Inverting amplifier + Non-inverting amplifier.

2023
(iii) Differentiator: R_f

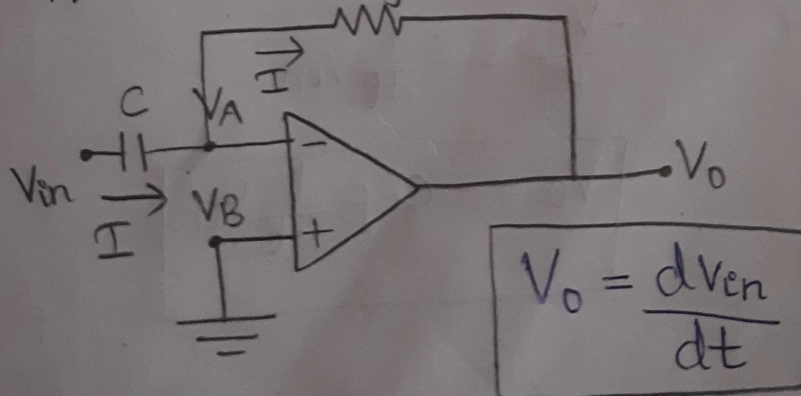

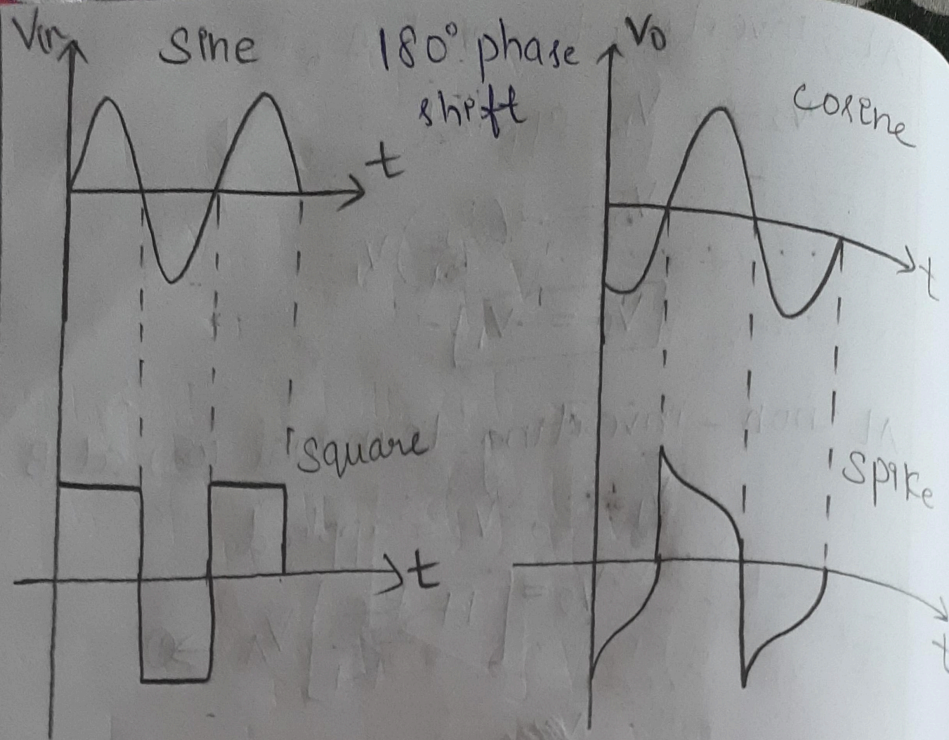

(i) $V_A = V_B$
 $V_A = 0$

$V_B = \text{grounded}$

Current at i/p side,
 → current passes through

$I = C \frac{d}{dt} (V_{in} - V_A)$ capacitor

$I = C \frac{dV_{in}}{dt} \rightarrow \textcircled{1}$

Current at o/p side,

$I = \frac{V_A - V_o}{R_f}$


$I = -\frac{V_o}{R_f} \rightarrow \textcircled{2}$

Equate $\textcircled{1}$ & $\textcircled{2}$,


$-\frac{V_o}{R_f} = C \frac{d}{dt} V_{in}$

$V_o = -CR_f \frac{d}{dt} V_{in}$

(iv) Integrator:

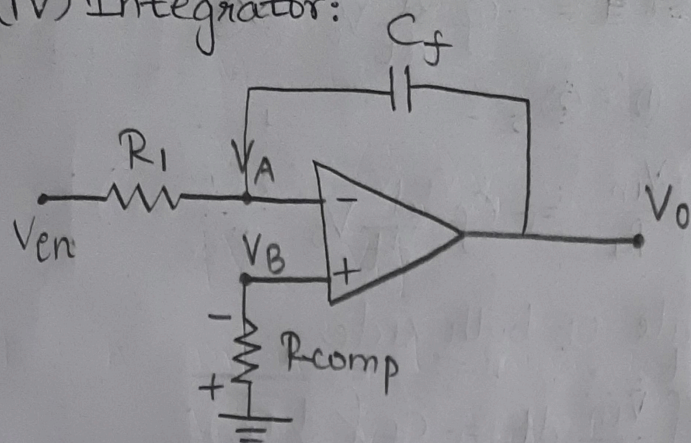

* O/p is the integral of input.

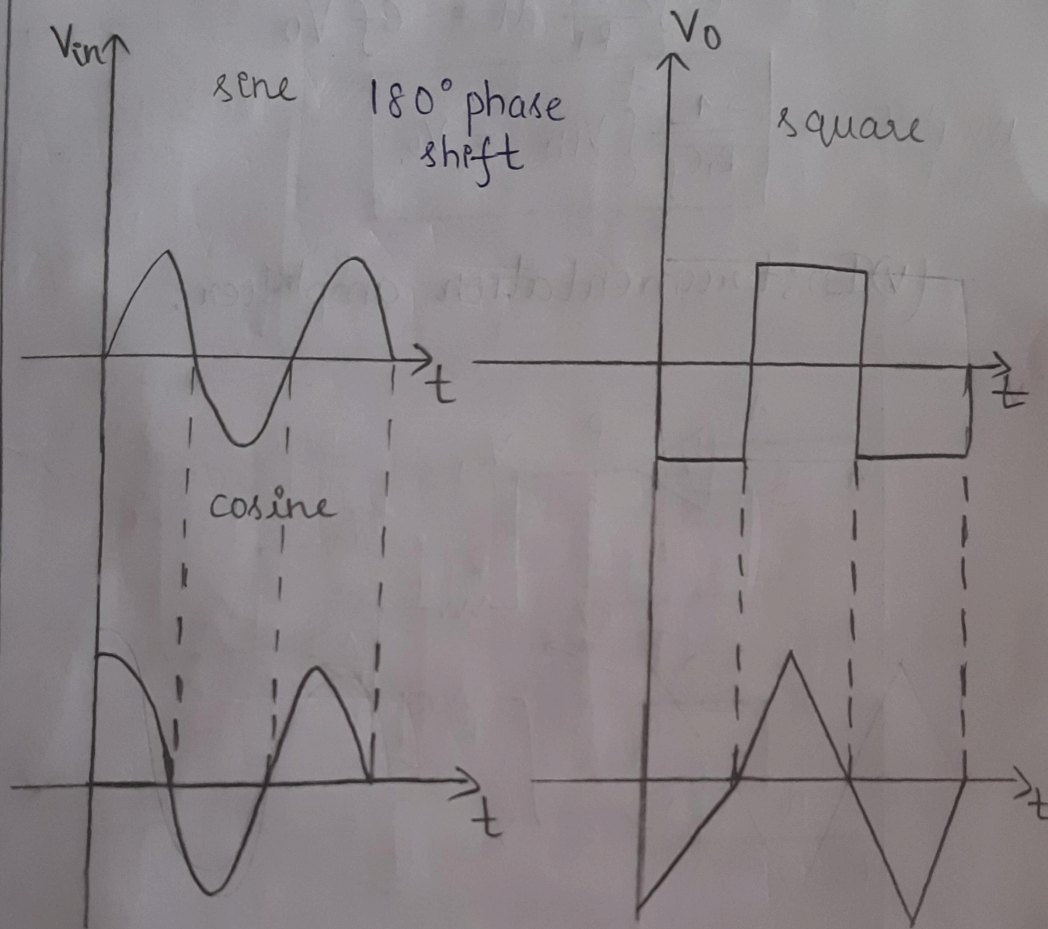

6/09/23 Instrumentation amplifier:

Find i at ip side,

$$I = \frac{V_{in} - V_A}{R_1}$$

$$I = \frac{V_{in}}{R_1}$$

'I' at op side,

$$I = C_f \frac{d}{dt} (V_A - V_o)$$

$$I = -C_f \frac{d}{dt} V_o \rightarrow \textcircled{2}$$

Equate ① + ②,

$$\frac{V_{en}}{R_1} = -C_f \frac{d}{dt} V_o$$

Integrate on both sides,


$$\int_0^t \frac{V_{en}}{R_1} dt = -C_f \int_0^t \frac{d}{dt} V_o$$

$$\int_0^t \frac{V_{en}}{R_1} dt = -C_f V_o$$

80° phase shift

$$\ominus \frac{1}{R_1 C_f} \int_0^t V_{en} = V_o$$

(v) Instrumentation amplifier:

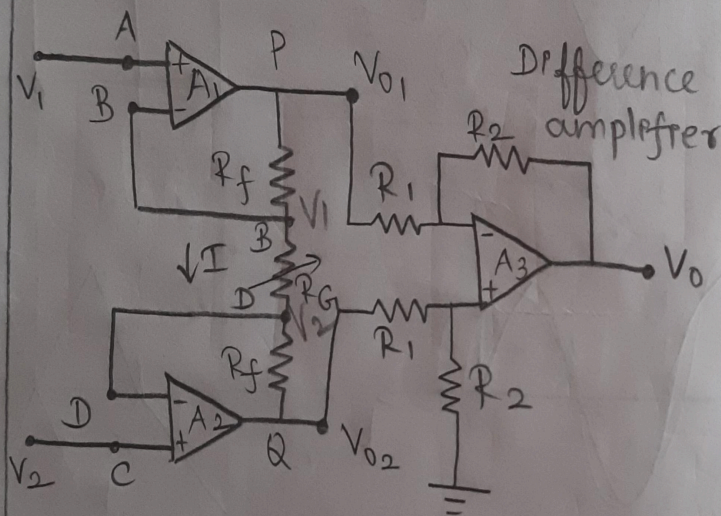

* Also known as data amplifier.

* Mainly used in industries.

* It is used to measure and control physical quantities.

(Temp, Pressure, Humidity, intensity, light)

* Transducers convert physical quantities to electrical quantities. Here the o/p is weak so for amplifying instrumentation amplifier is used.

Features:

- (i) High gain accuracy.
- (ii) High CMRR.

* A_1, A_2 = Voltage follower & act as a buffer stage.

* Gain can be varied by varying R_G .

Consider PQ,

$$\text{Node A} = V_1 \quad \text{so } V_B = V_1$$

$$\text{Node C} = V_2 \quad \text{so } V_D = V_2$$

$$I = \frac{V_{O1} - V_{O2}}{R_f + R_f + R_G}$$

$$I = \frac{V_{O1} - V_{O2}}{2R_f + R_G} \rightarrow \textcircled{1}$$

since o/p stage is difference amplifier.

$$\text{so } V_O = V_{O1} - V_{O2}$$

Apply ohm's law at BD,

$$I = \frac{V_1 - V_2}{R_G} \rightarrow \textcircled{2}$$

Equate $\textcircled{1}$ & $\textcircled{2}$,

$$\frac{V_{O1} - V_{O2}}{2R_f + R_G} = \frac{V_1 - V_2}{R_G}$$

$$V_{O1} - V_{O2} = \frac{V_1 - V_2}{R_G} (2R_f + R_G)$$

Output voltage,
(V_O)


$$V_O = \frac{R_2}{R_1} (V_{O1} - V_{O2})$$

$$V_0 = \frac{R_2}{R_1} \left(\frac{V_1 - V_2}{R_G} (2R_f + R_G) \right)$$



$$V_0 = \frac{R_2}{R_1} (V_1 - V_2) \left(\frac{2R_f}{R_G} + 1 \right)$$

$$\frac{V_0}{V_1 - V_2} = A = \frac{R_2}{R_1} \left(\frac{2R_f}{R_G} + 1 \right)$$

(vi) I to V amplifier:

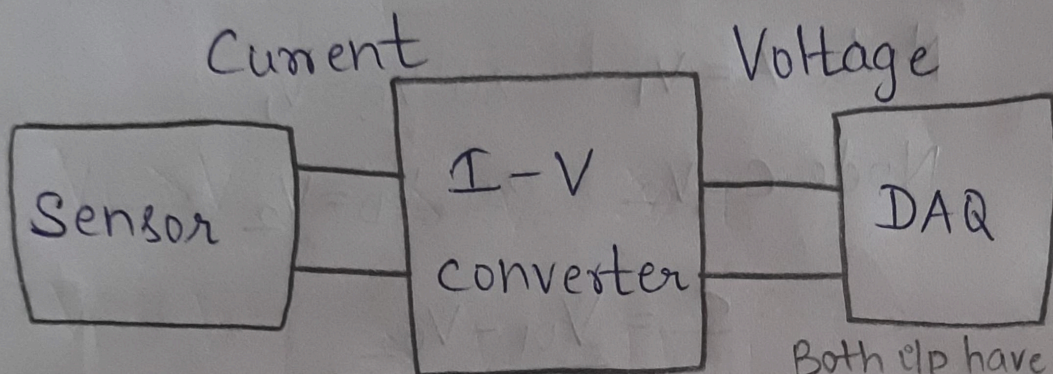

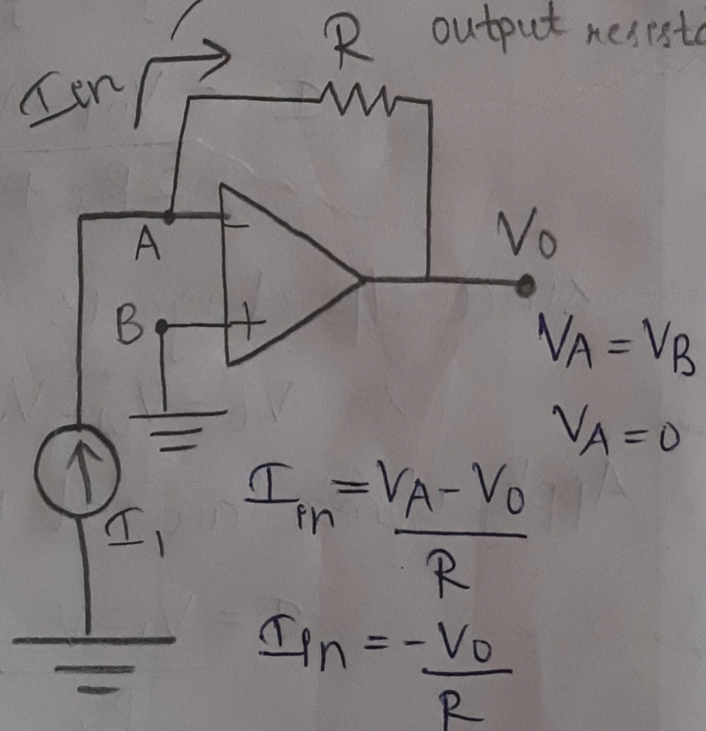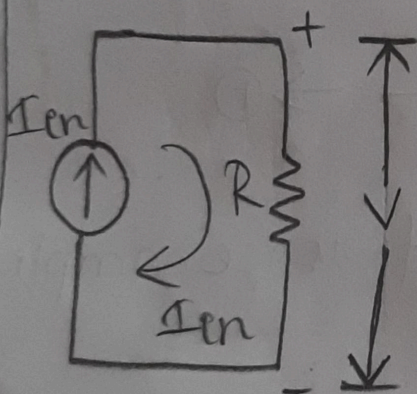Both op have no resistance so it flows through output resistance



$$V_0 = -I_{en}R$$