

$$= -V_R \left( \frac{2}{3} \right) R \Rightarrow \frac{-V_R}{4}$$

Inverting amplifier,

$$V_0 = -\frac{R_f}{R}$$

$$V_0 = -\frac{2R}{R} \times \left( -\frac{V_R}{4} \right)$$

$$V_0 = +\frac{V_R}{2}$$

10/2023 Types of ADC:

\*Direct type ADC

\*Indirect type ADC

(i) Direct type ADC:

\*If the ADC performs the A to D conversion directly by utilizing the internally generated equivalent digital (binary) code for comparing with the analog ip, then it is called as Direct type ADC.

Eg: Counter type ADC, Successive Approximation ADC, Flash type ADC.

(ii) Indirect type ADC:

\*If the ADC performs the analog to digital conversion by an indirect method, then it is called an Indirect type ADC. In general, first it converts the analog ip into a linear function of time (or frequency) and then it will produce the digital (binary) output.

\*Dual slope ADC is the best eg of an indirect type ADC.







No. of comparators required =  $2^N - 1$

Since it is a 3 bit comparator,

$$= 2^3 - 1$$


$$= 7$$

we used 8 comparators, because it has 8 line to 3 line priority encoder.

Disadvantage  $\Rightarrow$  More no. of comparators is used

Advantages  $\Rightarrow$  High speed, conversion time - (less) 100 nano second + conversion done simultaneously.

Successive approximation - ADC:

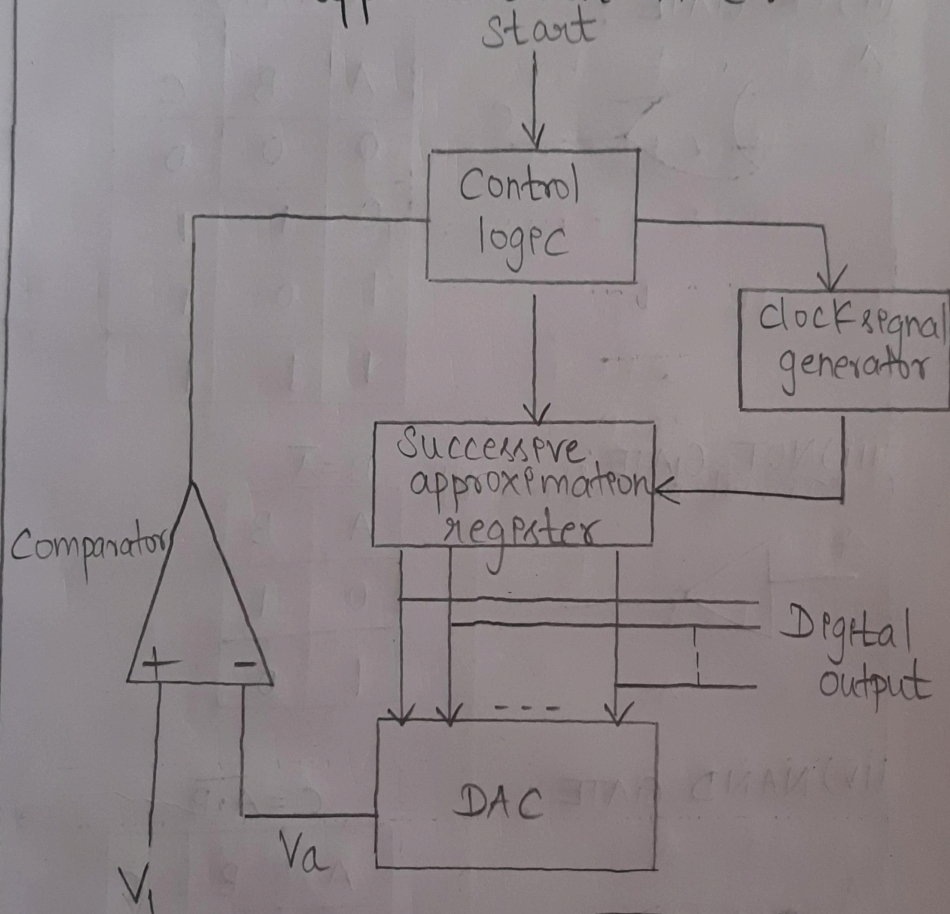

$e/p = 11V$

0000  
 Make MSB = 1 1000  
 if  $V_a > V_d$  1100  
 if  $V_a < V_d$  0100

8V  $\xrightarrow{1000}$  12V  $\xrightarrow{1100}$  10V  $\xrightarrow{1010}$   
 $V_a > V_d$   $V_a < V_d$   $V_a > V_d$   
 BCD  
 8 4 2 1  
 $2^3 \ 2^2 \ 2^1 \ 2^0$   
 1 0 0 0  
 $10V$   
 $V_a = V_d$

$0 \times 2^0 = 0$   
 $0 \times 2^1 = 0$   
 $0 \times 2^2 = 0$   
 $1 \times 2^3 = 8$   
 } 8V