



# SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore - 641 107

AN AUTONOMOUS INSTITUTION



## ASTABLE MULTIVIBRATOR


### IC 555 Timer as Multivibrator

The 555 can operate in either mono/bi-stable or astable mode, depending on the connections to and the arrangement of the external components. Thus, it can either produce a single pulse when triggered, or it can produce a continuous pulse train as long as it remains powered.

#### *Astable multivibrator*

These circuits are not stable in any state and switch outputs after predetermined time periods. The result of this is that the output is a continuous square/rectangular wave with the properties depending on values of external resistors and capacitors. Thus, while designing these circuits following parameters need to be determined:

1. Frequency (or the time period) of the wave.
2. The duty cycle of the wave.

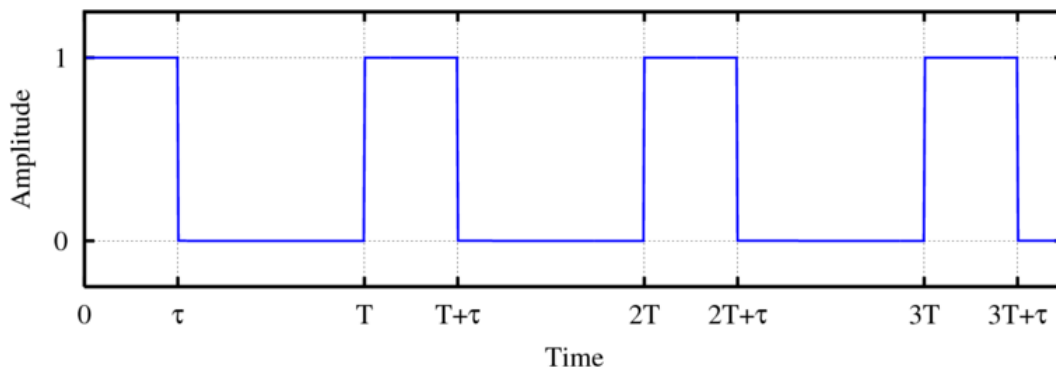

**Figure 1: A rectangular waveform**

Referring to the above figure of a rectangular waveform, the time period of the pulse is defined as  $T$  and duration of the pulse (ON time) is  $\tau$ . Duty cycle can be defined as the On time/Period that is,  $\tau/T$  in the above figure. Obviously, a duty cycle of 50% will yield a square wave.

The key external component of the **astable timer** is the *capacitor*. An astable multivibrator can be designed as shown in the circuit diagram (with typical component values) using IC 555, for a duty cycle of more than 50%. The corresponding voltage across the capacitor and voltage at output is also shown. The astable function is achieved by charging/discharging a capacitor through resistors connected, respectively, either to  $V_{CC}$  or GND. Switching between the charging and discharging modes is handled by

resistor divider R1-R3, two Comparators, and an RS Flip-Flop in IC 555. The upper or lower comparator simply generates a positive pulse if  $V_C$  goes above  $2/3 V_{CC}$  or below  $1/3 V_{CC}$ . And these positive pulses either SET or RESET the Q output.

The time for charging C from  $1/3$  to  $2/3 V_{CC}$ , i.e, **ON Time =  $0.693 (R_A + R_B) \cdot C$**

The time for discharging C from  $2/3$  to  $1/3 V_{CC}$ , i.e. **OFF Time =  $0.693 R_B \cdot C$**

To get the total oscillation period, just add the two:


$$T_{osc} = 0.693 \cdot (R_A + R_B) \cdot C + 0.693 \cdot (R_B) \cdot C = 0.693 \cdot (R_A + 2 \cdot R_B) \cdot C$$

Thus,

$$f_{osc} = 1/ T_{osc} = 1.44/ (R_A + 2 \cdot R_B) \cdot C$$

$$\text{Duty cycle} = R_A + R_B / R_A + 2 \cdot R_B$$

**Circuit Diagram:**

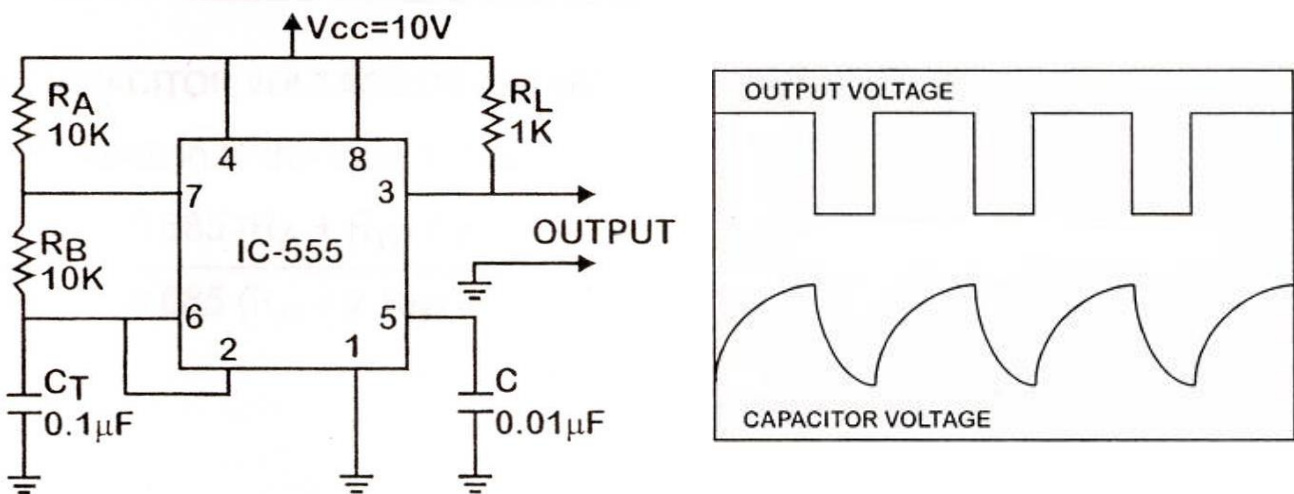


***Astable multivibrator with duty cycle less than 50%:***

Generally astable mode of IC 555 is used to obtain the duty cycle between 50 to 100%. But for a duty cycle less than 50%, the circuit can be modified as per the circuit diagram. Here a diode D1 is connected between the discharge and threshold terminals (as also across  $R_B$ ). Thus the capacitor now charges only through  $R_A$  (since  $R_B$  is shorted by diode conduction during charging) and discharges through  $R_B$ . Another optional diode D2 is also connected in series with  $R_B$  in reverse direction for better shorting of  $R_B$ . Therefore, the frequency of oscillation and duty cycle are

$$f_{osc} = 1/ T_{osc} = 1.44/ (R_A + R_B) \cdot C$$

$$\text{Duty Cycle} = R_A / (R_A + R_B)$$

**Circuit Diagram:**

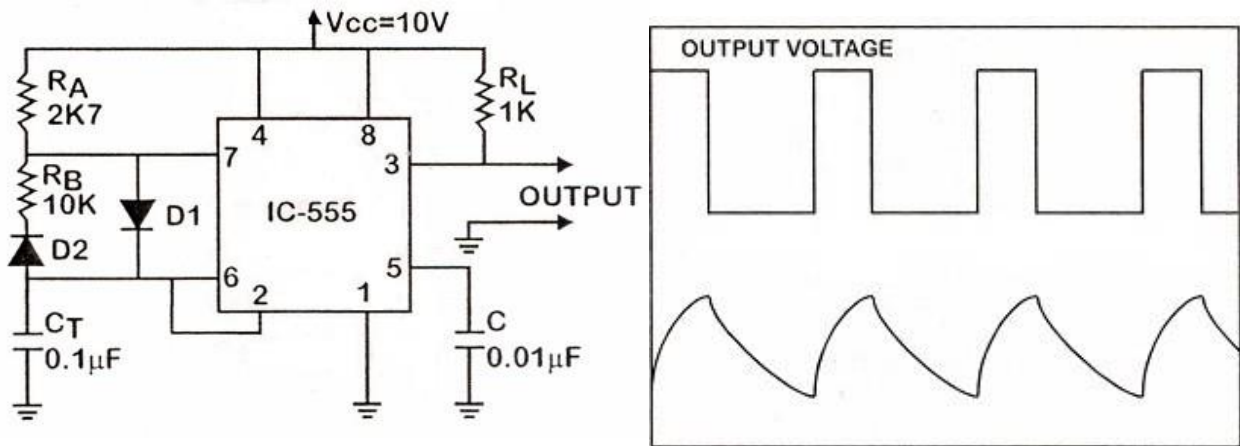

**Astable multivibrator with duty cycle variable from 0 to 100%:**

In some applications, it is needed to vary the duty cycle from about 0 to 100%. In that case the circuit is designed as shown in the circuit diagram. Here a potentiometer,  $R_X$ , is used so that  $R_A = R_1 + R_2$ ,  $R_B = R_X - R_2 + R_3$ . A diode is now connected across a variable  $R_B$ . Thus a variable duty cycle is achieved. Therefore, the frequency of oscillation and duty cycle can be derived as follows.

$$f_{osc} = 1/T_{osc} = 1.44/(R_A + R_B) \cdot C = 1.44/(R_1 + R_X + R_3) \cdot C$$

$$\text{Min. Duty Cycle} = R_1/(R_1 +$$

$$R_X + R_3) \text{ Max. Duty Cycle} = (R_1$$

$$+ R_X)/(R_1 + R_X + R_3)$$

**Circuit Diagram:**

