



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore – 641 107

An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A’ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING


COURSE NAME : 19EC306 – Digital Circuits

II YEAR / III SEMESTER

Unit I- **COMBINATIONAL CIRCUITS**
Topic : Binary multiplier, MUX and DEMUX

Multiplexer

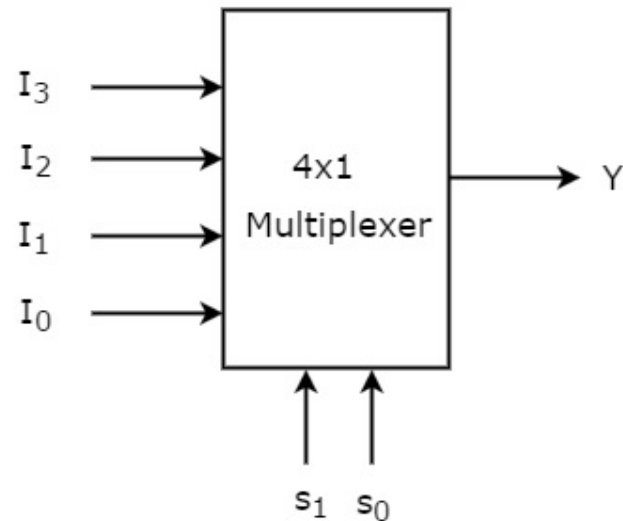
- Multiplexer is a combinational circuit that has maximum of 2^n data inputs, 'n' selection lines and single output line.
- One of these data inputs will be connected to the output based on the values of selection lines..






- 4x1 Multiplexer has four data inputs I_3, I_2, I_1 & I_0 , two selection lines s_1 & s_0 and one output Y .
- One of these 4 inputs will be connected to the output based on the combination of inputs present at these two selection lines.

Selection Lines		Output
S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

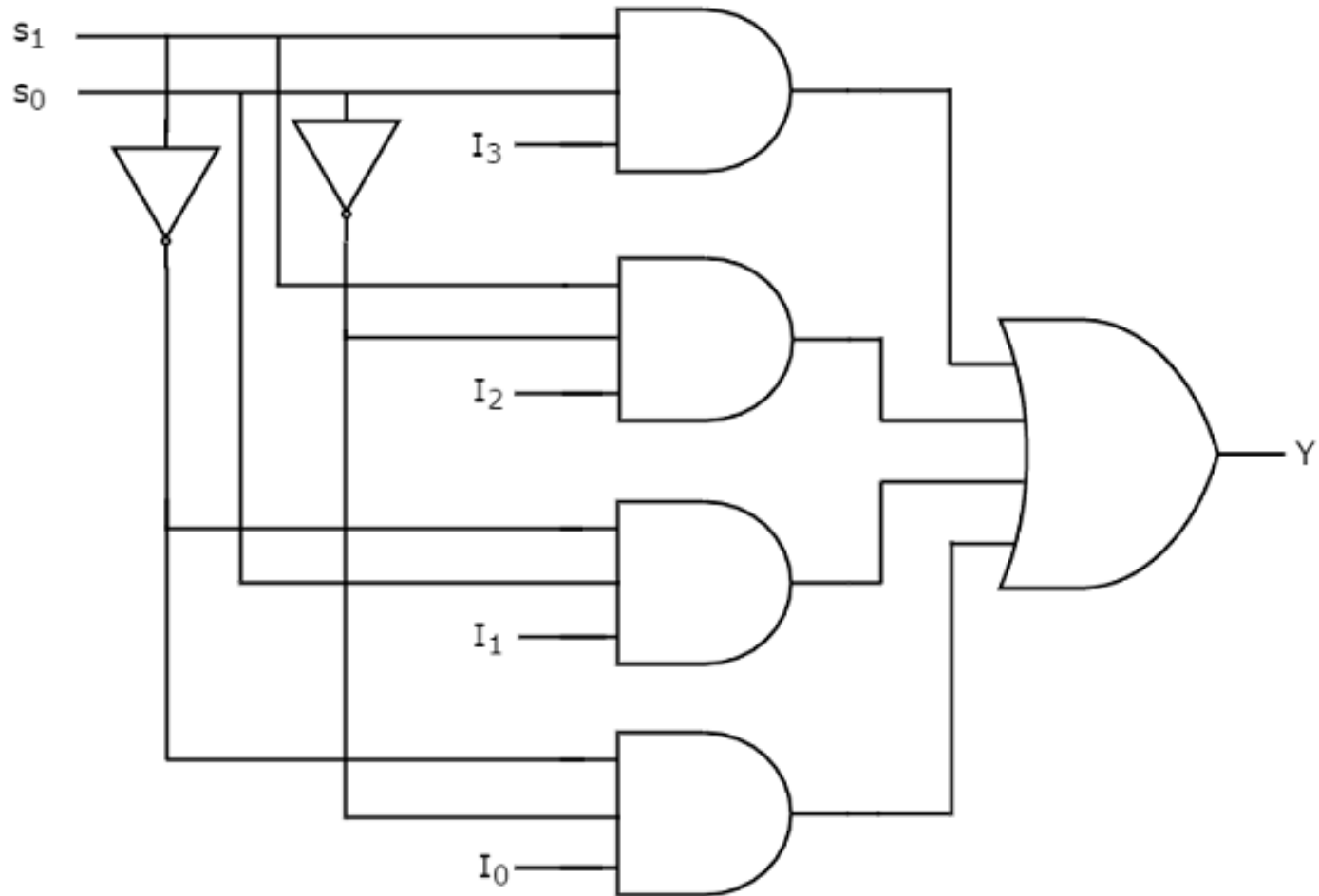


De Multiplexer

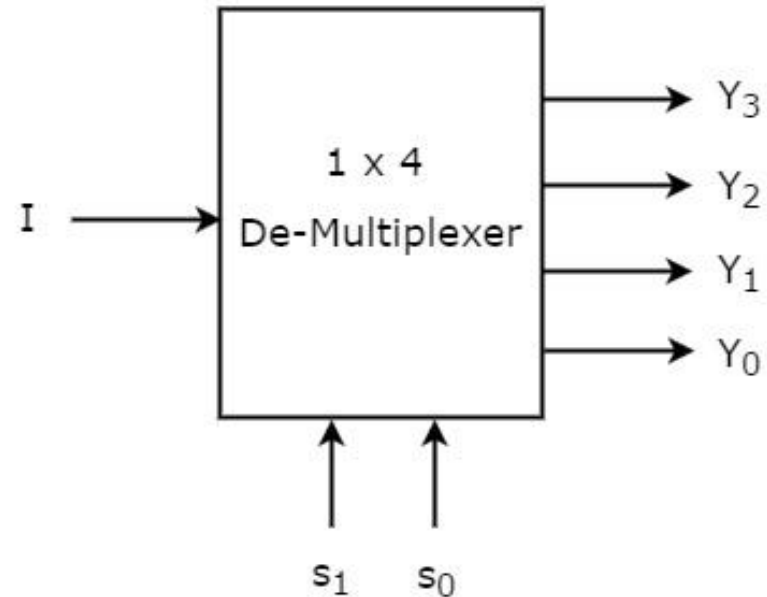- De-Multiplexer is a combinational circuit that performs the reverse operation of Multiplexer. It has single input, 'n' selection lines and maximum of 2^n outputs.
- One of these data inputs will be connected to the output based on the values of selection lines..



Selection Inputs		Outputs			
S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

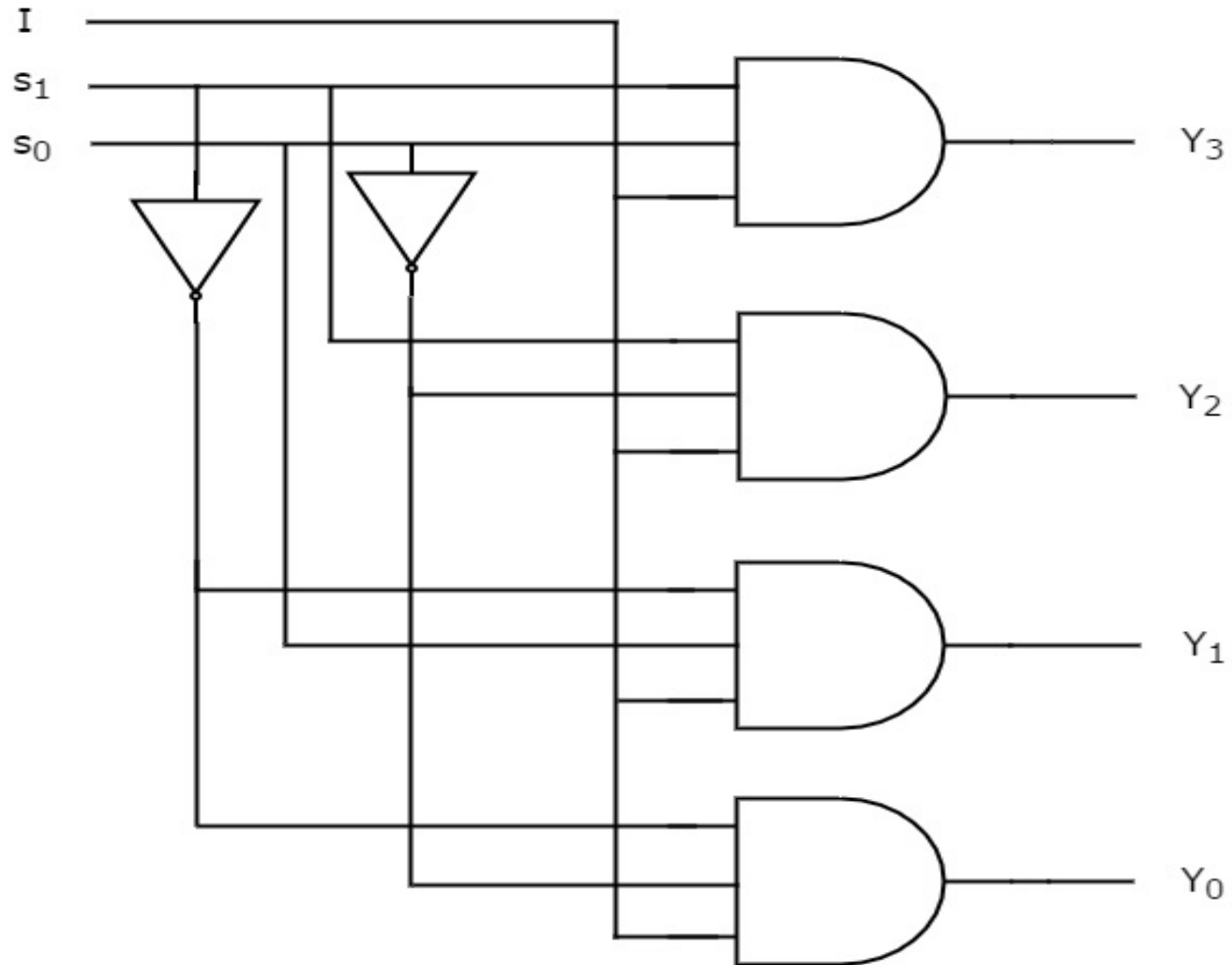- The single input '1' will be connected to one of the four outputs, Y_3 to Y_0 based on the values of selection lines s_1 & s_0 . The Truth table of 1x4 De-Multiplexer is shown below.






Binary multiplier:

A binary multiplier is used to multiply two binary numbers. It is a basic electronic circuit in digital electronics, such as a computer. The binary multiplier is also called an **add-shift adder**.

A digital multiplier can be implemented using a variety of computer arithmetic techniques. The majority of techniques involve computing a set of partial products, which are then summed using binary adders.
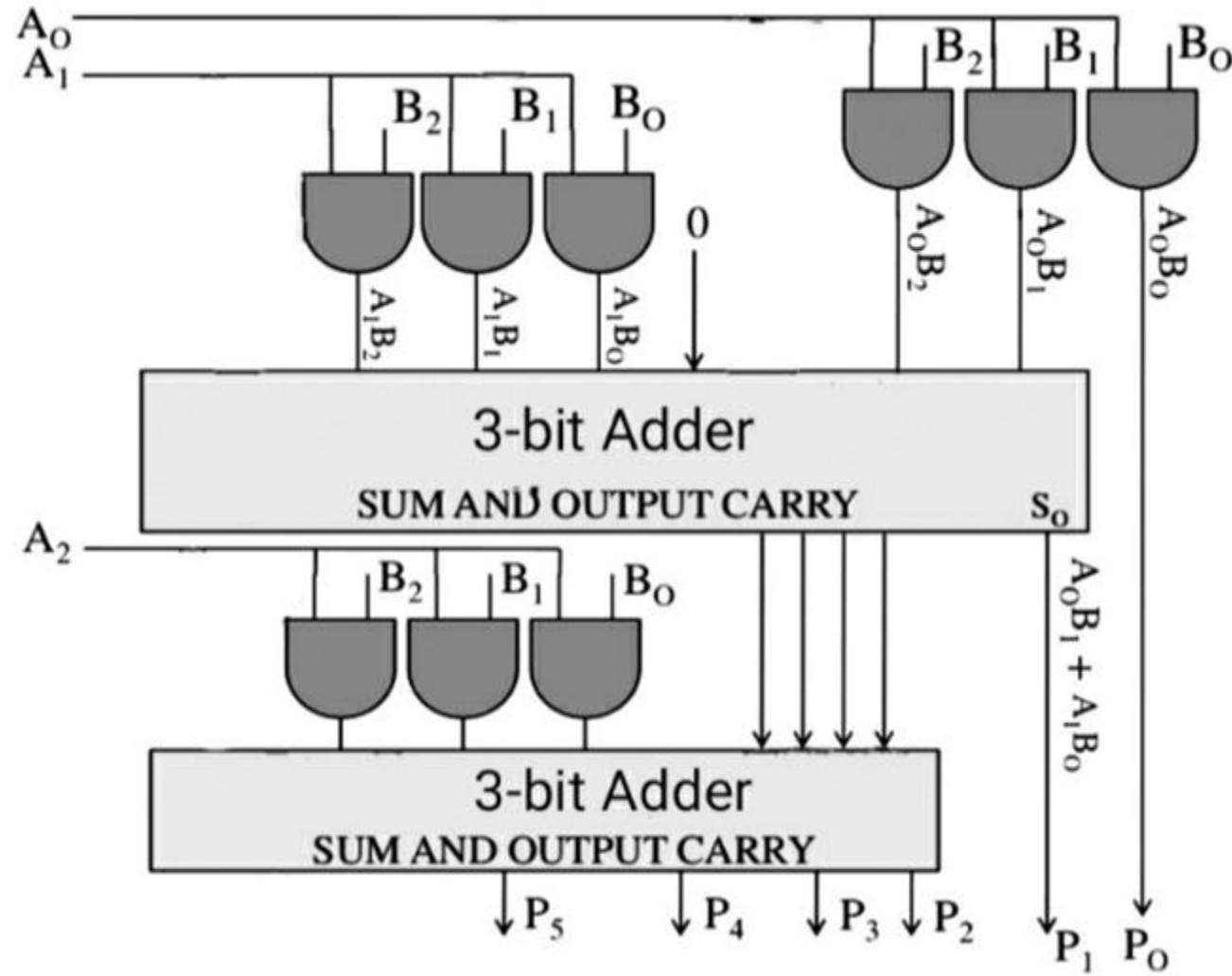
$$\begin{array}{r}
 A2 \ A1 \ A0 \ (\text{multiplicand}) \\
 \times \ B2 \ B1 \ B0 \ (\text{multiplier}) \\
 \hline
 A2B0 \ A1B0 \ A0B0 \\
 A2B1 \ A1B1 \ A0B1 \ X \\
 A2B2 \ A1B2 \ A0B2 \ X \ X \\
 \hline
 A2B2+C+C \ A2B2+A1B2+A2B2+C+C \ A1B1+C+A0B2+A2B0 \ A0B1+A1B0 \\
 A0B
 \end{array}$$





Any Query????

Thank you.....