



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore – 641 107

An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A’ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

COURSE NAME : 19EC306 – Digital Circuits

II YEAR / III SEMESTER

Unit I- COMBINATIONAL CIRCUITS

Topic : Fast adder - CLA



Carry Look-Ahead Adder



The adder produce carry propagation delay while performing other arithmetic operations like multiplication and divisions as it uses several additions or subtraction steps.


This is a major problem for the adder and hence improving the speed of addition will improve the speed of all other arithmetic operations. Hence reducing the carry propagation delay of adders is of great importance.

There are different logic design approaches that have been employed to overcome the carry propagation problem. One widely used approach is to employ a carry look-ahead which solves this problem by calculating the carry signals in advance, based on the input signals. This type of adder circuit is called a carry look-ahead adder.

Here a carry signal will be generated in two cases:

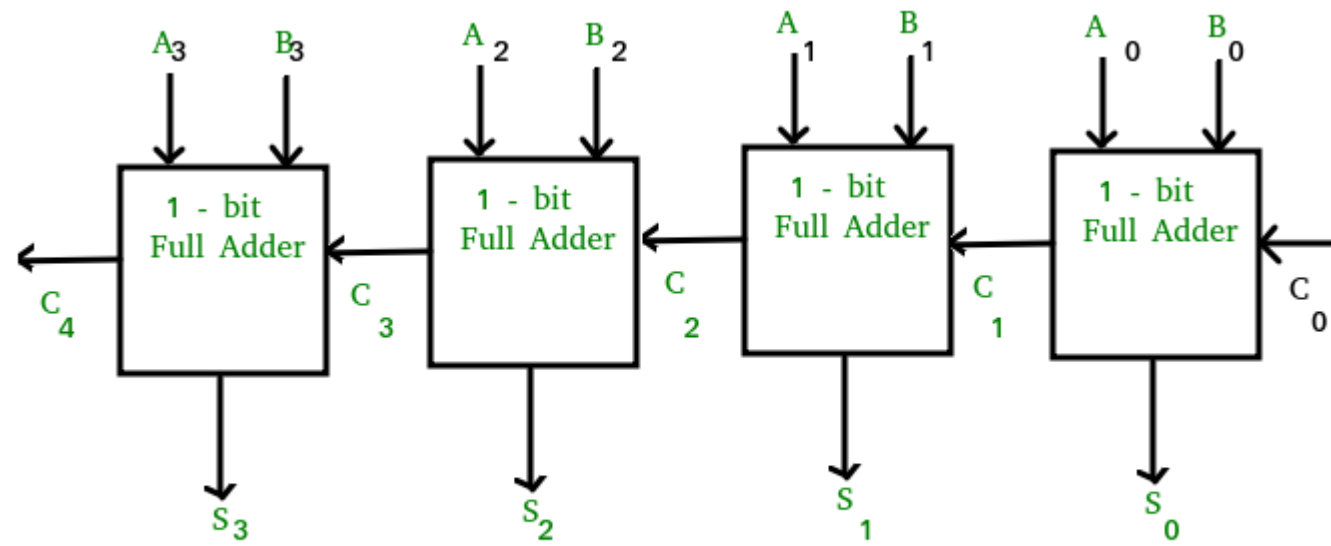1. Input bits A and B are 1
2. When one of the two bits is 1 and the carry-in is 1.

In ripple carry adders, for each adder block, the two bits that are to be added are available instantly. However, each adder block waits for the carry to arrive from its previous block. So, it is not possible to generate the sum and carry of any block until the input carry is known. The i^{th} block waits for the $i - 1^{th}$ block to produce its carry. So there will be a considerable time delay which is carry propagation delay.






Consider the above 4-bit ripple carry adder. The sum S_3 is produced by the corresponding full adder as soon as the input signals are applied to it. But the carry input is not available on its final steady-state value until carry C_3 is available at its steady-state value.

Therefore, though the carry must propagate to all the stages in order that output and carry settle their final steady-state value.

The propagation time is equal to the propagation delay of each adder block, multiplied by the number of adder blocks in the circuit. For example, if each full adder stage has a propagation delay of 20 nanoseconds, then will reach its final correct value after 60 (20 × 3) nanoseconds. The situation gets worse, if we extend the number of stages for adding more number of bits.

Carry Look-ahead Adder :

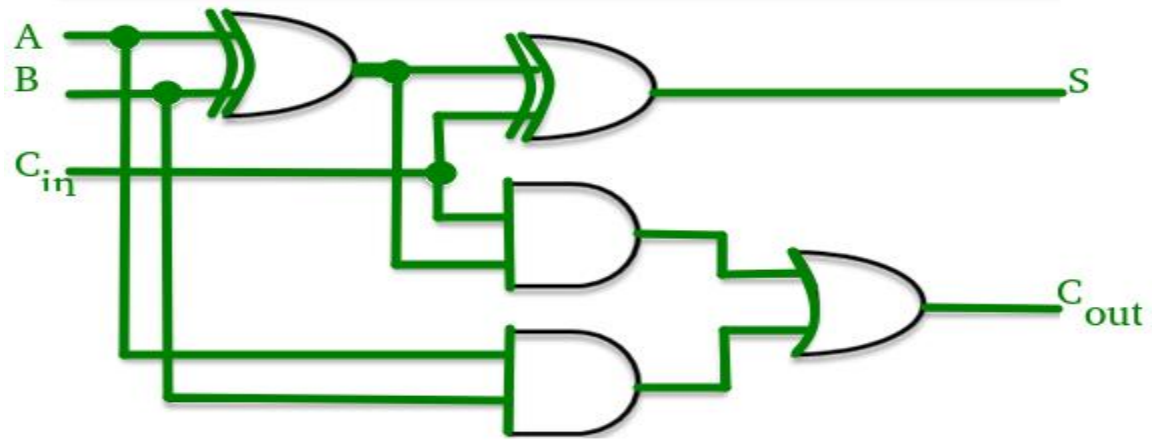A carry look-ahead adder reduces the propagation delay by introducing more complex hardware. In this design, the ripple carry design is suitably transformed such that the carry logic over fixed groups of bits of the adder is reduced to two-level logic. Let us discuss the design in detail.



A	B	C	C + 1	Condition
0	0	0	0	No Carry Generate
0	0	1	0	
0	1	0	0	
0	1	1	1	No Carry Propagate
1	0	0	0	
1	0	1	1	
1	1	0	1	Carry Generate
1	1	1	1	



Consider the full adder circuit shown above with corresponding truth table. We define two variables as 'carry generate' G_i and 'carry propagate' P_i then,

$$P_i = A_i \oplus B_i$$
$$G_i = A_i B_i$$

The sum output and carry output can be expressed in terms of carry generate and carry propagate as

$$S_i = P_i \oplus C_i$$
$$C_{i+1} = G_i + P_i C_i$$


The carry output Boolean function of each stage in a 4 stage carry look-ahead adder can be expressed as

$$C_1 = G_0 + P_0C_{in}$$

$$C_2 = G_1 + P_1C_1 = G_1 + P_1G_0 + P_1P_0C_{in}$$

$$C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_{in}$$
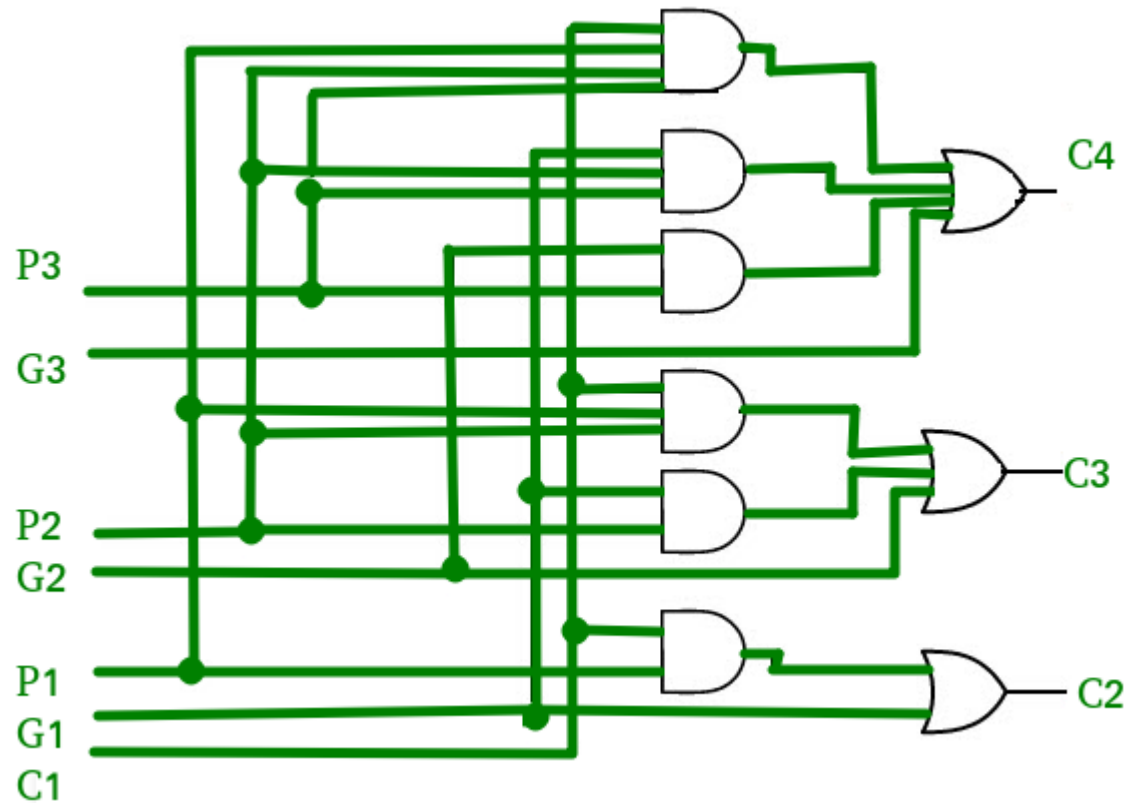
$$C_4 = G_3 + P_3C_3 = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1P_0C_{in}$$





Any Query?????

Thank you.....