



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (PO), Coimbatore – 641 107

Accredited by NAAC-UGC with 'A' Grade

Approved by AICTE, Recognized by UGC & Affiliated to Anna University, Chennai


DEPARTMENT OF ECE

COURSE NAME: 19IT301 COMPUTER ORGANIZATION AND ARCHITECTURE

II YEAR/ III SEM

Unit 2 : ARITHMETIC OPERATIONS

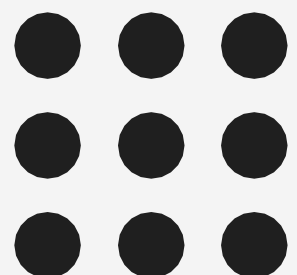Topic 1: **Addition and subtraction of signed numbers**



9/30/2023

K.Sangeetha/AP/ECE / SNSCE / III Sem / COA / UNIT - 2



Binary, signed integer representation



b_3 b_2 b_1 b_0	Sign and Magnitude	2's Complement
0 1 1 1	+7	+7
0 1 1 0	+6	+6
0 1 0 1	+5	+5
0 1 0 0	+4	+4
0 0 1 1	+3	+3
0 0 1 0	+2	+2
0 0 0 1	+1	+1
0 0 0 0	+0	+0
1 0 0 0	-0	-8
1 0 0 1	-1	-7
1 0 1 0	-2	-6
1 0 1 1	-3	-5
1 1 0 0	-4	-4
1 1 0 1	-5	-3
1 1 1 0	-6	-2
1 1 1 1	-7	-1

Logic specification for a stage of binary addition

At the i^{th} stage:

Input:

c_i is the carry-in

Output:

s_i is the sum


c_{i+1} carry-out to $(i+1)^{st}$ state

x_i	y_i	Carry-in c_i	Sum s_i	Carry-out c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$s_i = \bar{x}_i \bar{y}_i c_i + \bar{x}_i y_i \bar{c}_i + x_i \bar{y}_i \bar{c}_i + x_i y_i c_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = y_i c_i + x_i c_i + x_i y_i$$

Example:

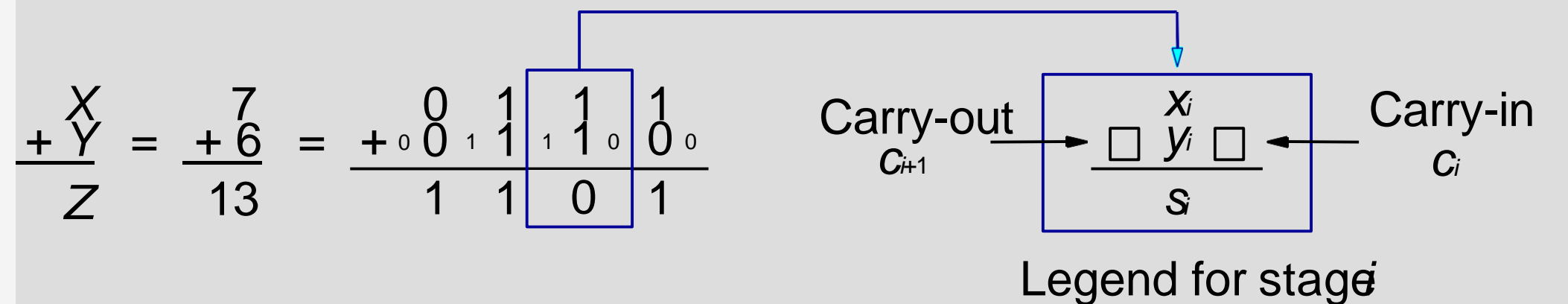


Addition logic for a single stage

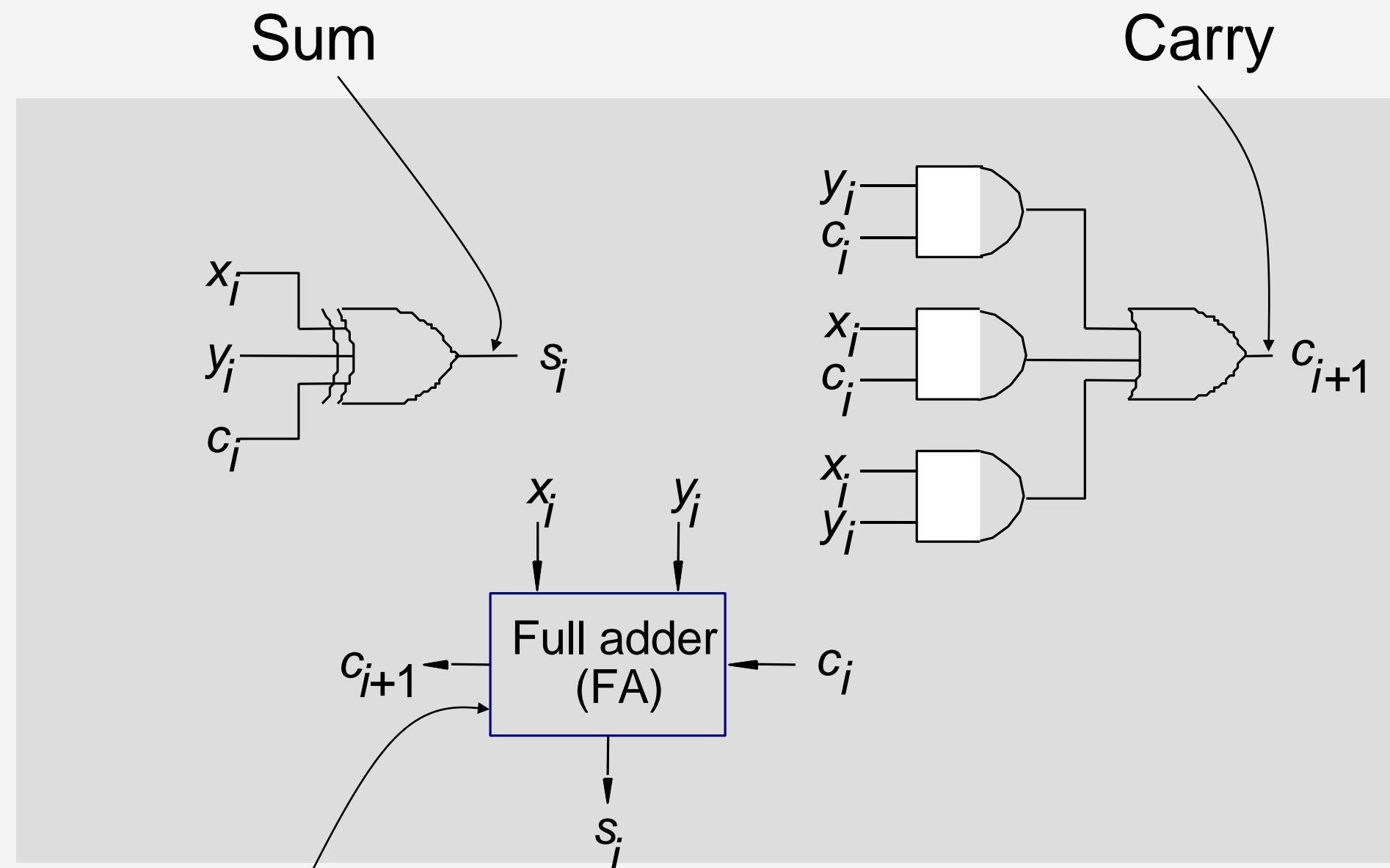

Full Adder (FA): Symbol for the complete circuit for a single stage of addition


n-bit ripple carry adder

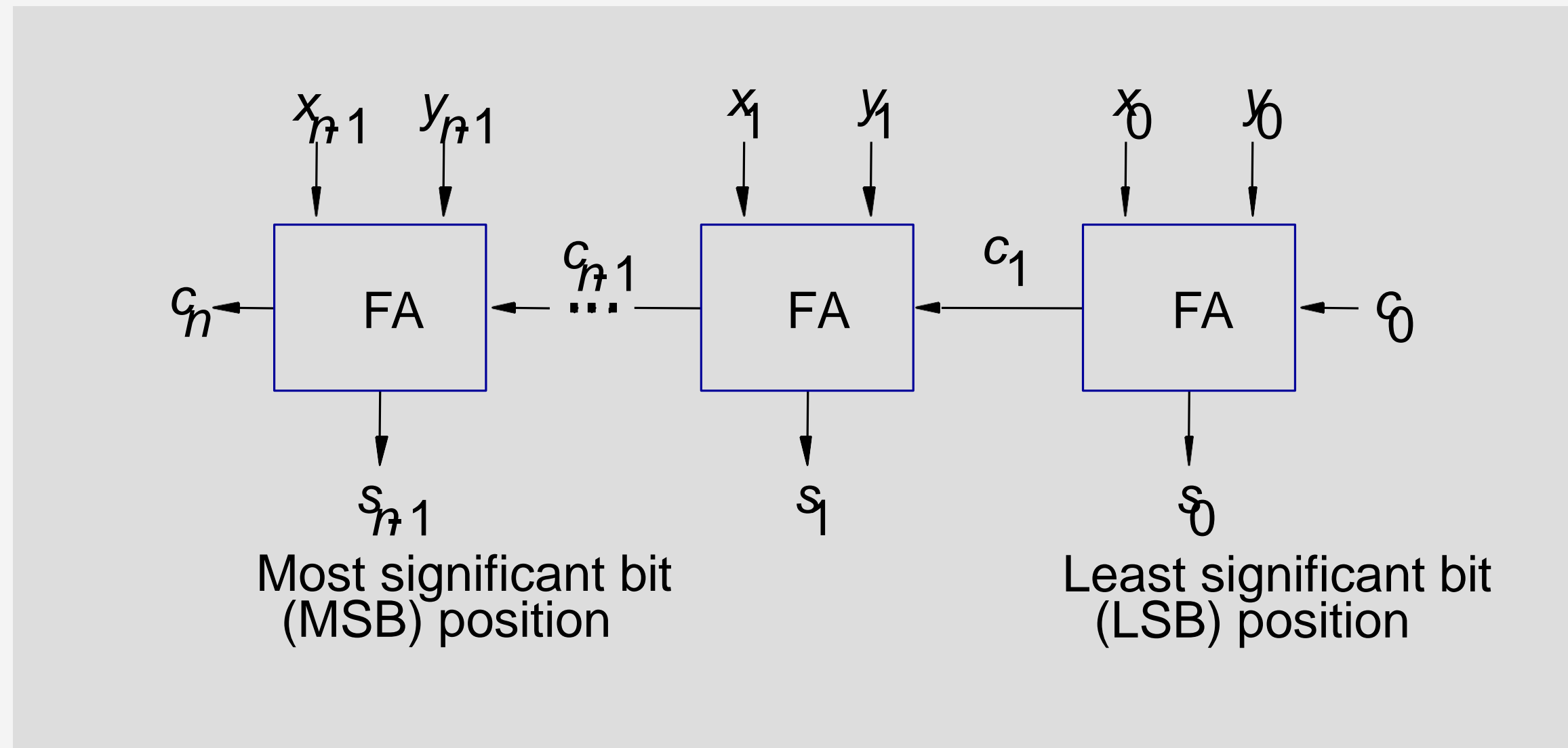- Cascade n-full adder (FA) blocks to form a n-bit adder.
- Carries propagate or ripple through this cascade, n-bit ripple carry adder.




K n-bit adder

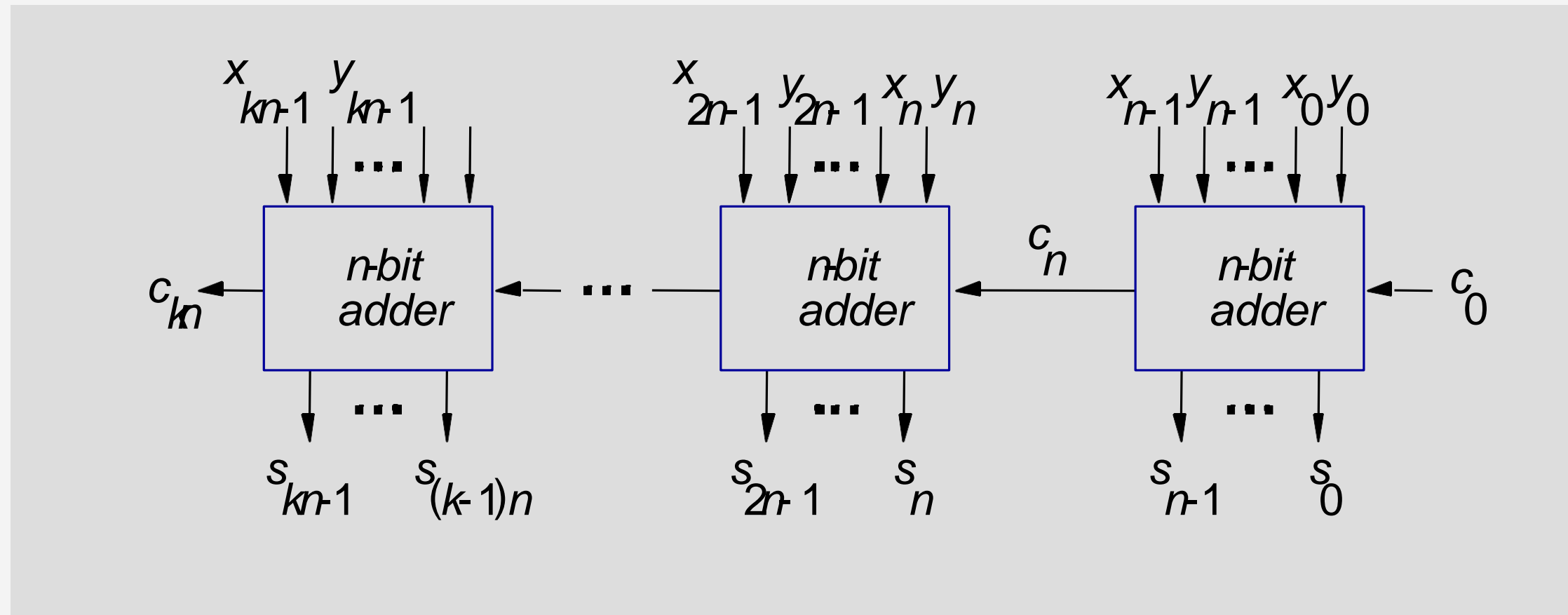
- K n-bit numbers can be added by cascading k n-bit adders



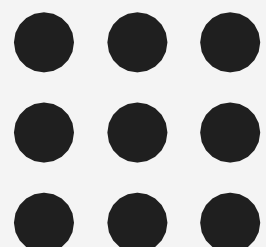
- Carry-in c_0 into the LSB position provides a convenient way to perform subtraction
- Each n-bit adder forms a block, so this is cascading of blocks.
- Carries ripple or propagate through blocks, Blocked Ripple Carry Adder



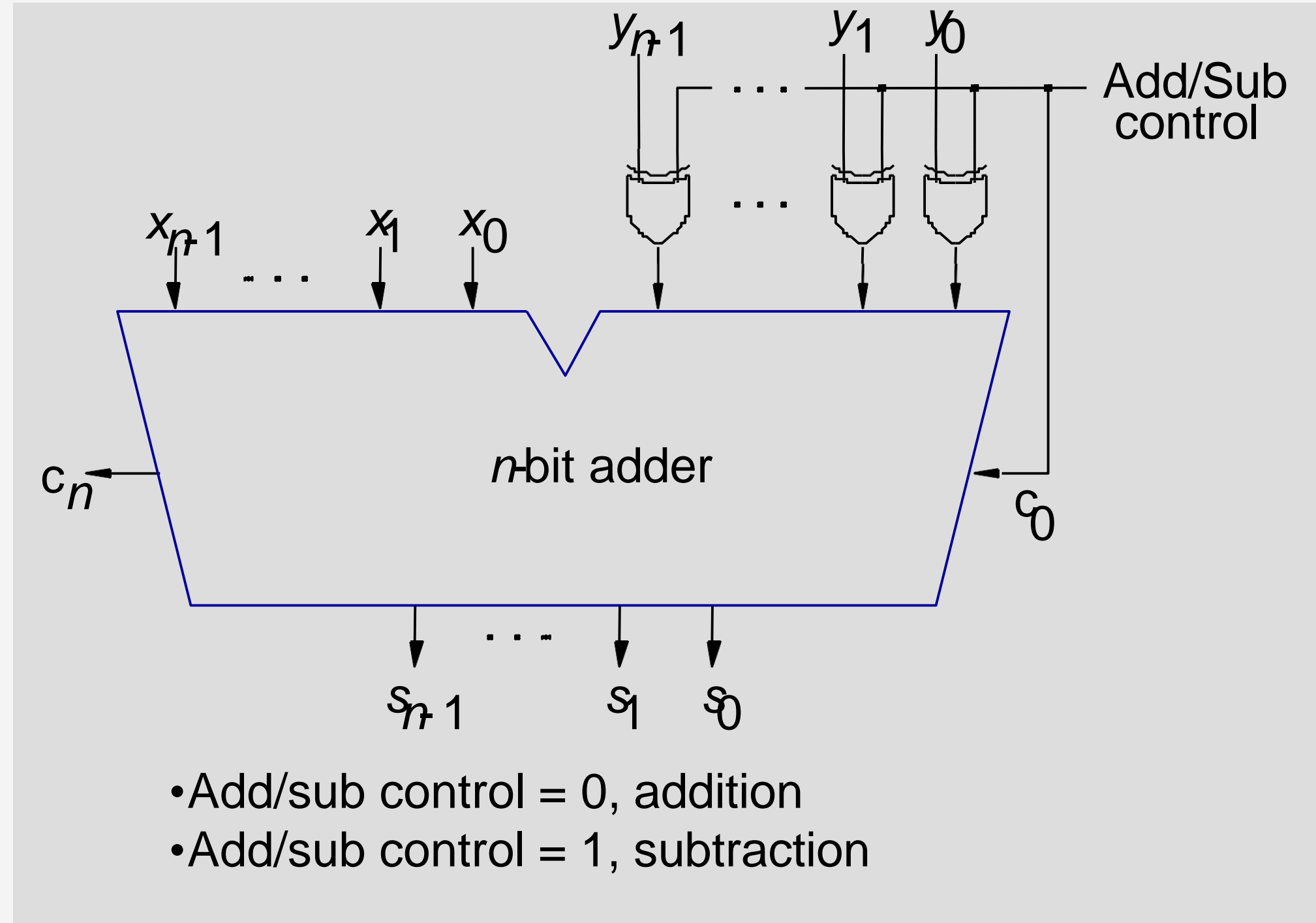Binary addition- subtraction logic network



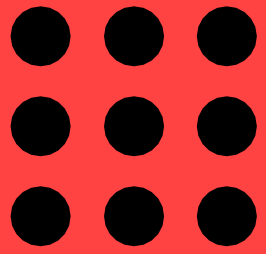- $X - Y$ is equivalent to adding 2's complement of Y to X
- 2's complement is equivalent to 1's complement + 1
- $X - Y = X + Y + 1$



Detecting overflows



- Overflows can only occur when the sign of the two operands is the same.
- Overflow occurs if the sign of the result is different from the sign of the operands.
- Circuit to detect overflow can be implemented by the following logic expressions:

$$\text{Overflow} = x_{n-1}y_{n-1}\bar{s}_{n-1} + \bar{x}_{n-1}\bar{y}_{n-1}s_{n-1}$$

$$\text{Overflow} = c_n \oplus c_{n-1}$$



Thank You