



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (PO), Coimbatore – 641 107

Accredited by NAAC-UGC with 'A' Grade

Approved by AICTE, Recognized by UGC & Affiliated to Anna University, Chennai


DEPARTMENT OF ECE

COURSE NAME: 19IT301 COMPUTER ORGANIZATION AND ARCHITECTURE

II YEAR/ III SEM

Unit 2 : ARITHMETIC OPERATIONS


Topic 2: Design of Fast Adders

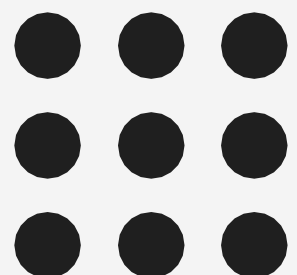

9/30/2023


K.Sangeetha/AP/ECE / SNSCE / III Sem / COA / UNIT - 2

Computing the add time

 


Consider 0^{th} stage:

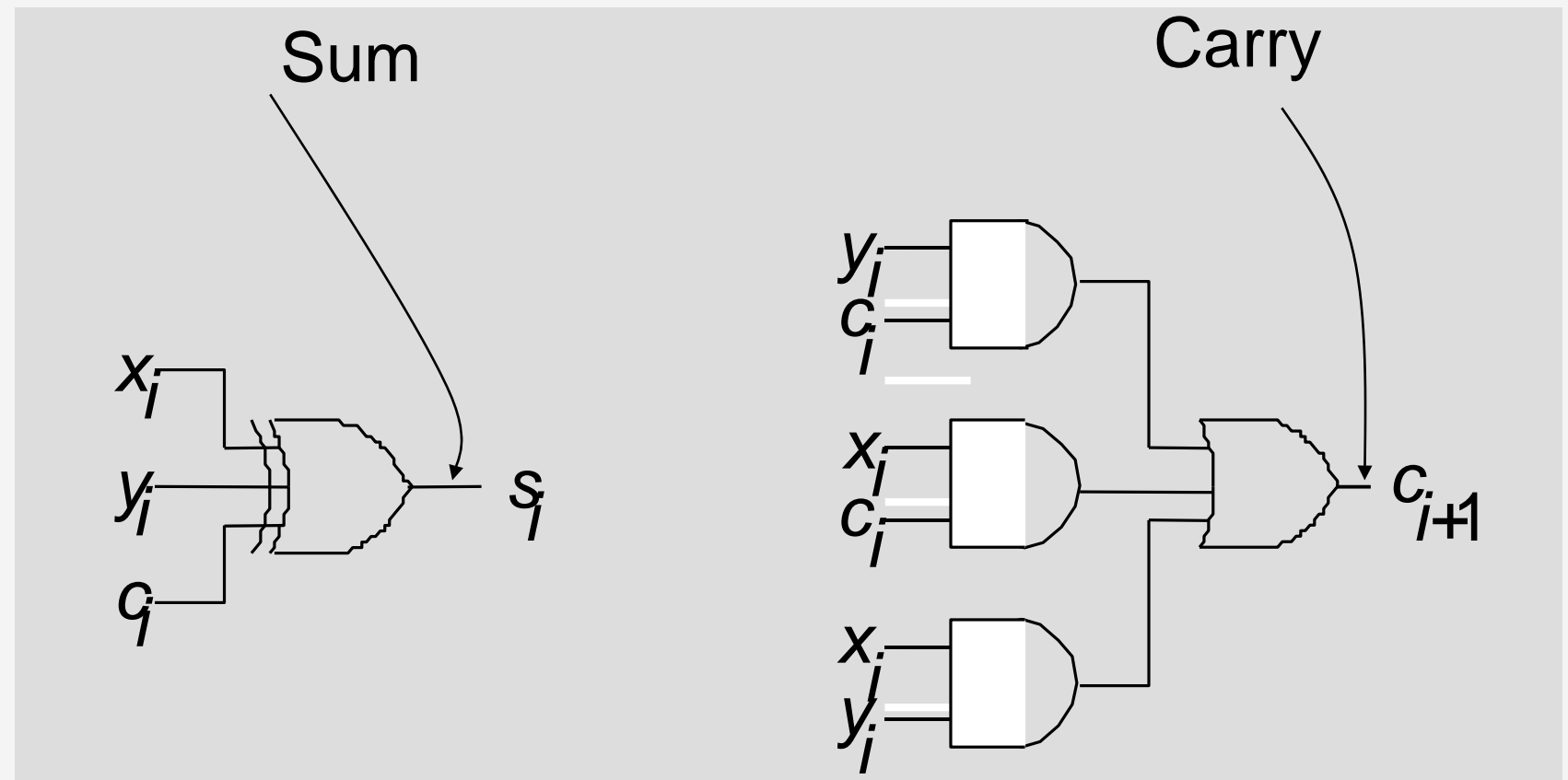- c_1 is available after 2 gate delays.
- s_1 is available after 1 gate delay.



Computing the add time

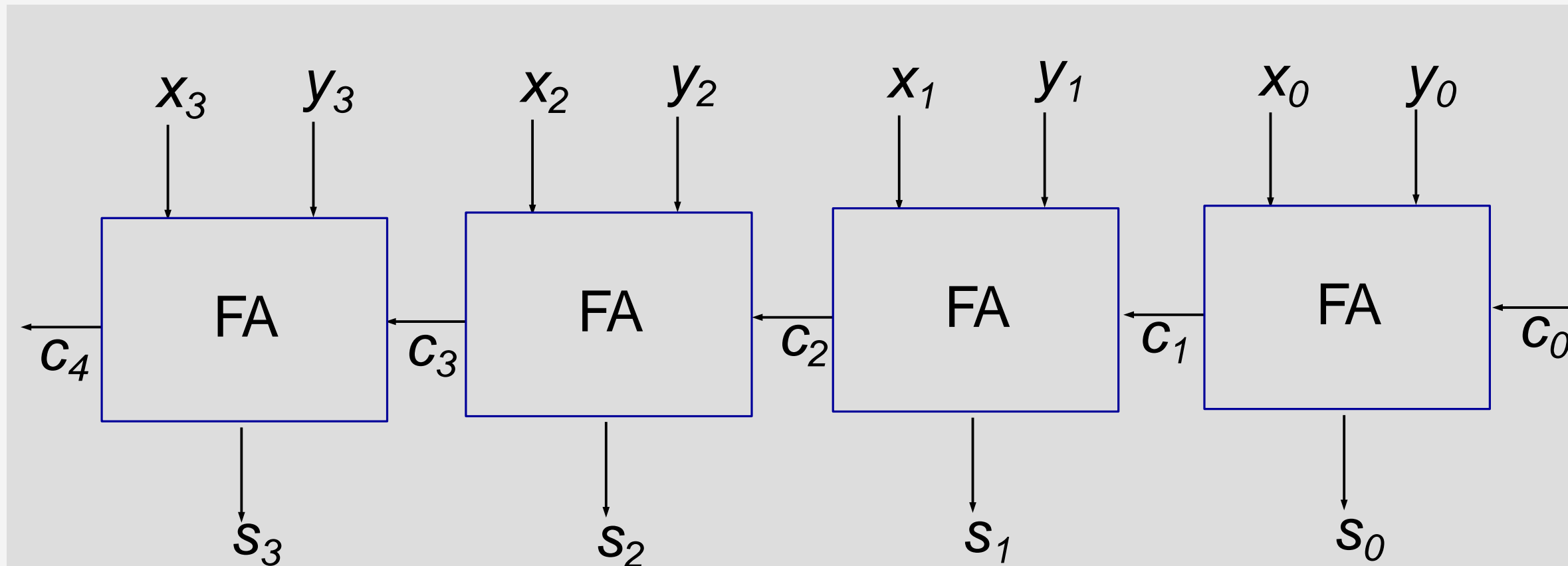Cascade of 4 Full Adders, or a 4-bit adder



- s_0 available after 1 gate delays, c_1 available after 2 gate delays.
- s_1 available after 3 gate delays, c_2 available after 4 gate delays.
- s_2 available after 5 gate delays, c_3 available after 6 gate delays.
- s_3 available after 7 gate delays, c_4 available after 8 gate delays.

For an n -bit adder, s_{n-1} is available after $2n-1$ gate delays
 c_n is available after $2n$ gate delays.



Drawback of ripple carry adder



All sum bits are available in $2n$ gate delays.

- Two approaches can be used to reduce delay in adders:
 - 1) Use the fastest possible electronic technology in implementing the ripple-carry design.
 - 2) Use an augmented logic-gate network structure.



Design of fast adders

Recall the equations:

$$s_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Second equation can be written as:

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

We can write:

$$c_{i+1} = G_i + P_i c_i$$

$$\text{where } G_i = x_i y_i \text{ and } P_i = x_i + y_i$$

- G_i is called **generate function** and P_i is called **propagate function**
- G_i and P_i are computed only from x_i and y_i and not c_i , thus they can be computed in one gate delay after X and Y are applied to the inputs of an n -bit adder.

Carry-Lookahead Addition

$$c_{i+1} = G_i + P_i c_i$$

$$c_i = G_{i-1} + P_{i-1} c_{i-1}$$

$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} c_{i-1})$$

continuing

$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} c_{i-2}))$$


until

$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0$$

- All carries can be obtained 3 gate delays after X , Y and c_0 are applied.
 - One gate delay for P_i and G_i
 - Two gate delays in the AND-OR circuit for c_{i+1}
- All sums can be obtained 1 gate delay after the carries are computed.
- Independent of n , n -bit addition requires only 4 gate delays.
- This is called **Carry look-ahead** adder.



Carry-Lookahead Adder

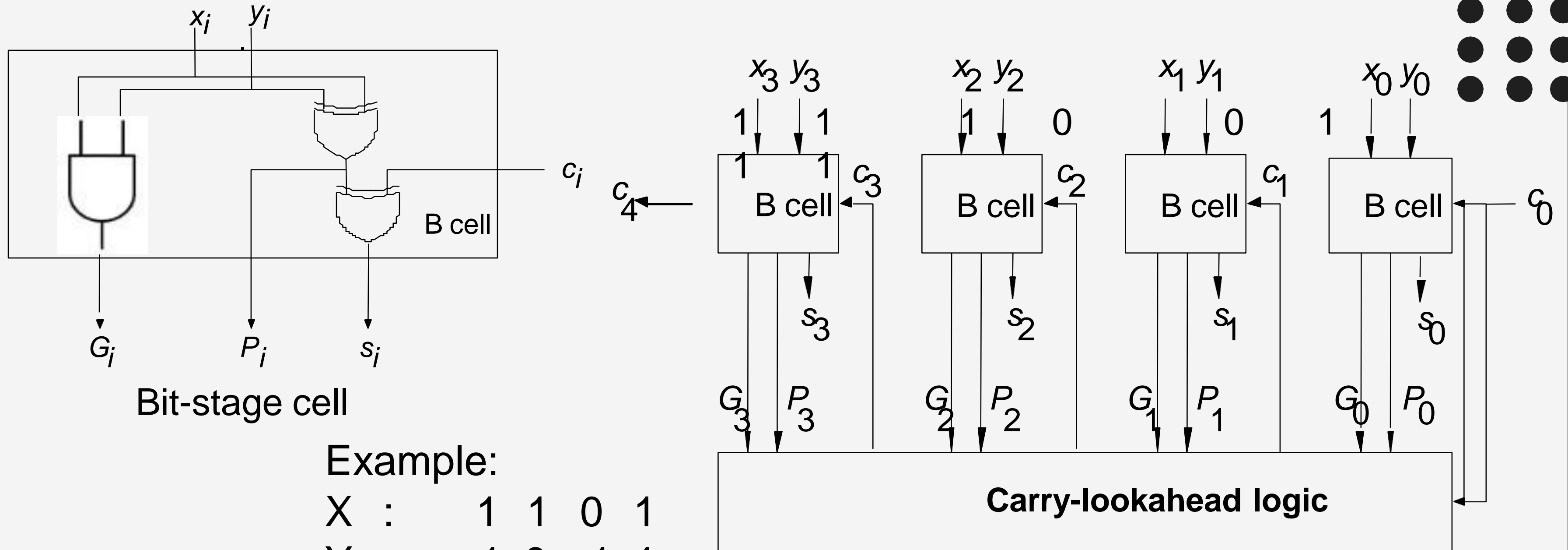

Bit-stage cell

Example:

X :	1	1	0	1
Y:	1	0	1	1
	1	1	0	0

0

Actually $P_i = x_i + y_i$

But, $P_i = x_i \oplus y_i$

4-bit carry look-ahead adder



Example

$$S_0 = x_0 \oplus y_0 \oplus c_0 = 1 \oplus 1 \oplus 0 = 0$$

$$c_0 = 0$$

$$G_0 = x_0 y_0 = 1 \cdot 1 = 1$$

$$P_0 = x_0 \oplus y_0 = 1 \oplus 1 = 0$$

$$c_{i+1} = G_i + P_i c_i$$

$$c_1 = G_0 + P_0 c_0$$

$$c_1 = 1 + 0 = 1$$

$$S_1 = x_1 \oplus y_1 \oplus c_1 = 0 \oplus 1 \oplus 1 = 0$$

$$c_2 = G_1 + P_1 c_1$$


$$= G_1 + P_1 (G_0 + P_0 c_0)$$

$$c_2 = G_1 + P_1 G_0 + P_1 P_0 c_0$$

$$G_1 = x_1 y_1 = 0 \cdot 1 = 0$$

$$P_1 = x_1 \oplus y_1 = 0 \oplus 1 = 1$$
 
$$c_2 = 0 + 1 \cdot 1 + 1 \cdot 0 \cdot 0 = 1$$



Truth table for OR

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

Truth table for Ex-or

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0



Example(cntd)

$$S_2 = x_2 \oplus y_2 \oplus c_2 = 1 \oplus 0 \oplus 1 = 0$$

$$C_3 = G_2 + P_2 C_2 \\ = G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0)$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$G_2 = x_2 y_2 = 1 \cdot 0 = 0$$

$$P_2 = x_2 \oplus y_2 = 1 \oplus 0 = 1$$

$$C_3 = 0 + 1 \cdot 0 + 1 \cdot 1 \cdot 1 + 1 \cdot 1 \cdot 0 \cdot 0 = 1$$

$$S_3 = x_3 \oplus y_3 \oplus c_3 = 1 \oplus 1 \oplus 1 = 1$$

$$C_4 = G_3 + P_3 C_3 \\ = G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0)$$


$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

$$G_3 = x_3 y_3 = 1 \cdot 1 = 1$$

$$P_3 = x_3 \oplus y_3 = 1 \oplus 1 = 0$$

$$C_4 = 1 + 0 \cdot 0 + 0 \cdot 1 \cdot 0 + 0 \cdot 1 \cdot 1 \cdot 1 + 0 \cdot 1 \cdot 1 \cdot 0 \cdot 0 = 1 + 0 + 0 + 0 + 0$$

$$= 1$$

 

Carry-Lookahead Adder



- Performing n -bit addition in 4 gate delays independent of n is good only theoretically because of fan-in constraints.
- Last AND gate and OR gate require a fan-in of $(n+1)$ for a n -bit adder.
 - For a 4-bit adder ($n=4$) fan-in of 5 is required.
 - Practical limit for most gates.
- In order to add operands longer than 4 bits, we can cascade 4-bit carry look-ahead adders.
- Cascade of carry look-ahead adders is called **Blocked Carry look-ahead adder.**



Higher-level Generate & Propagate Functions



Carry-out from a 4-bit block can be given as:

$$c_4 = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0c_0$$

$$c_3 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0c_0$$

Rewrite this as:


$$P_0^I = P_3P_2P_1P_0$$

$$G_0^I = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0$$

Subscript / denotes the blocked carry look-ahead and identifies the block cascade 4 4-bit adders, c_{16} can be expressed as:


$$c_{16} = G_3^I + P_3^I G_2^I + P_3^I P_2^I G_1^I + P_3^I P_2^I P_1^I G_0^I + P_3^I P_2^I P_1^I P_0^I c_0$$

Blocked Carry Look-ahead adder

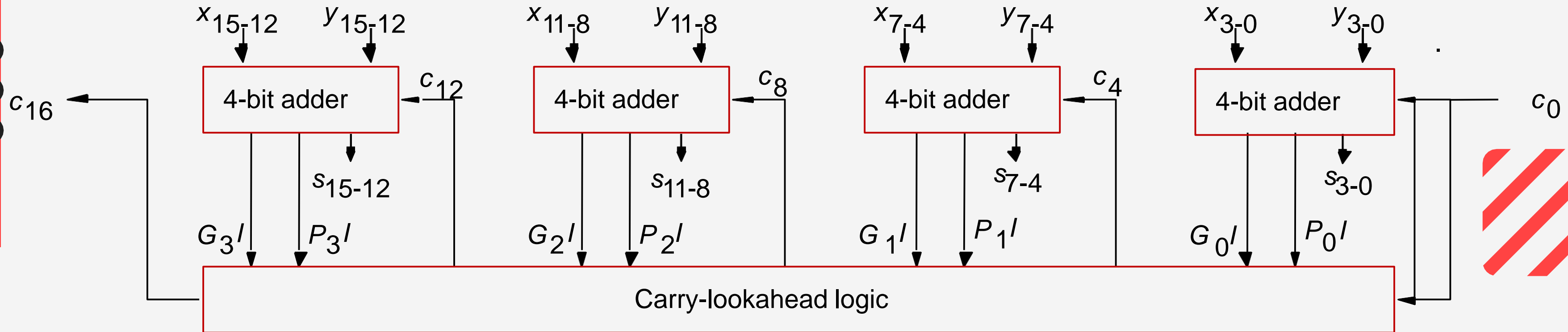

After x_i , y_i and c_0 are applied as inputs:

 - G_i and P_i for each stage are available after 1 gate delay.
- P^l is available after 2 and G^l after 3 gate delays.
- All carries are available after 5 gate delays.
- c_{16} is available after 5 gate delays.



Assessment




1. What distinguishes the look-ahead-carry adder?
 - a) It is slower than the ripple-carry adder
 - b) It is easier to implement logically than a full adder
 - c) It is faster than a ripple-carry adder
 - d) It requires advance knowledge of the final answer

2. Carry look-ahead logic uses the concepts of _____
 - a) Inverting the inputs
 - b) Complementing the outputs
 - c) Generating and propagating carries
 - d) Ripple factor



Assessment

 



3. What is one disadvantage of the ripple-carry adder?

- a) The interconnections are more complex
- b) More stages are required to a full adder
- c) It is slow due to propagation time
- d) All of the mentioned

4. The carry propagation delay in 4-bit full-adder circuits _____

 - a) Is cumulative for each stage and limits the speed at which arithmetic operations are performed
- b) Is normally not a consideration because the delays are usually in the nanosecond range
- c) Decreases in direct ratio to the total number of full-adder stages
- d) Increases in direct ratio to the total number of full-adder stages, but is not a factor in limiting the speed of arithmetic operations



 

Answers



1. C
2. C
3. C
4. A





Thank You