



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore – 641 107

An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A’ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

COURSE NAME : 19EC306 – Digital Circuits

II YEAR / III SEMESTER


Unit III- Sequential circuits


Topic : JK FF - Characteristic table and equation



J-K Flip Flop:

 In JK flip flops, the diagram over here represents the basic structure of the flip flop which consists of Clock (CLK), Clear (CLR), Preset (PR).



 

TRUTH TABLE

J	K	Q_N	Q_{N+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0



Operations:

Case 1:

$PR=CLR=0$ This condition is in its invalid state.

Case 2:

$PR=0$ and $CLR=1$ The PR is activated which means the output in the Q is set to 1. Therefore, the flip flop is in the set state.

Case 3:

$PR=1$ and $CLR=0$ The CLR is activated which means the output in the Q' is set to 1. Therefore, the flip flop is in the reset state.



Case 4:

PR=CLR=1 In this condition the flip flop works in its normal way whereas the PR and CLR gets deactivated.

Race around condition:

When the J and K both are set to 1, the input remains high for a longer duration of time, then the output keeps on toggling. Toggle means that switching in the output instantly i.e. Q=0, Q'=1 will immediately change to Q=1 and Q'=0 and this continuation keeps on changing. This change in output leads to race around condition.

Characteristics Equation for JK Flip Flop: $Q_{N+1} = JQ'_N + K'Q_N$



Any Query????

Thank you.....