



# **SNS COLLEGE OF ENGINEERING**

Kurumbapalayam (Po), Coimbatore – 641 107

**An Autonomous Institution**

Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A’ Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING**

**COURSE NAME : 19EC306 – Digital Circuits**

**II YEAR / III SEMESTER**


**Unit III- Sequential circuits**

**Topic : Up/ Down Counter**

## 3-bit Synchronous Up/Down Counter
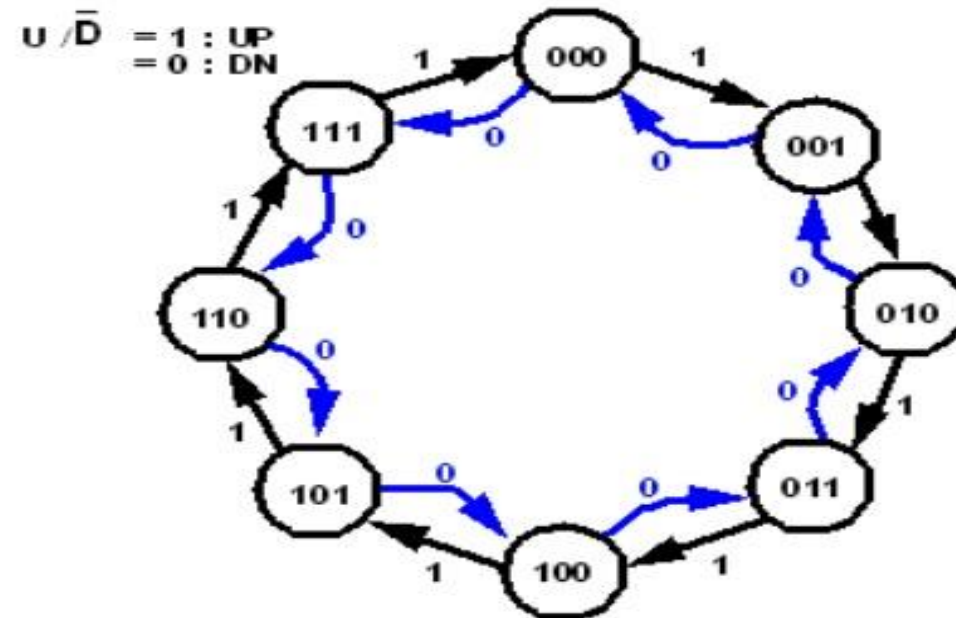
### Up/Down Counters

- A 3-bit binary up/down counter (State diagram)



26

## 3-bit Synchronous Down Counter

State Table

CP	UP	Q <sub>C</sub>	Q <sub>B</sub>	Q <sub>A</sub>	DOWN
0	↻	0	0	0	↻
1	↻	0	0	1	↻
2	↻	0	1	0	↻
3	↻	0	1	1	↻
4	↻	1	0	0	↻
5	↻	1	0	1	↻
6	↻	1	1	0	↻
7	↻	1	1	1	↻




# 3-bit Synchronous Down Counter

Excitation table


Input UP/DOWN (UD)	Present State			Next State			Flip-flop Inputs		
	$Q_C$	$Q_B$	$Q_A$	$Q_{C+1}$	$Q_{B+1}$	$Q_{A+1}$	$T_C$	$T_B$	$T_A$
0	0	0	0	1	1	1	1	1	1
0	0	0	1	0	0	0	0	0	1
0	0	1	0	0	0	1	0	1	1
0	0	1	1	0	1	0	0	0	1
0	1	0	0	0	1	1	1	1	1
0	1	0	1	1	0	0	0	0	1
0	1	1	0	1	0	1	0	1	1
0	1	1	1	1	1	0	0	0	1
1	0	0	0	0	0	1	0	0	1
1	0	0	1	0	1	0	0	1	1
1	0	1	0	0	1	1	0	0	1
1	0	1	1	1	0	0	1	1	1
1	1	0	0	1	0	1	0	0	1
1	1	0	1	1	1	0	0	1	1
1	1	1	0	1	1	1	0	0	1
1	1	1	1	0	0	0	1	1	1

## 3-bit Synchronous Down Counter

### K-map simplification

 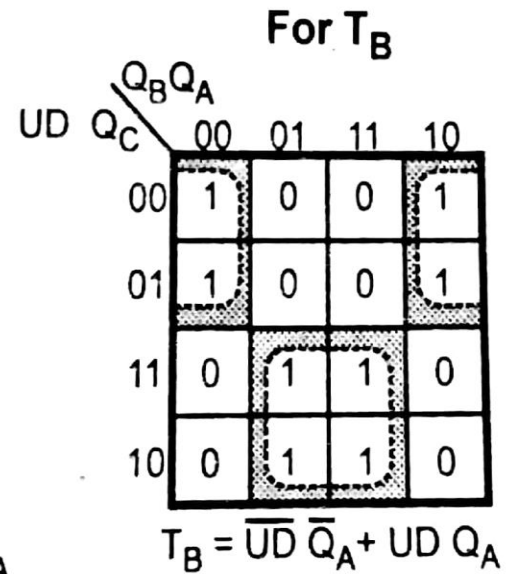 

# Logic Diagram

 





Any Query????

Thank you.....