



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



19ECB231/ Digital Electronics


Fast Adder - Carry Look Ahead adder






INTRODUCTION:-

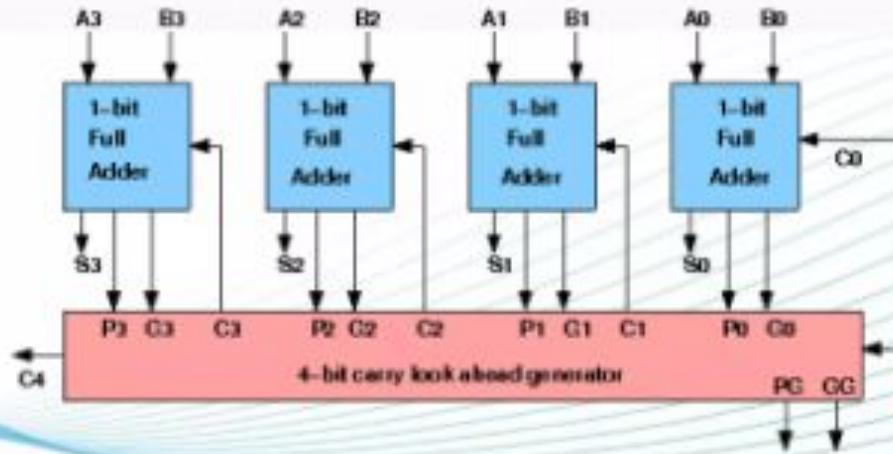A look ahead carry adder is fast adder which improves speed by reducing the amount of time required to determine carry bits. It reduces the time which are delayed at each stage.





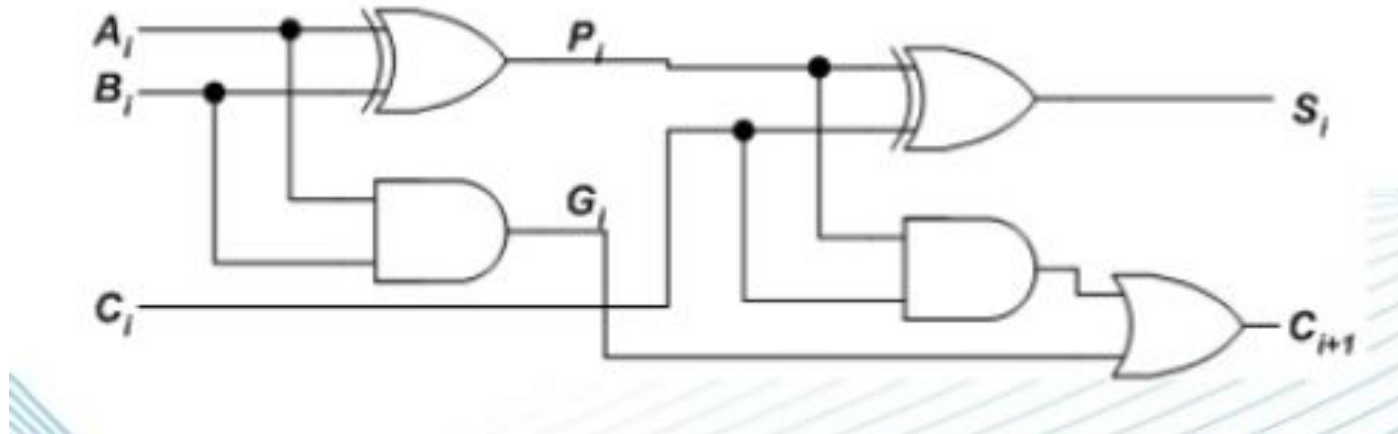FULL ADDER CKT TO SHOW CARRY GENERATION AND PROPAGATION





**TRUTH TABLE OF FULL
ADDER TO SHOW CARRY
GENERATION AND**

INPUT			OUTPUT			
Row	A	B	C_{in}	Sum	C_{out}	
0	0	0	0	0	0	No carry generation $C_{out} = 0$
1	0	0	1	1	0	
2	0	1	0	1	0	Carry propagation $C_{out} = C_{in}$
3	0	1	1	0	1	
4	1	0	0	1	0	
5	1	0	1	0	1	
6	1	1	0	0	1	Carry generation $C_{out} = 1$
7	1	1	1	1	1	



EXPRESSION FOR CARRY GENERATION AND PROPAGATION

- From truth table , carry generation in row 6th and 7th is given by :-

$$G_i = A_i B_i$$

- Similarly the carry propagation P_i occur with either $A_i = 1$ and $B_i = 0$ or vice versa

$$P_i = A_i \oplus B_i$$


G_i is known as the carry Generate signal

P_i is known as the carry propagate signal

- The new expressions for the output sum and the carryout are given by:-

$$S_i = P_i \oplus C_{in}$$

$$C_{out} = G_i + P_i C_i$$

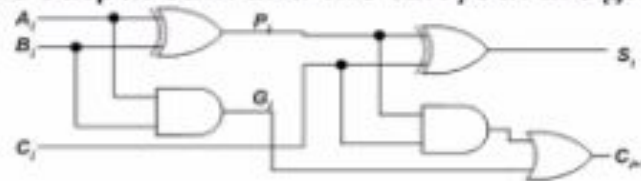



❖ Boolean expression of the carry outputs of various stages

$$C_1 = G_0 + P_0 C_0$$


$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

The general expression is :-----
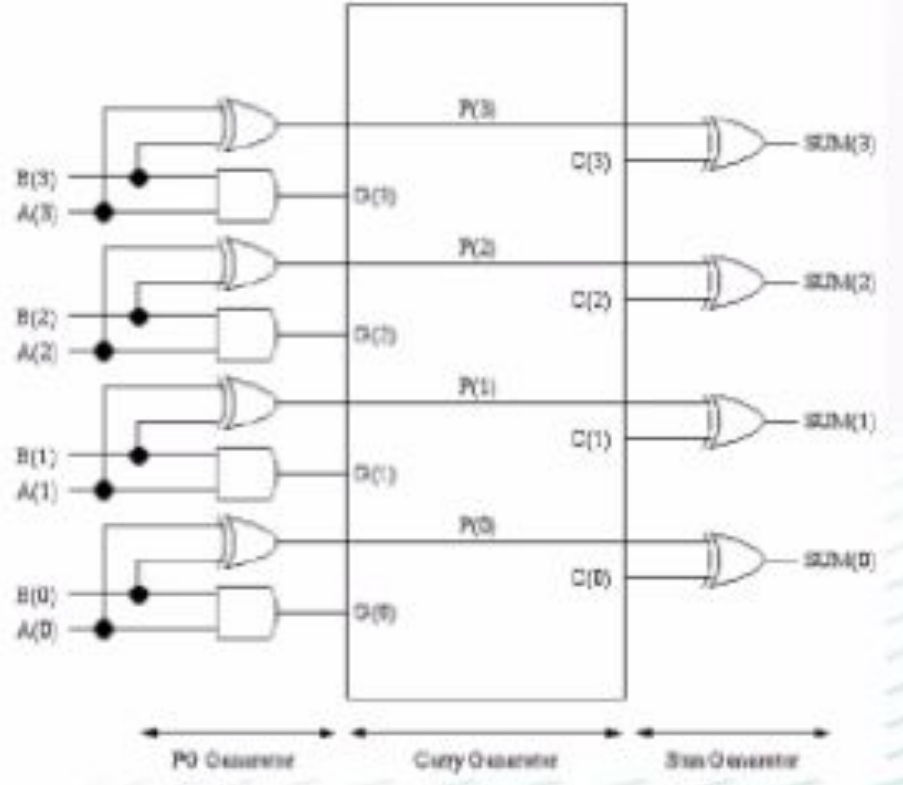
$$C_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_2 P_1 G_0 + P_i P_{i-1} \dots P_1 P_0 C_0$$





RECAP



Thank You!