



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**  
**An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **19ECB204 – LINEAR AND DIGITAL CIRCUITS**

II YEAR/ III SEMESTER  
1

**UNIT 1 – FUNDAMENTALS OF OPAMP**

**TOPIC 5 – Instrumentation amplifiers**



Guess?????



+





# Why instrumentation amplifier?



- ❑ To amplify small signals in the presence of noise has gone through an evolution over the years
- ❑ The simplest approach, the discrete operational amplifier, isn't suitable as an instrumentation amplifier
- ❑ An instrumentation amplifier is used to amplify very low-level signals, rejecting noise and interference signals



# What is an instrumentation amplifier?



- An instrumentation amplifier is used to amplify very low-level signals, rejecting noise and interference signals
- Inputs to the **instrumentation amplifiers** will have very low signal energy
- High gain and accurate
- High CMRR



# Instrumentation Amplifier using Op Amp




- Op-amps 1 & 2 are non-inverting amplifiers
- Op-amp 3 is a difference amplifier
- Instrumentation amplifier's final output  $V_{out}$  is the amplified difference of the input signals applied to the input terminals of op-amp 3
- Let the outputs of op-amp 1 and op-amp 2 be  $V_{o1}$  and  $V_{o2}$  respectively

$$\text{Then, } V_{out} = (R_3/R_2)(V_{o1}-V_{o2})$$

- The potential at node A is the input voltage  $V_1$ . Hence the potential at node B is also  $V_1$ , from the virtual short concept. Thus, the potential at node G is also  $V_1$



# Activity

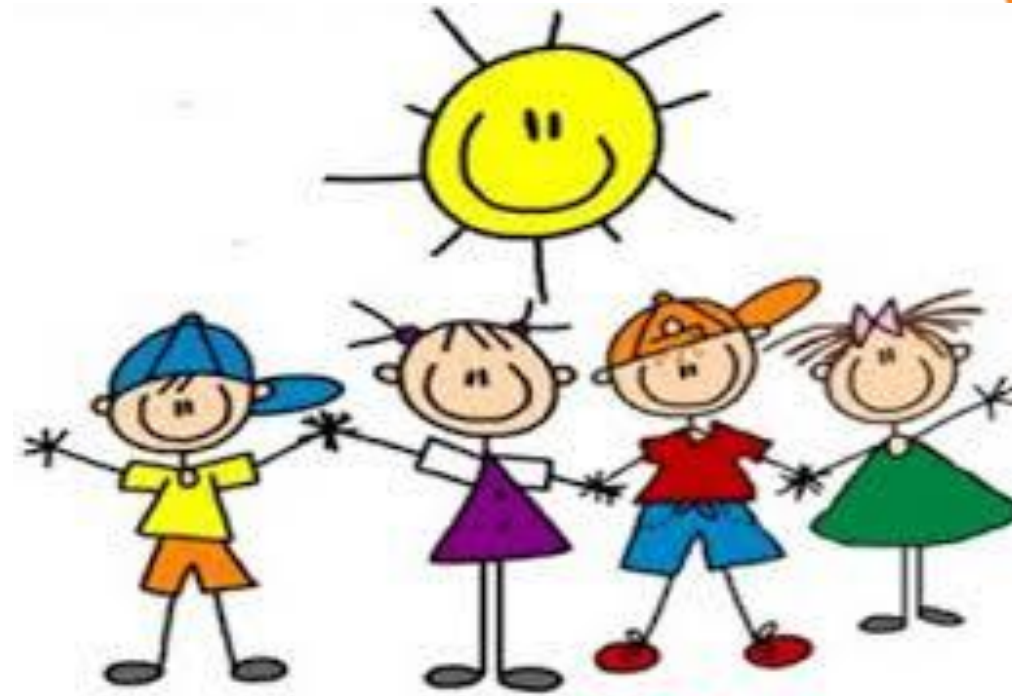

## *In class activity*


Students should make the correct shape from the given tangram kit.


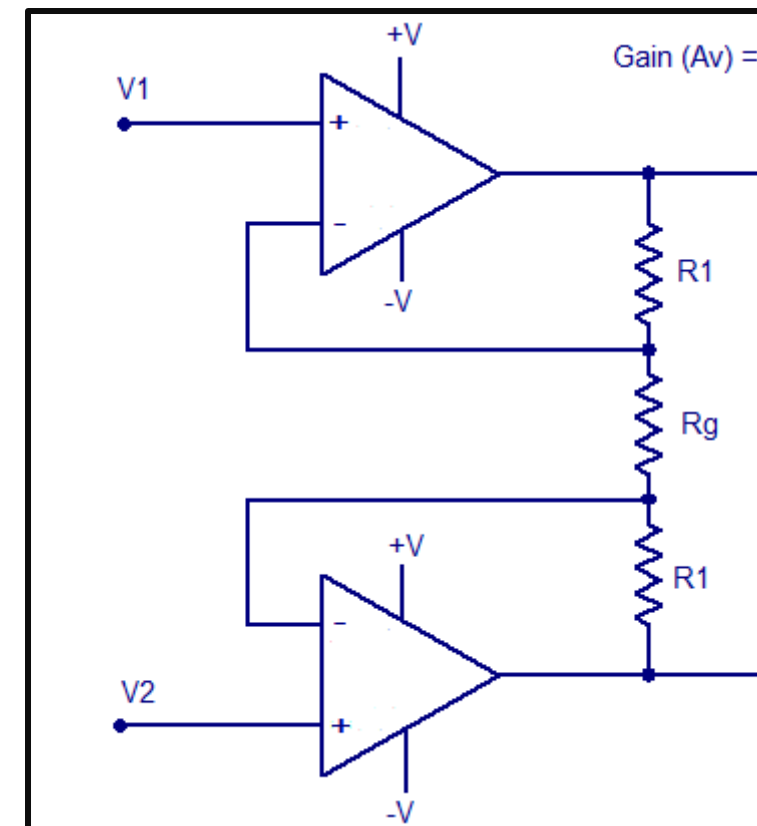
# Input Stage




- ❖ The circuit is divided into two stages.
- ❖ The input stage has two non-inverting buffer amplifiers
- ❖ The input-stage amplifiers also provide high impedance, which minimizes loading of the sensors.
- ❖ The gain-setting resistor ( $R_G$ ) allows the designer to select any gain within the operating region of the device.





# Output Stage

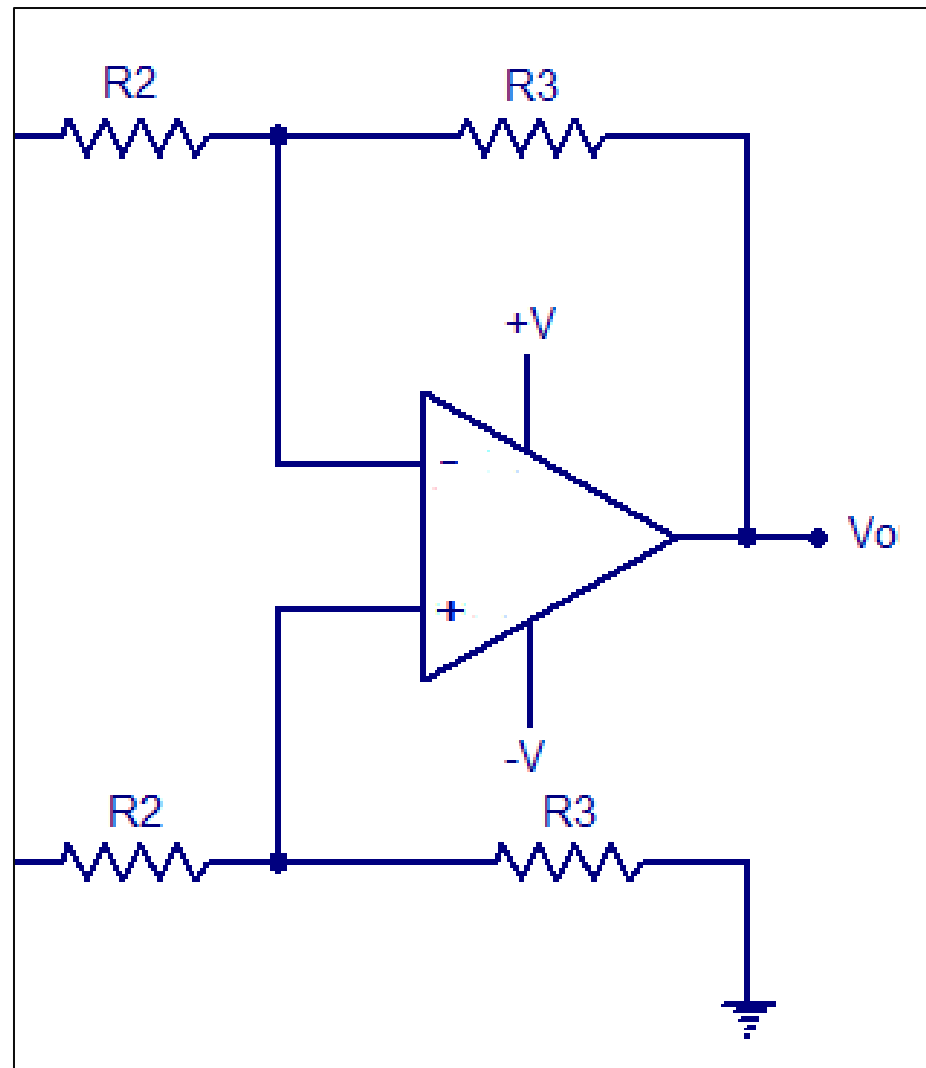


- ❖ The output stage is a traditional difference amplifier.
- ❖ The ratio of internal resistors,  $R2/R1$ , sets the gain of the internal difference amplifier
- ❖ Typically  $G = 1 \text{ V/V}$  for most instrumentation amplifiers
- ❖ The balanced signal paths from the input to the output yield excellent CMRR.





# Instrumentation Amplifier

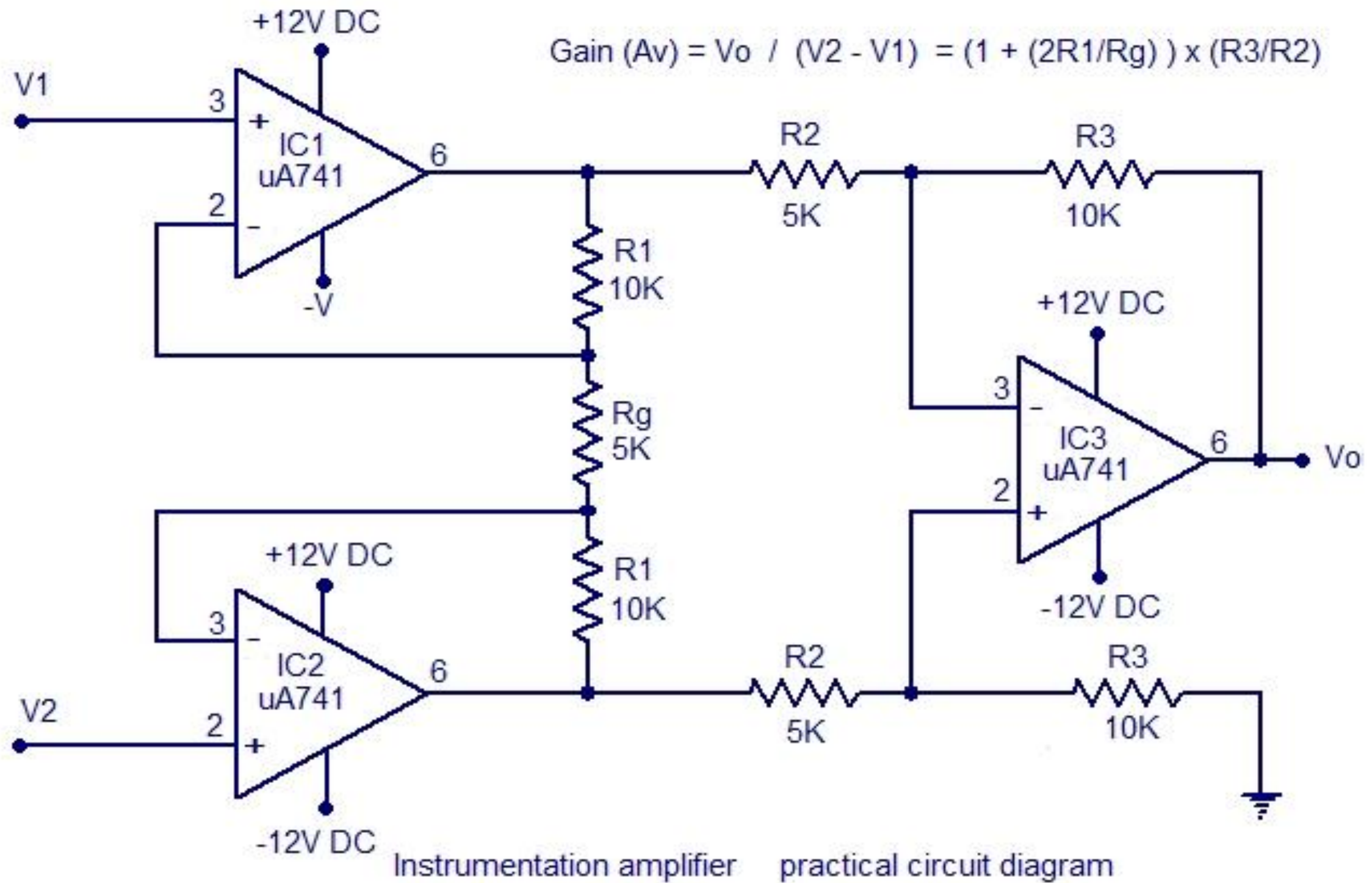



# Applications



EEG



ECG



BP



Light Intensity Meter



Analog Weighing  
scale



# Advantages



- Accurate Testing and Measurement
- Stable and Easy to Use
- Reliability of the Setup and Results
- Highly Scalable



# Disadvantages



## Long Range Transmission Issues

- Superimposing of the original wave when the sound or noise gets transmitted over a long range.
- The system will depend on special cables that can cancel this noise or superimposition



# Assessment



## 1. An instrumentation system does not include

- a) Transducer
- b) Instrumentation amplifier
- c) Automatic process controller
- d) Tester

Answer: d

## 2. Why output of transducer is not directly connected to indicator or display?

- a) Low level output is produced
- b) High level output is produced
- c) No output is produced
- d) Input is fed directly

Answer: a

## 3. What are the features of instrumentation amplifier?

- a) Low noise
- b) High gain accuracy
- c) Low thermal and time drift
- d) All of the mentioned

Answer: d





**THANK YOU**