



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**  
**An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **19ECB204 – LINEAR AND DIGITAL CIRCUITS**

II YEAR/ III SEMESTER  
1

#### **UNIT 1 – FUNDAMENTALS OF OPAMP**

#### **TOPIC 7 – Op-Amp circuits using diodes**



Guess?????





## Why?



- In digital circuits, an adder–subtractor is a circuit that is capable of adding or subtracting numbers
- A circuit that does adding or subtracting depends on a control signal.
- It is also possible to construct a circuit that performs both addition and subtraction at the same time.
- The Subtract or also called a differential amplifier, uses both the inverting and non-inverting inputs to produce an output signal which is the difference between the two input voltages  $V_1$  and  $V_2$  .



# RECTIFIER



➤ An electronic circuit, which produces either DC signal or a pulsated DC signal, when an AC signal is applied to it is called as a **rectifier**

## *Types of Rectifiers*

Two types:


- **Half wave rectifier**
- **Full wave rectifier**


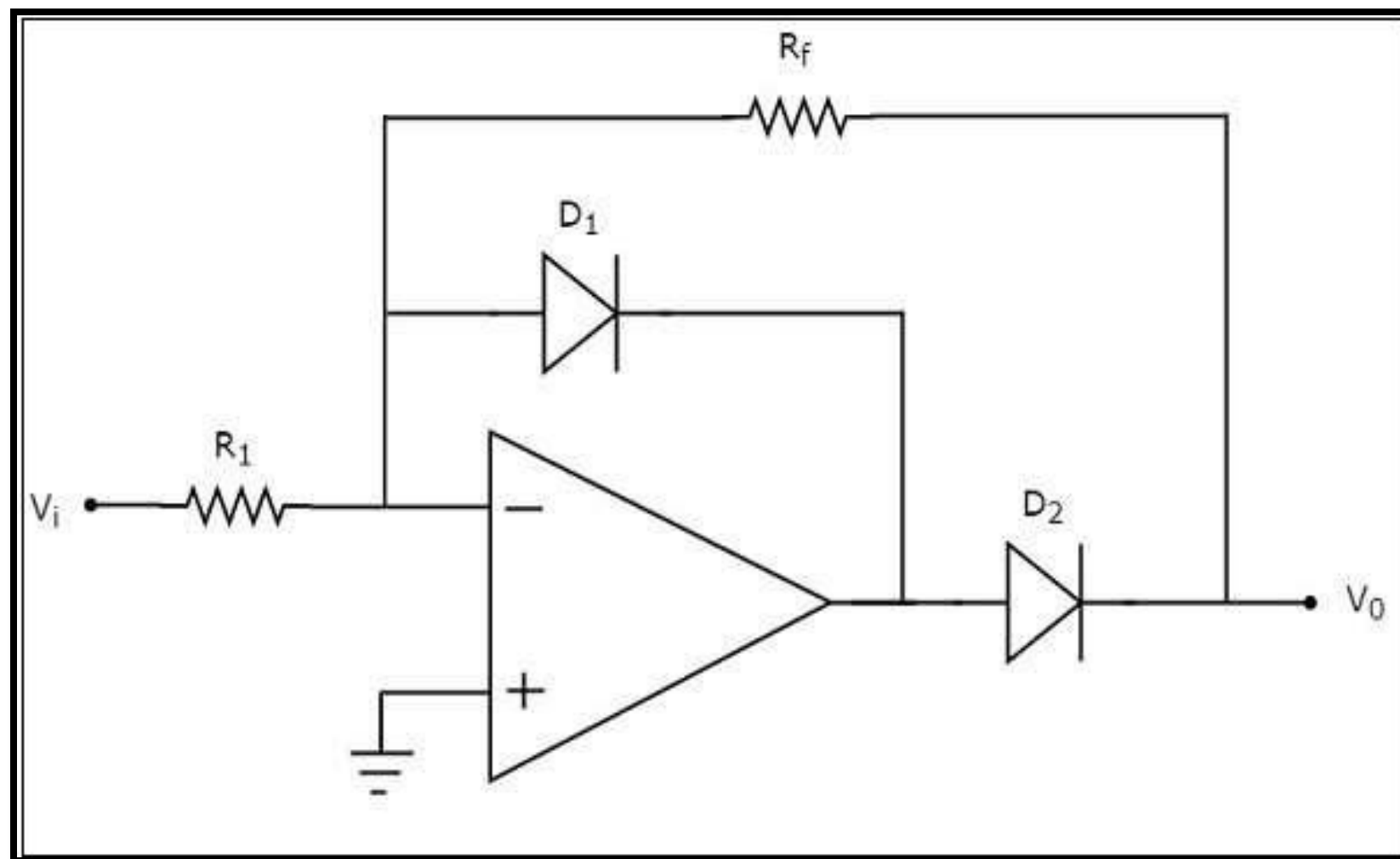
# Half wave Rectifier



□ A **half wave rectifier** is a rectifier that produces positive half cycles at the output for one half cycle of the input and zero output for the other half cycle of the input





# Subtractor using Op Amp



- An inverting amplifier, with two diodes  $D_1$  and  $D_2$  in addition
- If the input resistance are unequal then the circuit become a differential amplifier
- For the **positive half cycle** of the sinusoidal input, the output of the op-amp will be negative
- Hence, diode  $D_1$  will be forward biased.
- When diode  $D_1$  is in forward bias, output voltage of the op-amp will be  $-0.7\text{ V}$
- So, diode  $D_2$  will be reverse biased. Hence, the **output voltage** of the above circuit is **zero** volts



# Subtractor using Op Amp



❑ There is **no (zero) output** of half wave rectifier for the positive half cycle of a sinusoidal input

❑ For the **negative half cycle** of sinusoidal input, the output of the op-amp will be positive

❑ Hence, the diodes  $D_1$  and  $D_2$  will be reverse biased and forward biased respectively

❑ So, the output voltage of above circuit will be

$$V_0 = -(R_f / R_1) V_1$$

❑ Therefore, the output of a half wave rectifier will be a **positive half cycle** for a negative half cycle of the sinusoidal input Wave forms





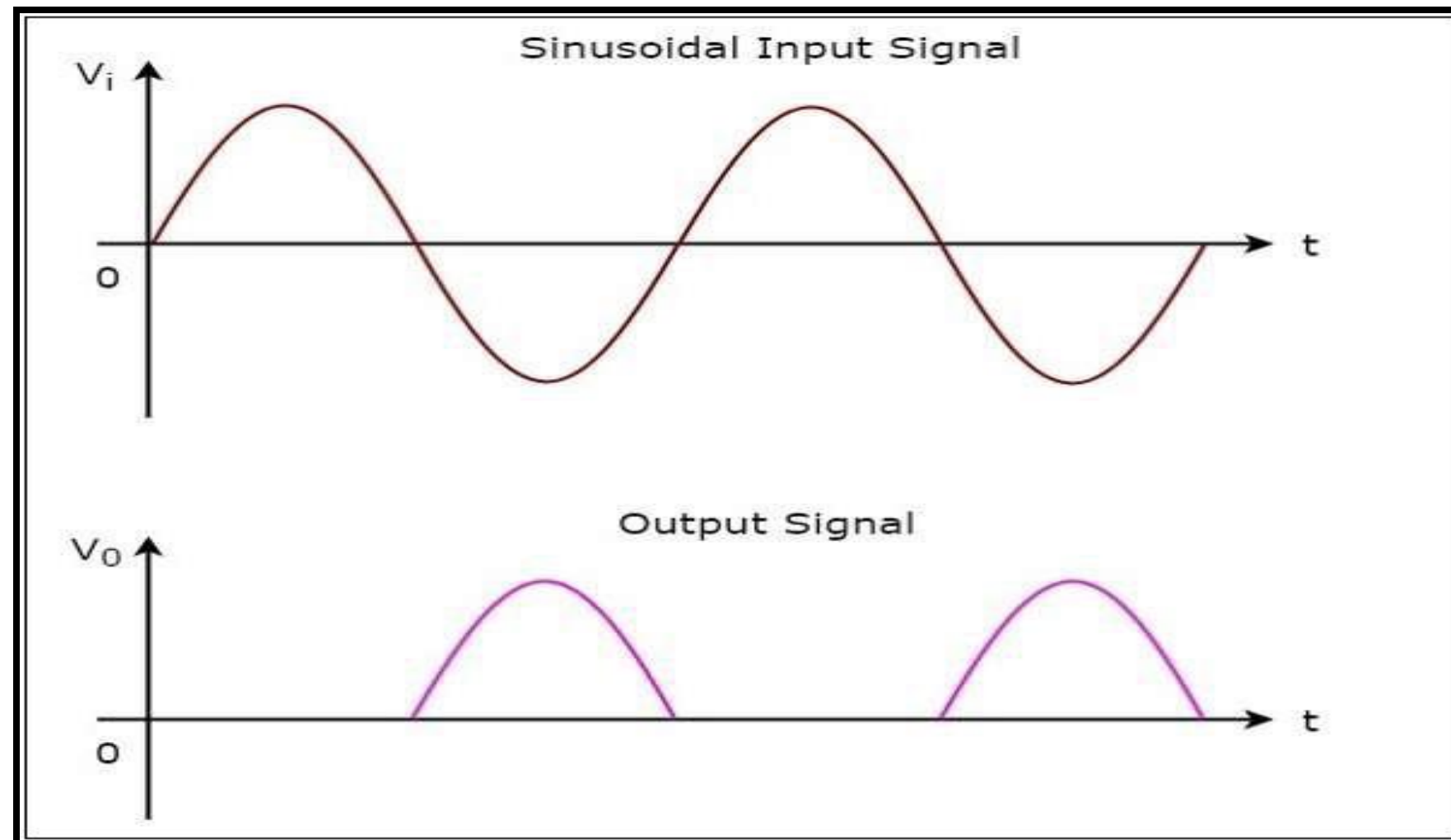
# Waveform




The **input** and **output waveforms** of a half wave rectifier are shown in the following figure







# Activity

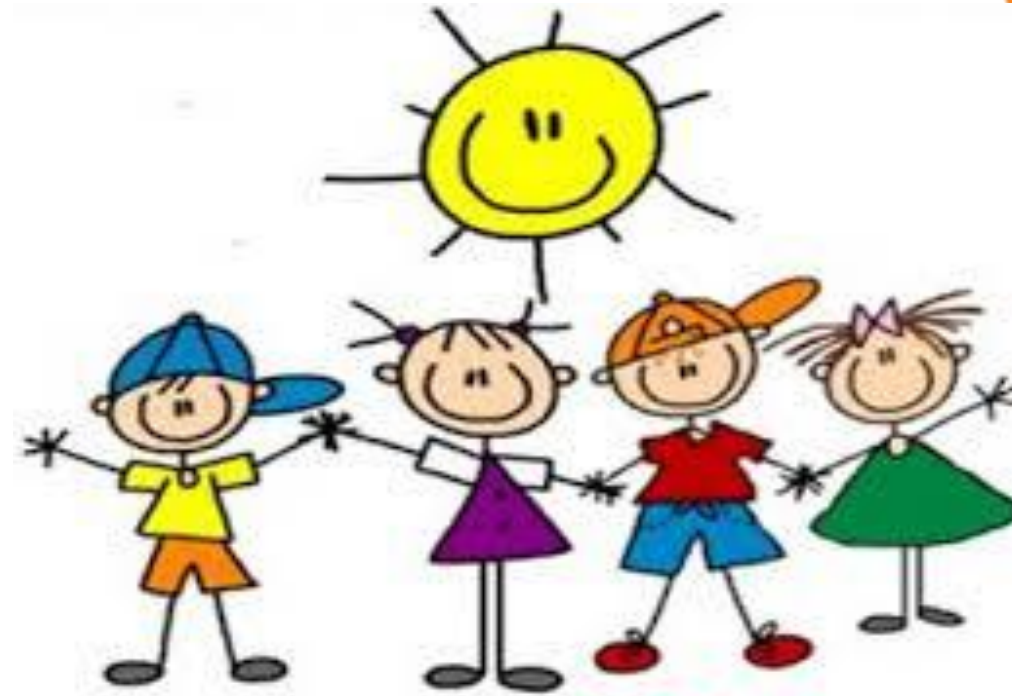

## *In class activity*


Students should make the correct shape from the given tangram kit.


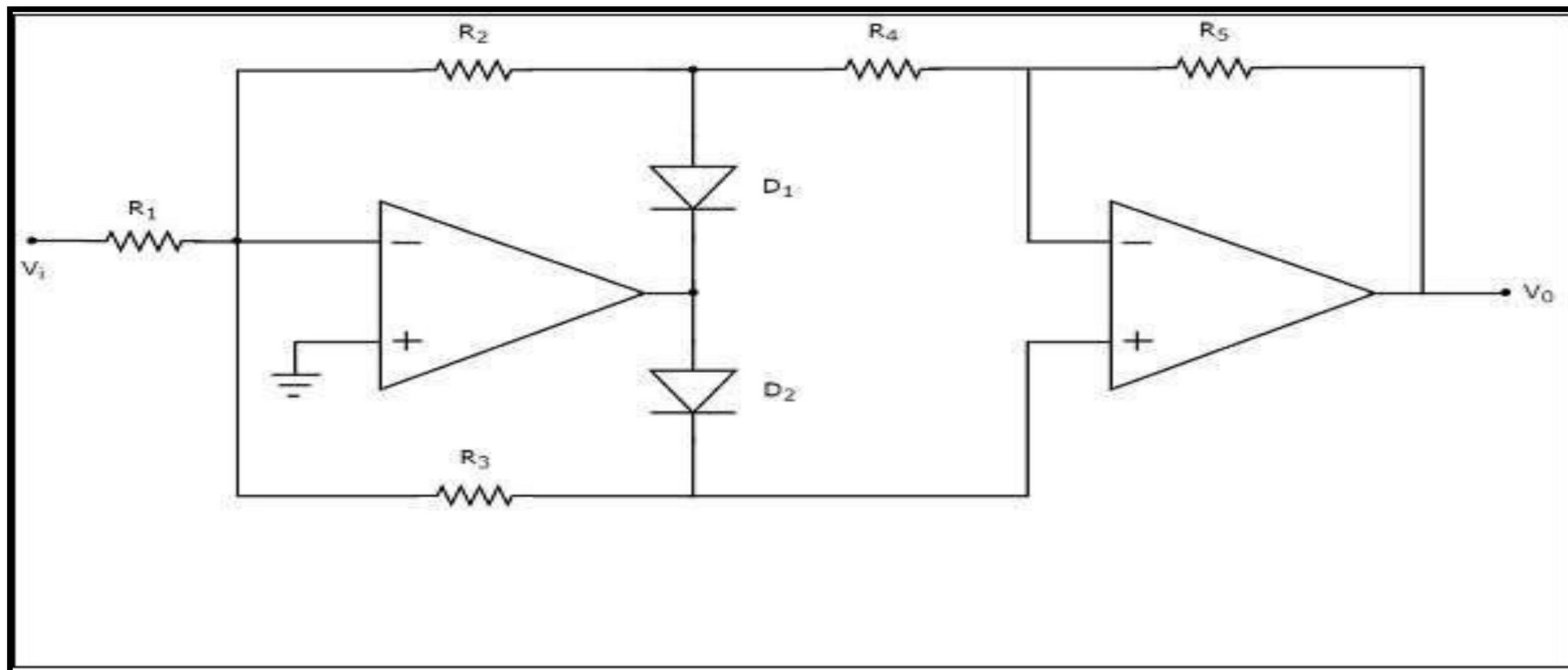
# Full wave Rectifier



- ❑ A **full wave rectifier** produces positive half cycles at the output for both half cycles of the input.
- ❑ The **circuit diagram** of a full wave rectifier is





# Digital to Analog conversion



- It consists of two op-amps, two diodes,  $D_1$  &  $D_2$  and five resistors,  $R_1$  to  $R_5$
- For the **positive half cycle** of a sinusoidal input, the output of the first op-amp will be negative.
- Hence, diodes  $D_1$  and  $D_2$  will be forward biased and reverse biased respectively
- Then, the output voltage of the first op-amp will be

$$V_{O1} = -(R_2/R_1)V_i$$



# Output



- Observe that the output of the first op-amp is connected to a resistor  $R_4$ , which is connected to the inverting terminal of the second op-amp.
- The voltage present at the non-inverting terminal of second op-amp is 0 V. So, the second op-amp with resistors,  $R_4$  and  $R_4$  acts as an **inverting amplifier**.

$$V_0 = -(R_5/R_4)V_{01}$$

**Substituting** the value of  $V_{01}$  in the above equation,

we get

$$\Rightarrow V_0 = -(R_5/R_4)\{- (R_2/R_1)V_i\}$$

$$\Rightarrow V_0 = (R_2R_5/R_1R_4)V_i$$



# Full Wave Rectifier



- Therefore, the output of a full wave rectifier will be a positive half cycle for the **positive half cycle** of a sinusoidal input.
- In this case, the gain of the output is  $R_2R_5R_1R_4$
- If we consider  $R_1=R_2=R_4=R_5=R$ , then the gain of the output will be one
- For the **negative half cycle** of a sinusoidal input, the output of the first op-amp will be positive.
- Hence, diodes  $D_1$  and  $D_2$  will be reverse biased and forward biased respectively.



# Full Wave Rectifier



- The output voltage of the first op-amp will be

$$V_{01} = -(R_3/R_1)V_i$$

- The output of the first op-amp is directly connected to the non-inverting terminal of the second op-amp

- $R_4$  and  $R_5$  acts as a non-inverting amplifier

- The output voltage of the second op-amp will be

$$V_0 = (1 + R_5/R_4)V_{01}$$

Substituting the value of  $V_{01}$  in the above equation,

$$\Rightarrow V_0 = (1 + R_5/R_4)\{- (R_3/R_1)V_i\}$$

$$\Rightarrow V_0 = - (R_3/R_1)(1 + R_5/R_4)V_i$$





# Full Wave Rectifier



- The output of a full wave rectifier will be a **positive half cycle** for the negative half cycle of sinusoidal input also
- The magnitude of the gain of the output is  
$$(R_3 R_1)(1 + R_5 R_4)$$
- If we consider  $R_1 = 2R_3 = R_4 = R_5 = R$  then the gain of the output will be **one**.





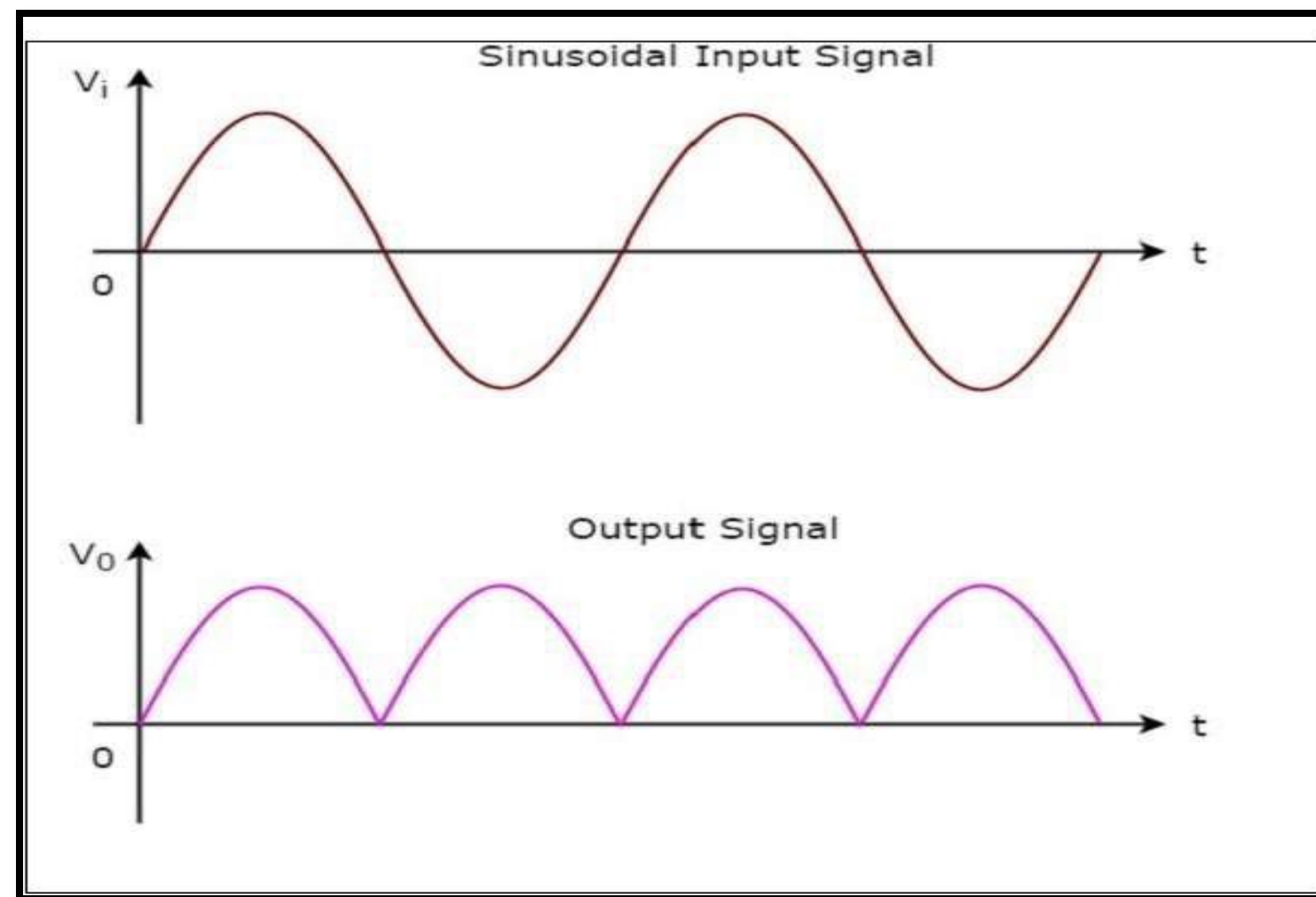
# Full Wave Rectifier



The **input** and **output waveforms** of a full wave rectifier







**THANK YOU**