



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**  
**An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **19ECB202 – LINEAR AND DIGITAL CIRCUITS**

II YEAR/ III SEMESTER  
1

**UNIT 2 – COMPARATORS AND SPECIAL FUNCTION IC's**

**TOPIC 2 – Timer IC 555**



# GUESS?????







# 555 IC TIMER?



- ❖ The 555 Timer is one of the most popular and versatile integrated circuits ever produced!
- ❖ “Signetics” Corporation first introduced this device as the SE/NE 555 in early 1970
- ❖ It is a combination of digital and analog circuits
- ❖ It is known as the “**Time Machine**” as it performs a wide variety of timing tasks.
- ❖ The **555 Timer IC** got its name from the three  $5K\Omega$  resistors that are used in its voltage divider network
- ❖ This **IC** is useful for generating accurate time delays and oscillations



# IC 555 PIN DIAGRAM

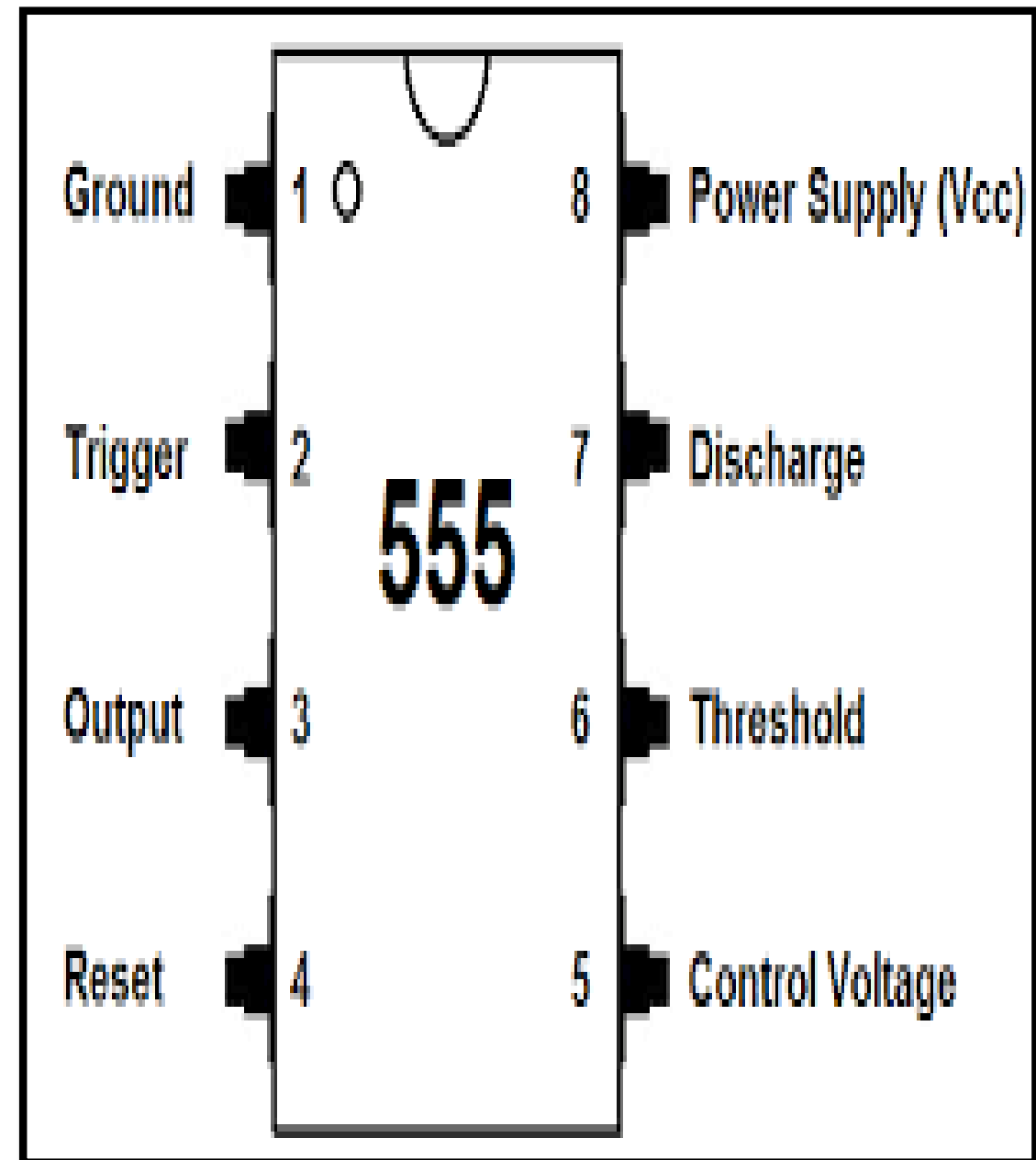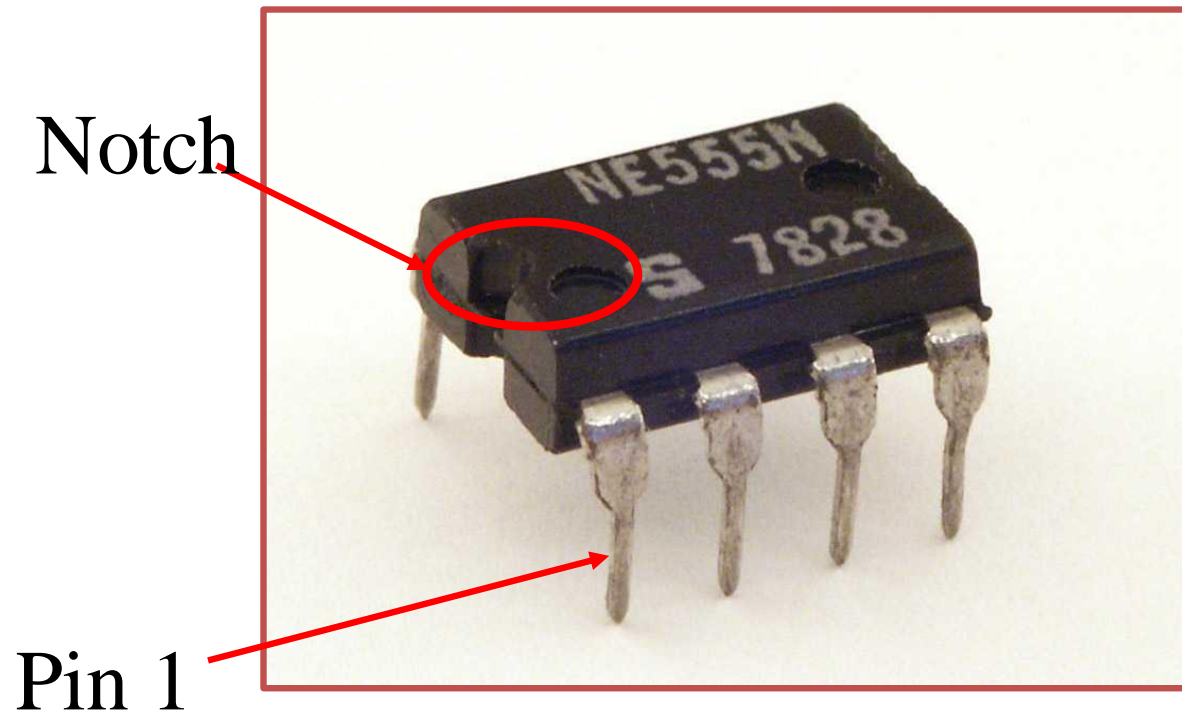



# PIN DETAILS




Pin	Name	Purpose
1	GND	Ground, low level (0 V)
2	TRIG	OUT rises, and interval starts, when this input falls below $1/3 V_{CC}$ .
3	OUT	This output is driven to approximately 1.7V below $+V_{CC}$ or GND.
4	RESET	A timing interval may be reset by driving this input to GND, but the timing does not begin again until RESET rises above approximately 0.7 volts. Overrides TRIG which overrides THR.
5	CTRL	"Control" access to the internal voltage divider (by default, $2/3 V_{CC}$ ).
6	THR	The interval ends when the voltage at THR is greater than at CTRL.
7	DIS	Open collector output; may discharge a capacitor between intervals. In phase with output.
8	$V+$ , $V_{CC}$	Positive supply voltage is usually between 3 and 15 V.




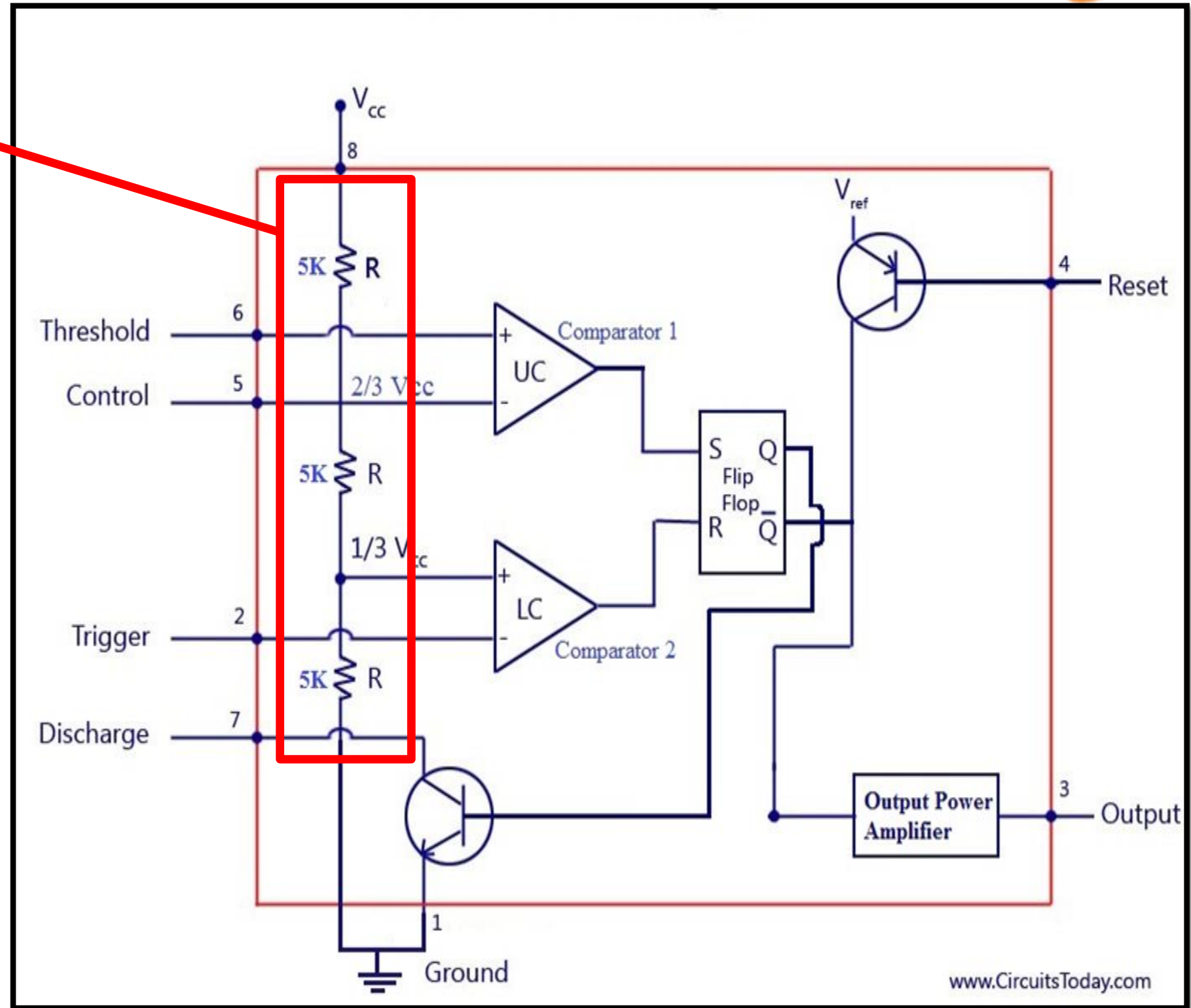
# BLOCK DIAGRAM

The three  $5K\Omega$  resistors that are used in its voltage divider network so it called IC 555 timer.





# WORKING PRINCIPLE



- The voltage divider has three equal 5K resistors. It divides the input voltage ( $V_{cc}$ ) into three equal parts.
- The two comparators are op-amps that compare the voltages at their inputs and saturate depending upon which is greater.
  - The Threshold Comparator saturates when the voltage at the Threshold pin (pin 6) is greater than  $(2/3)V_{cc}$ .
  - The Trigger Comparator saturates when the voltage at the Trigger pin (pin 2) is less than  $(1/3)V_{cc}$



# WORKING PRINCIPLE




- The flip-flop is a bi-stable device. It generates two values, a “high” value equal to  $V_{CC}$  and a “low” value equal to  $0V$ 
  - When the Threshold comparator saturates, the flip flop is Reset (R) and it outputs a low signal at pin 3
  - When the Trigger comparator saturates, the flip flop is Set (S) and it outputs a high signal at pin 3
- The transistor is being used as a switch, it connects pin 7 (discharge) to ground when it is closed.
  - When Q is low, Q bar is high. This closes the transistor switch and attaches pin 7 to ground.
  - When Q is high, Q bar is low. This open the switch and pin 7 is no longer grounded





# COMPARATOR OUTPUT

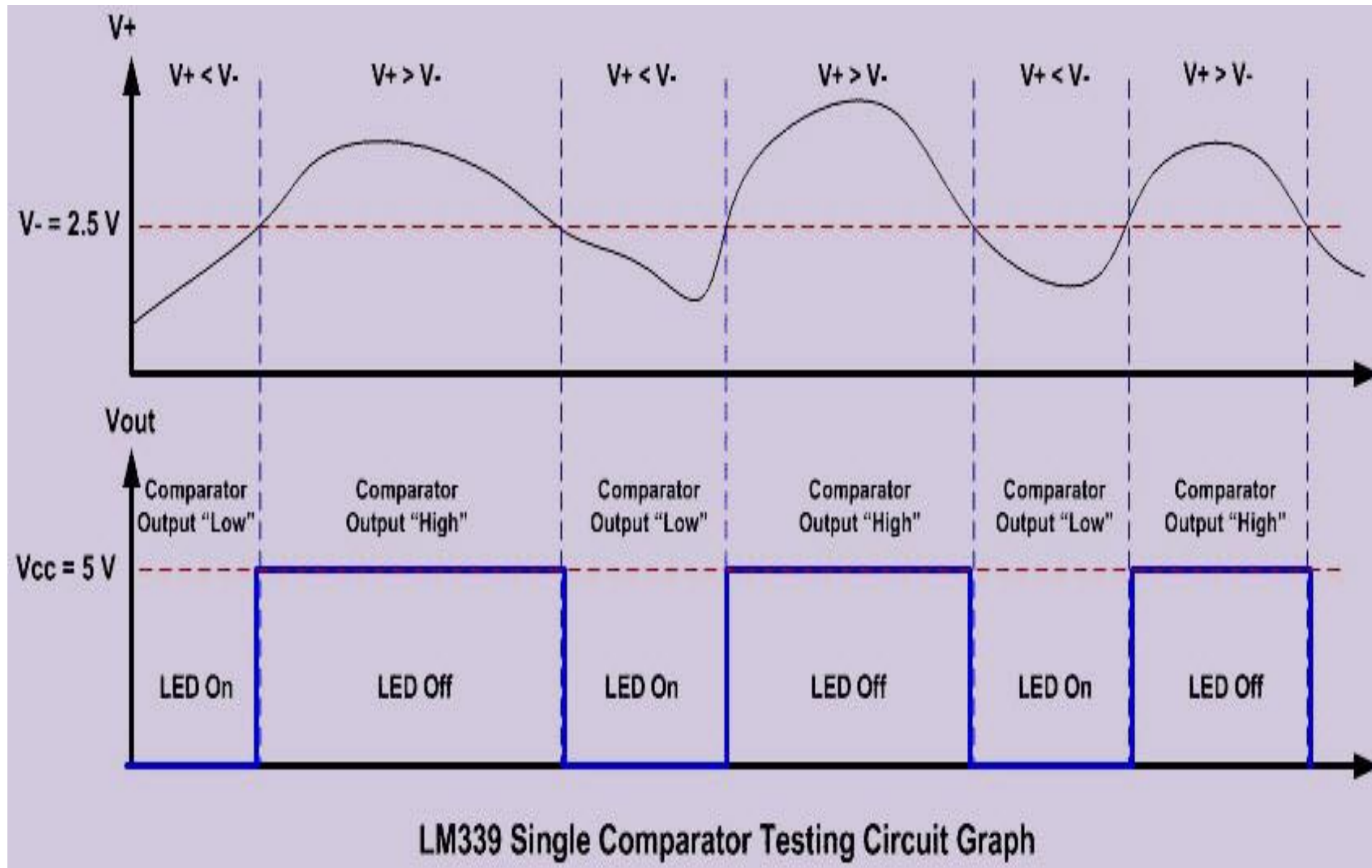



# USES OF 555 TIMER



➤ To switch on or off an output after a certain time delay

i.e. Games timer, Childs mobile, Exercise timer

➤ To continually switch on and off an output


i.e. Warning lights, Bicycle indicators

➤ As a pulse generator


i.e. To provide a series of clock pulses for a counter



# Activity

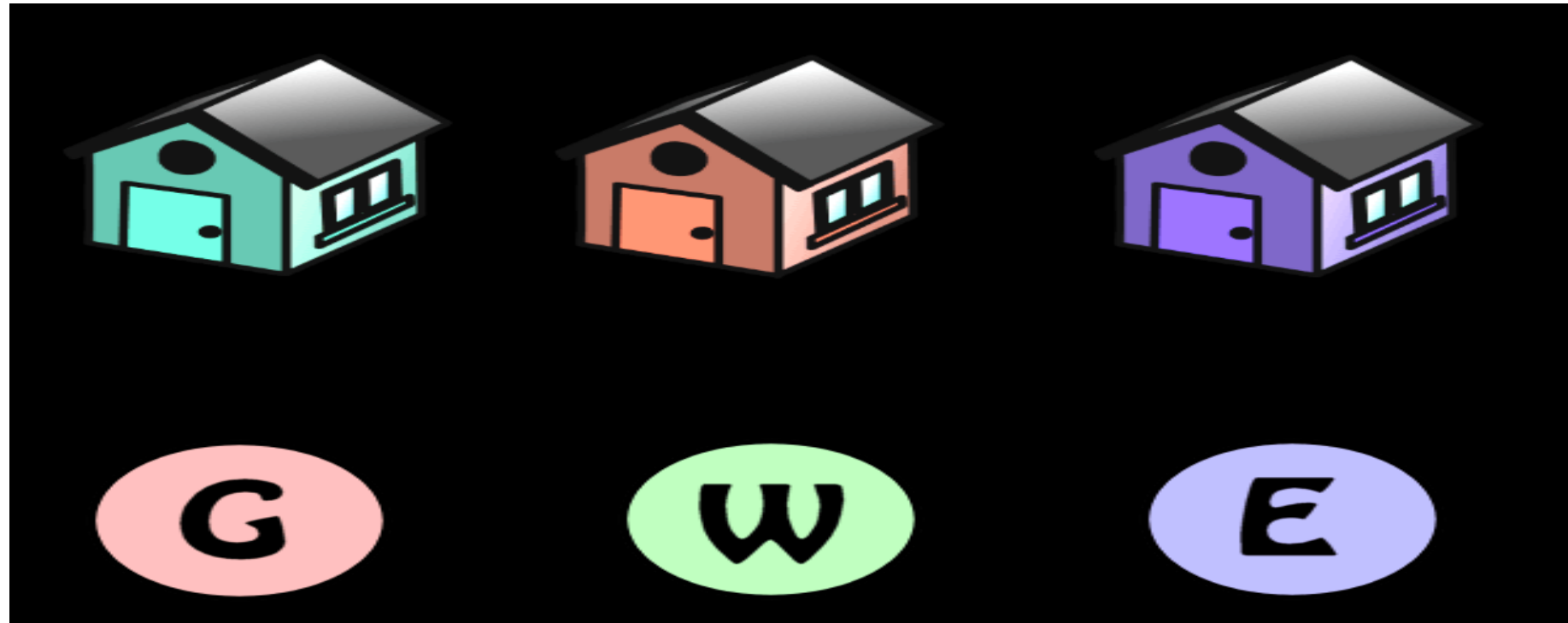


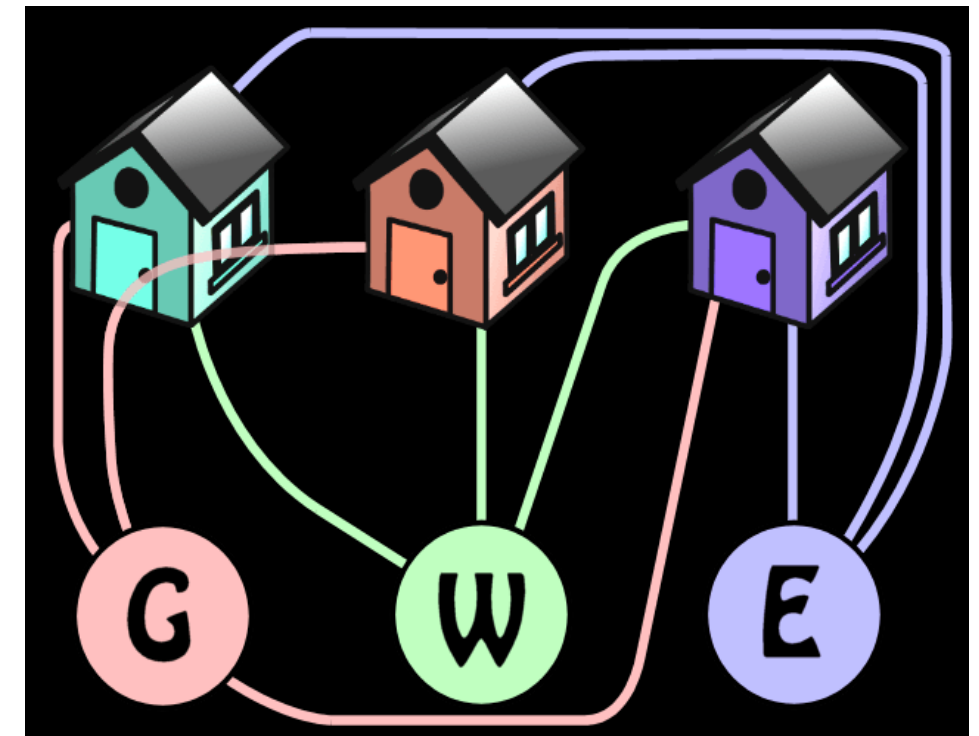- A man has built three houses. Nearby there are gas water and electric plants.
- The man wishes to connect all three houses to each of the gas, water and electricity supplies.
- Unfortunately the pipes and cables must not cross each other.
- How would you connect each of the 3 houses to each of the gas, water and electricity supplies?





# 555 TIMER AS MONOSTABLE MULTIVIBRATOR

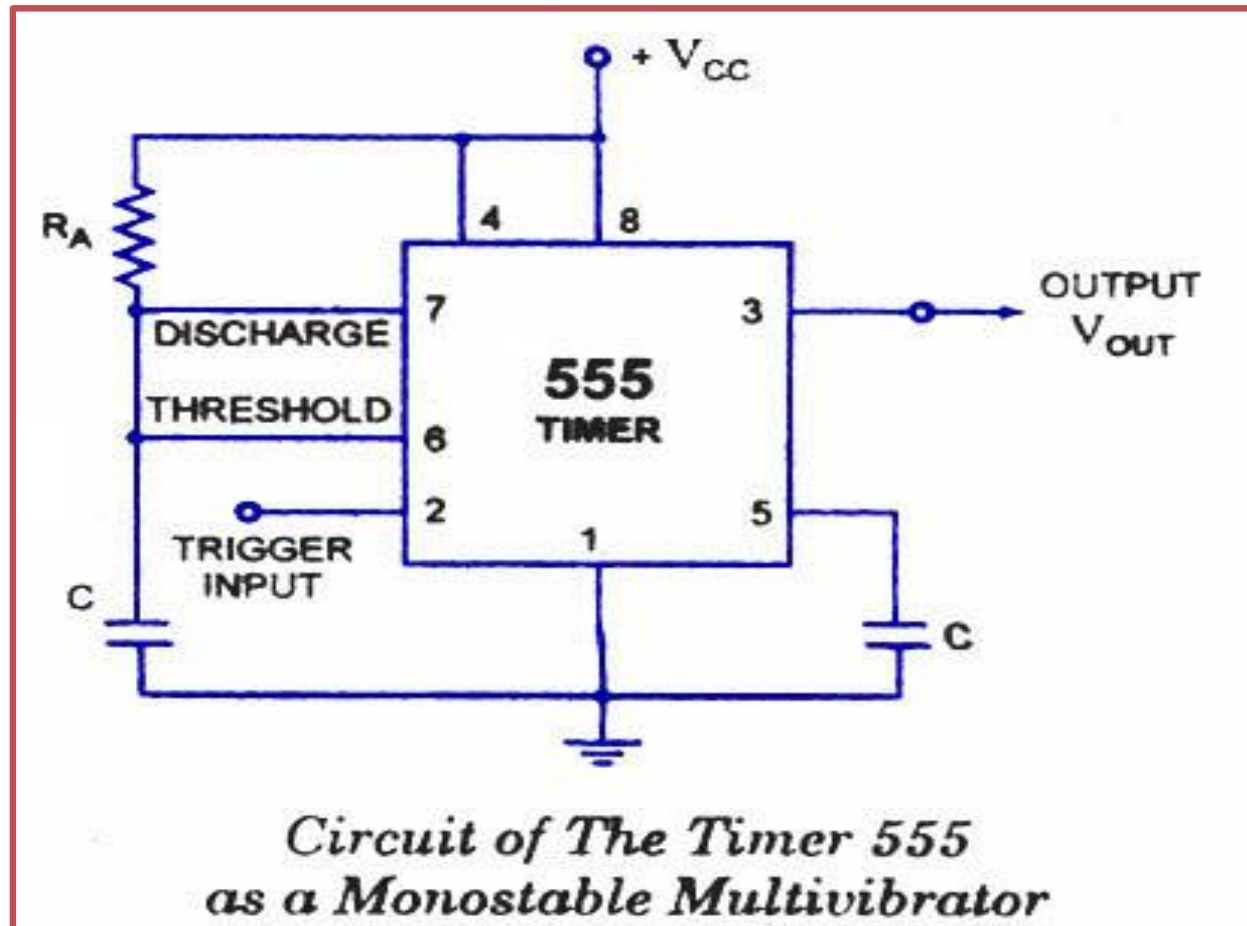

## Description:

- In the standby state, FF holds transistor Q1 ON, thus clamping the external timing capacitor C to ground. The output remains at ground potential. i.e. Low

- As the trigger passes through  $V_{CC}/3$ , the FF is set, i.e.  $Q\text{ bar}=0$ , then the transistor Q1 OFF and the short circuit across the timing capacitor C is released. As Q bar is low, output goes HIGH





# MONOSTABLE MULTIVIBRATOR

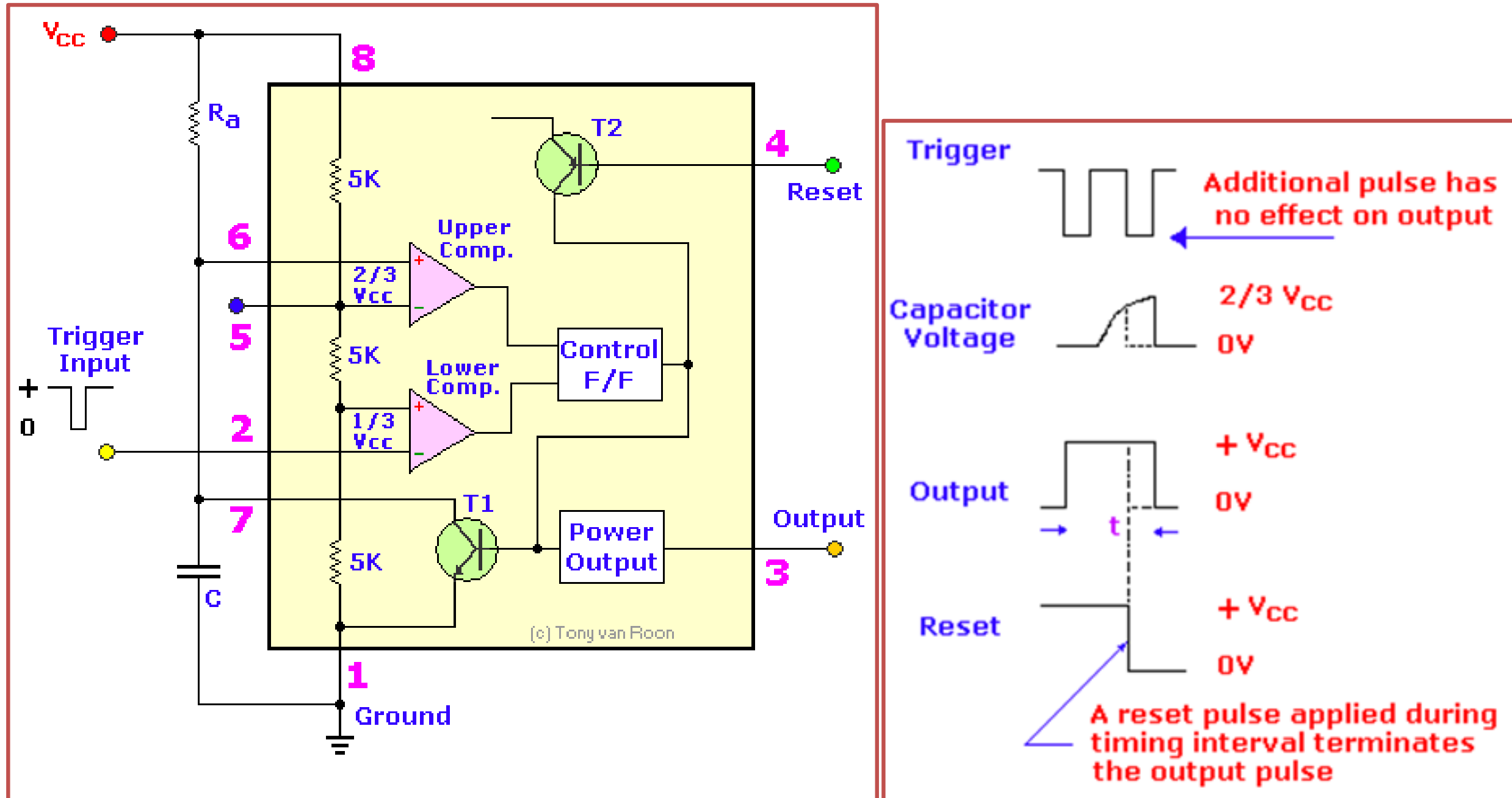


Fig (a): Timer in Monostable Operation with Functional Diagram  
Fig (b): Output wave Form of Monostable





# OUTPUT



- Voltage across it rises exponentially through R towards  $V_{CC}$  with a time constant RC.
- After Time Period T, the capacitor voltage is just greater than  $2V_{CC}/3$  and the upper comparator resets the FF, i.e. R=1, S=0. This makes  $\bar{Q} = 1$ , C rapidly to ground potential.
- The voltage across the capacitor as given by,

$$v_C = V_{CC} (1 - e^{-t/RC})$$

$$t = T, v_C = \frac{2}{3} V_{CC}$$

$$\frac{2}{3} V_{CC} = V_{CC} (1 - e^{-T/RC})$$

$$T = RC \ln\left(\frac{1}{3}\right) \Rightarrow T = 1.1RC \text{ sec}$$

- If -ve going reset pulse terminal (pin 4) is applied, then transistor Q2- $\rightarrow$  OFF, Q1- $\rightarrow$  ON & the external timing capacitor C is immediately discharged.



# ASTABLE MULTIVIBRATOR

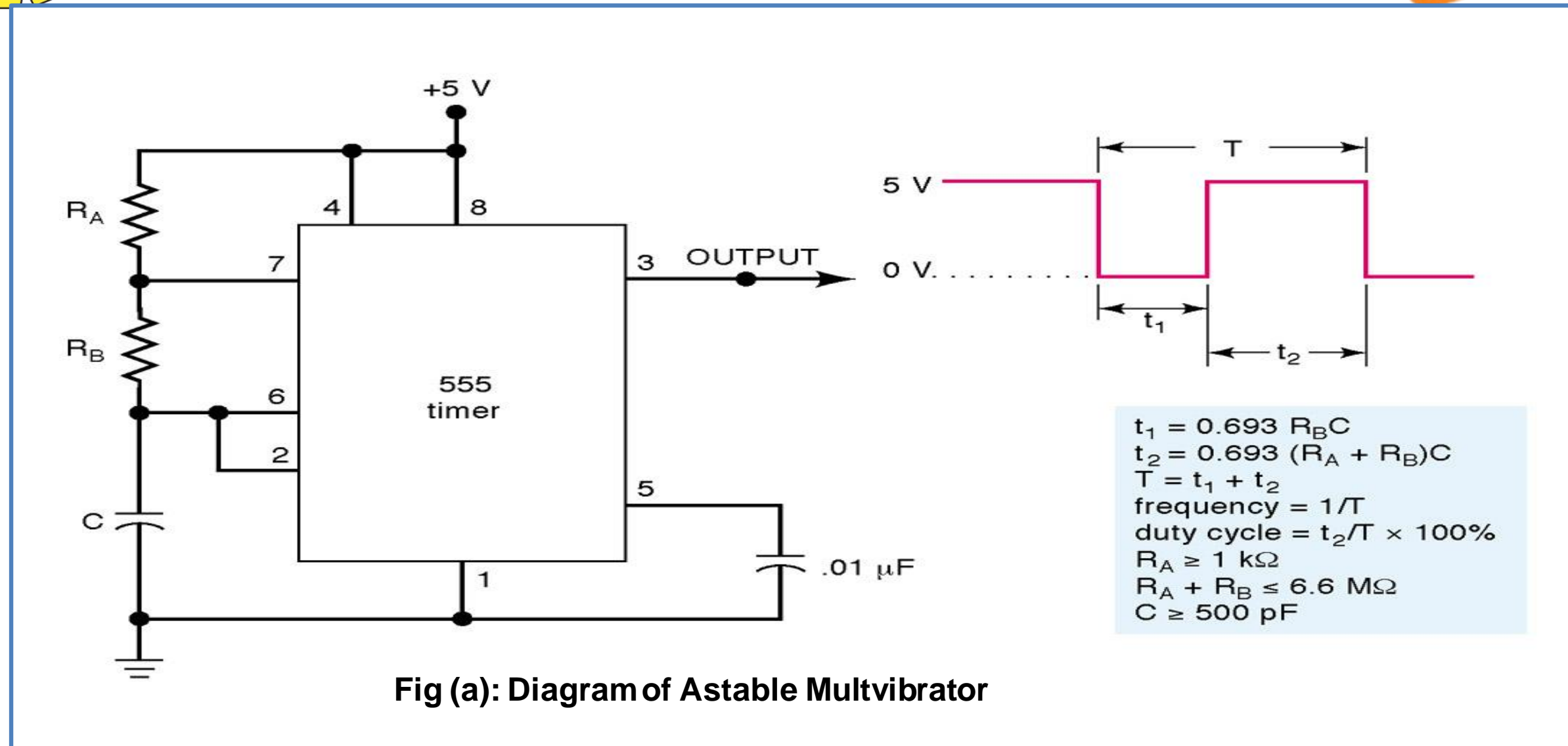



Fig (a): Diagram of Astable Multivibrator

1 – Ground  
2 – Trigger  
3 – Output  
4 – Reset

5 – FM Input (Tie to ground via bypass cap)  
6 – Threshold  
7 – Discharge  
8 – Voltage Supply (+5 to +15 V)



# ASTABLE MULTIVIBRATOR

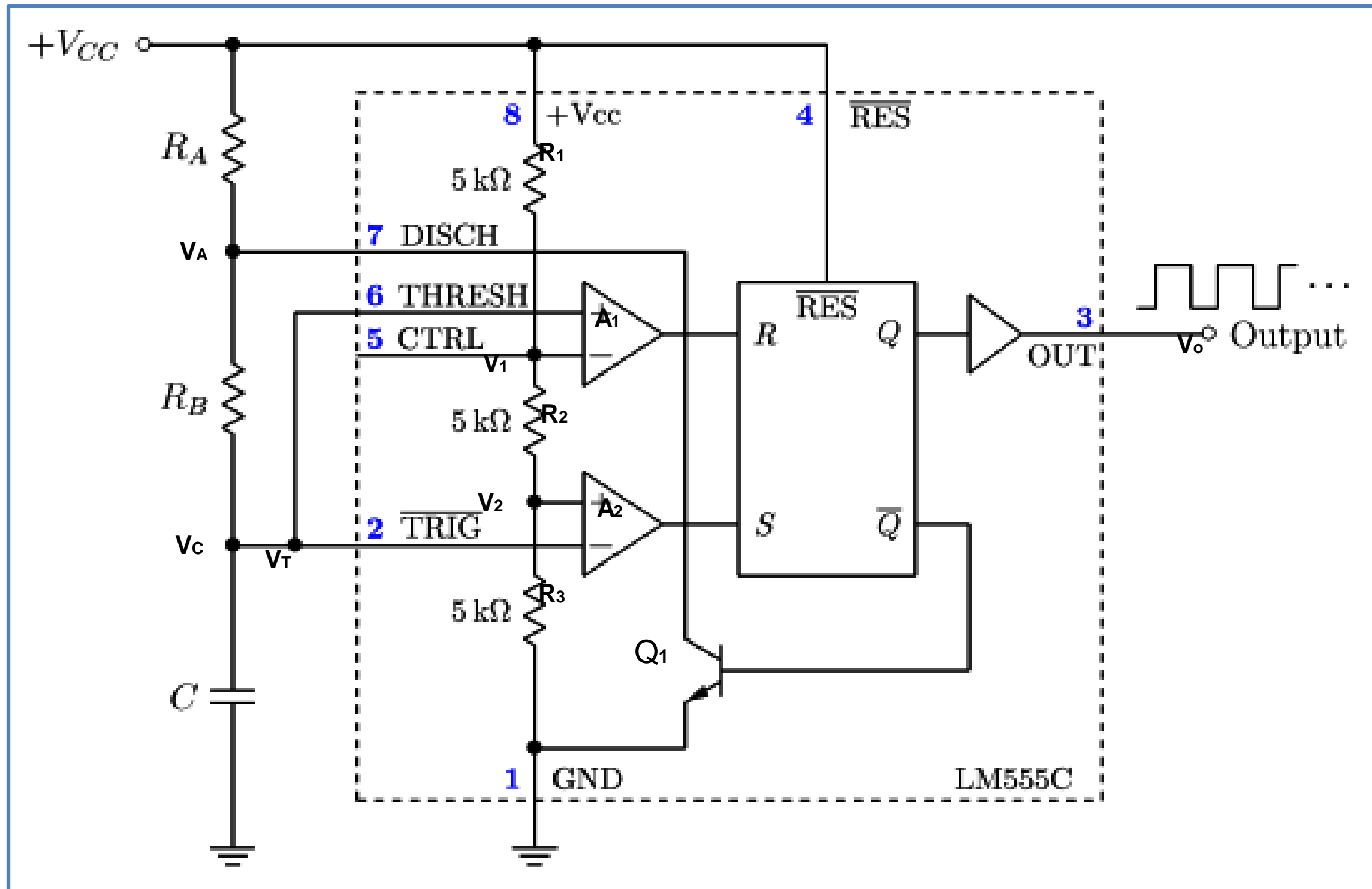



# ASTABLE MULTIVIBRATOR



- Connect external timing capacitor between trigger point (pin 2) and Ground.
- Split external timing resistor R into RA & RB, and connect their junction to discharge terminal (pin 7).
- Remove trigger input, monostable is converted to Astable multivibrator.
- This circuit has no stable state. The circuit changes its state alternately. Hence the operation is also called free running oscillator



# ASTABLE MULTIVIBRATOR



- Resistive voltage divider (equal resistors) sets threshold voltages for comparators

$$V_1 = V_{TH} = 2/3 V_{CC} \quad V_2 = V_{TL} = 1/3 V_{CC}$$

- Two Voltage Comparators

- For A1, if  $V_+ > V_{TH}$  then  $R = \text{HIGH}$

- For A2, if  $V_- < V_{TL}$  then  $S = \text{HIGH}$

- RS FF

- If  $S = \text{HIGH}$ , then FF is **SET**,  $\bar{Q} = \text{LOW}$ , Q1 OFF,  
 $V_{OUT} = \text{HIGH}$

- If  $R = \text{HIGH}$ , then FF is **RESET**,  $\bar{Q} = \text{HIGH}$ , Q1 ON,  
 $V_{OUT} = \text{LOW}$

- Transistor  $Q_1$  is used as a Switch






# ASTABLE MULTIVIBRATOR




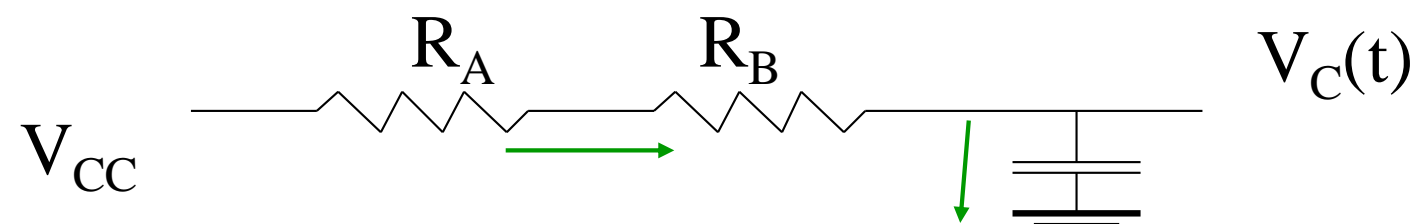- 1) Assume initially that the capacitor is discharged.
  - a) For A1,  $V_+ = V_C = 0V$  and for A2,  $V_- = V_C = 0V$ , so R=LOW, S=HIGH, **= LOW, Q1 OFF,  $V_{OUT} = V_{CC}$**
  - b) Now as the capacitor charges through  $R_A$  &  $R_B$ , eventually  $V_C > V_{TL}$  so R=LOW & S=LOW.  
FF does not change state.
- 2) Once  $V_C \geq V_{TH}$ 
  - a) R=HIGH, S=LOW, **= HIGH, Q1 ON,  $V_{OUT} = 0$**
  - b) Capacitor is now discharging through  $R_B$  and  $Q_1$  to ground.
  - c) Meanwhile at FF, R=LOW & S=LOW since  $V_C < V_{TH}$ .
- 3) Once  $V_C < V_{TL}$ 
  - a) R=LOW, S=HIGH, **= LOW, Q1 OFF,  $V_{OUT} = V_{CC}$**
  - b) Capacitor is now charging through  $R_A$  &  $R_B$  again.




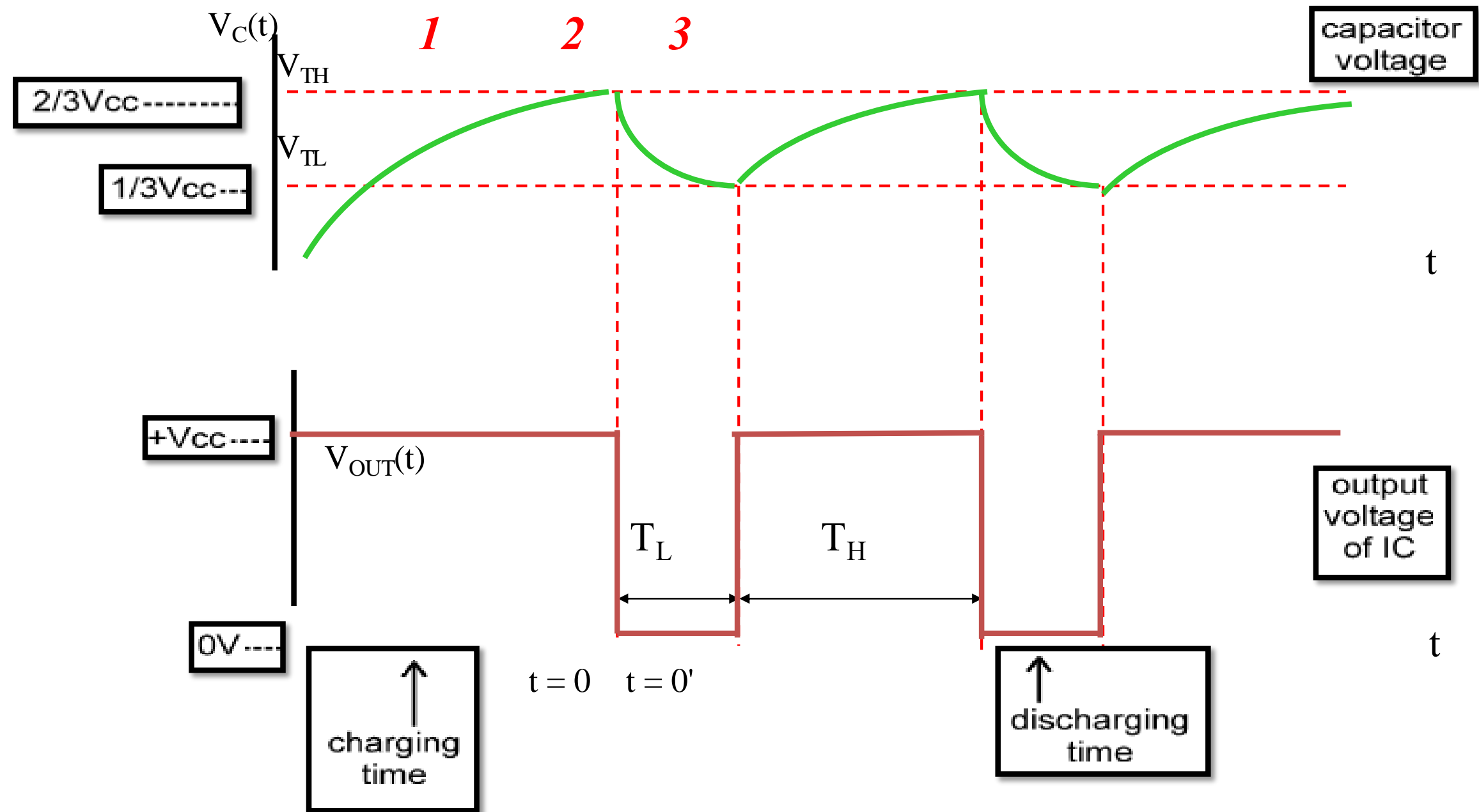
# TIMING DIAGRAM OF A 555 ASTABLE MULTIVIBRATOR





# BEHAVIOR OF THE ASTABLE MULTIVIBRATOR



- w The astable multivibrator is simply an oscillator. The astable multivibrator generates a continuous stream of rectangular off-on pulses that switch between two voltage levels.
- w The frequency of the pulses and their duty cycle are dependent upon the RC network values.
- w The capacitor C charges through the series resistors  $R_A$  and  $R_B$  with a time constant  $(R_A + R_B)C$ .
- w The capacitor discharges through  $R_B$  with a time constant of  $R_B C$



# USES OF THE ASTABLE MULTIVIBRATOR



- Flashing LED's
- Pulse Width Modulation
- Pulse Position Modulation
- Periodic Timers
- Uses include LEDs, pulse generation, logic clocks, security alarms and so on.



# Assessment



1. A555 timer in monostable application mode can be used for
  - a) Pulse position modulation
  - b) Frequency shift keying
  - c) Speed control and measurement
  - d) Digital phase detector

Answer: c

2. How to obtain symmetrical waveform in Astable multivibrator?
  - a) Use clocked RS flip-flop
  - b) Use clocked JK flip-flop
  - c) Use clocked D-flip-flop
  - d) Use clocked T-flip-flop

Answer: b







**THANK YOU**