



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35

An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

19ECB231 – DIGITAL ELECTRONICS

II YEAR/ III SEMESTER

UNIT 2 – COMBINATIONAL CIRCUITS

TOPIC - CARRY LOOK AHEAD ADDER



Ripple Carry Adder

- n-bit Ripple Carry Adder
 - Composed of n 1-bit Full Adders
 - Carries ripple from LSB stage to MSB stage
 - Delay $\sim (n) \cdot (\text{delay of single FA stage})$
 - Area required is linear in n
- 4-bit Ripple Carry Adder
 - Composed of 4 1-bit Full Adders



The Ripple Carry Adder is slow!

Why?

How can the speed of the adder be increased?




- Carry Lookahead Adder

Generate signal: g_i

Propagate signal: p_i



Carry Look-Ahead Adder Design

 



Expressions

4-Bit Carry Look-Ahead Adder

$$G_i = A_i B_i$$

$$P_i = A_i + B_i$$

$$\Rightarrow C_i = G_i + P_i C_{i-1}$$

$$C_0 = G_0 + P_0 C_{-1} = G_0$$

$$C_1 = G_1 + P_1 C_0 = G_1 + P_1 G_0$$

$$C_2 = G_2 + P_2 C_1 = G_2 + P_2 (G_1 + P_1 C_0) = G_2 + P_2 G_1 + P_2 P_1 C_0$$


$$C_3 = G_3 + P_3 C_2 = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 C_0))$$


$$= G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 C_0)$$


$$= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 C_0$$



Logic circuit

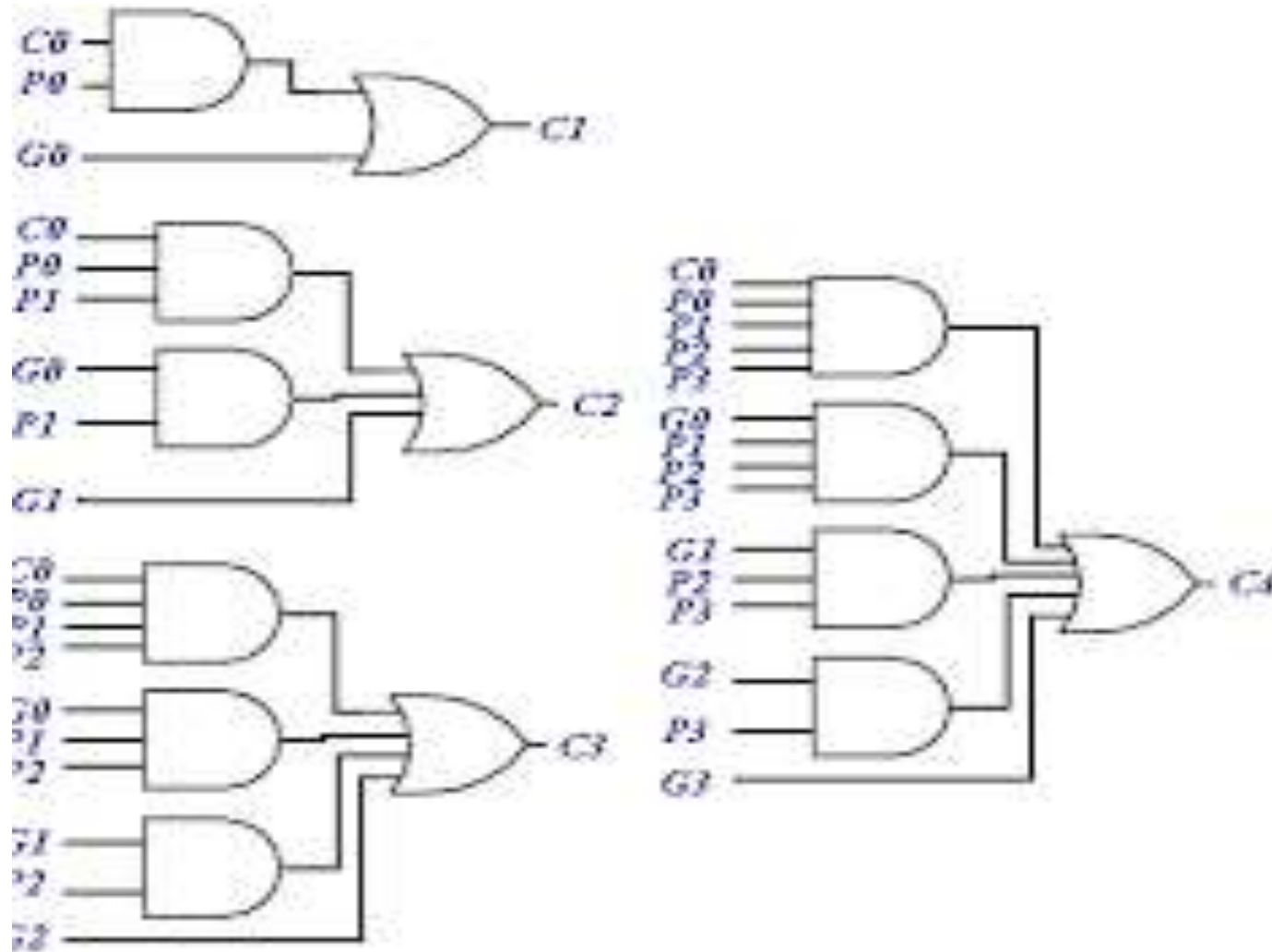

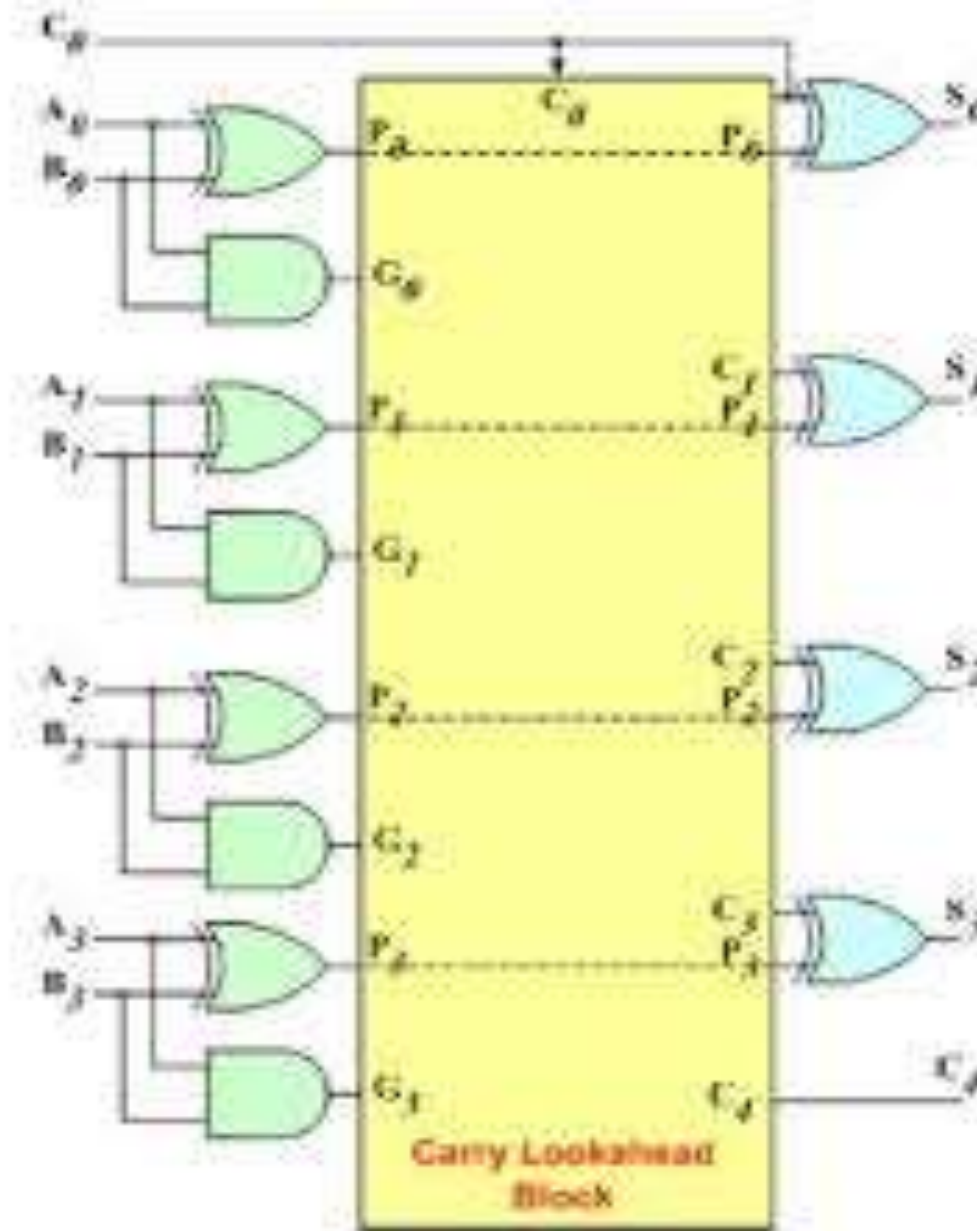

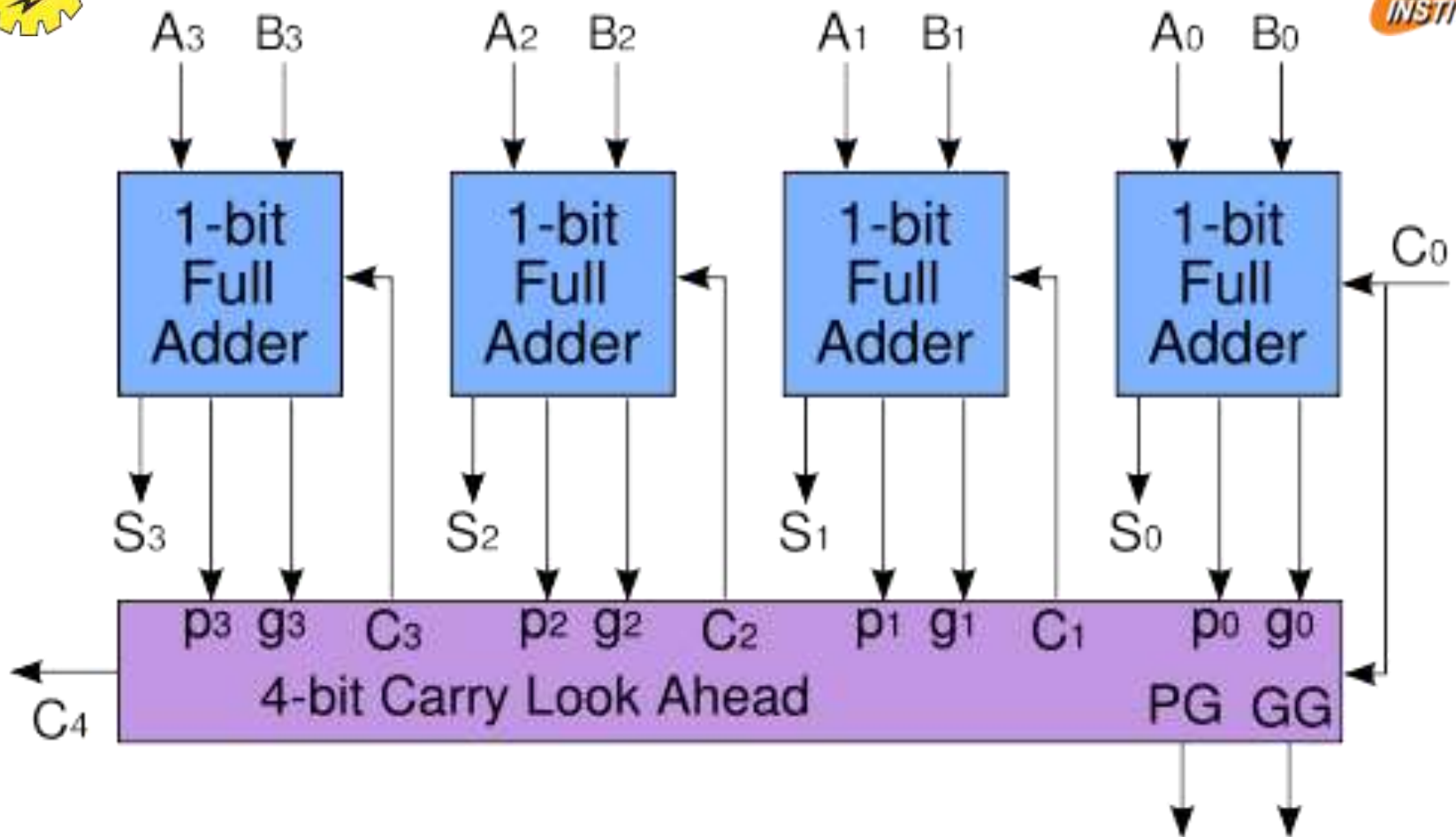



Assessment Questions



1. Assume that the XOR gate has a propagation delay of 10ns and that the AND or OR gates have a propagation delay of 5ns. What is the total propagation delay time in the four bit adder.

2. Derive the two level Boolean expression for the output carry C_4 for a look ahead carry generator.



THANK YOU