

SNS COLLEGE OF TECHNOLOGY

Coimbatore-35 An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF COMPUTER SCIENCE ENGINEERING

19ECB231 – DIGITAL ELECTRONICS

II YEAR/ III SEMESTER

UNIT 2 – COMBINATIONAL CIRCUITS

TOPIC – DEMULTIPLEXER








What is De Multiplexer?

> De-Multiplexer is a combinational circuit that performs the reverse operation of Multiplexer. It has single input, 'n' selection lines and maximum of 2n outputs.

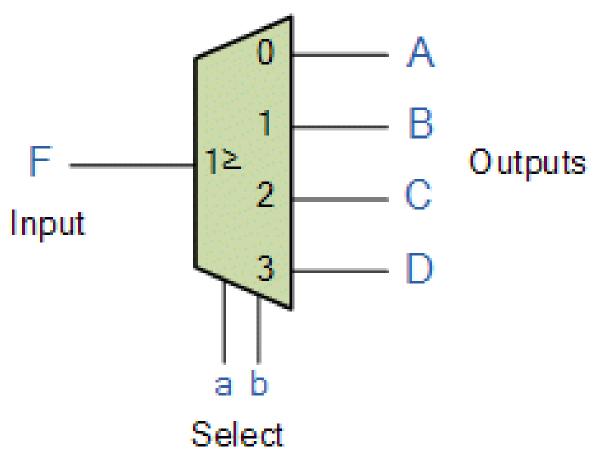 \succ One of these data inputs will be connected to the output based on the values of selection lines.










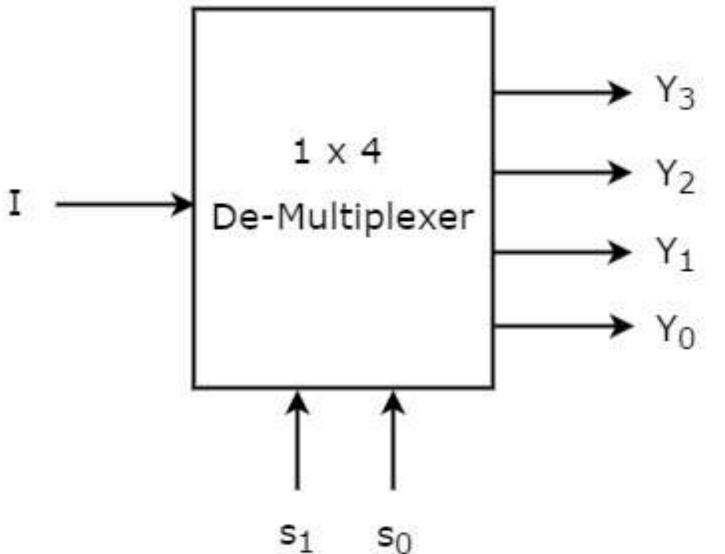 \geq 1x4 De-Multiplexer has one input I, two selection lines, s1 & s0 and four outputs Y3, Y2, Y1 &Y0.










The single input 'I' will be connected to one of the four outputs, Y3 to Y0 based on the values of selection lines s1 & s0. The Truth table of 1x4 De-Multiplexer is shown below.

| Selectio | on Inputs | Outputs | | | | | |
|----------------|----------------|-----------------------|----------------|----------------|----------------|--|--|
| S ₁ | S ₀ | Y ₃ | Y ₂ | Y ₁ | Y ₀ | | |
| 0 | 0 | 0 | 0 | 0 | I | | |
| 0 | 1 | 0 | 0 | I | 0 | | |
| 1 | 0 | 0 | I | 0 | 0 | | |
| 1 | 1 | I | 0 | 0 | 0 | | |





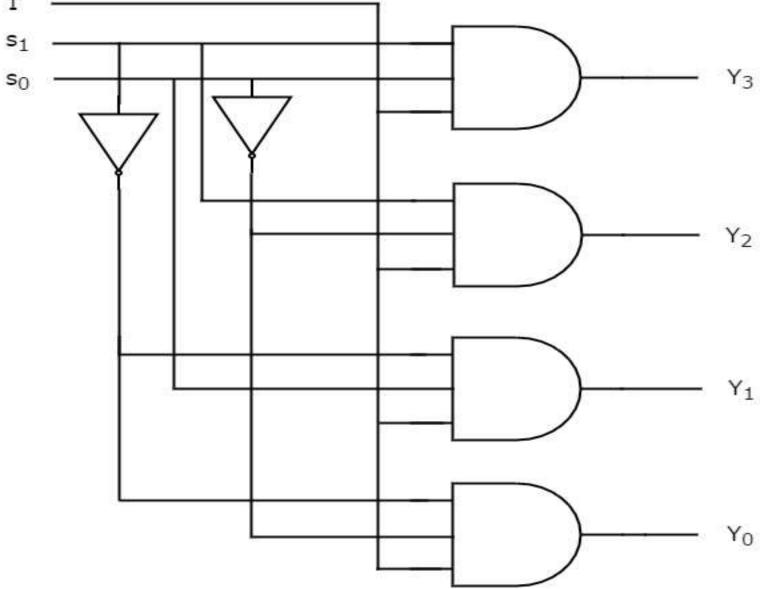We can implement these Boolean functions using Inverters & 3-input AND gates. The circuit diagram of 1x4 De-Multiplexer is shown in the following figure.








1x8 De-Multiplexer

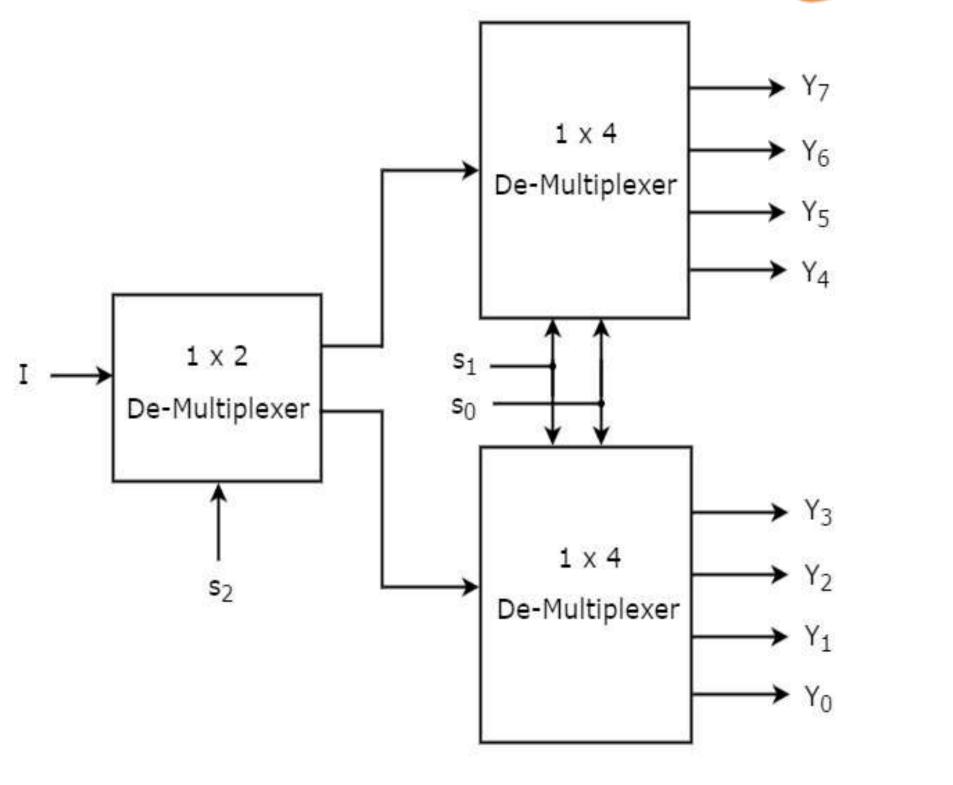1x8 De-Multiplexer has single input, three selection lines and eight outputs.







1x8 De-Multiplexer has one input I, three selection lines s2, s1 & s0 and outputs Y7 to Y0. The Truth table of 1x8 De-Multiplexer is shown below.


| Selection Inputs | | | Outputs | | | | | | | |
|------------------|----------------|----------------|-----------------------|------------------|----------------|----------------|-----------------------|----------------|----------------|----------------|
| s ₂ | s ₁ | s ₀ | Y ₇ | \mathbf{Y}_{6} | \mathbf{Y}_5 | Y ₄ | Y ₃ | Y ₂ | Y ₁ | Y ₀ |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | I |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | I | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | I | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | I | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | I | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | I | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | I | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | I | 0 | 0 | 0 | 0 | 0 | 0 | 0 |






Applications

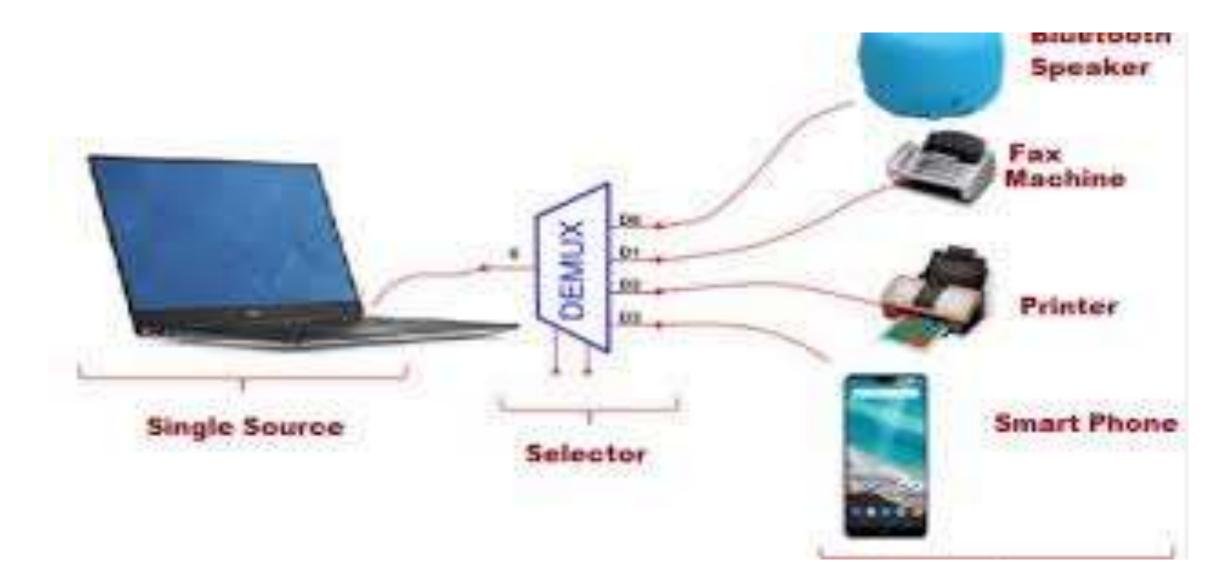Demultiplexer is used to connect a single source to multiple destinations. The main application area of demultiplexer is communication system where multiplexer are used.







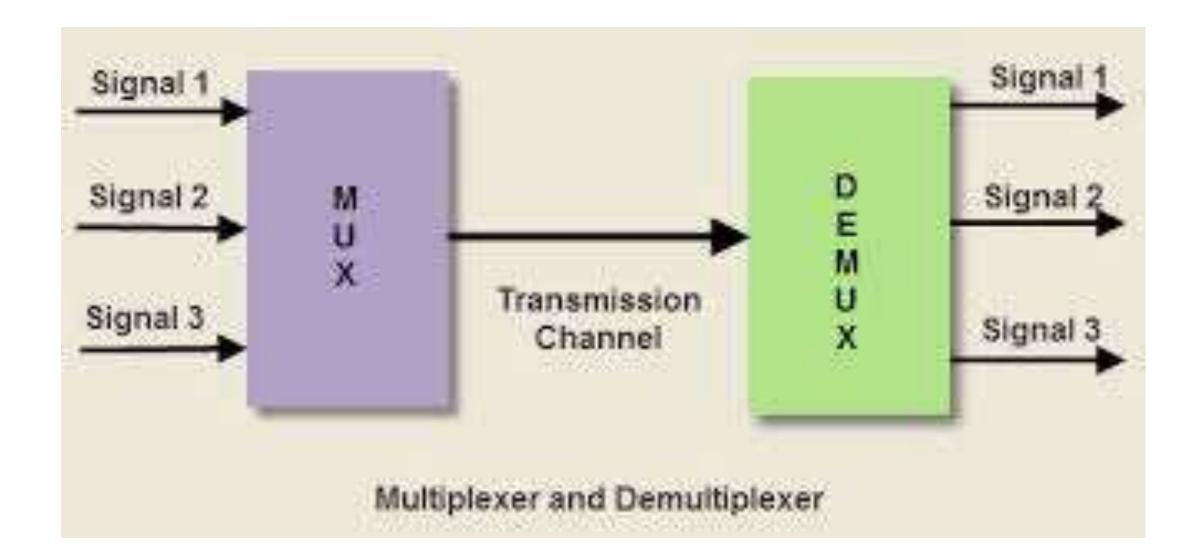





THANK YOU

10/26/2023



