



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**  
**An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **19ECB204 – LINEAR AND DIGITAL CIRCUITS**


II YEAR/ III SEMESTER  
1

**UNIT 2 – COMPARATORS AND SPECIAL FUNCTION IC's**

**TOPIC 6 – D/A converter – Types**



# WHAT IS A DAC?

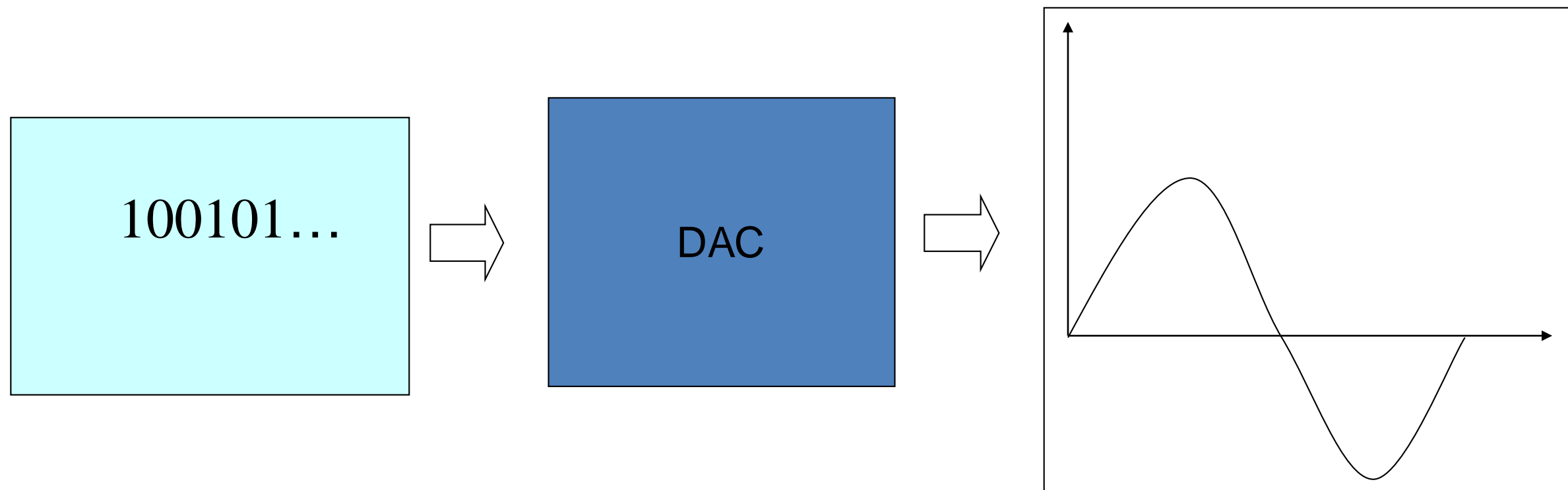

- A Digital-to-analog converter(DAC) takes a digital code as its input and produce an analog voltage or current as its output
- This analog output is proportional to the digital input



# TYPES OF DACS




- Many types of DACs available.
- Usually switches, resistors, and op-amps used to implement conversion
- Two Types:
  - Binary Weighted Resistor
  - R-2R Ladder


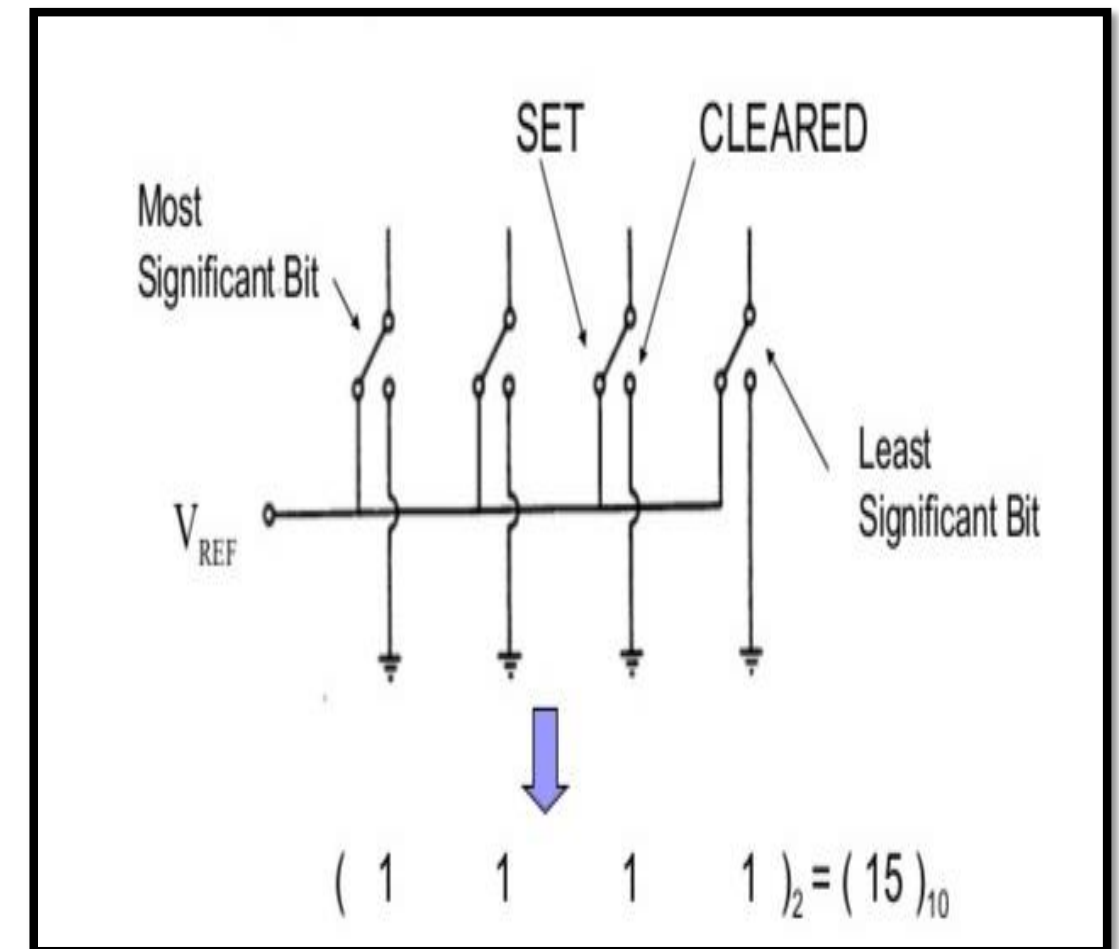
# BINARY WEIGHTED RESISTOR



- Utilizes a summing op-amp circuit
- Weighted resistors are used to distinguish each bit from the most significant to the least significant
- Transistors are used to switch between  $V_{ref}$  and ground (bit high or low)





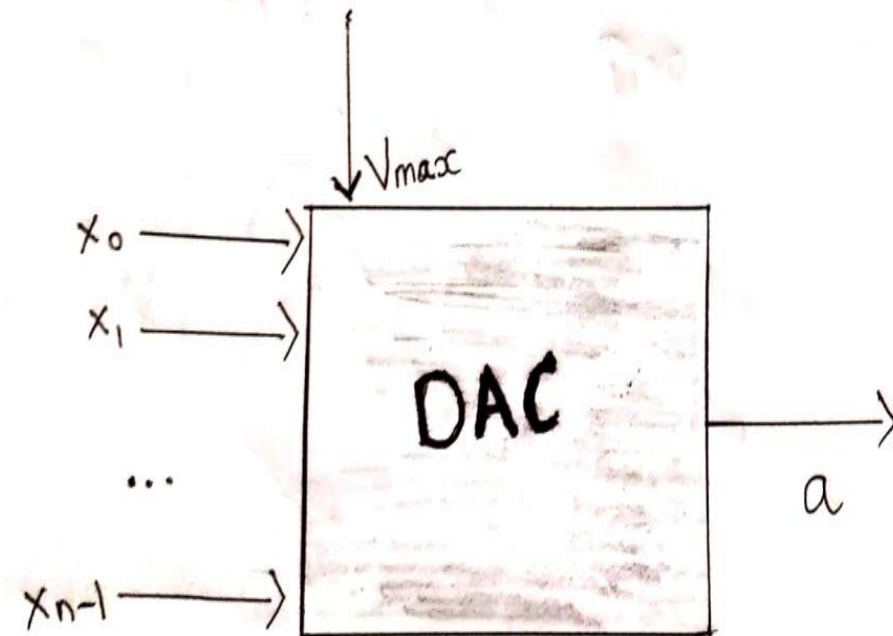
# BINARY WEIGHTED RESISTOR




- Smallest analog increment corresponding to 1 LSB change
- An N-bit resolution can resolve  $2^N$  distinct analog levels
- Common DAC has a 8-16 bit resolution





# BINARY WEIGHTED RESISTOR

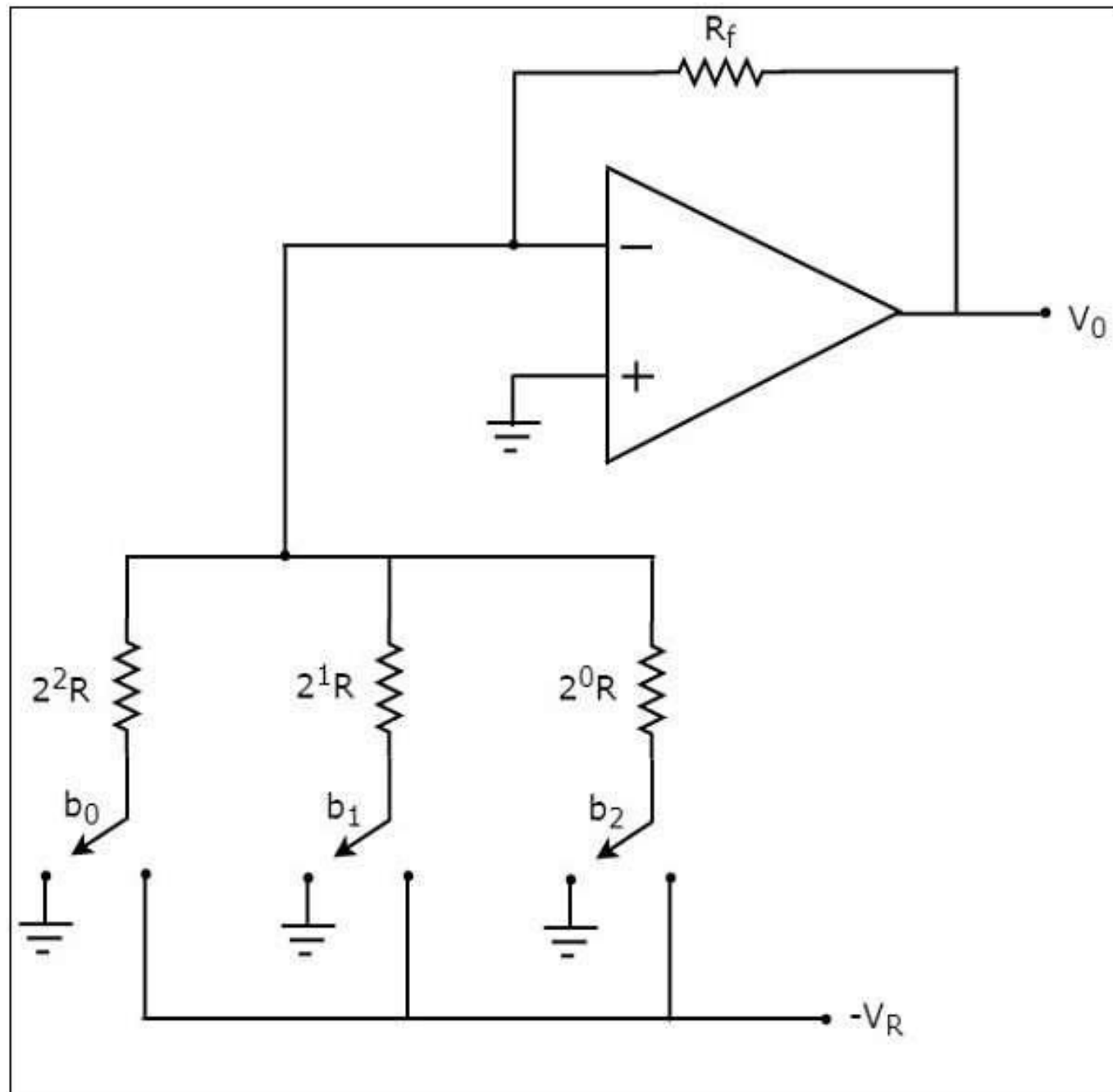

- Assume Ideal Op-amp
- No current into op-amp
- Utilizes an inverting weighted OP-AMP circuit.
- Weighted resistors are used to distinguish each bit from the MSB to the LSB.
- Virtual ground at inverting input
- $V_{out} = -IR_f$





# BINARY WEIGHTED RESISTOR




➤ Voltages  $V_1$  through  $V_n$  are  $V_{ref}$  if corresponding bit is high

➤ Voltages  $V_1$  through  $V_n$  are Ground if corresponding bit is low

➤  $V_1$  is most significant bit

➤  $V_n$  is least significant bit

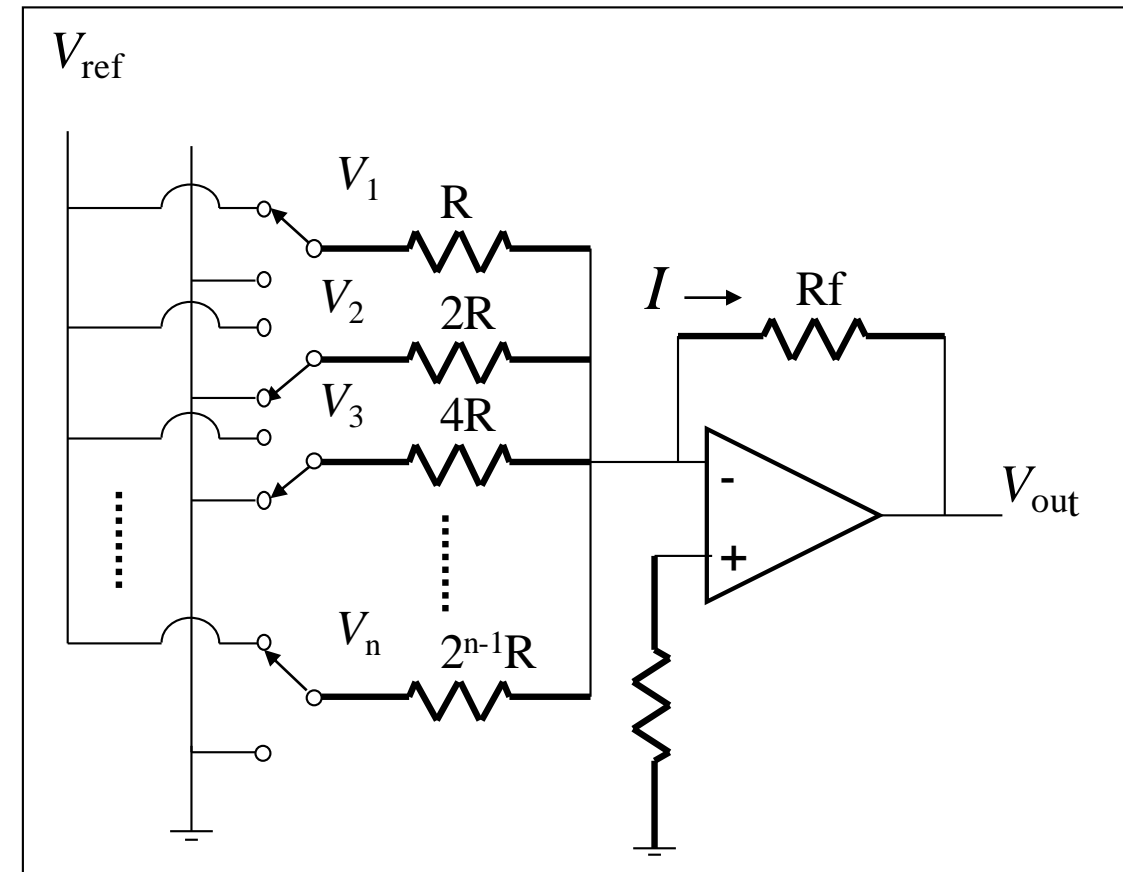

$$V_{out} = -IR_f = -R_f \left( \overset{\text{MSB}}{\frac{V_1}{R}} + \frac{V_2}{2R} + \frac{V_3}{4R} + \dots + \frac{V_n}{2^{n-1}R} \right) \overset{\text{LSB}}$$



# BINARY WEIGHTED RESISTOR



If  $R_f = R/2$

$$V_{\text{out}} = -IR_f = -\left(\frac{V_1}{2} + \frac{V_2}{4} + \frac{V_3}{8} + \dots + \frac{V_n}{2^n}\right)$$

For example, a 4-Bit converter yields

$$V_{\text{out}} = -V_{\text{ref}} \left( b_3 \frac{1}{2} + b_2 \frac{1}{4} + b_1 \frac{1}{8} + b_0 \frac{1}{16} \right)$$

Where  $b_3$  corresponds to Bit-3,  $b_2$  to Bit-2, etc.





# ADVANTAGES



- Advantages
  - Simple Construction/Analysis
  - Fast Conversion



# DISADVANTAGES



- Disadvantages
  - Requires large range of resistors (2000:1 for 12-bit DAC)  
with necessary high precision for low resistors
  - Requires low switch resistances in transistors
  - Can be expensive. Therefore, usually limited to 8-bit resolution.



# Activity



## Odd or Even?

Name: \_\_\_\_\_

Directions: Cut out numbers. Sort them into even or odd. Glue in the correct box.

Odd

Even




© First Grade Brain

7	54	28	53	16	42	105	75
11	38	91	100	89	64	33	86



# R-2R LADDER

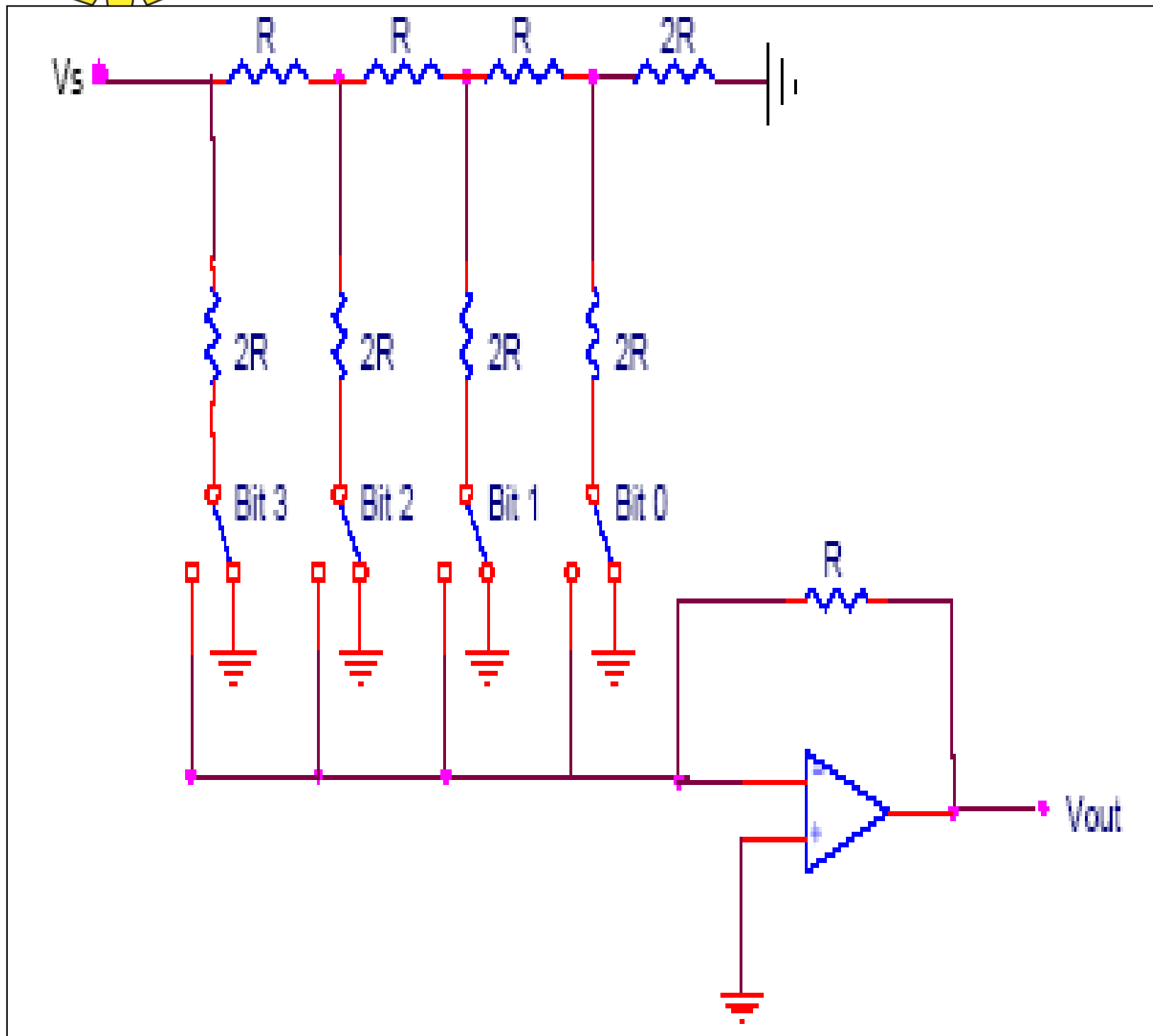


- Each bit corresponds to a switch:
- If the bit is high, the corresponding switch is connected to the inverting input of the op-amp.
- If the bit is low, the corresponding switch is connected to ground.


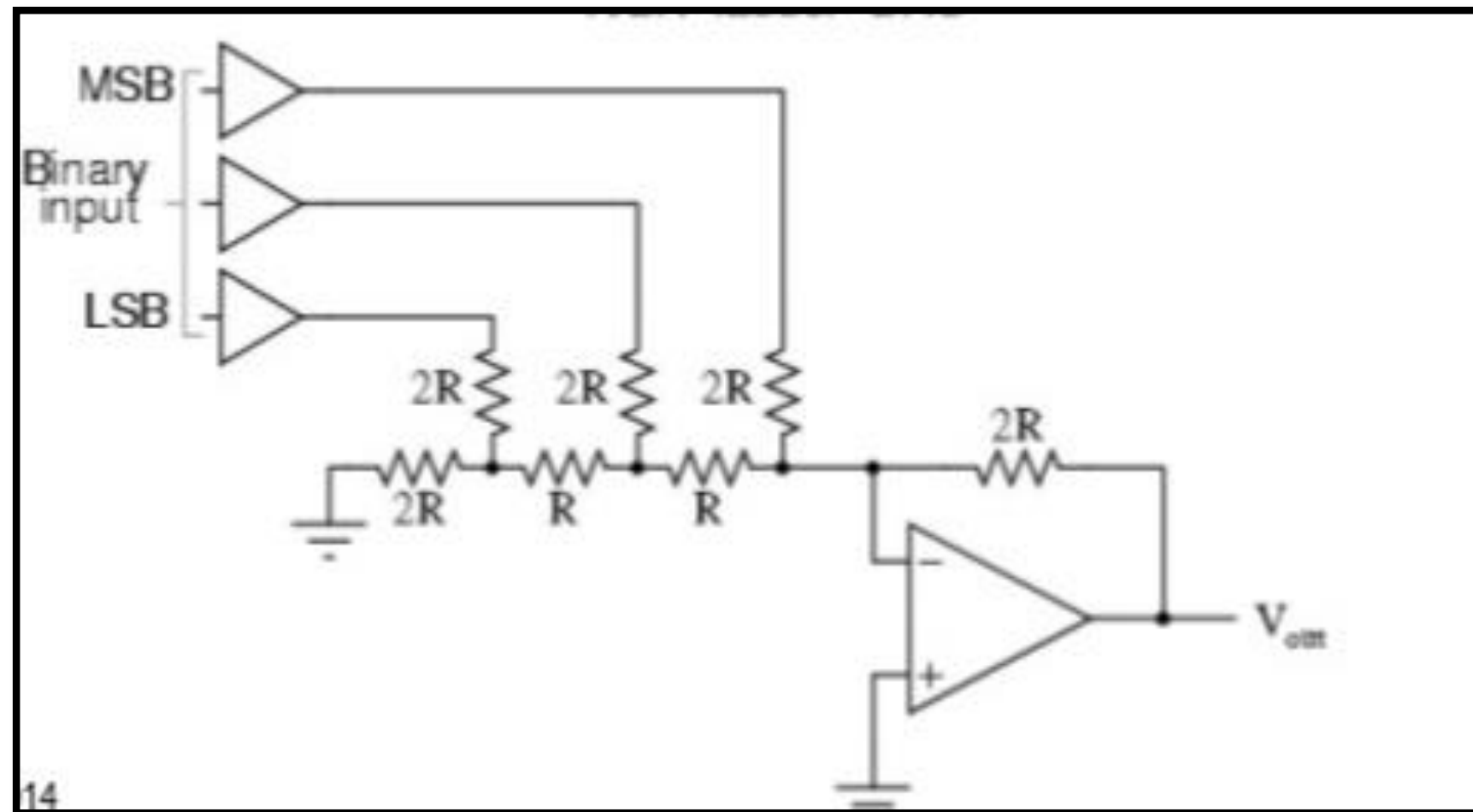
# R-2R LADDER




- Current Dependent on bits position.
- The current is divided by a factor of 2 at each node.







# R-2R LADDER

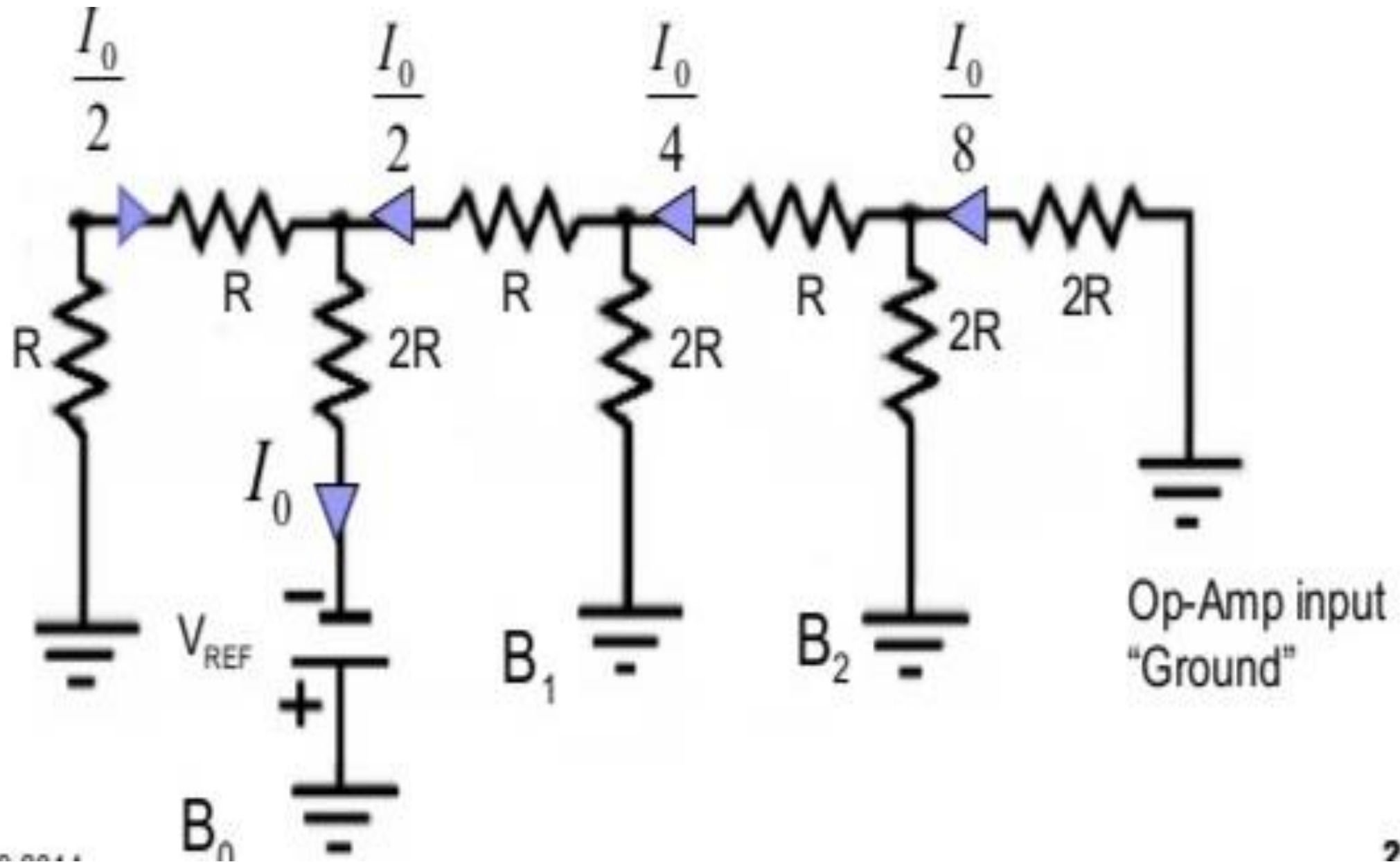



# R-2R LADDER

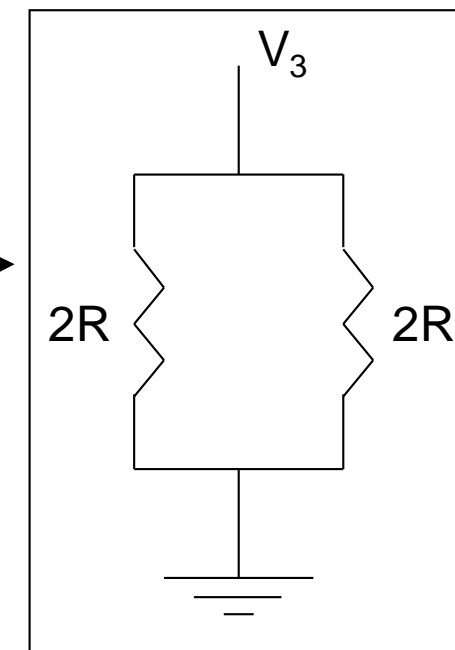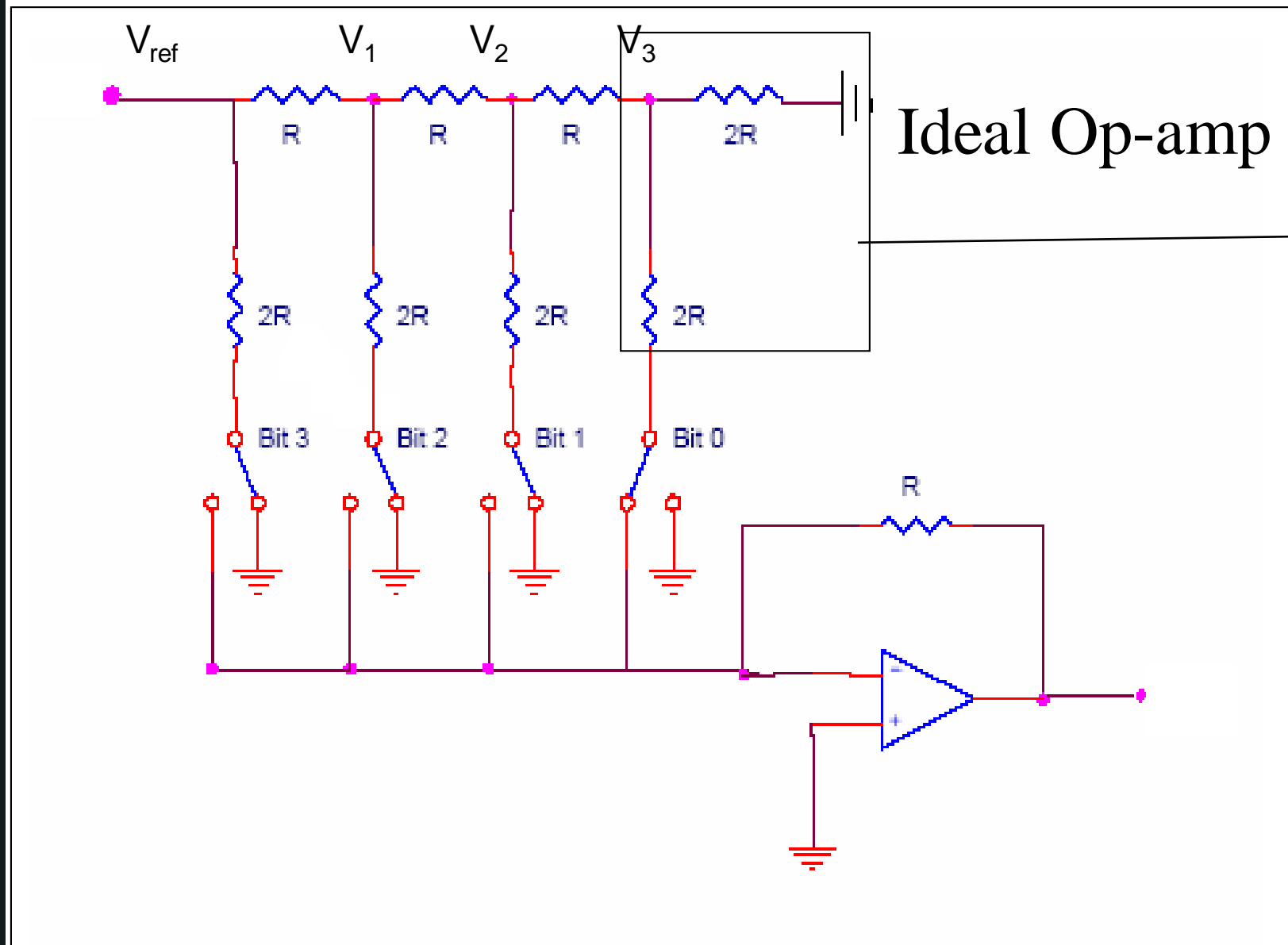


$$R_{eq} = \frac{(2R)(2R)}{(2R + 2R)} = R$$





# R-2R LADDER

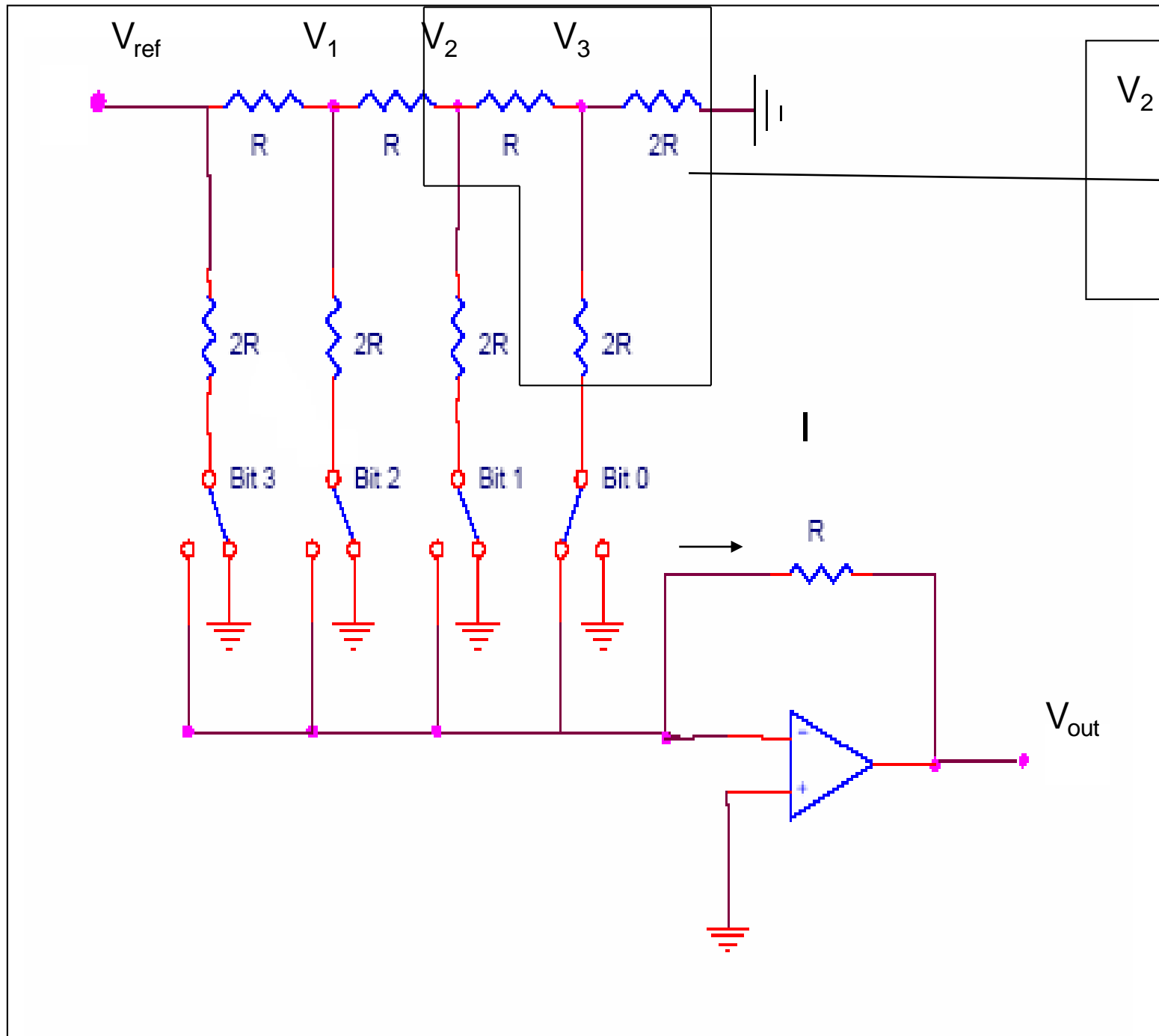

Likewise,

$$V_3 = \left( \frac{R}{R+R} \right) V_2 = \frac{1}{2} V_2$$


$$V_2 = \frac{1}{2} V_1$$

$$V_1 = \frac{1}{2} V_{\text{ref}}$$

$$V_{\text{out}} = -IR$$



# R-2R LADDER

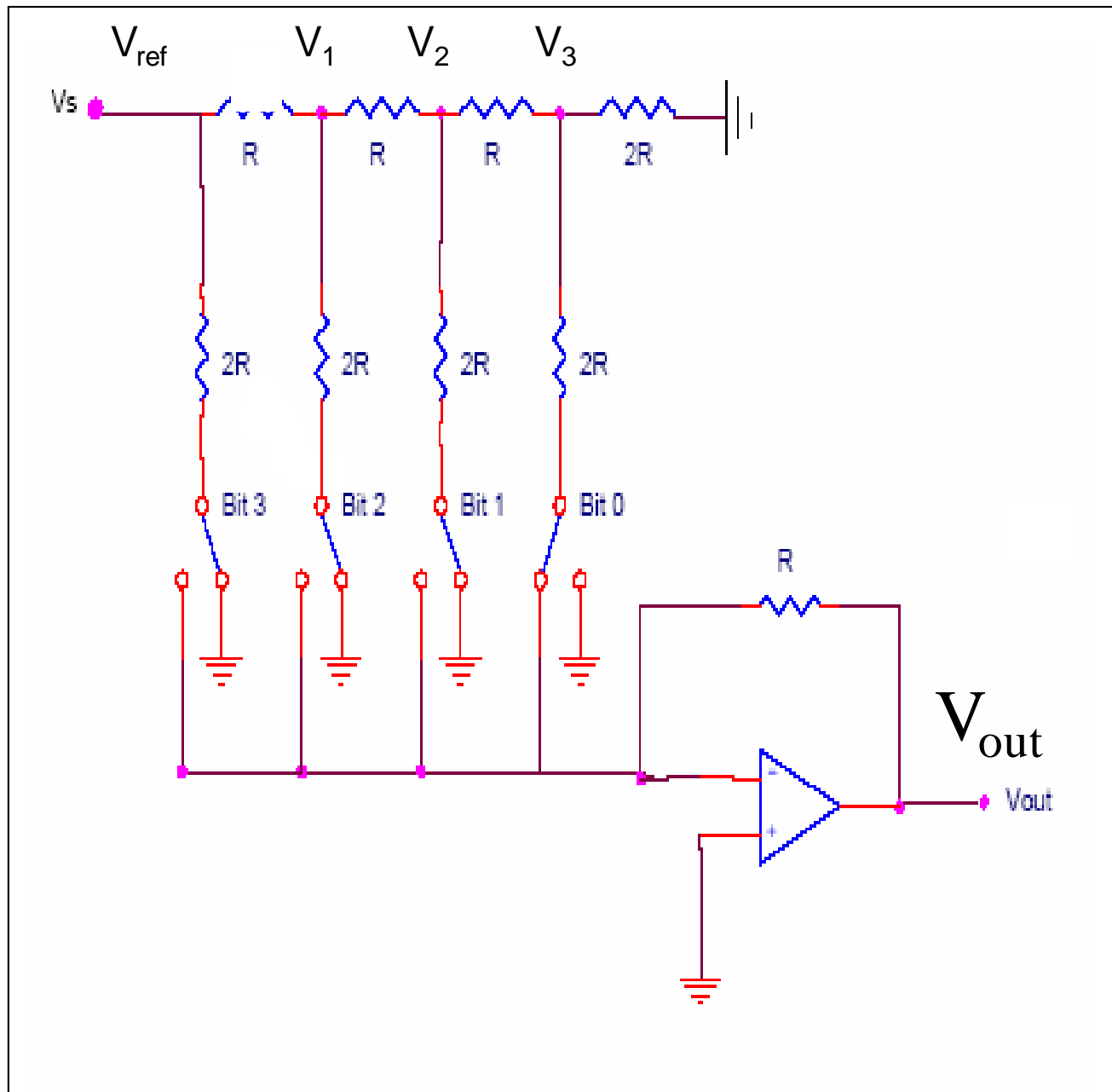

$$V_3 = \frac{1}{8} V_{\text{ref}}, V_2 = \frac{1}{4} V_{\text{ref}}, V_1 = \frac{1}{2} V_{\text{ref}}$$

$$V_{\text{out}} = -R \left( b_3 \frac{V_{\text{ref}}}{2R} + b_2 \frac{V_{\text{ref}}}{4R} + b_1 \frac{V_{\text{ref}}}{8R} + b_0 \frac{V_{\text{ref}}}{16R} \right)$$

Where  $b_3$  corresponds to bit 3,  
 $b_2$  to bit 2, etc.

If bit  $n$  is set,  $b_n=1$

If bit  $n$  is clear,  $b_n=0$



# R-2R LADDER



For a 4-Bit R-2R Ladder

$$V_{\text{out}} = -V_{\text{ref}} \left( b_3 \frac{1}{2} + b_2 \frac{1}{4} + b_1 \frac{1}{8} + b_0 \frac{1}{16} \right)$$

For general n-Bit R-2R Ladder or Binary Weighted Resistor DAC

$$V_{\text{out}} = -V_{\text{ref}} \sum_{i=1}^n b_{n-i} \frac{1}{2^i}$$



# R-2R LADDER




- Advantages
  - Only two resistor values ( $R$  and  $2R$ )
  - Does not require high precision resistors
- Disadvantage
  - Lower conversion speed than binary weighted DAC


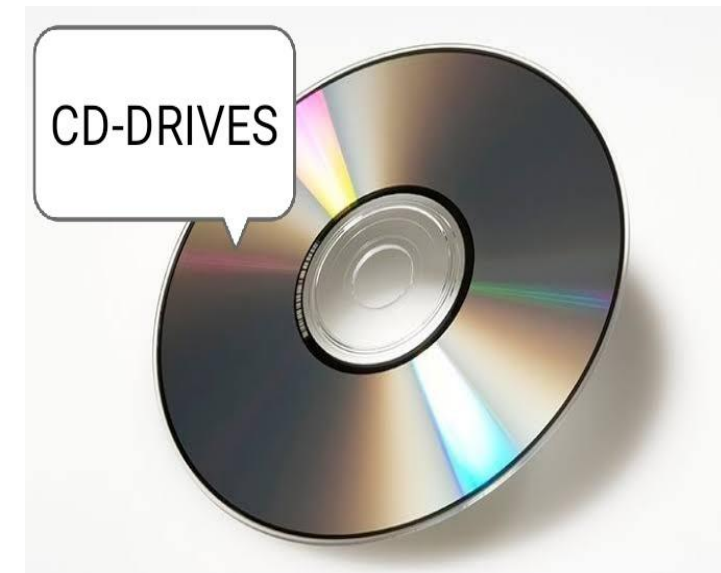
# APPLICATIONS



- Digital Motor Control
- Computer Printers
- Sound Equipment (e.g. CD/MP3  
Players, etc.)






# APPLICATIONS



## ■ Digital Oscilloscopes



## ■ Signal Generators

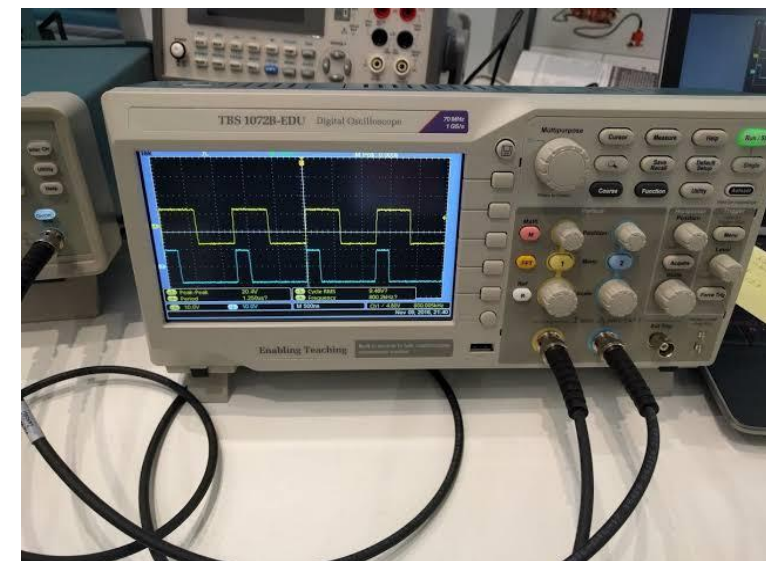






# APPLICATIONS



- Motor controllers



Cruise Control

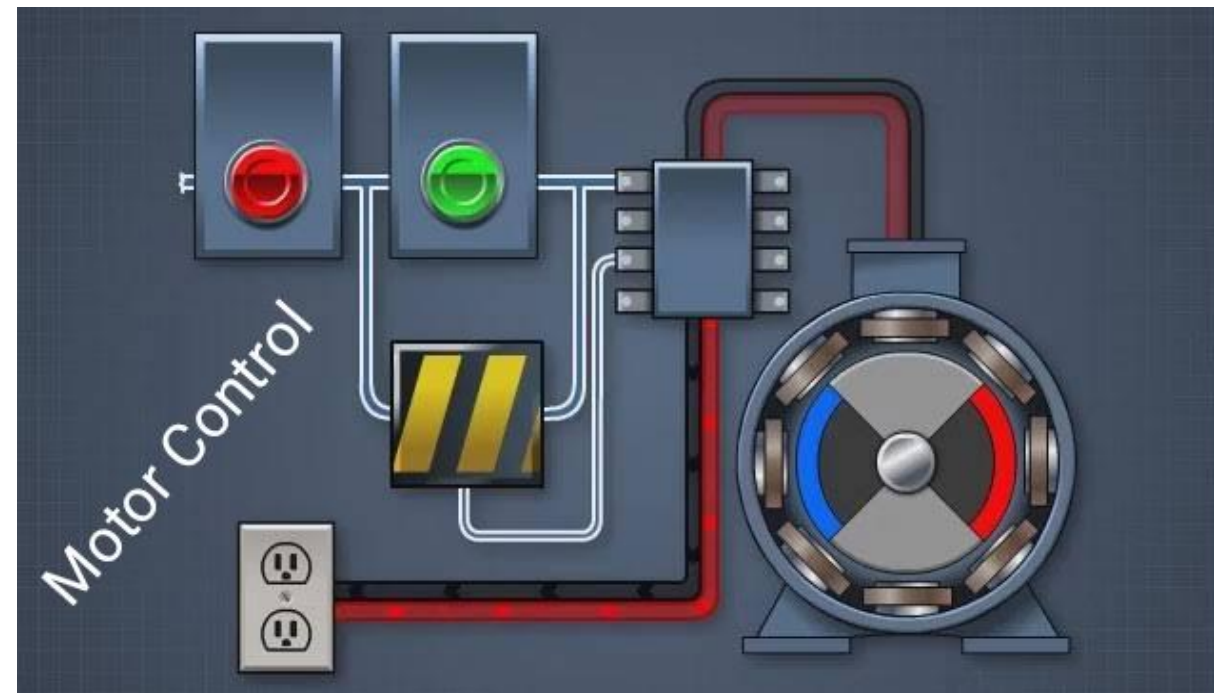

Motor Control



Valve Control





# Assessment



1. A type of resistor network known as an R-2R ladder is often used in digital-to-analog conversion circuits: why?
2. The output voltage magnitude stands independent of the number of bits(sections) in the R-2R ladder network because-----





**THANK YOU**