



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

19ECB202 – LINEAR AND DIGITAL CIRCUITS

II YEAR/ III SEMESTER


UNIT 5 – SEQUENTIAL CIRCUITS

TOPIC 3 – D,T FLIP FLOPS, Master Slave




D Flip-Flop

 D flip-flop operates with only positive clock transitions or negative clock transitions. Whereas, D latch operates with enable signal. That means, the output of D flip-flop is insensitive to the changes in the input, D except for active transition of the clock signal.





D Flip-Flop- Truth Table

 

(b)

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state



D Flip-Flop- Working

- When storing data, a memory element's excitation input is simply the data to be stored.
- A device (which is called a delay latch or D latch) is needed that transfers a logic value on its excitation input D into the cross-coupled storage cell of a latch.
- The D latch can be created from a gated SR latch, by assigning $S = D$ and $R = \bar{D}$.



D Flip-Flop- Working



Characteristic equation:


- This equation can be derived from that of the gated SR latch by substituting D for S and D for R:

$$Q^* = DC + CQ$$

- When the enable signal is low, ($C = 0$), the equation reduces to $Q^* = Q$, the latch is placed in hold mode (no change) operating mode with the latch holding the last value of D that was entered
- When the enable signal is high ($C = 1$), $Q^* = D$, the excitation input D is gated directly to output Q (gated or enabled mode).



D Flip-Flop- Timing Diagram

 





T Flip-Flop

- T flip-flop is the simplified version of JK flip-flop.
- It is obtained by connecting the same input 'T' to both inputs of JK flip-flop.
- It operates with only positive clock transitions or negative clock transitions.

- The name T flip-flop is termed from the nature of toggling operation
- The major applications of T flip-flop are counters and control circuits
- T flip flop is modified form of JK flip-flop making it to operate in toggling region
- Whenever the clock signal is LOW, the input is never going to affect the output state



T Flip-Flop

 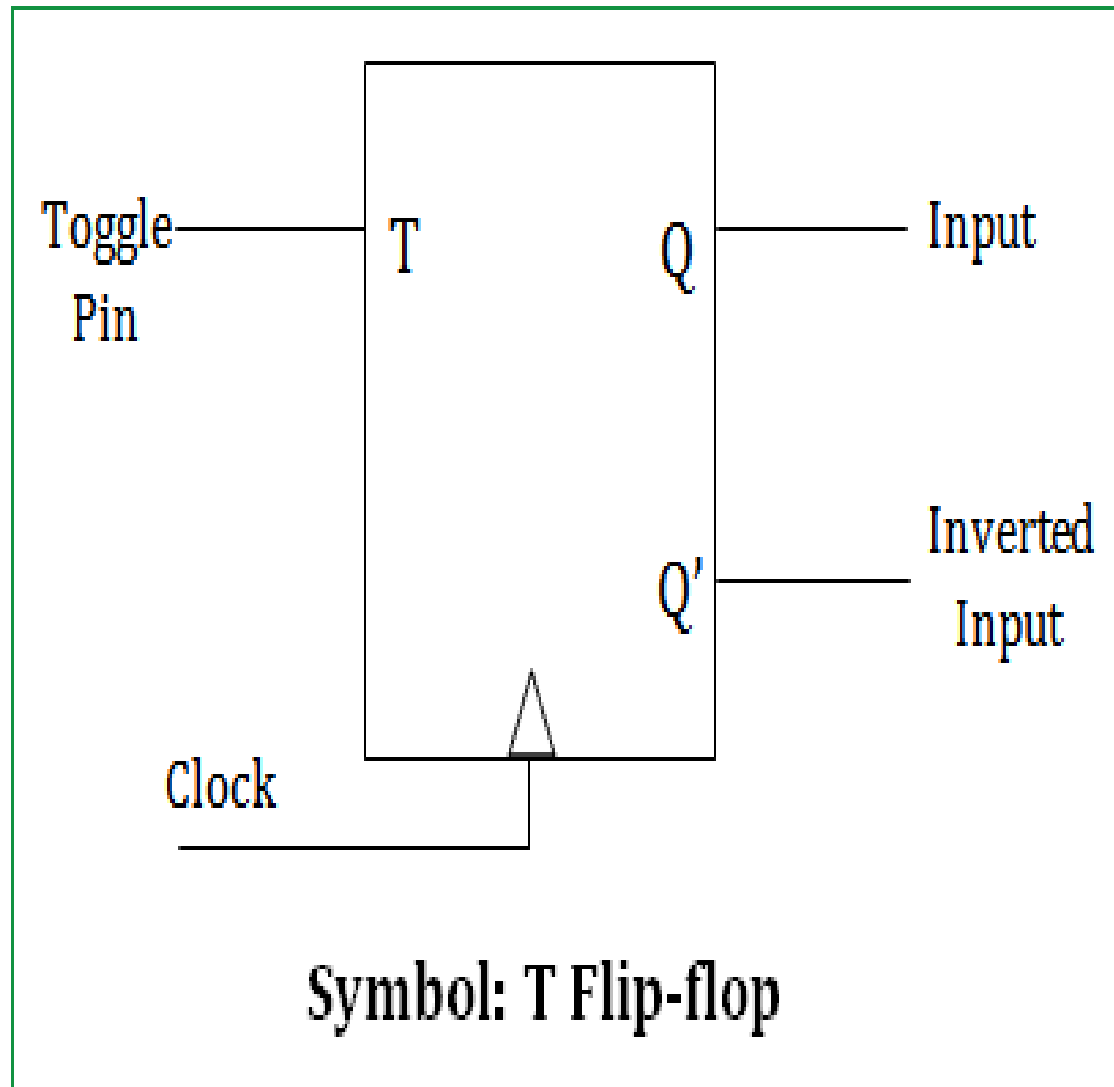



T Flip-Flop- Truth Table

	Previous		Next	
T	Q_{Prev}	Q'_{Prev}	Q_{Next}	Q'_{Next}
0	0	1	0	1
0	1	0	1	0
1	0	1	1	0
1	1	0	0	1



T Flip-Flop- Truth Table

- When the T input is low, then the next state of the T flip flop is same as the present state.
 - $T = 0$ and present state = 0 then the next state = 0
 - $T = 0$ and present state = 1 then the next state = 1
- When the T input is high and during the positive transition of the clock signal, the next state of the T flip –flop is the inverse of present state.
 - $T = 1$ and present state = 0 then the next state = 1
 - $T = 1$ and present state = 1 then the next state = 0

Applications

- Frequency Division Circuits.
- 2 –Bit Parallel Load Registers.




T Flip-Flop- Characteristic Table & Equation



T flip-flop		
Q(t)	Q(t+1)	DR
0	0	0
0	1	1
1	0	1
1	1	0



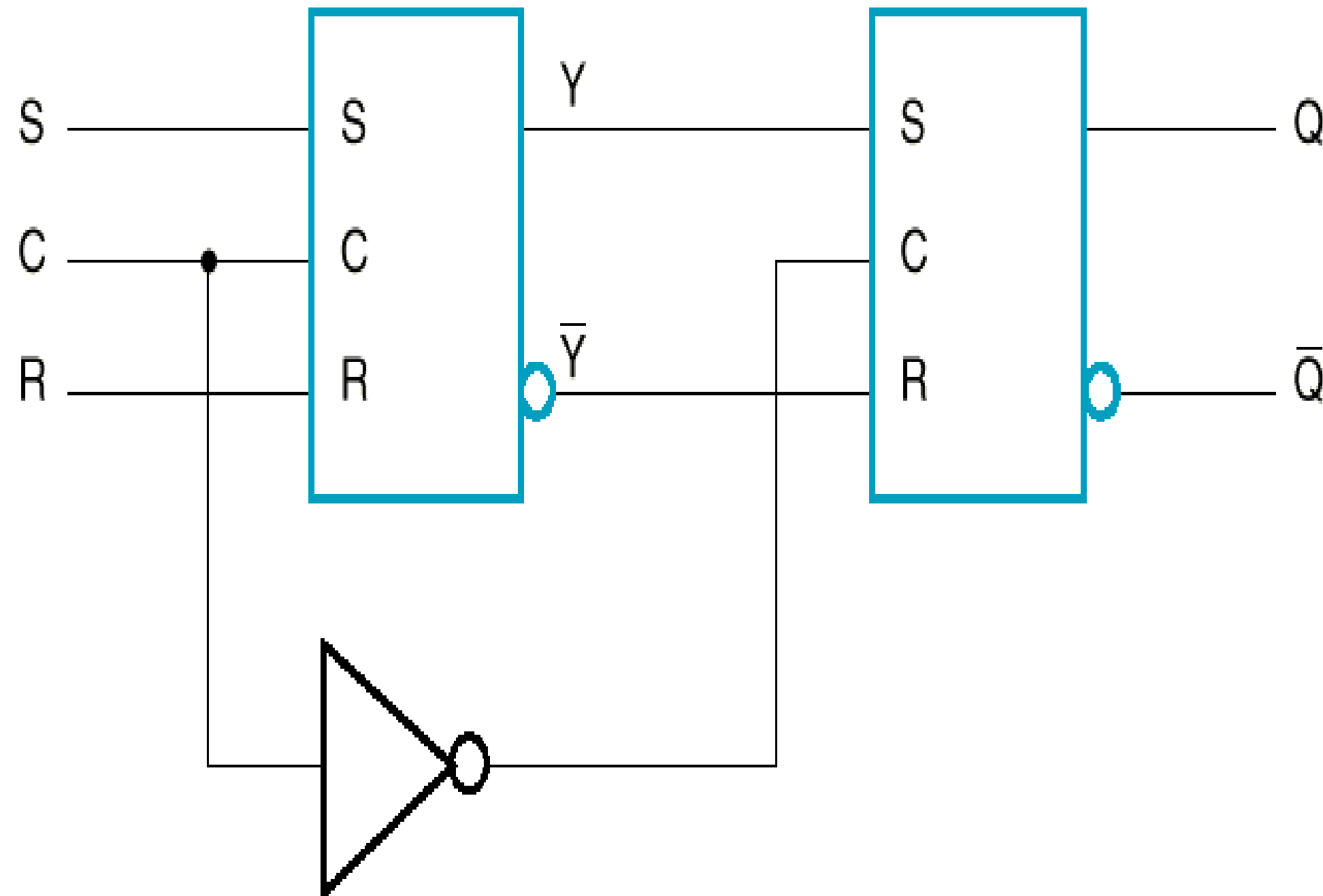Master-Slave FF configuration using SR latches






Master-Slave FF configuration using SR latches

S	R	CLK	Q	Q'	
0	0	1	Q_0	Q_0'	Store
0	1	1	0	1	Reset
1	0	1	1	0	Set
1	1	1	1	1	Disallowed
X	X	0	Q_0	Q_0'	Store

- When $C=1$, master is enabled and stores *new* data, slave stores *old* data.

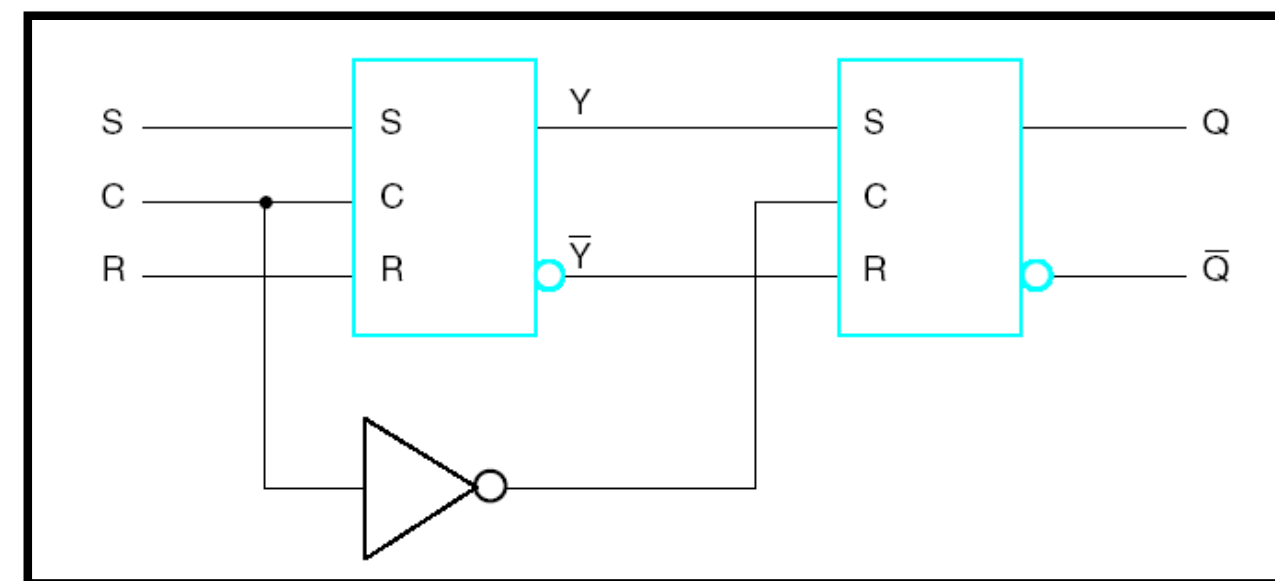- When $C=0$, master's state passes to enabled slave, master not sensitive to new data (disabled).






MASTER SLAVE J K Flip flop


- Clocked J-K FF (falling edge)
 - Realization using two S-R latches
 - Note where J and K change.
 - One flip-flop acts as the “Master” circuit, which triggers on the leading edge of the clock pulse
 - while the other acts as the “Slave” circuit, which triggers on the falling edge of the clock pulse.
 - This results in the two sections, the master section and the slave section being enabled during opposite half-cycles of the clock signal.
 - The slave section being enabled during opposite half-cycles of the clock signal.



MASTER SLAVE J K Flip flop

 

(a) Master-slave J-K flip-flop

 

(b) Internal timing diagram for master-slave J-K flip-flop



Excitation Tables

SR Flip-flop				D Flip-flop		
Q(t)	Q(t+1)	S	R	Q(t)	Q(t+1)	DR
0	0	0	X	0	0	0
0	1	1	0	0	1	1
1	0	0	1	1	0	0
1	1	X	0	1	1	1

JK flip-flop				T flip-flop		
Q(t)	Q(t+1)	J	K	Q(t)	Q(t+1)	DR
0	0	0	x	0	0	0
0	1	1	x	0	1	1
1	0	x	1	1	0	1
1	1	x	0	1	1	0



THANK YOU