



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

19ECB302–VLSI DESIGN

III YEAR/ V SEMESTER

UNIT 3 –SEQUENTIAL LOGIC CIRCUITS

TOPIC 3 –TIMING ISSUES




OUTLINE



- **SYNCHRONOUS TIMING**
- **LATCH PARAMETERS**
- **REGISTER PARAMETERS**
- **CLOCK UNCERTAINTIES**
- **CLOCK NONIDEALITIES**
- **CLOCK SKEW AND JITTER**
- **POSITIVE AND NEGATIVE SKEW**
- **TIMING CONSTRAINTS**
- **ACTIVITY**
- **IMPACT OF JITTER**
- **SHORTEST PATH**
- **HOW TO COUNTER CLOCK SKEW?**
- **LATCH TIMING**
- **ASSESSMENT**
- **SUMMARY & THANKYOU**




SYNCHRONOUS TIMING

 



LATCH PARAMETERS

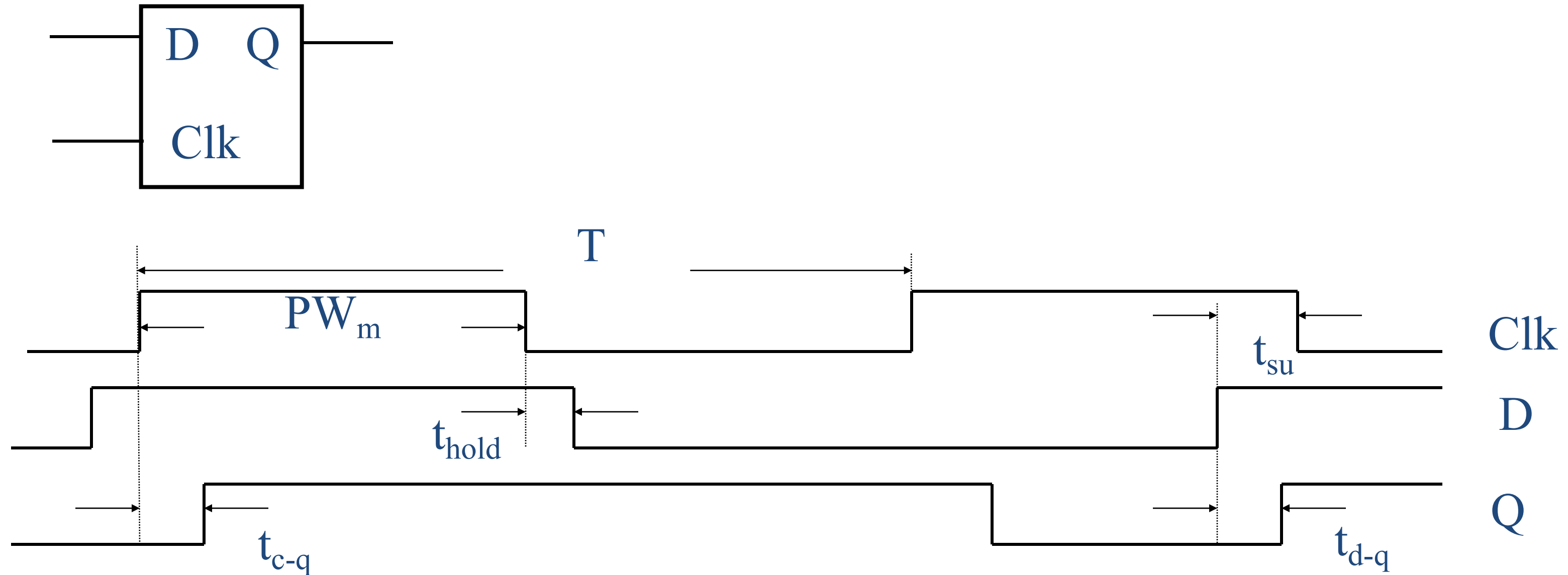


Delays can be different for rising and falling data transitions

11/24/2023



REGISTER PARAMETERS

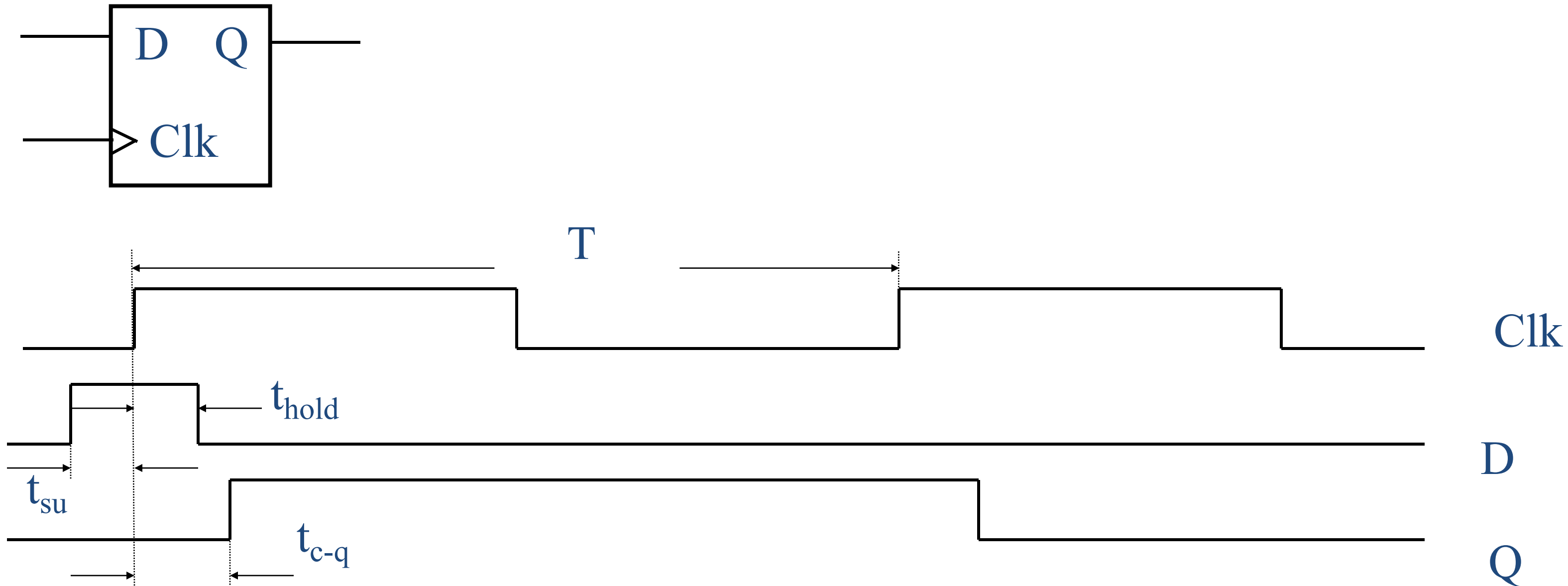


Delays can be different for rising and falling data transitions

11/24/2023



CLOCK UNCERTAINTIES

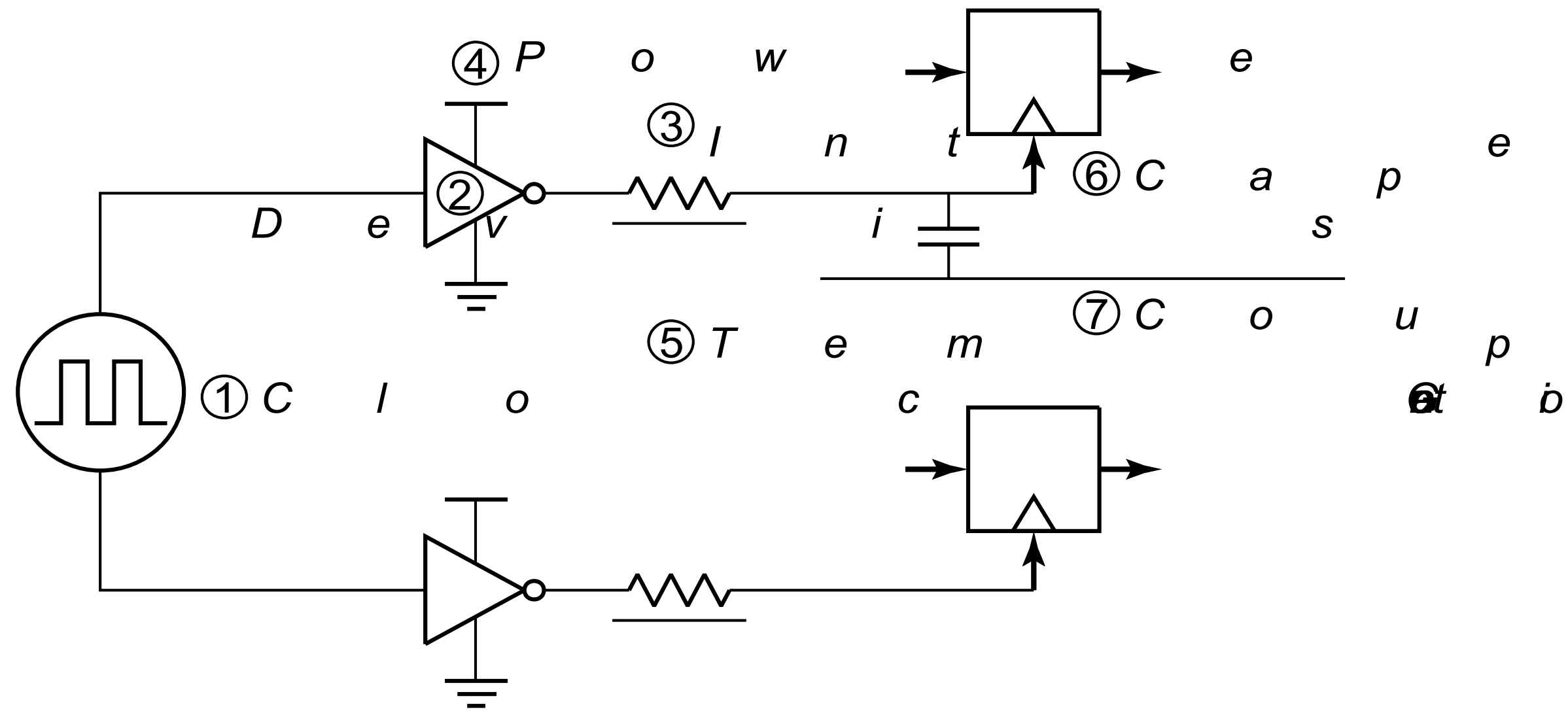

11/24/2023




CLOCK NONIDEALITIES



- **Clock skew**
 - Spatial variation in temporally equivalent clock edges; deterministic + random, t_{SK}
- **Clock jitter**
 - Temporal variations in consecutive edges of the clock signal; modulation + random noise
 - Cycle-to-cycle (short-term) t_{JS}
 - Long term t_{JL}
- **Variation of the pulse width**
 - Important for level sensitive clocking




CLOCK SKEW AND JITTER

 

- Both skew and jitter affect the effective cycle time
- Only skew affects the race margin





CLOCK SKEW

 



POSITIVE AND NEGATIVE SKEW

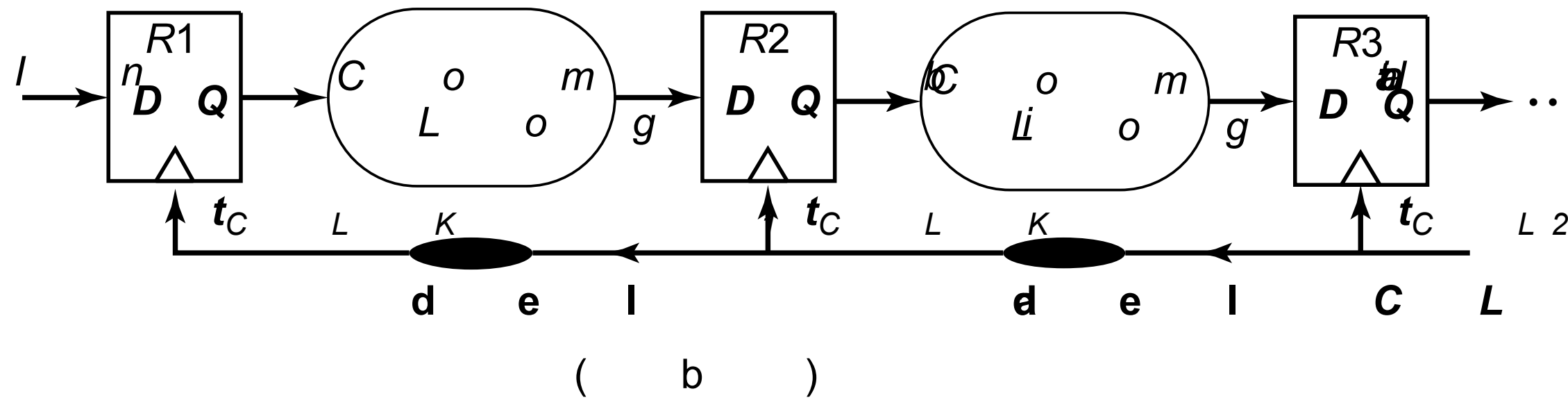
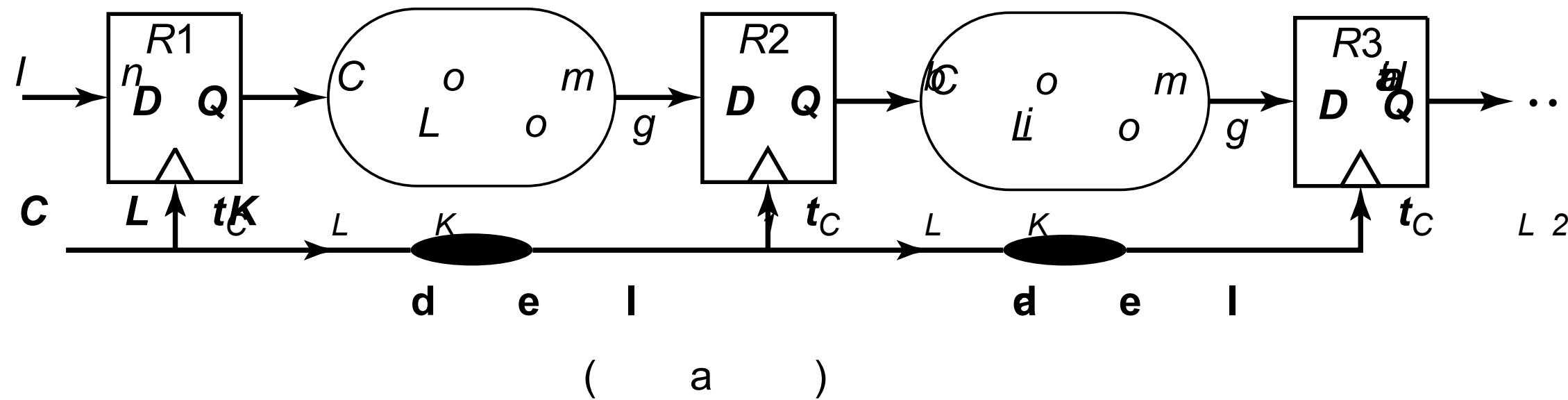




POSITIVE SKEW & NEGATIVE SKEW



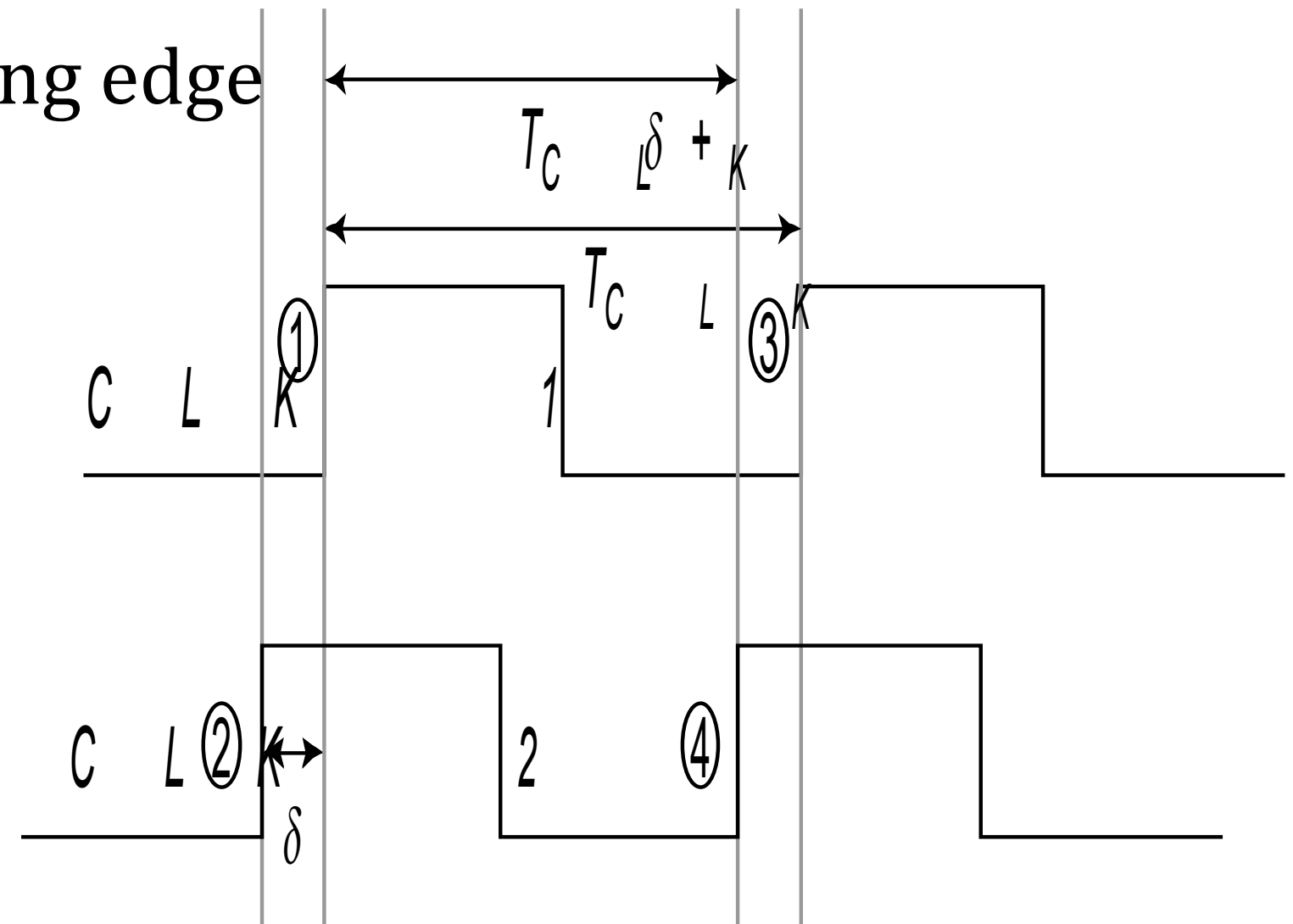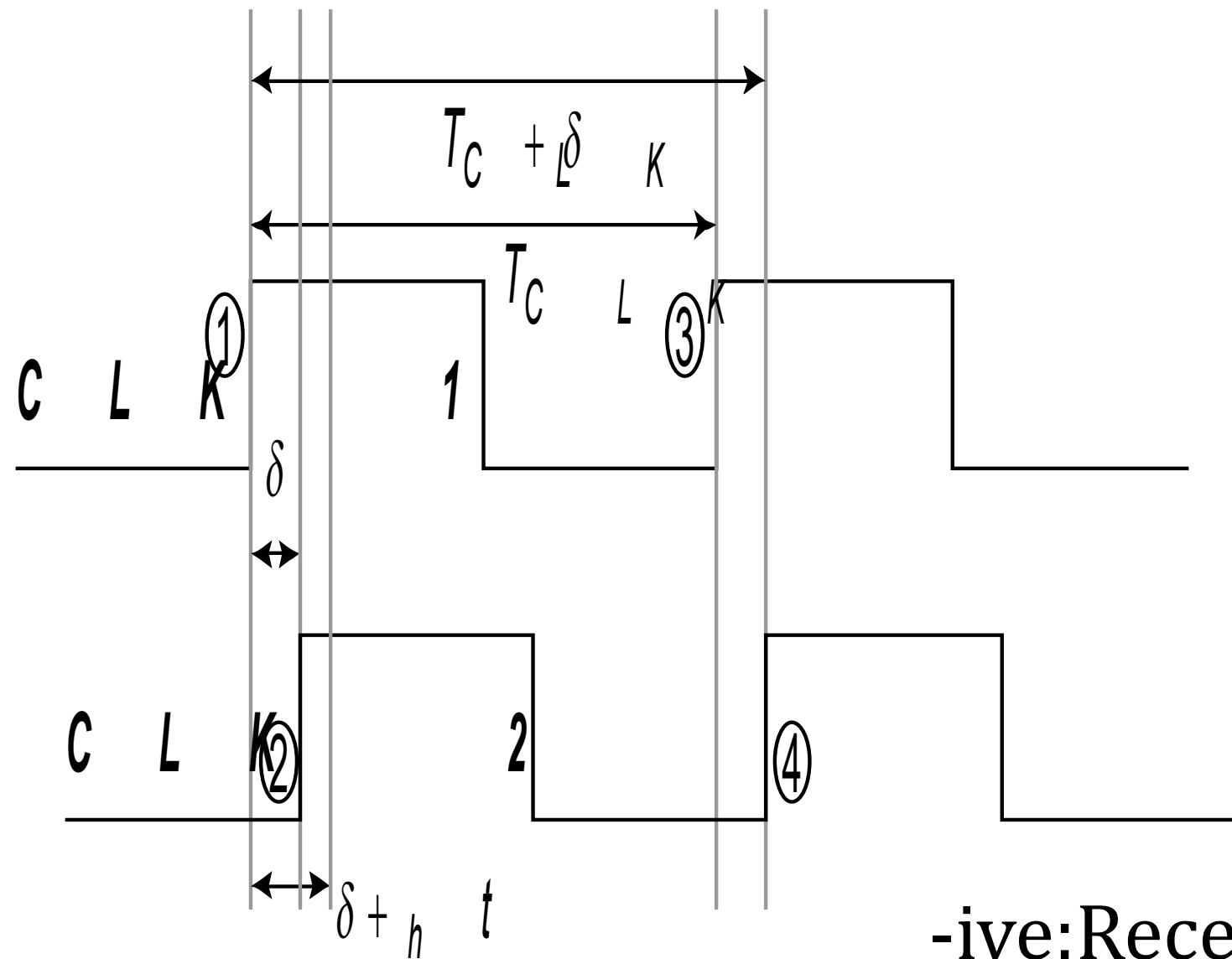
Launching edge arrives before the receiving edge



-ive: Receiving edge arrives before the launching edge



TIMING CONSTRAINTS

 

Minimum cycle time:

$$T - \delta = t_{c-q} + t_{su} + t_{logic}$$

Worst case is when receiving edge arrives early (positive δ)



CLASS ROOM ACTIVITY




STUDY THE PYRAMID CAREFULLY.

			E			
		1110		D		
	446		679		681	
198		263		431		265

WHAT ARE THE VALUES OF E AND D?



IMPACT OF JITTER

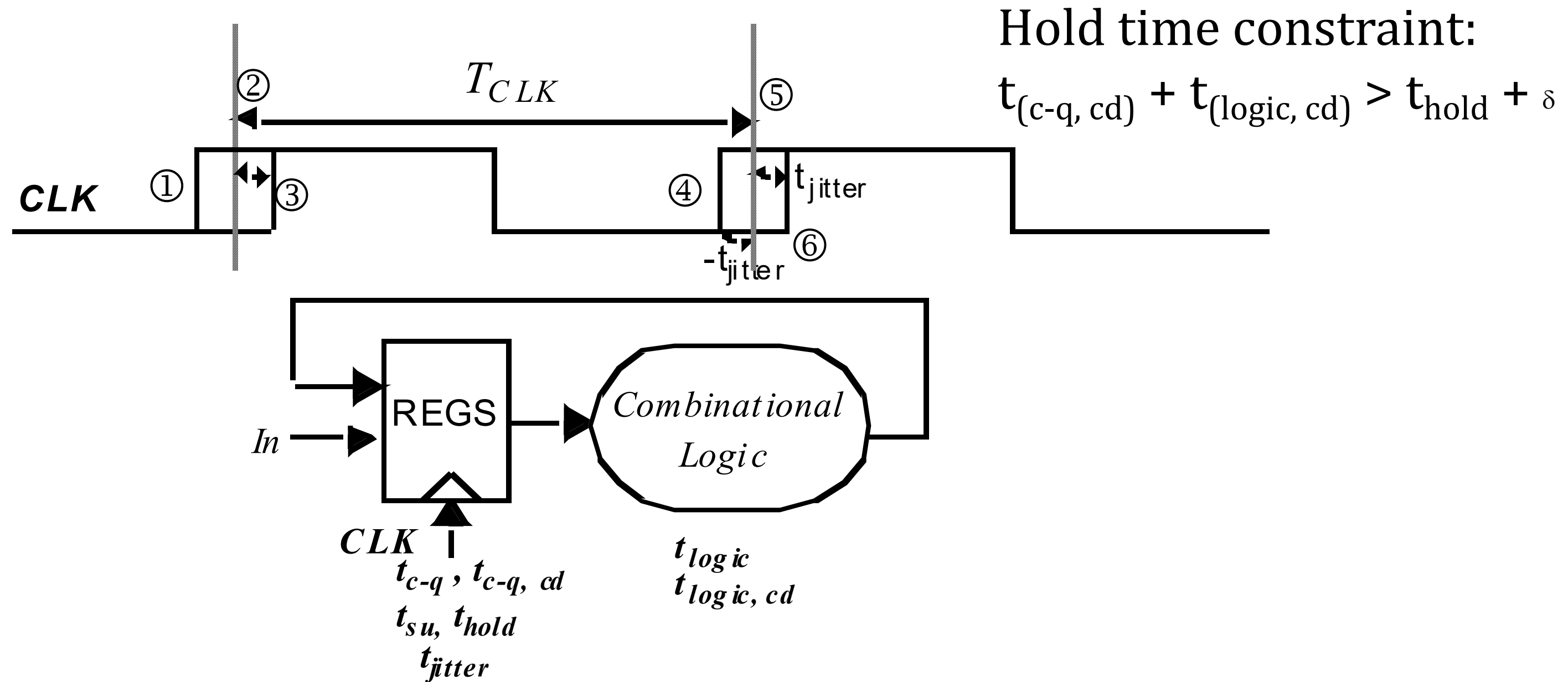




SHORTEST PATH




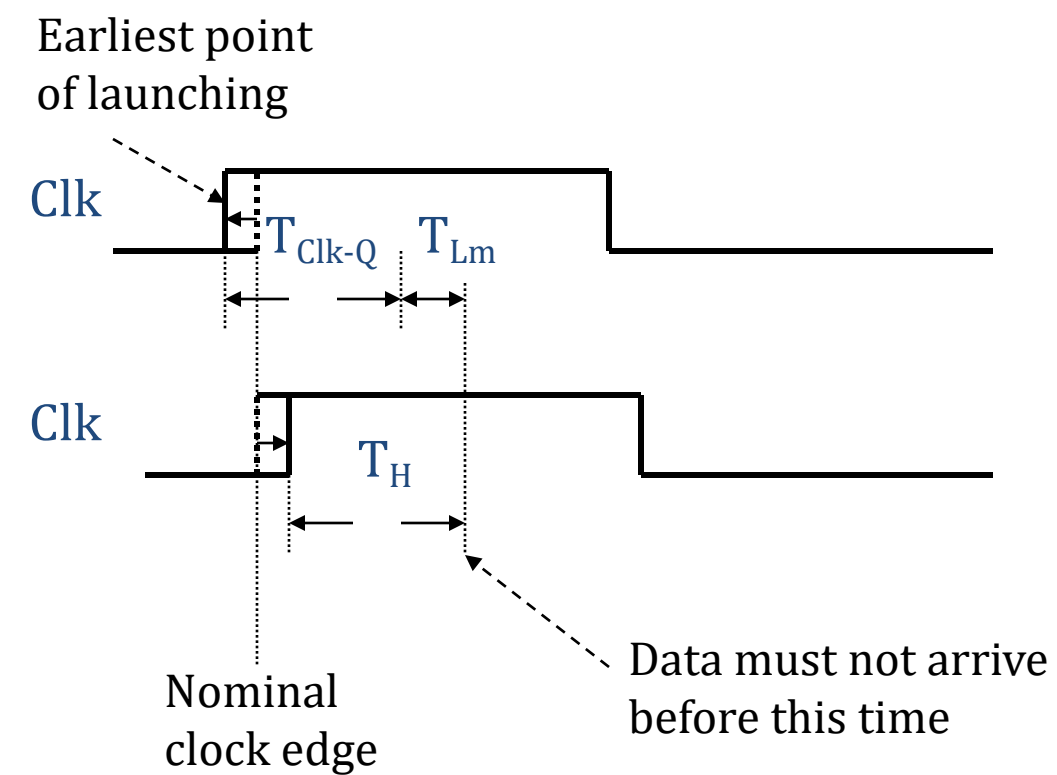Worst case is when receiving edge arrives late
Race between data and clock





HOW TO COUNTER CLOCK SKEW?

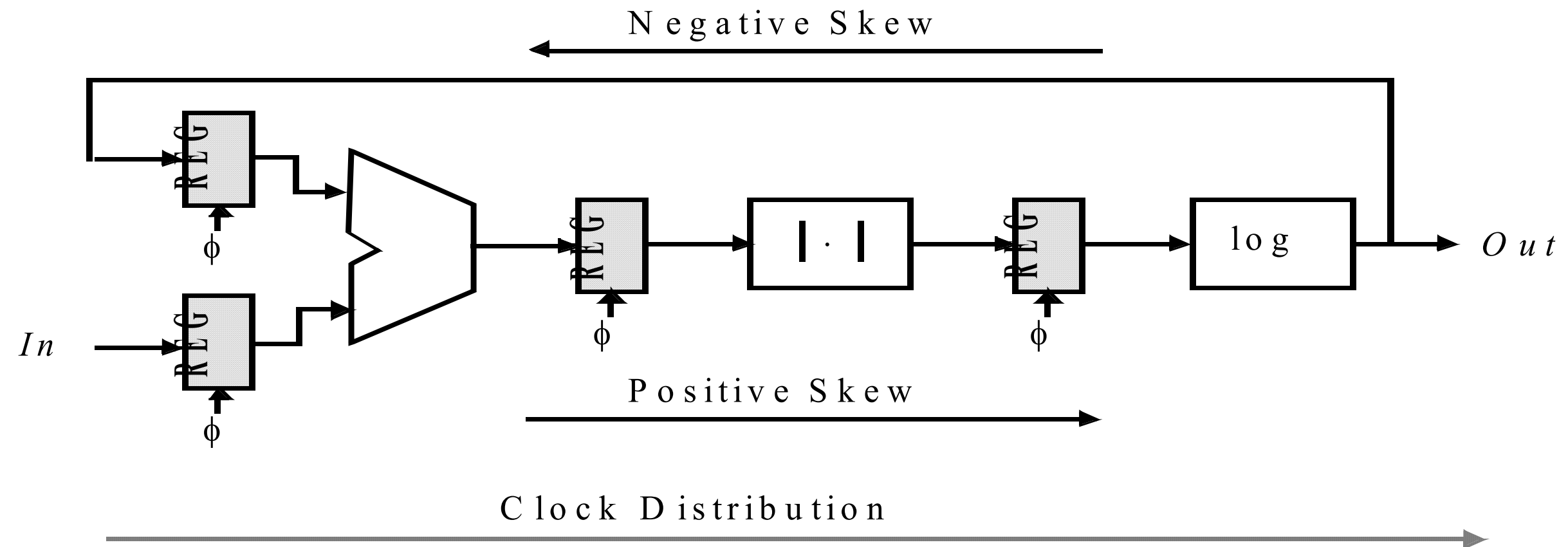


D a t a a n d C l o c k R o u t i n g



LATCH TIMING



 - When data arrives
- to closed latch
- Data has to be 're-launched'



•Latch is a 'soft' barrier

- When data arrives to transparent latch



ASSESSMENT



1. Compare latch & Register parameters
2. Define Clock Skew & Jitter
3. Differentiate positive skew & negative skew
4. How to counter clock skew?



SUMMARY & THANK YOU