



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**  
**An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **19ECB302–VLSI DESIGN**

**III YEAR/ V SEMESTER**

### **UNIT 5-SPECIFICATION USING VERILOG HDL**

### **TOPIC 9,10–DESIGN HIERARCHIES, BEHAVIORAL AND RTL MODELING**



# OUTLINE




- DESIGN HIERARCHIES
- WIRE AND VECTOR ASSIGNMENT
- VECTORS OF WIRES
- SIGNAL AND SIGNAL EDGE SENSITIVITY
- TWO ROLES OF HDL AND RELATED TOOLS
- SYNTHESIS VS SIMULATION
- ACTIVITY
- STRUCTURAL VS BEHAVIORAL HDL CONSTRUCTS
- THREE MODULE COMPONENTS-DATA FLOW,BEHAVIOURAL(RTL),STRUCTURAL
- MIXED MODELING STYLE
- ASSESSMENT
- SUMMARY



# DESIGN HIERARCHIES



- Represent the hierarchy of a design

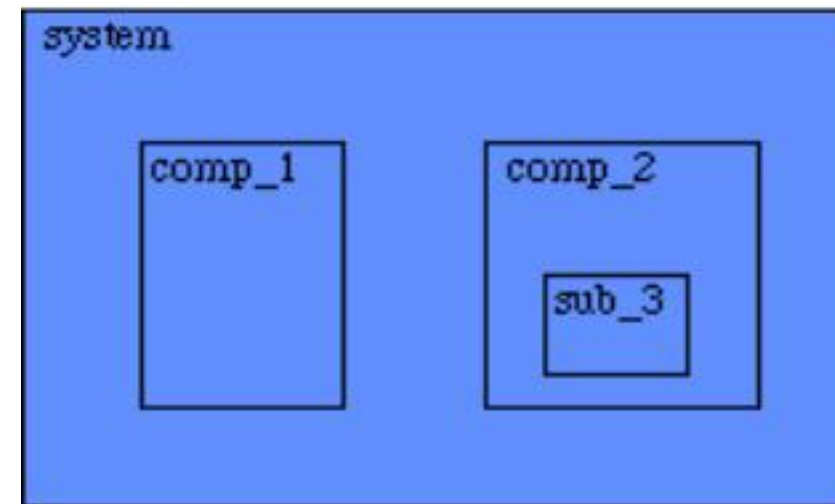


– modules

- the basic building blocks

– ports

 - the I/O pins in hardware
- input, output or inout





# DESIGN HIERARCHIES



- The module is the basic building block in Verilog
  - Modules can be interconnected to describe the structure of your digital system
  - Modules start with keyword module and end with keyword endmodule

- Module Ports
  - Similar to pins on a chip
  - Provide a way to communicate with outside world
  - Ports can be input, output or inout

## Module AND <port list>


- 
- 
- 

**endmodule**

## Module CPU <port list>

- 
- 
- 

**endmodule**

 

## Module AND (i0, i1, o);

**input i0, i1;**  
**output o;**

**endmodule**

- Modules have ports for interconnection with other modules



# DESIGN HIERARCHIES



- Can (should) specify module connections by name
  - Helps keep the bugs away
  - Example

```
mux2to1 mux1 (.A (A[1])
```

```
    .B (B[1]),
```

```
    .O (O[1]),
```

```
    .S (Sel) );
```

- Verilog won't complain about the order (but it is still poor practice to mix them up):



# WIRE AND VECTOR ASSIGNMENT



- Wire assignment: “continuous assignment”
  - Connect combinational logic block or other wire to wire input
  - **Order of statements not important to Verilog**, executed totally in parallel
  - But order of statements can be important to clarity of thought!
  - When right-hand-side changes, it immediately flows through to left
  - Designated by the keyword **assign**

**wire c;**

**assign c = a | b;**

**wire c = a | b; // same thing**



# VECTORS OF WIRES



- Wire vectors:

**wire [7:0] W1; // 8 bits, w1[7] is MSB**

– Also called “buses”

- Operations

– Bit select: **W1[3]**

– Range select: **W1[3:2]**

– Concatenate:

**vec = {x, y, z};**

**{carry, sum} = vec[0:1];**

– e.g., swap high and low-order bytes of 16-bit vector

**wire [15:0] w1, w2;**

**assign w2 = {w1[7:0], w1[15:8]}**



# SIGNAL AND SIGNAL EDGE SENSITIVITY



- Signal sensitivity: evaluate block on any signal change  
**always @(CLK)**
- Edge sensitivity: evaluate block on particular signal change  
**always @(posedge CLK)**





## TWO ROLES OF HDL AND RELATED TOOLS

- **#1: Specifying digital logic**
  - Specify the logic that appears in final design
  - Either
    - Translated automatically (called *synthesis*) or
    - Optimized manually (automatically checked for equivalence)
- **#2: Simulating and testing a design**
  - High-speed simulation is crucial for large designs
  - Many HDL *interpreters* optimized for speed
  - Testbench: code to test design, but not part of final design



# DESIGN HIERARCHIES




- Build up more complex modules using simpler modules
- Example: 4-bit wide mux from four 1-bit muxes
  - Again, just “drawing” boxes and wires

```
module mux2to1_4(  
    input [3:0] A,  
    input [3:0] B,  
    input Sel,  
    output [3:0] O );
```

```
    mux2to1 mux0 (Sel, A[0], B[0], O[0]);  
    mux2to1 mux1 (Sel, A[1], B[1], O[1]);  
    mux2to1 mux2 (Sel, A[2], B[2], O[2]);  
    mux2to1 mux3 (Sel, A[3], B[3], O[3]);  
endmodule
```

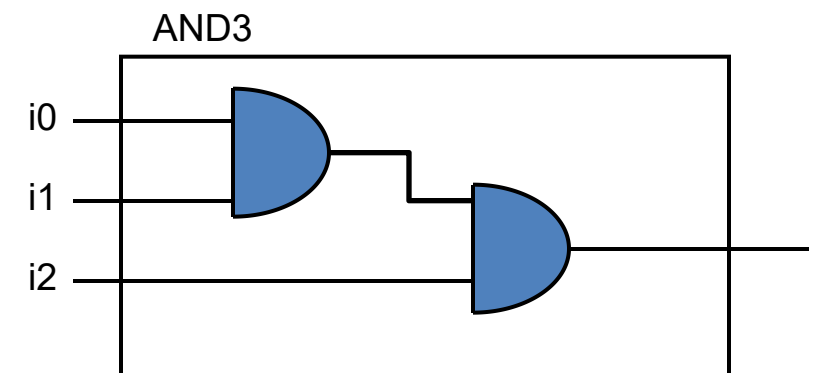- Module instances
  - Verilog models consist of a hierarchy of module *instances*
  - In C++ speak: modules are classes and instances are objects



```
Module AND3 (i0, i1, i2, o);  
    input i0, i1, i2;  
    output o;  
    wire temp;  
    AND a0 (.i0(i0), .i1(i1), .o(temp));  
    AND a1 (.i0(i2), .i1(temp), .o(o));  
endmodule
```



# DESIGN HIERARCHIES



- **Top-Down Design Methodology**

```
module CPA4b(Cout, Sum, a,b,Cin);
```

```
output Cout;  
output [3:0] Sum;
```

```
input [3:0]
```

```
Input a,b; Cin; c;
```

```
wire [2:0]
```

```
a d d e fa0(c[0], Sum[0], a[0], b[0], Cin);
```

//by position mapping

```
a d d e fa1(.a(a[1]), .b(b[1]), .cin(c[0]), .carry(c[1]), .sum(Sum[1]));
```

//by name mapping

```
a d d e fa2(c[2], Sum[2], a[2], b[2], c[1]);
```

```
adder fa3(Cout, Sum[3], a[3], b[3], c[2]);
```


```
endmodule
```

```
module adder (carry, sum, a, b, cin);
```

```
output carry, sum;  
input a, b, cin;
```

```
assign {carry, sum} = a + b + cin;
```

```
endmodule
```

 



## SYNTHESIS VS SIMULATION

- HDLs have features for *both* synthesis and simulation
  - E.g., simulation-only operations for error messages, reading files
  - Obviously, these can be simulated, but not synthesized into circuits
  - Also has constructs such as for-loops, while-loops, etc.
    - These are either un-synthesizable or (worse) synthesize poorly
  - **You need procedural code for testbench and *only* for testbench**
- Trends: a moving target
  - Good: better synthesis tools for higher-level constructs
  - Bad: harder than ever to know what is synthesizable or not
- Important distinction: What is a “higher-level” construct and what is “procedural code”?



## ACTIVITY



Translate this into words...Let's see who is smart



Ref.: <https://puzzlersworld.com>



# STRUCTURAL VS BEHAVIORAL HDL CONSTRUCTS



- **Structural** constructs specify actual hardware structures
  - Low-level, direct correspondence to hardware
    - Primitive gates (e.g., and, or, not)
    - Hierarchical structures via modules
  - Analogous to programming software in assembly
- **Behavioral** constructs specify an operation on bits
  - High-level, more abstract
    - Specified via equations, e.g.,  $out = (a \& b) | c$
- **Not all behavioral constructs are synthesizable**
  - We've already talked about the pitfalls of trying to "program"
  - But even some combinational logic won't synthesize well
  - $out = a \% b$  // modulo operation – what does this synthesize to?
  - We will not use:  $+ - * / \% > >= < <= >> <<$




# VERILOG STRUCTURAL VS BEHAVIORAL EXAMPLE


 
## Structural

```
module mux2to1(  
    input S, A, B,  
    output Out );  
    wire S_, AnS_, BnS;  
    not (S_, S);  
    and (AnS_, A, S_);  
    and (BnS, B, S);  
    or (Out, AnS_, BnS);  
endmodule
```



**Better:**  
`assign Out = S? B:A;`

## Behavioral

```
module mux2to1(  
    input S, A, B,  
    output Out );  
    assign Out = (~S & A) | (S & B);  
endmodule
```



# THREE MODULE COMPONENTS



- Interface specification – new style (Verilog 2001)  
**module mux2to1(  
input S, A, B,  
output O );**
  - Can also have **inout**: bidirectional wire (we will not need or use)
- Declarations
  - Internal wires, i.e., wires that remain within this module
  - Wires also known as “nets” or “signals”  
**wire S\_, AnS\_, BnS;**
- Implementation: primitive and module instantiations  
**and (AnS\_, A, S\_);**





# THREE MODULE COMPONENTS-1



- **Structural:** Logic is described in terms of Verilog gate primitives


- Example:

```
not n1(sel_n, sel);
```

```
and a1(sel_b, b, sel_b);
```

```
and a2(sel_a, a, sel);
```

```
or o1(out, sel_b, sel_a);
```

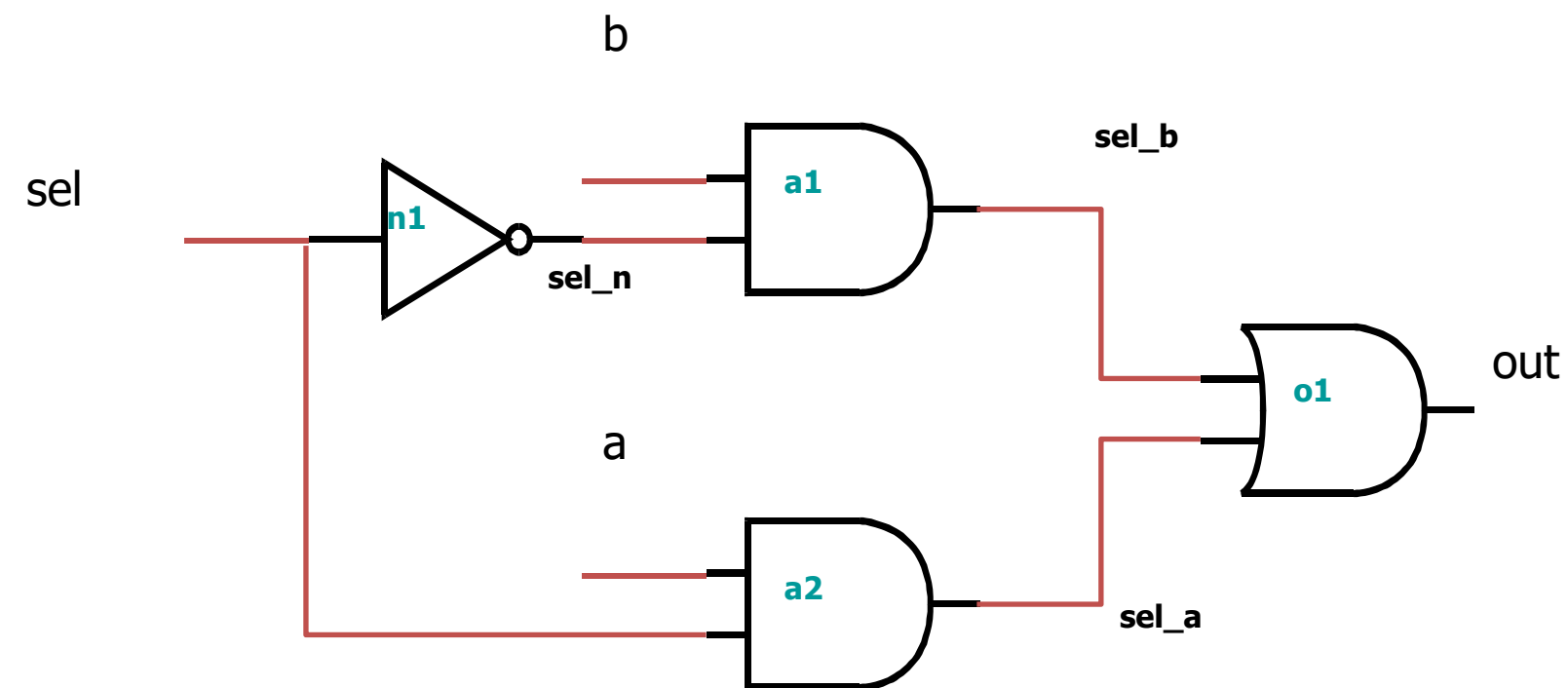




## THREE MODULE COMPONENTS-2



- **Dataflow:** Specify output signals in terms of input signals

- Example:

**assign** out = (sel & a) | (~sel & b);

 



## THREE MODULE COMPONENTS-3



- **Behavioral:** Algorithmically specify the behavior of the design

- Example:

```
if (select == 0) begin
```


```
    out = b;
```

```
end
```

```
else if (select == 1) begin
```

```
    out = a;
```

```
end
```

 



# BEHAVIORAL STATEMENTS



```
module mux2to1_4(A, B, Sel, O);
```

```
    input [3:0] A;
```

```
    input [3:0] B;
```

```
    input Sel;
```

```
    output [3:0] O;
```

```
    mux2to1 mux0 (Sel, A[0], B[0], O[0]);
```

```
    mux2to1 mux1 (Sel, A[1], B[1], O[1]);
```

```
    mux2to1 mux2 (Sel, A[2], B[2], O[2]);
```

```
    mux2to1 mux3 (Sel, A[3], B[3], O[3]);
```

```
endmodule
```

Like in C, but use **begin-end** instead of **{-}** to group

```
if (<expr>) <stmt> else if <stmt>
```

```
for (<stmt>;<expr>;<stmt>) <stmt>
```

Careful: No ++ operator in Verilog



## BEHAVIOR INVOCATION: ALWAYS



**always** @( <sensitivity> <or sensitivity>\*)

**begin**

<stmt>\*

**end**

- Defines reaction of module to changes in input
  - sensitivity list: signals or signal edges that trigger change
  - Keyword **or**: disjunction of multiple sensitivity elements
  - Multiple **always** sections are allowed
    - Careful: don't know order in which signals arrive
    - Best to use one



# THREE MODULE COMPONENTS



## Structural Modeling

- Execution: Concurrent
- Format (Primitive Gates):  
**and** G2(Carry, A, B);
- First parameter (Carry) – Output
- Other Inputs (A, B) - Inputs

## Dataflow Modeling

- Uses continuous assignment statement
  - Format: **assign** [ delay ] net = expression;
  - Example: **assign** sum = a ^ b;
- **Delay**: Time duration between assignment from RHS to LHS
- All continuous assignment statements execute concurrently
- Order of the statement does not impact the design



# THREE MODULE COMPONENTS



## Dataflow Modeling

- Delay can be introduced
  - Example: `assign #2 sum = a ^ b;`
  - “#2” indicates 2 time-units
  - No delay specified : 0 (default)
- Associate time-unit with physical time
  - ``timescale` time-unit/time-precision
  - Example: ``timescale 1ns/100 ps`
- Timescale
  - ``timescale 1ns/100ps`
  - 1 Time unit = 1 ns
  - Time precision is 100ps (0.1 ns)
  - 10.512ns is interpreted as 10.5ns

- Example:

```
`timescale 1ns/100ps
```

```
module HalfAdder (A, B, Sum, Carry);
```


```
input A, B;
```

```
output Sum, Carry;
```

```
assign #3 Sum = A ^ B;
```

```
assign #6 Carry = A & B;
```

```
endmodule
```

 



# THREE MODULE COMPONENTS



- **Example:**

```
module mux_2x1(a, b, sel,  
  out);  
  input a, a, sel;  
  output out;  
  always @(a or b or sel)  
  begin  
    if (sel == 1)  
      out = a;  
    else out = b;  
  end  
endmodule
```

Sensitivity List





# VERILOG MODULE EXAMPLE & RTL VS STRUCTURAL



```
module Full_Adder_Behavioral_Verilog(  
  input X1, X2, Cin,  
  output S, Cout  
);  
  reg[1:0] temp;  
  always @(*)  
  begin  
    temp = {1'b0,X1} + {1'b0,X2}+{1'b0,Cin};  
  end  
  assign S = temp[0];  
  assign Cout = temp[1];  
endmodule
```

11/24/2023



## STRUCTURAL MODEL EXAMPLE



```
Module Full_Adder_Structural_Verilog ( input X1, X2, Cin, output S,  
Cout );  
    wire a1, a2, a3;  
    xor u1(a1,X1,X2);  
and u2(a2,X1,X2);  
and u3(a3,a1,Cin);  
or u4(Cout,a2,a3);  
    xor u5(S,a1,Cin);  
endmodule
```



## MIXED MODELING STYLE



```
//mixed-design full adder
module full_adder_mixed (a, b, cin, sum, cout);
//list inputs and outputs
input a, b, cin;
output sum, cout;
//define reg and wires
reg cout;
wire a, b, cin;
wire sum;
wire net1;
//built-in primitive
xor (net1, a, b);
//behavioral
always @ (a or b or cin)
begin
    cout = cin & (a ^ b) | (a & b);
end
//dataflow
assign sum = net1 ^ cin;    endmodule
```



## ASSESSMENT



### 1. Quiz: what's the difference?

`always @(D or CLK) if (CLK) Q <= D;`

`always @(posedge CLK) Q <= D;`

### 2. Fill up the blanks

`module mux_2x1(a, b, sel, out);`

`input a, b, sel;`

`output out;`

`always @(-----)`

`begin`

`if (sel == 1)`

`out = a;`

`else out = -----;`

`end`

`endmodule`

### 3. List out the three modeling styles name

### 4. Write the Verilog HDL code for mixed modeling



## SUMMARY & THANK YOU