



**SNS COLLEGE OF TECHNOLOGY**  
**An Autonomous Institution**  
**Coimbatore-35**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

**DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

IIYEAR/ III SEMESTER

**19ECT201 Electrical Engineering and Instrumentation**


unit 5-MEASUREMENT SYSTEMS  
,SCHERING'S BRIDGE


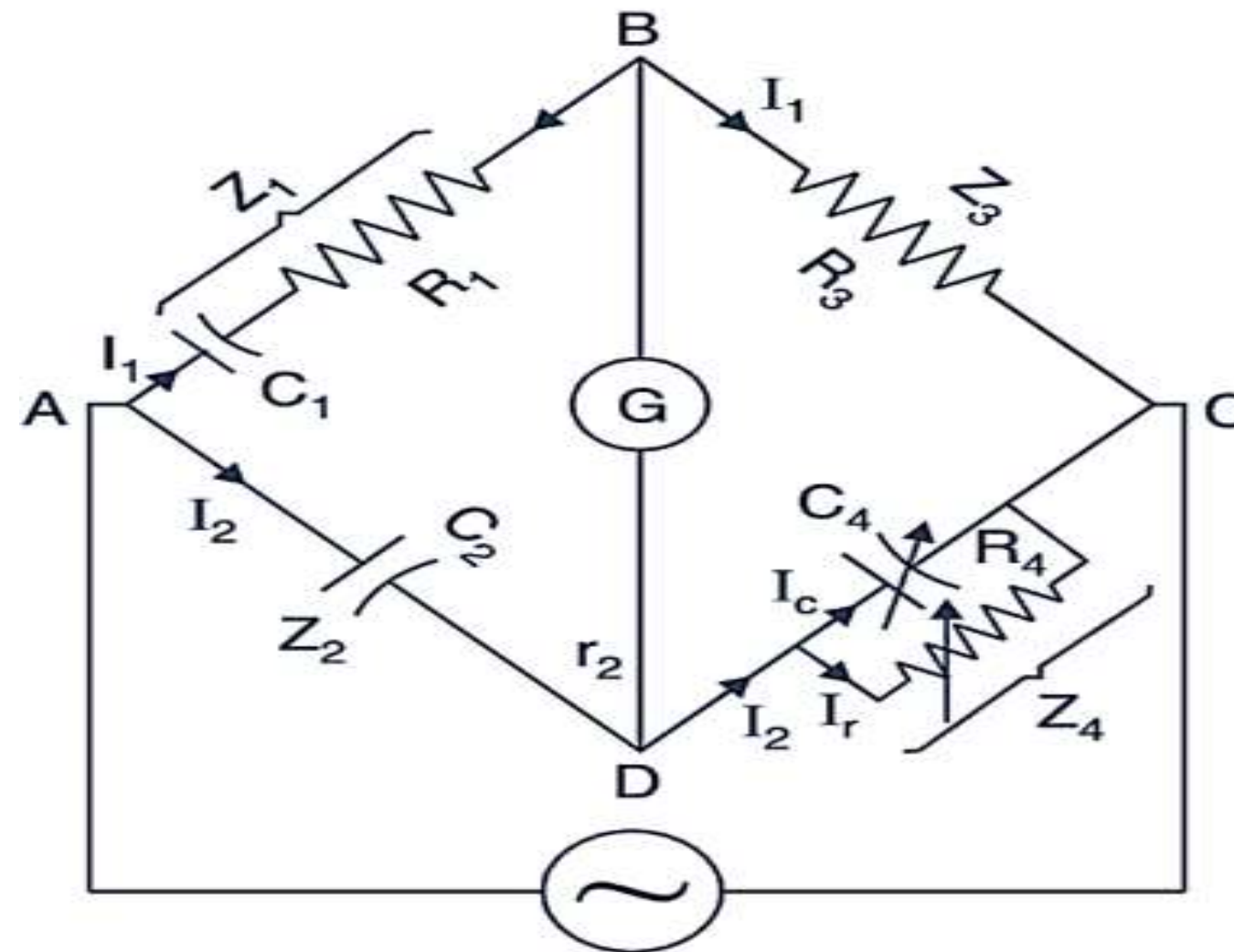
# SCHERING 'S BRIDGE



A **Schering Bridge** is a bridge circuit used for measuring an unknown electrical capacitance and its dissipation factor. The dissipation factor of a capacitor is the ratio of its resistance to its capacitive reactance. The Schering Bridge is basically a four-arm alternating-current (AC) bridge circuit whose measurement depends on balancing the loads on its arms





The components of the circuit are:

$C_1$  = The unknown capacitor

$R_1$  = A series resistance representing dielectric loss in the capacitor  $C_1$

Recall that power loss in an ideal capacitor is zero. This is the resistance contained in the capacitor, which causes power loss called dielectric loss.

$R_3$  = a non-inductive resistor

$R_4$  = a variable non-inductive resistor

$C_2$  = a standard capacitor, is an air capacitor and is loss free



$C_4$  = a variable capacitor parallel with  $R_4$

The balance is obtained by varying  $R_3$  (or  $R_4$ ).

At balance condition:

$$Z_1 Z_4 = Z_2 Z_3$$

or

$$\left[ R_1 + \frac{1}{j\omega C_1} \right] \left[ \frac{R_4}{1 + j\omega C_4 R_4} \right] = \left[ \frac{1}{j\omega C_2} \right] R_3$$

or

$$\left[ R_1 + \frac{1}{j\omega C_1} \right] R_4 = \frac{R_3}{j\omega C_2} (1 + j\omega C_4 R_4)$$





or

$$R_1 R_4 + \frac{1}{j\omega C_1} R_4 = \frac{R_3}{j\omega C_2} + \frac{j\omega C_4 R_4 R_3}{j\omega C_2} \dots (1)$$

Since,

$$\left( \frac{1}{j} = -j \right)$$

Thus, Equation 1 written as

$$R_1 R_4 - \frac{jR_4}{\omega C_1} = -\frac{jR_3}{j\omega C_2} + \frac{C_4 R_4 R_3}{C_2}$$

Now equating real terms



$$R_1 R_4 = \frac{C_4 R_4 R_3}{C_2}$$

or

$$R_1 = \frac{R_3 C_4}{C_2}$$

Equating imaginary terms

$$-\frac{jR_4}{\omega C_1} = -\frac{jR_3}{\omega C_2}$$

or

$$C_1 = \frac{R_4 C_2}{R_3}$$

Dissipation factor (D) is given by

$$D = \omega r_1 C_1 = \omega \times \frac{R_3 C_4}{C_2} \times C_2 \frac{R_4}{R_3}$$
$$D = \omega C_4 R_4$$



## **ADVANTAGES**

1. Balance equations are free from frequency.
2. The arrangement of the bridge is less costly as compared to the other bridges.

## **DRAWBACKS**

There is a difficulty in obtaining balance as  $R_3$  appears in both equations.

## **APPLICATIONS**

Some of the applications of using Schering bridge are  
Schering bridges used by generators  
Used by power engines  
Used in house industrial networks, etc