



SNS COLLEGE OF TECHNOLOGY
Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF COMPUTER SCIENCE ENGINEERING

19ECB231 – DIGITAL ELECTRONICS

II YEAR/ III SEMESTER

UNIT 4 – DESIGN OF SEQUENTIAL CIRCUITS

TOPIC –REGISTERS,SHIFT REGISTERS



REGISTERS



- A **register** is basically a storage space for units of memory that are used to transfer data for immediate use by the CPU (Central Processing Unit) for data processing.
- Also known as memory registers, they can actually form part of the computer processor as a processor register.
- The register is large enough to hold any kind of data, such as dates, instruction sets, storage addresses, bits, sequences, and characters.



- Some instruction sets are partly formed by registers.
- Types of registers include memory address register, memory buffer register, input output address register, input output buffer register, and shift register.



Shift Register



- One flip-flop can store one-bit of information.
- In order to store multiple bits of information, we require multiple flip-flops.
- The group of flip-flops, which are used to hold and store the binary data is known as **register**.
- If the register is capable of shifting bits either towards right hand side or towards left hand side is known as **shift register**.



Types of Shift Register



The types of shift registers based on applying inputs and accessing of outputs.

- Serial In – Serial Out shift register
- Serial In – Parallel Out shift register
- Parallel In – Serial Out shift register
- Parallel In – Parallel Out shift register
- Bidirectional shift register
- Universal shift register



Serial In – Serial Out shift register (SISO)




- The shift register, which allows serial input and produces serial output is known as Serial In – Serial Out shift register.
- The circuit diagram consists of three D flip-flops, which are **cascaded**. The output of one D flip-flop is connected as the input of next D flip-flop. All these flip-flops are synchronous with each other since, the same clock signal is applied to each one.



- In this shift register, the bits can be sent serially from the input of left most D flip-flop. Hence, this input is also called as **serial input**.
- For every positive edge triggering of clock signal, the data shifts from one stage to the next. So, we can receive the bits serially from the output of right most D flip-flop. Hence, this output is also called as **serial output**.



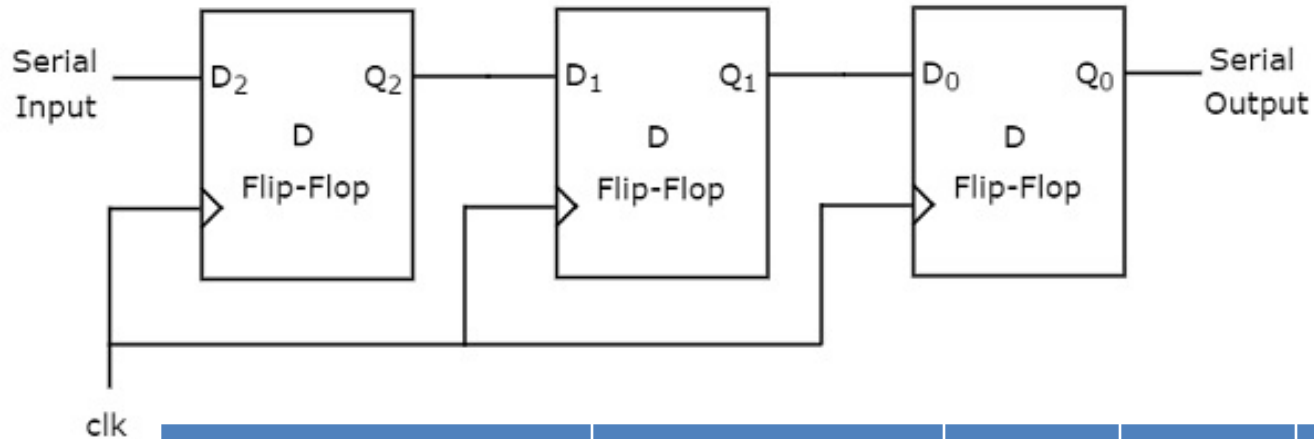Serial In – Serial Out shift register (SISO)



No of positive edge of Clock	Serial Input	Q ₂	Q ₁	Q ₀
0	-	0	0	0
1	1LSB	1	0	0
2	1	1	1	0
3	0MSB	0	1	1 LSB
4	-	-	0	1
5	-	-	-	0 MSB



Serial In - Parallel Out Shift Register




- The shift register, which allows serial input and produces parallel output is known as Serial In – Parallel Out SIPO shift register.
- This circuit consists of three D flip-flops, which are cascaded. The output of one D flip-flop is connected as the input of next D flip-flop. All these flip-flops are synchronous with each other since.



- In this shift register, the bits can be sent serially from the input of left most D flip-flop. Hence, this input is also called as **serial input**.
- For every positive edge triggering of clock signal, the data shifts from one stage to the next. In this case, we can access the outputs of each D flip-flop in parallel. So, will get **parallel outputs** from this shift register.



Serial In - Parallel Out Shift Register

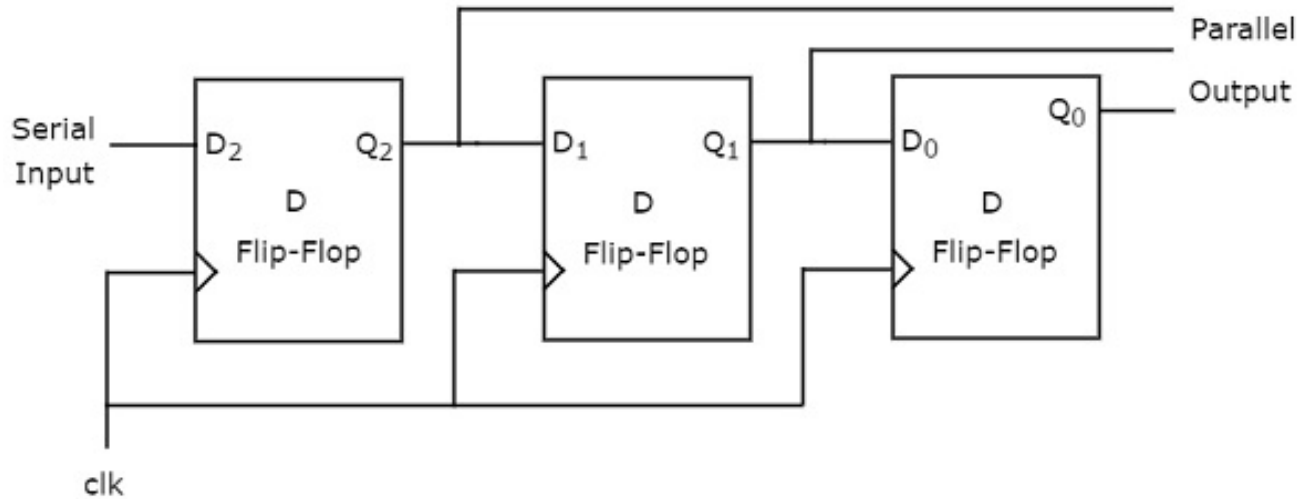

No of positive edge of Clock	Serial Input	Q ₂ MSB	Q ₁	Q ₀ LSB
0	-	0	0	0
1	1LSB	1	0	0
2	1	1	1	0
3	0MSB	0	1	1



Parallel In – Serial Out Shift Register




- The shift register, which allows parallel input and produces serial output is known as Parallel In – Serial Out PISO
- This circuit consists of three D flip-flops, which are cascaded. The output of one D flip-flop is connected as the input of next D flip-flop.
- All these flip-flops are synchronous with each other since, the same clock signal is applied to each one.



- In this shift register, we can apply the **parallel inputs** to each D flip-flop by making Preset Enable to 1.
- For every positive edge triggering of clock signal, the data shifts from one stage to the next. So, we will get the **serial output** from the right most D flip-flop.



Parallel In – Serial Out Shift Register

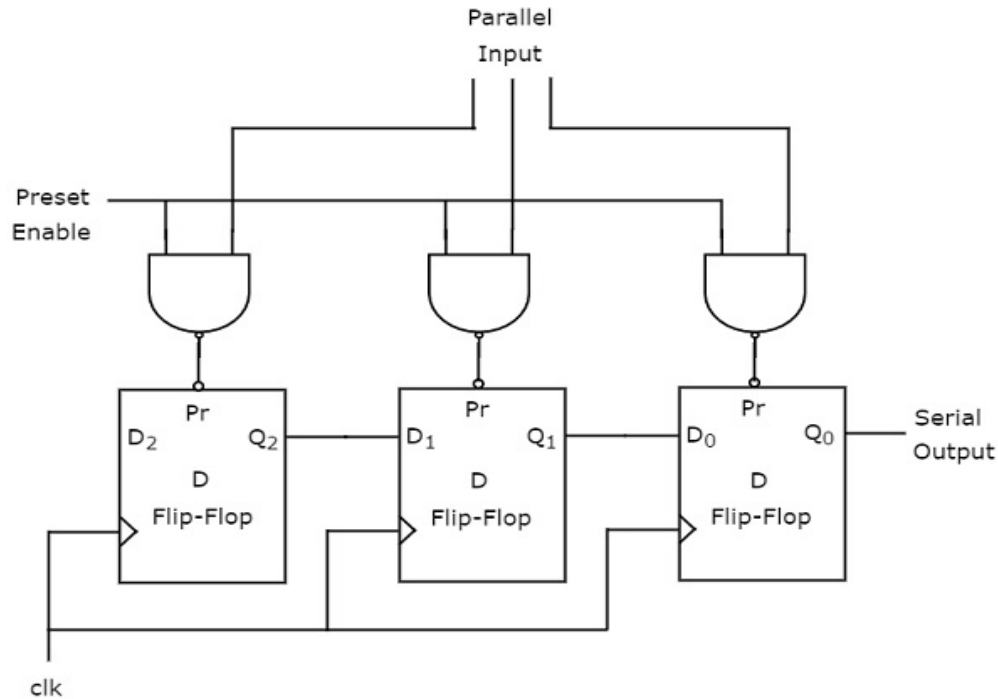

No of positive edge of Clock	Q ₂	Q ₁	Q ₀
0	0	1	1LSB
1	-	0	1
2	-	-	0LSB



Parallel In - Parallel Out Shift Register




- The shift register, which allows parallel input and produces parallel output is known as Parallel In – Parallel Out PIPO shift register.
- This circuit consists of three D flip-flops, which are cascaded. The output of one D flip-flop is connected as the input of next D flip-flop. All these flip-flops are synchronous with each other since, the same clock signal is applied to each one.



- In this shift register, we can apply the **parallel inputs** to each D flip-flop by making Preset Enable to 1. We can apply the parallel inputs through preset or clear. These two are asynchronous inputs.
- The flip-flops produce the corresponding outputs, based on the values of asynchronous inputs. In this case, the effect of outputs is independent of clock transition. So, we will get the **parallel outputs** from each D flip-flop.



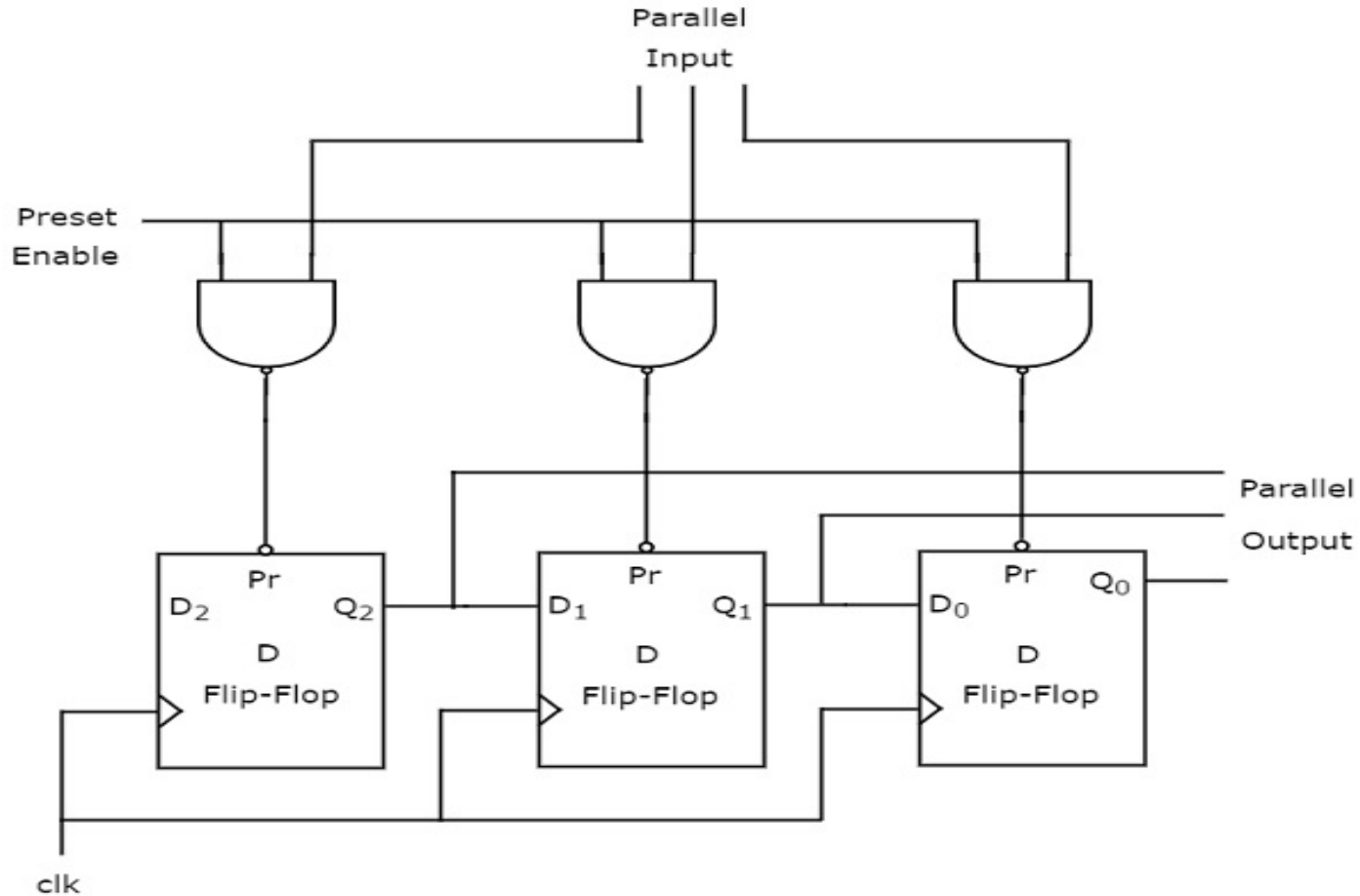Parallel In - Parallel Out Shift Register





Applications of shift Registers

- The shift registers are used for temporary data storage.
- The shift registers are also used for data transfer and data manipulation.
- The serial-in serial-out and parallel-in parallel-out shift registers are used to produce time delay to digital circuits.
- The serial-in parallel-out shift register is used to convert serial data into parallel data thus they are used in communication lines where demultiplexing of a data line into several parallel line is required.
- A Parallel in Serial out shift register is used to convert parallel data to serial data.



THANK YOU