



# **SNS COLLEGE OF TECHNOLOGY Coimbatore-35**



**An Autonomous Institution**

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF COMPUTER SCIENCE ENGINEERING**

### **19ECB231 – DIGITAL ELECTRONICS**

II YEAR/ III SEMESTER

### **UNIT 4 – DESIGN OF SEQUENTIAL CIRCUITS**

TOPIC – STATE MINIMIZATION & ASSIGNMENT



# State Reduction and Assignment

- The analysis of sequential circuits starts from a circuit diagram and culminates in a state table or diagram.
- The design of a sequential circuit starts from a set of specifications and culminates discusses certain properties of sequential circuits that may be used to **reduce the number of gates and flip-flops during the design.**



# State Reduction

- The reduction of the number of flip-flops in a sequential circuit is referred to as the **state-reduction** problem. **State-reduction** algorithms are concerned with procedures for reducing the number of states in a state table, while keeping the external input-output requirements unchanged.
- Since **m flip-flops produce  $2^m$  states**, a reduction in the number of states may result in a reduction in the number of flip-flops. **An unpredictable effect in reducing the number of flip-flops is that sometimes the equivalent circuit may require more combinational gates.**



# State Reduction



Example :

state	a	a	b	c	d	e	f	f	g	f	g	a
input	0	1	0	1	0	1	1	0	1	0	0	
output	0	0	0	0	0	1	1	0	1	0	0	

Initial point

 


Fig. 5-22 State Diagram



# State Reduction

We now proceed to reduce the number of states for this example. First, we need the **state table**; it is more convenient to apply procedures for state reduction using a table rather than a diagram. The state table of the circuit is listed in Table 5-6 and is obtained directly from the state diagram.

**Table 5-6**  
*State Table*

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1



# State Reduction

States **g** and **e** are two such states: they both go to states **a** and **f** and have outputs of **0** and **1** for  $x=0$  and  $x=1$ , respectively. Therefore, states **g** and **e** are equivalent and one of these states can be removed. The procedure of removing a state and replacing it by its equivalent is demonstrated in Table 5-7. The row with present **g** is removed and state **g** is replaced by state **e** each time it occurs in the next-state columns.

**Table 5-7**  
*Reducing the State Table*

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>e</i>	<i>f</i>	0	1



# State Reduction

Present state **f** now has next states **e** and **f** and outputs **0** and **1** for  $x=0$  and  $x=1$ , respectively. The same next states and outputs appear in the row with present state **d**. Therefore, states **f** and **d** are equivalent and state **f** can be removed and replaced by **d**. The final reduced table is shown in Table 5-8. The state diagram for the reduced table consists of only five states and is shown in Fig. 5-23.

**Table 5-8**  
*Reduced State Table*

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1





# State Reduction



state	<i>a</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>d</i>	<i>d</i>	<i>e</i>
input	0	1	0	1	0	1	1	0	1
output	0	0	0	0	0	1	1	0	1

 


Fig. 5-23 Reduced State Diagram





# State Assignment

**Table 5-9**  
*Three Possible Binary State Assignments*

State	Assignment 1 Binary	Assignment 2 Gray code	Assignment 3 One-hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000

**Table 5-10**  
*Reduced State Table with Binary Assignment 1*

Present State	Next State		Output	
	<i>x</i> = 0	<i>x</i> = 1	<i>x</i> = 0	<i>x</i> = 1
000	000	001	0	0
001	010	011	0	0
010	000	011	0	0
011	100	011	0	1
100	000	011	0	1



## 5-7 Design Procedure

The procedure for designing synchronous sequential circuits can be summarized by a list of recommended steps.

1. From the word description and specifications of the desired operation, derive a state diagram for the circuit.
2. Reduce the number of states if necessary.
3. Assign binary values to the states.
4. Obtain the binary-coded state table.
5. Choose the type of flip-flops to be used.
6. Derive the simplified flip-flop input equations and output equations.
7. Draw the logic diagram.



# Design Procedure

 


Fig. 5-24 State Diagram for Sequence Detector



# Synthesis Using D Flip-Flops

$$A(t + 1) = D_A(A, B, x) = \Sigma (3, 5, 7)$$

$$B(t + 1) = D_B(A, B, x) = \Sigma (1, 5, 7)$$

$$y(A, B, x) = \Sigma (6, 7)$$

**Table 5-11**  
*State Table for Sequence Detector*

Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1



# Synthesis Using D Flip-Flops

$$D_A = Ax + Bx$$

$$D_B = Ax + B'x$$

$$y = AB$$

 


Fig. 5-25 Maps for Sequence Detector



# Synthesis Using D Flip-Flops

 


Fig. 5-26 Logic Diagram of Sequence Detector





# Synthesis Using JK Flip-Flops

**Table 5-12**  
Flip-Flop Excitation Tables

Q(t)	Q(t + 1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

(a) JK

Ref. Table 5-1

**Table 5-13**  
State Table and JK Flip-Flop Inputs





Present State			Input	Next State		Flip-Flop Inputs			
A	B	x		A	B	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>
0	0	0	0	0	0	0	X	0	X
0	0	1	1	0	1	0	X	1	X
0	1	0	0	1	0	1	X	X	1
0	1	1	1	0	1	0	X	X	0
1	0	0	0	1	0	X	0	0	X
1	0	1	1	1	1	X	0	1	X
1	1	0	0	1	1	X	0	X	0
1	1	1	1	0	0	X	1	X	1







# Synthesis Using JK Flip-Flops

    

ice Hall, Inc.

Fig. 5-27 Maps for  $J$  and  $K$  Input Equations



# Synthesis Using JK Flip-Flops

 


Fig. 5-28 Logic Diagram for Sequential Circuit with JK Flip-Flops



# Synthesis Using T Flip-Flops



The synthesis using **T flip-flops** will be demonstrated by designing a binary counter. An n-bit binary counter consists of n flip-flops that can count in binary from 0 to  $2^n - 1$ . The state diagram of a 3-bit counter is shown in Fig. 5-29.

$Q(t)$	$Q(t + 1)$	$T$
0	0	0
0	1	1
1	0	1
1	1	0

(b)  $T$

 


Fig. 5-29 State Diagram of 3-Bit Binary Counter



# Synthesis Using T Flip-Flops



**Table 5-14**  
*State Table for 3-Bit Counter*

Present State			Next State			Flip-Flop Inputs		
$A_2$	$A_1$	$A_0$	$A_2$	$A_1$	$A_0$	$T_{A2}$	$T_{A1}$	$T_{A0}$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1





# Synthesis Using T Flip-Flops

 


Fig. 5-30 Maps for 3-Bit Binary Counter





**THANK YOU**