



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35

An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A++’ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF COMPUTER SCIENCE ENGINEERING

19ECB231 – DIGITAL ELECTRONICS


II YEAR/ III SEMESTER

UNIT 4 – DESIGN OF SEQUENTIAL CIRCUITS

TOPIC –HAZARDS




HAZARDS

 

Initially:

$$X=Y=Z=1$$

 



Static Hazard




- **Definition:**

- A static-1 hazard is the possibility of a 0 glitch when we expect the output to remain at a nice steady 1 based on a static analysis

- **Formal Definition:**

 - A static-1 hazard is a pair of input combinations that:
 - (a) differ in only one input variable and
 - (b) both give a 1 output;such that it is possible for a momentary 0 output to occur during a transition in the differing input variable.



- Even though “static” analysis predicts that the output is 1 for both input combinations $X, Y, Z = 111$ and $X, Y, Z = 110$, F goes to 0 for one unit time.




Static-0 Hazard



- A properly designed **two-level sum-of-products** (AND-OR) circuit has no static-0 hazards.
- A static-0 hazard is just the **dual** of a static-1 hazard
 - → an **OR-AND circuit** that is the dual of the example circuit would have a static-0 hazard.





• تحلیل کنید :

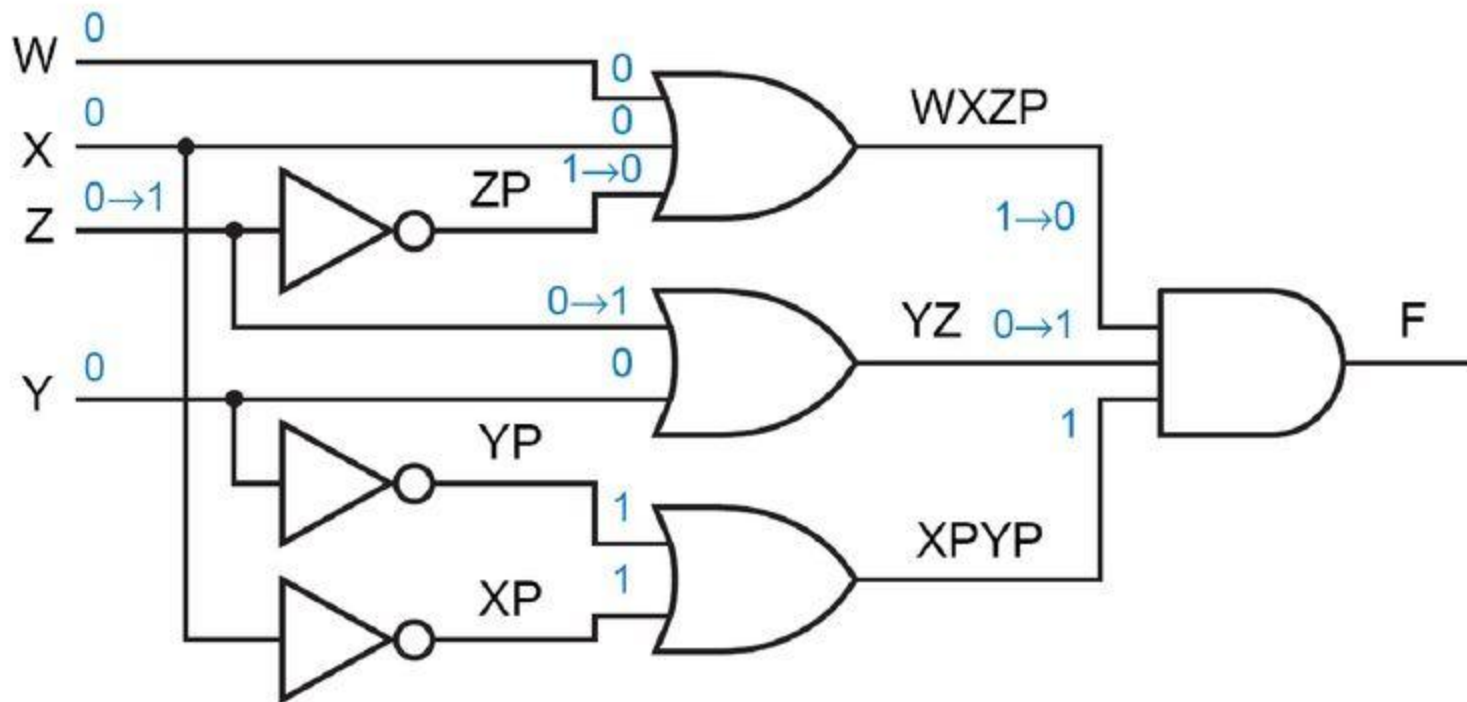




 
 
A Karnaugh map can be used to detect static hazards in a two-level SOP or POS circuit.




$$F = X \cdot Z' + Y \cdot Z$$

 

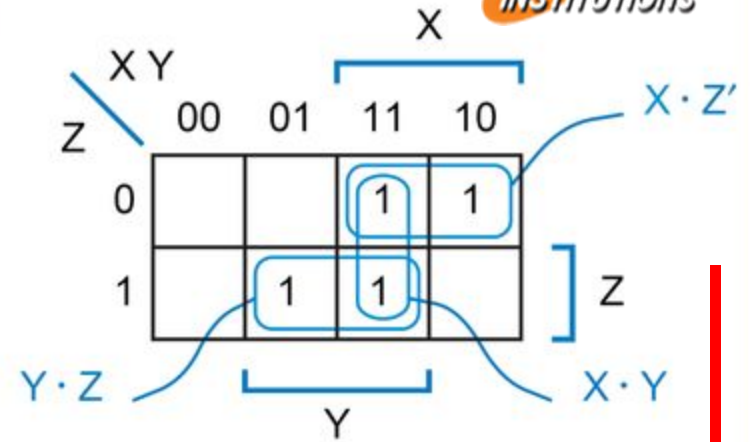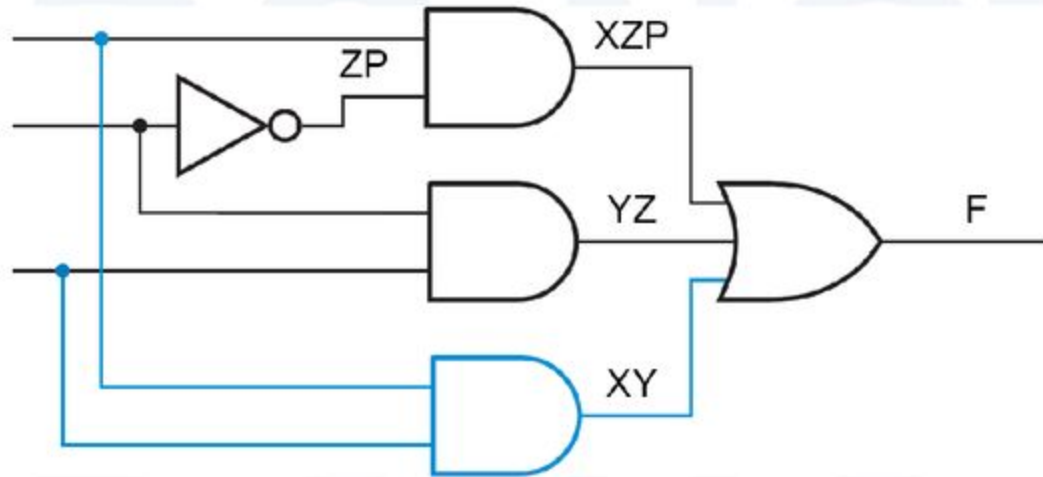
$$F = X \cdot Z' + Y \cdot Z + X \cdot Y$$


 
$$F = X \cdot Z' + Y \cdot Z + X \cdot Y$$


 
$$F = X \cdot Y' \cdot Z' + W' \cdot Z + W \cdot Y$$



$$F = X \cdot Y' \cdot Z' + W' \cdot Z + W \cdot Y + W' \cdot X \cdot Y' + Y \cdot Z + W \cdot X \cdot Z'$$




Dynamic Hazard



- **Dynamic hazard:**

 - the possibility of an output changing **more than once** as the result of a single input transition.
 - Multiple output transitions can occur if there are **multiple paths with different delays** from the changing input to the changing output.





- Techniques for finding hazards in arbitrary circuits, are rather difficult to use.
 - → when you require a hazard-free design, it's best to use a circuit structure that is easy to analyze.
- In particular, two-level AND-OR circuit has no static-0 or dynamic hazards.
- Static-1 hazards may exist in such a circuit but they can be found and eliminated using K-map.



- **Most Hazards are not hazardous:**

- A well-designed, *synchronous* digital system is structured so that hazard analysis is not needed for most of its circuits.
- In a synchronous system, all of the inputs to a combinational circuit are changed at a particular time, and the outputs are not “looked at” until they have had time to settle to a steady-state value.
- Hazard analysis and elimination are typically needed only in the design of *asynchronous sequential* circuits,
- Asynchronous circuits are not the mainstream but if you want to design them, an understanding of hazards will be absolutely essential for a reliable result.



THANK YOU