

Exp no: 1

OHM'S LAW AND RESISTANCE

AIM:

To determine the resistivity of two wire by plotting a graph for potential difference versus current.

MATERIALS REQUIRED:

Two resistance wires; A voltmeter and an ammeter of appropriate range, A battery (battery eliminator), A rheostat, A metre scale, one way key, connecting wires, A piece of sand paper, screw gauge.

THEORY:

i) Resistance per cm of the wire

$$R = \frac{V}{I} \text{ ohm}$$

$$R \text{ per cm} = \frac{R}{L} \text{ ohm/cm}$$

where R = resistance of the conductor in ohm.

V = potential difference in volt

I = current in ampere

L = length of the wire in cm.

ii) Specific resistance or resistivity of the wire


$$\rho = \frac{\pi r^2 R}{l}$$

ρ = resistivity of the material of the wire in ohm metre

r = radius of the cross-sectional area of the wire in mm.

l = length of the wire in cm.

CIRCUIT DIAGRAM

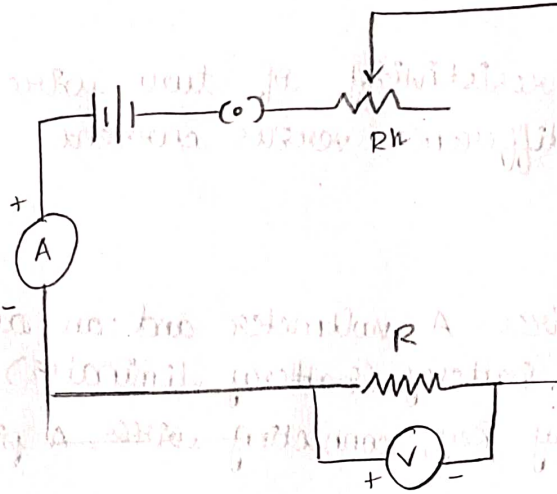

OBSERVATION:

Ammeter's Range = 0-5A

Voltmeter = 0-5V

Observation

L.C = 0.1A

L.C = 0.1V

Zero error = 0

Zero Error = 0

TABULATION:

S.NO.	Ammeter Reading	Voltmeter Reading (V)		Calculated Reading	
		Wire I	Wire II	Wire I (Ω)	Wire II (Ω)
				Average Ω	Ω

	length (m)	Radius (mm)	Area (A^2) (m^2)
Wire I			
Wire II			

$A = \pi r^2$

CALCULATION

$\rho = \frac{RA}{l}$

WIRE I =

WIRE II =

RESULT

→ The graph between V & I is a straight line.

→ Resistance of the given wire are found to be

i) By using formula (wire 1) = _____ Ωm
(wire 2) = _____ Ωm

ii) By using graph (wire 1) = _____ Ω
(wire 2) = _____ Ω

iii) Resistivity of the given wires (wire 1) = _____ Ωm
(wire 2) = _____ Ωm

PRECAUTIONS:


- i) The connections should be neat, clean and tight
- ii) Care should be taken to connect the voltmeter and ammeter in proper polarities

SOURCES OF ERROR:

- i) The instrument screws may be loose.
- ii) Thick connecting wire may not be available.

Include this under the theory.

Expected graph
(Wire I & Wire II)

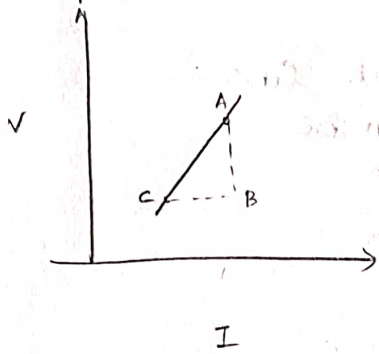

$$\text{Resistance (R)} = \frac{\Delta V}{\Delta I}$$

$$= \frac{AB}{BC} = \text{constant}$$

The graph shows a straight line passing through the origin, indicating a direct proportionality between potential difference (V) and current (I). The slope of this line represents the resistance (R) of the wire. The slope is calculated as the ratio of the change in potential difference (ΔV) to the change in current (ΔI), which is equal to the ratio of the vertical side (AB) to the horizontal side (BC) of the triangle formed by the line and the axes. This ratio is constant, confirming that the wire obeys Ohm's law.

The constant slope of the graph indicates that the resistance of the wire is constant and does not depend on the current or potential difference. This is characteristic of an ohmic conductor.

The graph is a straight line passing through the origin, which shows that the potential difference is directly proportional to the current. The slope of the line is constant, representing the resistance of the wire.

METRE BRIDGE RESISTANCE OF THE WIRE

AIM

To find the resistance of the given wire using metre bridge

MATERIALS REQUIRED

Metre bridge, Battery eliminator, jockey, Galvanometer, Resistance box, one way key, unknown resistance and connecting wire.


THEORY

The unknown resistance x is given by:

$$x = \frac{R(100-l)}{l}$$

where R - Resistance in the resistance box in ohm

l - Balancing length in cm

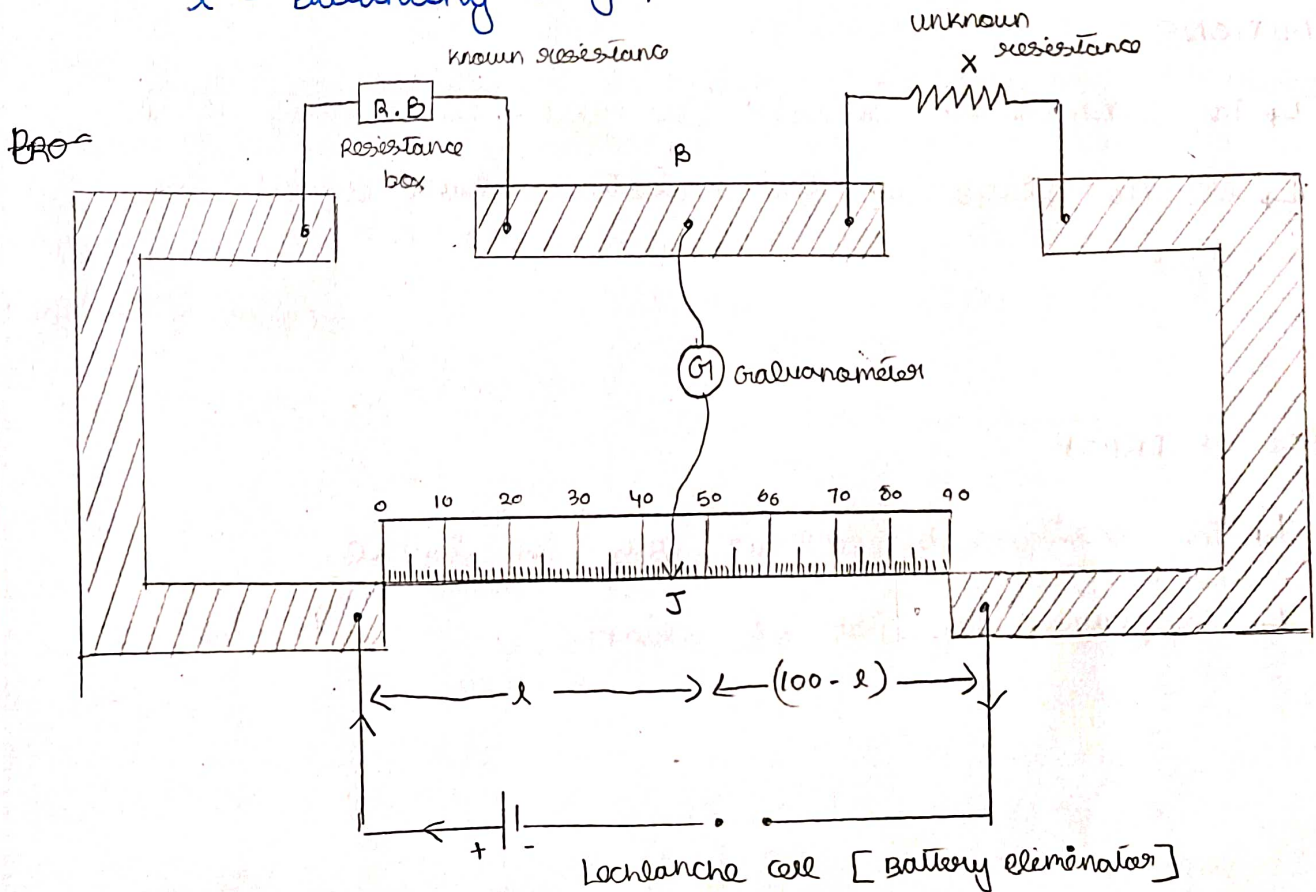

OBSERVATION

~~Least count of Meter Bridge Scale =~~

TABLATION

S.No	Resistance from the Resistance box 'R' (ohm)	Balancing length (from left) 'l' (cm)	Balancing length (100-l) (cm)	Unknown Resistance $X = R \frac{(100-l)}{l}$
1				
2				
3				
4				
5				

Mean value $x =$ _____ Ω

RESULT

The value of unknown resistance x is _____ Ω

PRECAUTIONS

- ↳ The connections should be neat, clean and tight
- ↳ All the plugs in the resistance box should be tight

SOURCE OF ERROR

- ↳ The instrument screws may be loose
- ↳ The plugs may not be clean

METRE BRIDGE - SERIES

AIM:

To verify the laws of combination (series) of resistance using a metre bridge.

APPARATUS:

A metre bridge, Battery eliminator, a galvanometer, a resistance box, a jockey, two resistance wires, a set square, sand paper and connecting wires.

THEORY:

(i) The resistance (x) of a resistance wire given by

$$x = \frac{(100-l)}{l} \times R$$


where, R is the resistance from the resistance box in the left gap and l is the length of the metre bridge wire from zero end up to balance point.

(ii) When two resistance x_1 and x_2 are connected in series, then their combined resistance,

$$R_s = x_1 + x_2$$

CIRCUIT DIAGRAM:

(i) Series combination of resistance

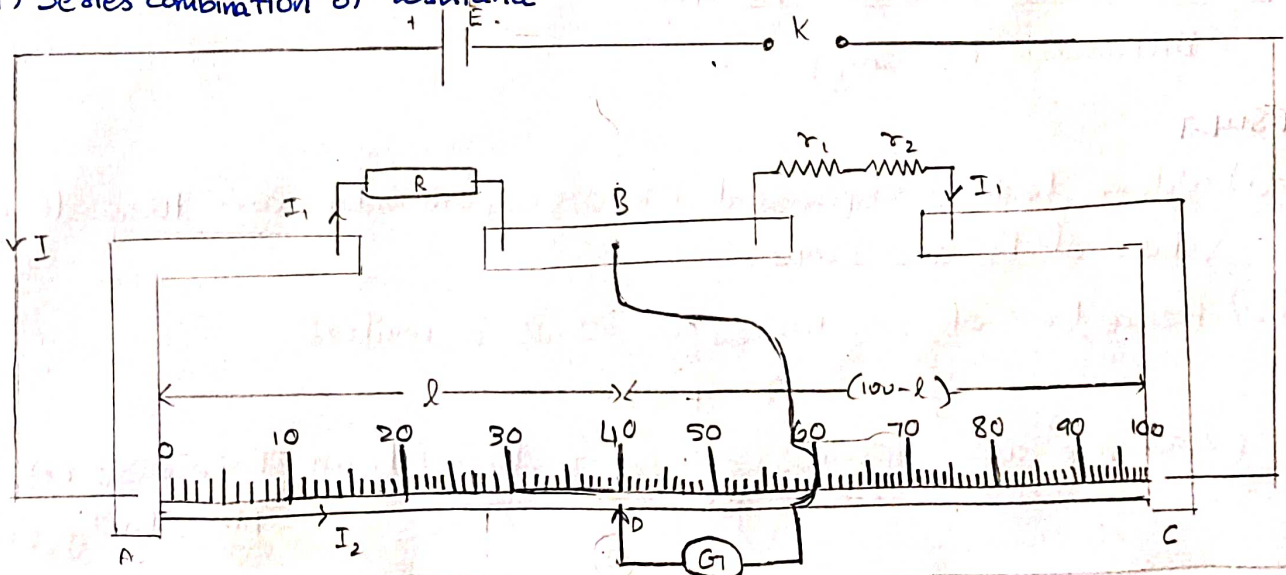

(ii) Resistance in series



OBSERVATIONS

Resistance coil	S.No	Resistance from the resistance box R (ohm)	Length AD = l (cm)	Length DC = 100 - l (cm)	Resistance $r = \frac{(100-l)}{l} \times R$	Mean Resistance (ohm)
r_1 only	1					$r_1 =$
	2					
	3					
r_2 only	1					$r_2 =$
	2					
	3					
r_1 and r_2 in series	1					$r_3 =$
	2					
	3					

CALCULATIONS

(i) Calculation for r_1 only, r_2 only, r_1 and r_2 in series

$$r = \frac{(100-l)}{l} \times R$$

(ii) Calculation for verification of laws

Experimental value of $R_s =$

Theoretical value of $R_s = r_1 + r_2$

Difference (if any) =

RESULT

(i) Within limits of experimental errors, experimental and theoretical values of R_s are same.

(ii) Hence, law of resistances in series is verified.

For precautions and sources of errors learn from Experiment (2) - Meter Bridge (wire)

EXPERIMENT-4 CONVEX LENS-FOCAL LENGTH

AIM:

To find the focal length of a convex lens by plotting graphs between u and v .

APPARATUS:

An optical bench with three uprights, a convex lens with lens holder, two optical needles, a knitting needle and a half metre scale.

THEORY:

The relation between u , v and f for a convex lens is,

$$\frac{1}{f} = \frac{1}{v} - \frac{1}{u}$$

Where, f = focal length of convex lens

u = distance of object needle from optical centre of the lens.


v = distance of the image needle from the optical centre of the lens.

Applying sign convention,

u is negative


v is positive

$$\Rightarrow f = \frac{uv}{u+v}$$

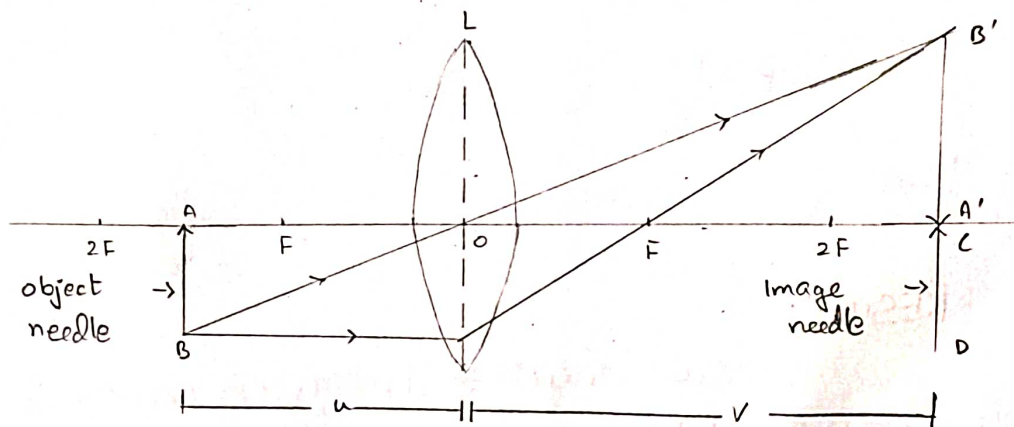

RAY DIAGRAM

Expected graph:

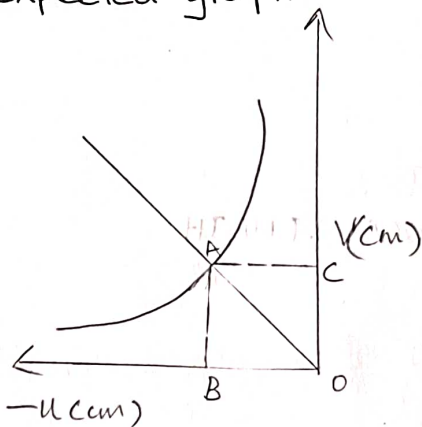

From graph

$$f = \frac{OB}{2} = \frac{OC}{2}$$

OBSERVATIONS:

Rough focal length of the given convex lens = cm

TABULATION:

S.No	Position of			Observed distance		$f = \frac{uv}{u+v}$ (cm)
	Object needle A (cm)	Lens O (cm)	Image needle	OA=u (cm)	OC=v (cm)	
1.						
2.						

mean $f =$ cm

CALCULATIONS:

focal length (f) = cm

from graph,

$$f = \frac{OB}{2} = \quad \text{cm}$$

$$f = \frac{OC}{2} = \quad \text{cm}$$

Mean $f =$ cm

RESULT:

Focal length of the given convex lens:

i) focal length $f = \frac{uv}{u+v} =$ cm

ii) u-v graph = cm

PRECAUTIONS:

1. Tips of the object and image needles should lie at the same height as the centre of the lens.
2. Index correction for u and v should be applied.

SOURCES OF ERROR:

1. The uprights may not be the vertical
2. Parallax removal may not be perfect

AIM:


To find the focal length of a convex mirror, using convex lens.

MATERIALS REQUIRED:

Metre scale, convex mirror, convex lens, candle, screen, lens holder, mirror holder.

THEORY:

Focal length of the convex mirror, $f = R/2$ where R is the radius of curvature of the mirror.

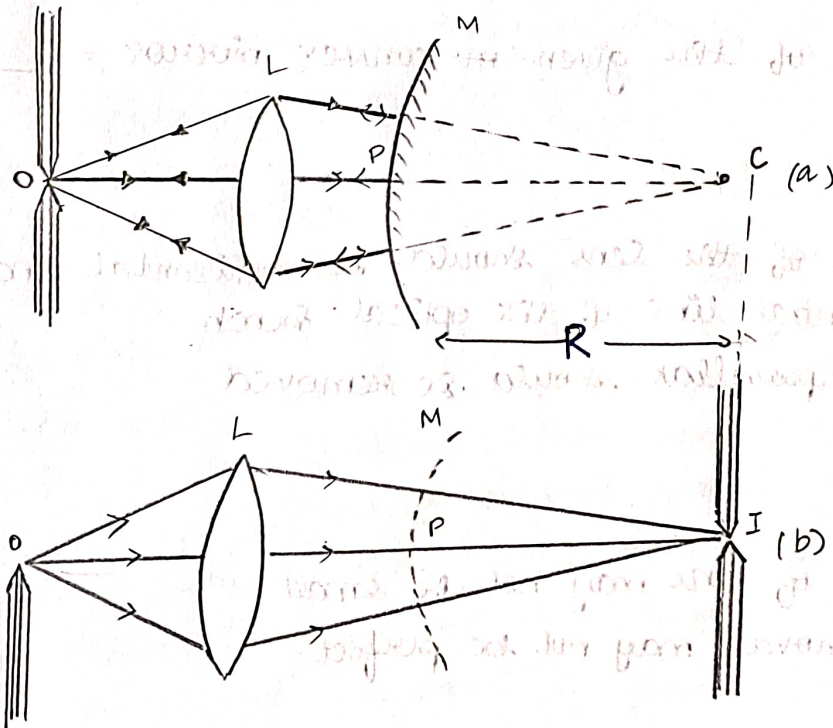RAY DIAGRAM

Focal length of convex mirror.

OBSERVATION

Rough focal length of convex lens = ~~25~~ _____ cm.

Table for focal length of convex mirror.

S.NO.	Position of		Radius of Curvature R (cm)	Focal length $f = \frac{R}{2}$ (cm)
	Convex mirror P (cm)	Image needle I (cm)		

Mean focal length (f) = _____ cm.

RESULT :

The focal length of the given ~~at~~ convex mirror = _____ cm.

PRECAUTIONS

- i) Principal axis of the lens should be horizontal and parallel to the central line of the optical bench.
- ii) Tip-to-tip parallax should be removed.

SOURCES OF ERROR :

- i) Focal length of lens may not be small.
- ii) Parallax removal may not be perfect.

AIM:

To draw the V-I characteristic curve of a p-n junction in forward bias and reverse bias.

APPARATUS:

A p-n junction diode, 2 voltmeter of appropriate range, 2 ammeters of appropriate range, one-way key, connecting wires and piece of sand paper.

THEORY:


FORWARD-BIAS CHARACTERISTICS.

When the p-section of the diode is connected to positive terminal of a battery and n-section is connected to negative terminal of the battery then junction is said to be forward biased. With increase in bias voltage, the forward current increases slowly in the beginning and then rapidly. The variation of forward current with respect to forward voltage is noted.


REVERSE-BIAS CHARACTERISTICS.

When the p-section of the diode is connected to negative terminal of high voltage battery and n-section of the diode is connected to positive terminal of the same battery, then junction is said to be reverse biased. When reverse bias voltage increases, initially there is a very small reverse current flow, which remains almost constant with bias. But when reverse bias voltage increases to a significantly sufficient high value, the reverse current suddenly increase to a large value. The variation of reverse current with respect to reverse voltage is noted.

DIAGRAM :

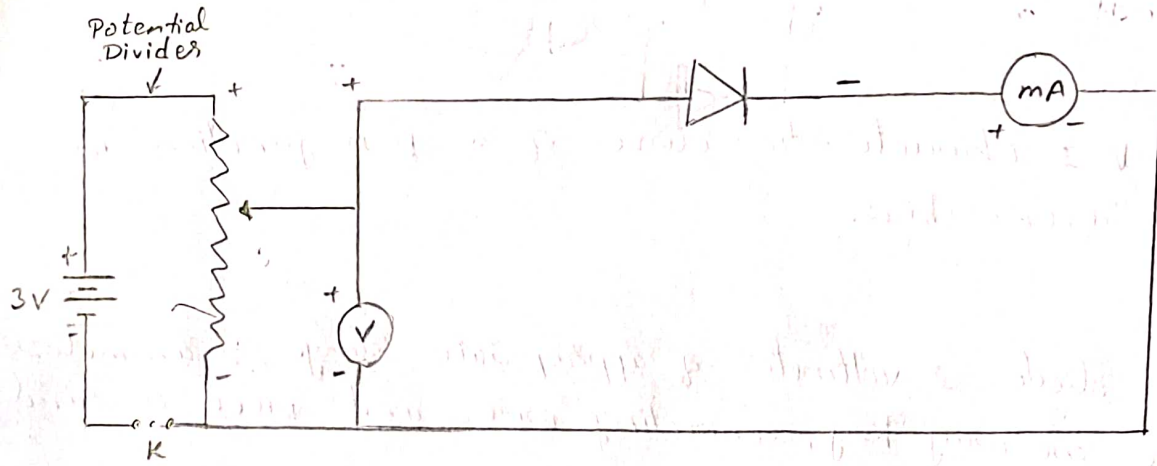


p-n junction diode - forward biased

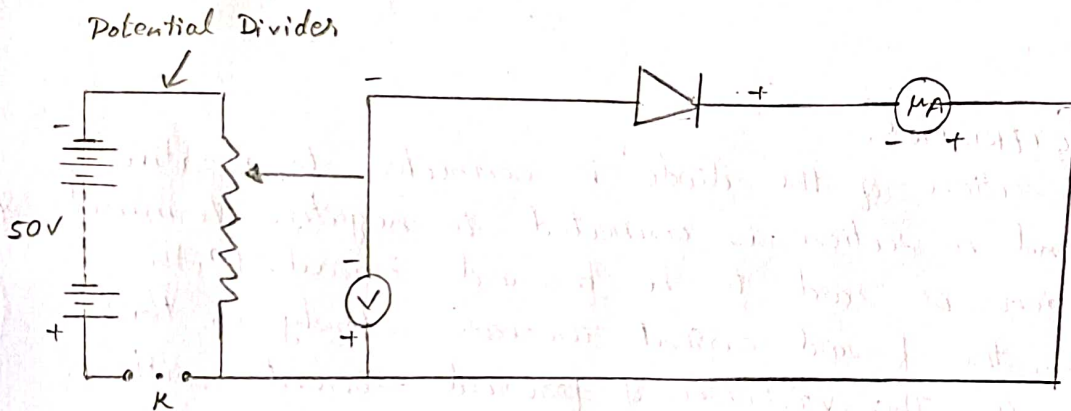


p-n junction diode - reverse biased

EXPECTED GRAPH :

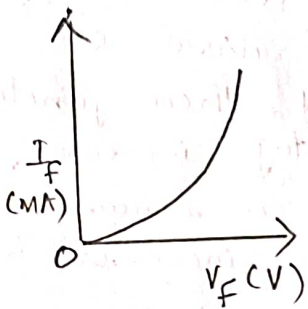

Forward bias

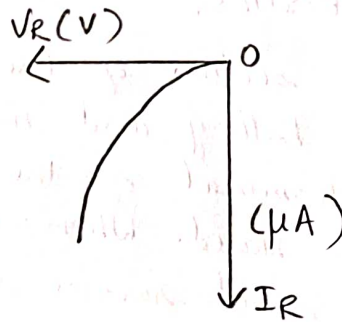

Reverse bias

OBSERVATIONS :

FOR FORWARD-BIAS

- Range of voltmeter
- least count of voltmeter
- Range of milli-ammeter
- least count of milli-ammeter

- = V
- = V
- = mA
- = mA

Serial No. of obs.	Forward - bias Voltage V_F (V)	Forward current I_F (mA)
1.		
2.		
3.		

R REVERSE - BIAS

- Range of voltmeter = V
- least count of voltmeter = V
- Range of micro-ammeter = ~~mA~~
- least count of micro-ammeter = ~~mA~~

Serial No. of obs.	Reverse - bias Voltage V_R (V)	Reverse current I_R (mA)
1		
2		
3.		

CALCULATIONS:

Junction resistance for forward - bias.

$$r = \frac{\Delta V_F}{\Delta I_F} = \dots \text{ ohms.}$$

Junction resistance for reverse - bias.

$$r = \frac{\Delta V_R}{\Delta I_R} = \dots \text{ ohms.}$$

RESULT:

- Junction resistance for forward - bias =
- Junction resistance for reverse - bias =

PRECAUTIONS:

- All connections should be neat, clean, and tight.
- Forward - bias voltage beyond breakdown should not be applied.

SOURCE OF ERROR:

- Error may occur due to carelessness of the student.
The terminals of battery may not be connected properly