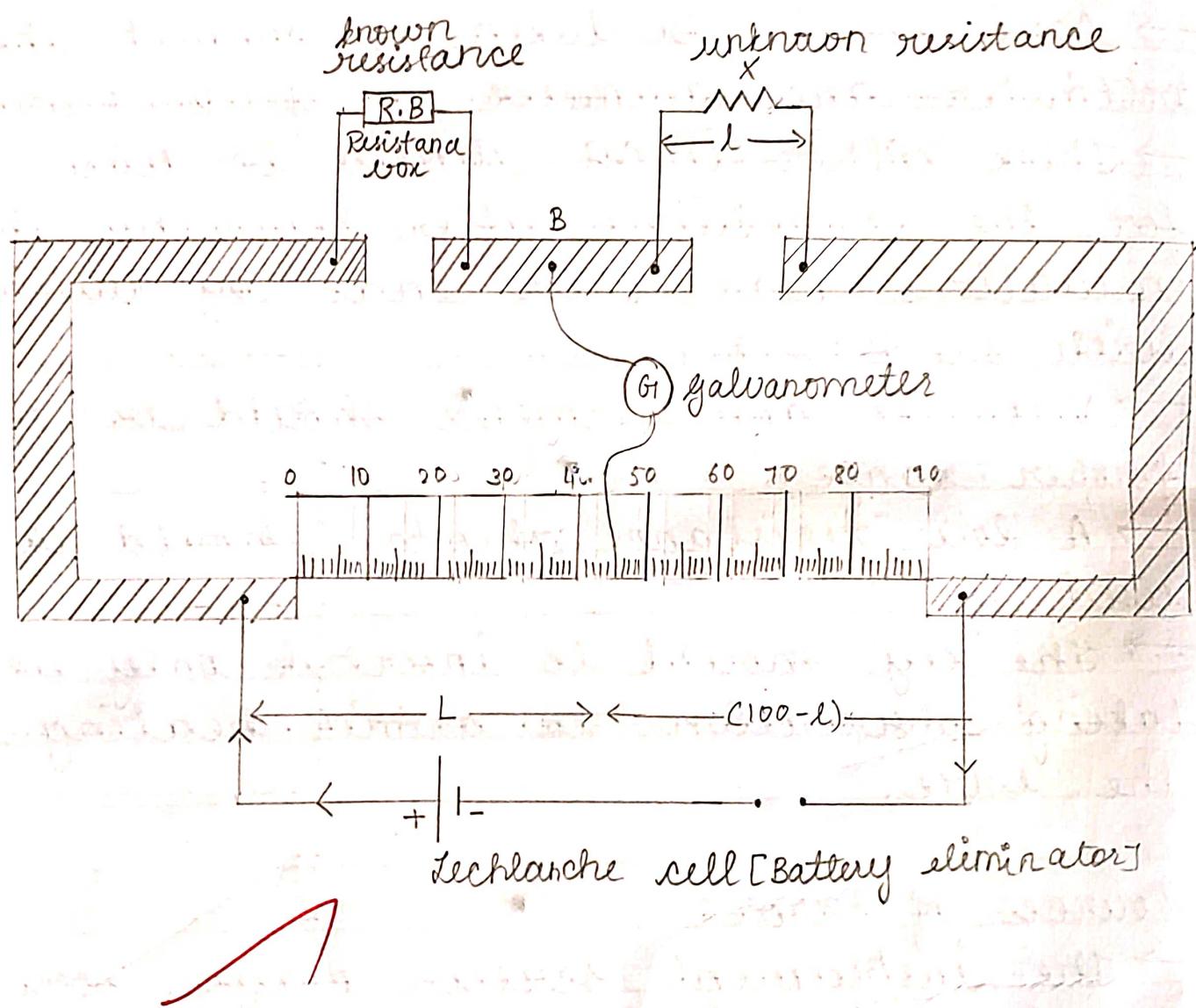


Circuit Diagram



METRE BRIDGE - RESISTANCE OF THE WIRE

Aim:

To find resistance of the given wire using metre bridge

Materials Required:

Metre bridge, Battery eliminator, jockey, galvanometer, Resistance Box, One way key, unknown resistance and connecting wire.

Formula:

The unknown resistance X is given by:

$$X = \frac{R(100-l)}{l}$$

where R - Resistance in the resistance box
in ohm

~~✓~~ l - Balancing length in cm

Procedure:

→ Make the connections as shown in the circuit

Observation :

Least count of Metre Bridge Scale = 0.1 cm

Tabulation :

S.N.O	Resistance from the Resistance Box 'R' ohm	Balancing length (from left) 'l' cm	Balancing length (100-l) cm	unknown resistance $X = \frac{R(100-l)}{(l)}$
1	1	91.5	8.5	0.92
2	2	88	12	0.27
3	3	98	2	0.061
4	4	97	3	0.123
5	5	90.5	9.5	0.52
6	6	96	4	0.25




- Include some known value of resistance in the left gap
- Move the jockey from end A to B and observe the point of zero deflection in the galvanometer
- Let the balancing length be 'l'. Repeat the experiment by including different values of resistances
- Find the balancing length in each case. Tabulate the readings and calculate the resistance of the wire.

Result:

The value of unknown resistance X is
 0.3573Ω

Precautions:

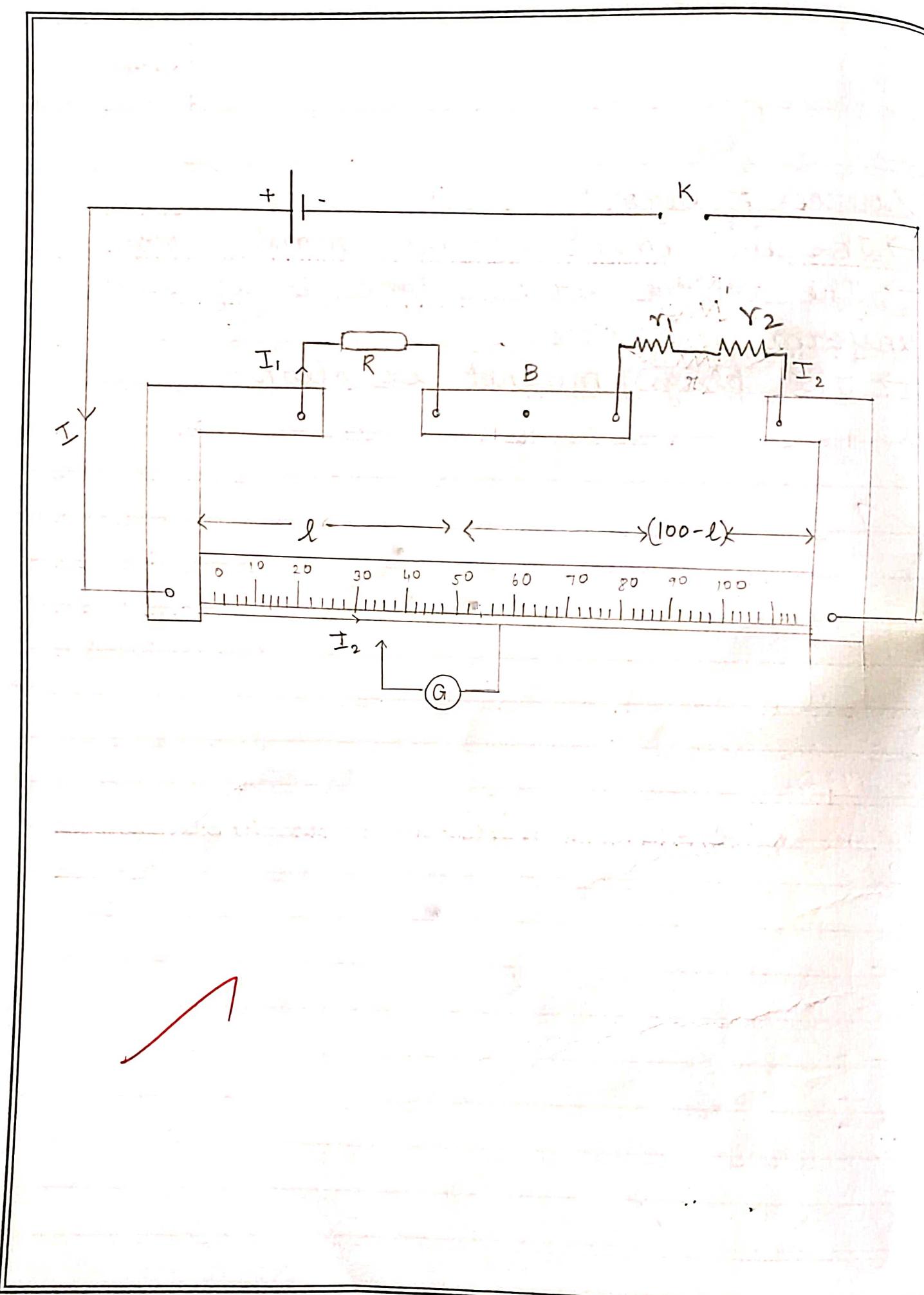- The connections should be neat, clean and tight
- Move the jockey gently over the bridge wire and do not rub it
- Null point should be brought between 40 cm and 60 cm to avoid end resistances



METRE BRIDGE - RESISTORS IN PARALLEL.

Aim :

To verify the law of combination (series) of resistances using a metre bridge.

Apparatus :

Metre bridge, Lechlanche cell, galvanometer, Resistance box, jockey, key, unknown resistance and connecting wires.

Formula :

1) The unknown resistance x is given by :

$$x = \frac{lr}{100-l} \quad (1) \qquad x = \frac{(100-l)r}{l}$$

where,

~~R~~ is known resistance in ohms

l is the balancing length in cm

2) Effective resistance of resistors in parallel

$$R_p = \frac{R_1 R_2}{R_1 + R_2} \qquad R_s = R_1 + R_2$$

where,

Observation:

Least count of the metre bridge scale = 0.1 cm

Tabulation:

S.No	Resistance coil	Resistance from resistivity box (Ω)	length AD = l	length DC = (100 - l)	Mean resistance $r = \frac{(100-l)}{l} R (Ω)$
1	r_1 only 2	2	68.4	31.6	0.92
2	5	5	71.3	28.7	2.01
3	r_2 only 2	2	78.3	21.7	0.55
4	5 $r_1, 8 r_2$	5	82.1	18	1.097
	2	2	86.3	14.6	0.325
	5	5	87.7	12.3	0.701

R_1 and R_2 are the resistance of the resistors in ^{Series} ~~parallel~~ (in ohms)

Procedure :

- Mark the two resistance coils as R_1 and R_2 .
- To find R_1 and R_2 ,
 - (i) Make the connections as shown in the circuit
 - (ii) Include some known value of resistance
 - (iii) Move the jockey from end A to B and observe the point of zero deflection in the galvanometer
 - (iv) Let the balancing length be 'l'
 - (v) Repeat the experiment by including different values of resistance
 - (vi) Find the balancing length in each case
 - (vii) Tabulate the readings and calculate the resistance R ,
 - (viii) Repeat the same for R_2 ,
 - Connect two coils R_1 and R_2 in ^{series} ~~parallel~~ as shown in circuit in the right gap of metre bridge and find the resistance of the combination
 - Record your observation

Result:

experimental value of $R_s = 0.513\Omega$

calculated value of $R_s = 0.525\Omega$

law of combination of resistances ~~parallel~~^{series} is verified

Precautions:

- The connections should be neat, clean and tight
- Move the jockey gently over the bridge wire and donot rub it.

Sources of error:

- The instruments screws may be loose
- The plugs may not be clean