

SNS COLLEGE OF ALLIED HEALTH SCIENCE
Affiliated to The Tamil Nadu Dr. M.G.R Medical University, Chennai



DEPARTMENT OF RADIOGRAPHY AND IMAGING TECHNOLOGY

**COURSE NAME : GENERAL PHYSICS RELATED TO RADIATION PHYSICS
AND DIAGNOSTIC PHYSICS**

UNIT : 5 Physics of Diagnostic Radiology

TOPICS : FULL VALVE PULSATING CIRCUIT

FACULTY NAME : Ms. DHANALAKSHMI M

INTRODUCTION (Define)


❖ Full Wave Rectifier: Producing Pulsating DC

Voltage


❖ Converts AC to pulsating DC using both half-cycles

❖ Key topic in power electronics and AC-DC

conversion

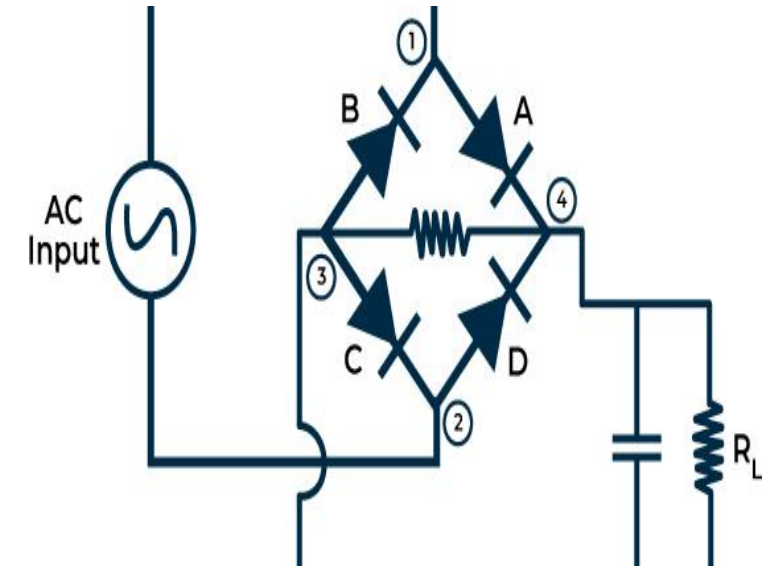


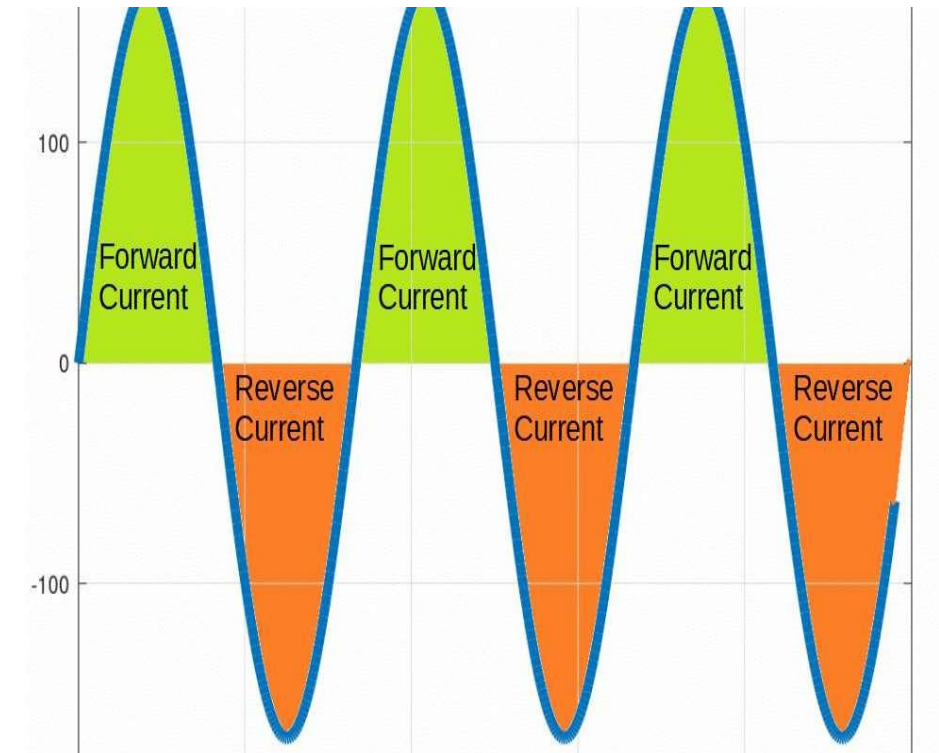- ❖ Converts entire AC waveform into pulsating DC
- ❖ Utilizes **both positive and negative** half-cycles of input
- ❖ Output is unidirectional but pulsating (not steady DC)




Types of Full Wave Rectifiers

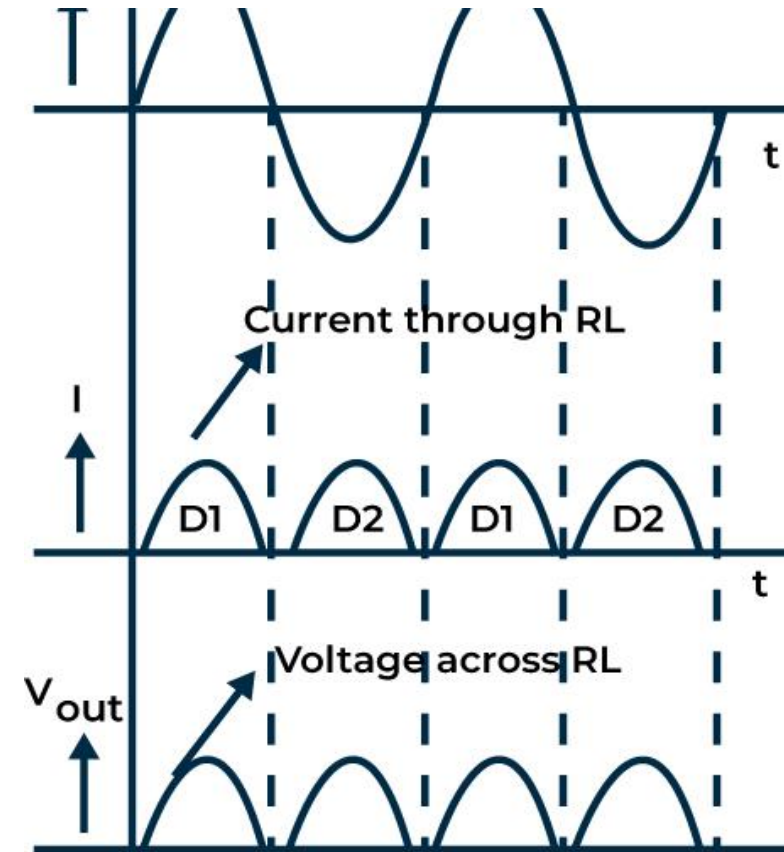- ❖ Center-Tapped (uses 2 diodes + center-tapped transformer)
- ❖ Bridge Rectifier (uses 4 diodes, no center tap needed)
- ❖ Bridge type is more common and cost-effective




Center-Tapped Circuit Operation

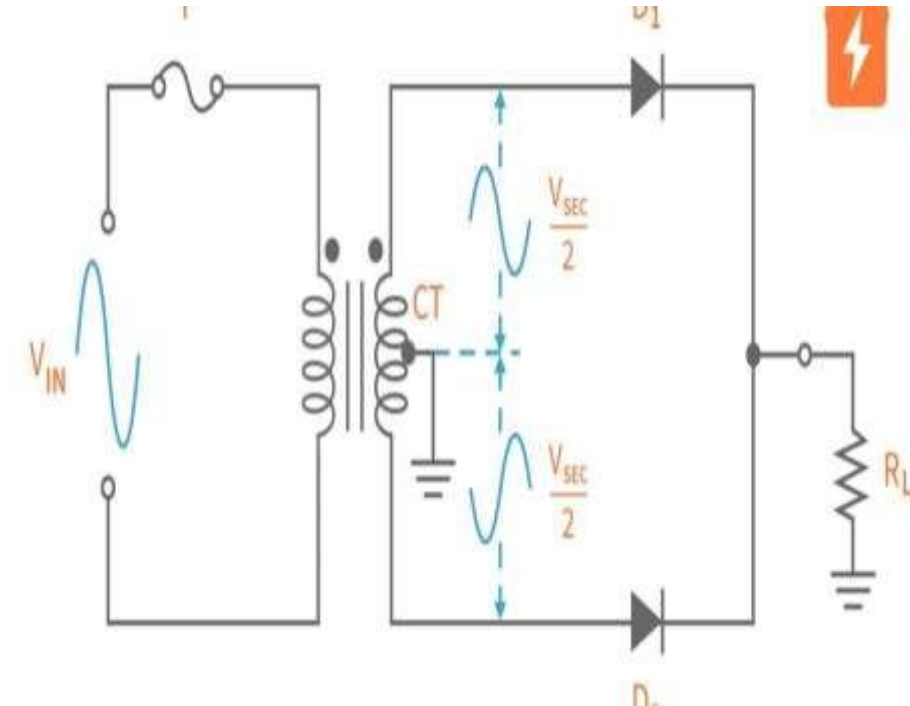- ❖ Positive half-cycle: One diode conducts, other reverse-biased
- ❖ Negative half-cycle: Roles reverse, current flows same direction
- ❖ Requires center-tapped transformer for splitting phases




Bridge Rectifier Circuit

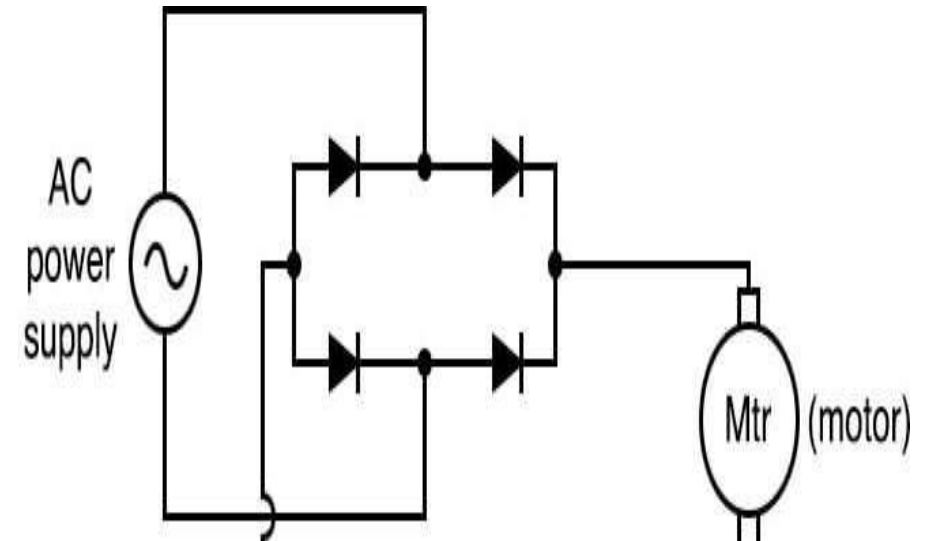- ❖ Input: Sinusoidal AC (alternates +ve and -ve)
- ❖ Output: Pulsating DC (full humps, twice the frequency)
- ❖ No negative portion in output




Advantages Over Half-Wave

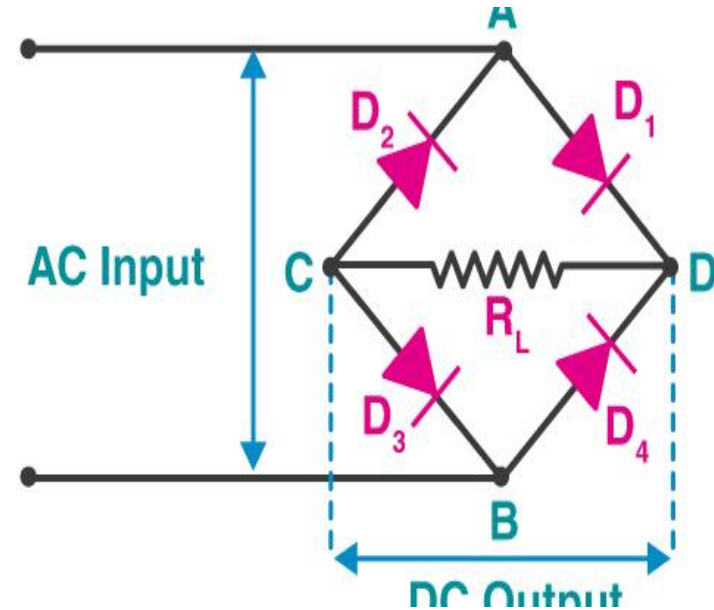- ❖ Higher average DC output ($0.637 \times V_m$ vs $0.318 \times V_m$)
- ❖ Lower ripple, better efficiency (81.2% vs 40.6%)
- ❖ Smoother output, higher power delivery




Core Concept & Types

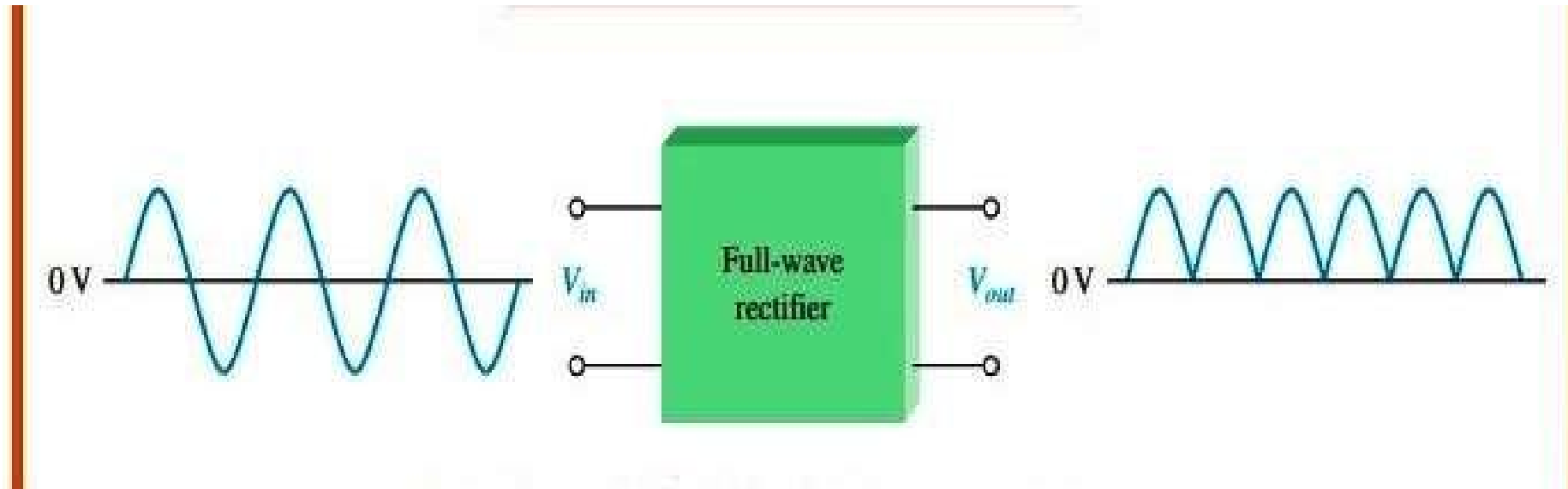- Converts complete AC sine wave into pulsating DC
- Uses **BOTH positive and negative half-cycles** (100% utilization)
- Two main types: Center-Tapped & Bridge Rectifier
- Bridge type needs NO center-tapped transformer
- Output frequency = $2 \times$ input frequency (**e.g., 50 Hz \rightarrow 100 Hz ripple**)
- Foundation of every mobile charger and SMPS.




Bridge Rectifier – Circuit & Working

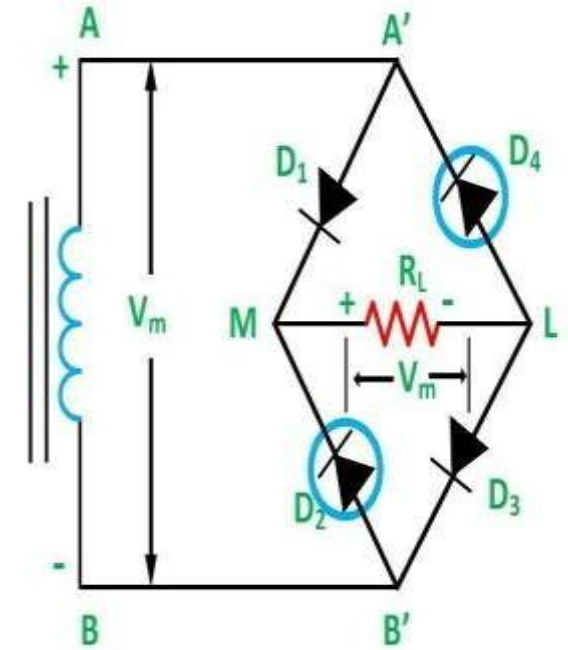
- ❖ 4 diodes arranged in **diamond/bridge shape**
- ❖ Positive half-cycle → D1 & D2 conduct, D3 & D4 reverse biased
- ❖ Negative half-cycle → D3 & D4 conduct, D1 & D2 reverse biased
- ❖ Load current always flows in **SAME direction**
- ❖ Peak output voltage = $V_m - 1.4 \text{ V}$ (two diode drops)
- ❖ Most popular because it's cheap, reliable & efficient



Waveforms & Performance Advantages

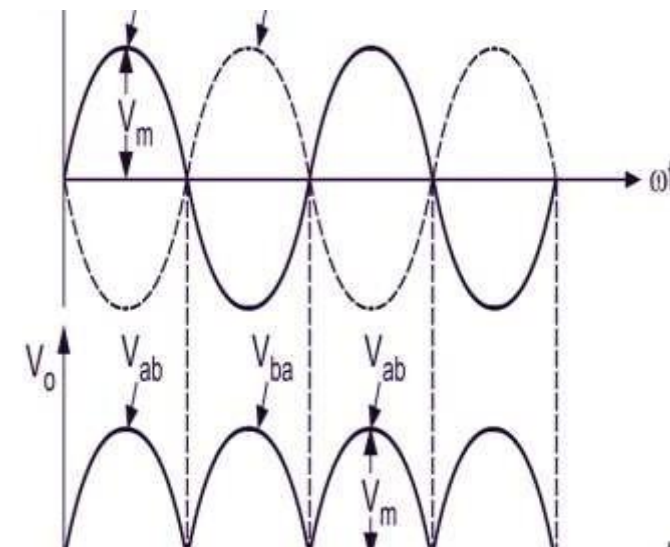- **input:** Pure sine wave ($\pm V_m$)
- **Output:** Full-wave rectified (0 to V_m , 100 Hz humps)
- **Average DC value** = $0.637 \times V_m$ (twice that of half-wave)
- **Ripple factor** = 48% (much better than 121% of half-wave)
- **Efficiency** = 81.2% (double the half-wave 40.6%)



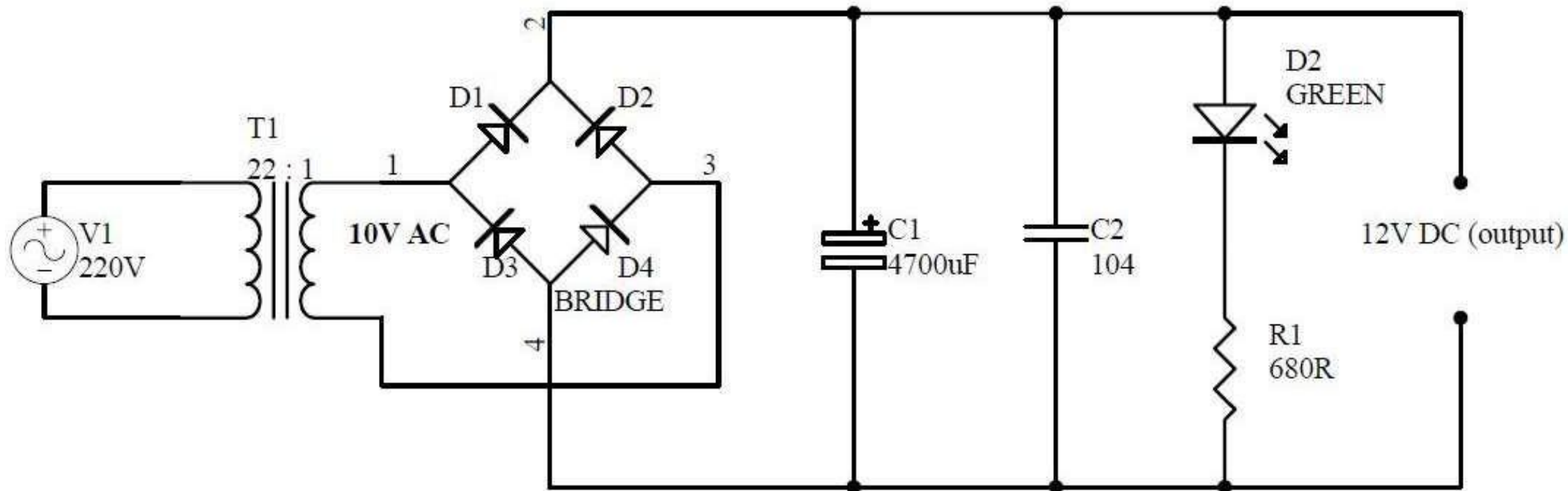

SUMMARY



References

- https://www.electronics-tutorials.ws/diode/diode_6.html
- <https://www.electrical4u.com/full-wave-rectifiers/>
- <https://testbook.com/physics/full-wave-rectifier>