
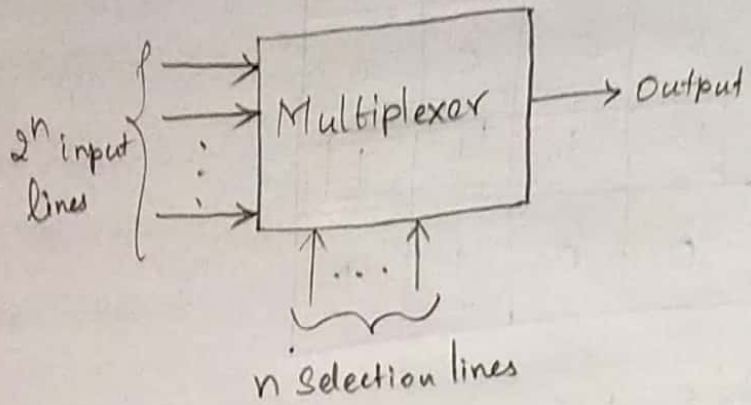


# MULTIPLEXER.

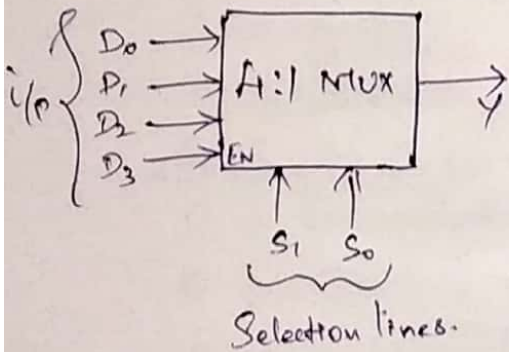


## A:1 Multiplexer.

A A:1 mux has A inputs  $D_3, D_2, D_1, D_0$ , two selection lines ( $S_1, S_0$ ) and single output line 'Y'



$S_1$	$S_0$	Y
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

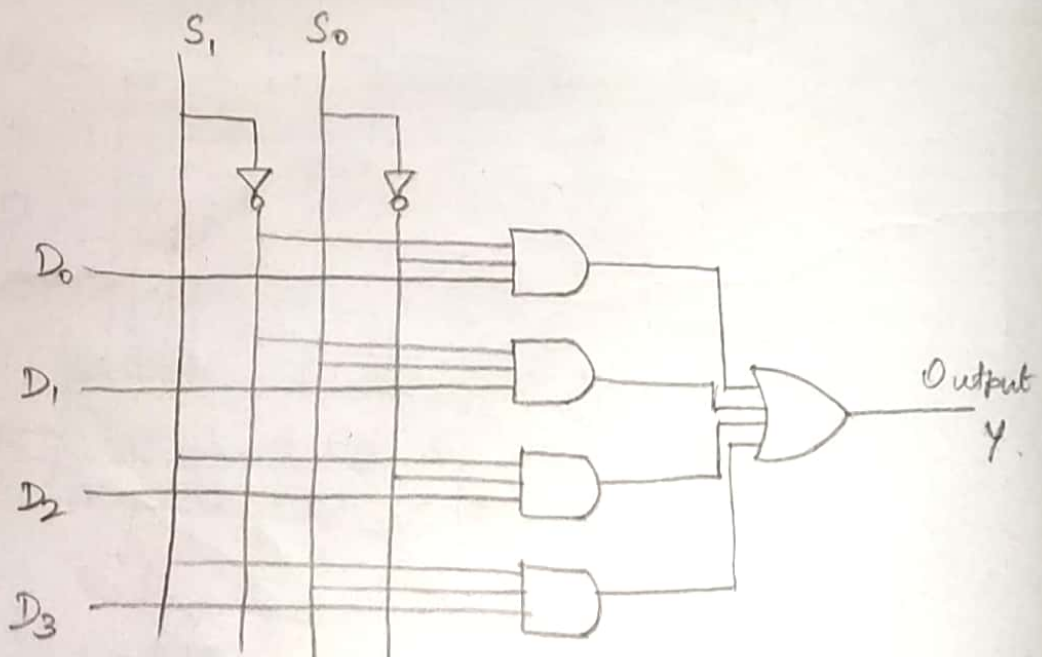

## 8:1 MULTIPLEXER.

Select lines			Output
$S_2$	$S_1$	$S_0$	$Y$
0	0	0	$D_0$
0	0	1	$D_1$
0	1	0	$D_2$
0	1	1	$D_3$
1	0	0	$D_4$
1	0	1	$D_5$
1	1	0	$D_6$
1	1	1	$D_7$

$$Y = \bar{S}_2 \bar{S}_1 \bar{S}_0 D_0 + \bar{S}_2 \bar{S}_1 S_0 D_1 + S_2 \bar{S}_1 \bar{S}_0 D_2 + S_2 \bar{S}_1 S_0 D_3 \\ + \bar{S}_2 S_1 \bar{S}_0 D_4 + \bar{S}_2 S_1 S_0 D_5 + \bar{S}_2 \bar{S}_1 S_0 D_6 + \bar{S}_2 S_1 S_0 D_7$$


# PROBLEM:

1) Implement the following Boolean function using Multiplexer.

$$F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15)$$

Solu:

	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
$\bar{A}$	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	1	1	0	$\bar{A}$	$\bar{A}$	0	0	A

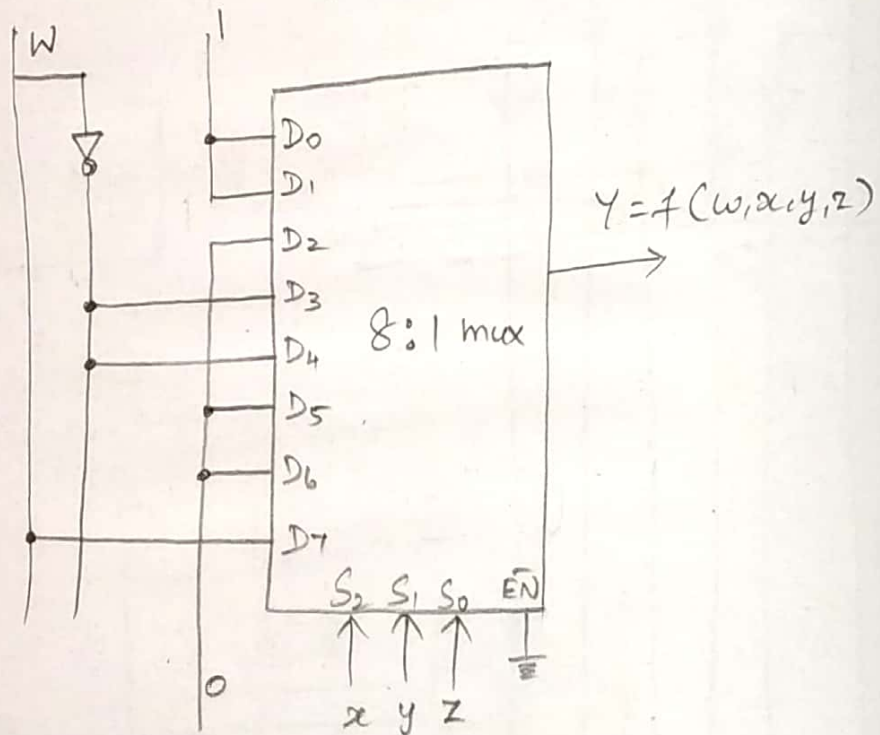

29) Implement the following Boolean function using  
 4:1 mux.

$$F(w, x, y, z) = \sum_m (0, 1, 2, 4, 6, 9, 12, 14)$$

Solu:

	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
$\bar{w}$	0	1	2	3	4	5	6	7
w	8	9	10	11	12	13	14	15
	$\bar{w}$	1	$\bar{w}$	0	1	0	1	0

