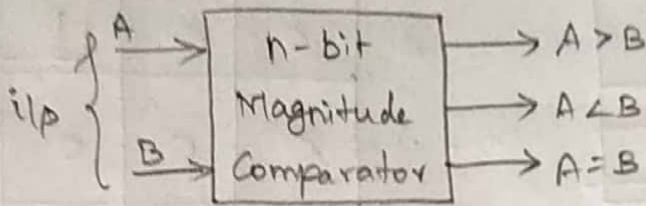


# MAGNITUDE COMPARATOR.

## 2-BIT MAGNITUDE COMPARATOR.



Inputs				Outputs		
A <sub>1</sub>	A <sub>0</sub>	B <sub>1</sub>	B <sub>0</sub>	A > B	A < B	A = B
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	0	1	0	0	1
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	0	1	1	0	1	0
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	0	1

$A > B$

	$B_1 B_0$	$00$	$01$	$11$	$10$
$A_1 A_0$	$00$	0	0	0	0
	$01$	1	0	0	0
	$11$	1	1	0	1
	$10$	1	1	0	0

$$A > B = A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_0$$

$A < B$

	$B_1 B_0$	$00$	$01$	$11$	$10$
$A_1 A_0$	$00$	0	1	1	1
	$01$	0	0	1	1
	$11$	0	0	0	0
	$10$	0	0	1	0

$$A < B = \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_1 B_0$$

$A = B$

	$B_1 B_0$	$00$	$01$	$11$	$10$
$A_1 A_0$	$00$	1	0	0	0
	$01$	0	1	0	0
	$11$	0	0	1	0
	$10$	0	0	0	1

$$\begin{aligned} (A=B) &= \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 \bar{A}_0 B_1 B_0 + A_1 A_0 B_1 B_0 \\ &\quad + A_1 \bar{A}_0 B_1 \bar{B}_0 \\ &= \bar{A}_1 \bar{B}_1 (\bar{A}_0 \bar{B}_0 + A_0 B_0) + A_1 B_1 (\bar{A}_0 B_0 + \bar{A}_0 \bar{B}_0) \\ &= \bar{A}_1 \bar{B}_1 (A_0 \odot B_0) + A_1 B_1 (A_0 \odot B_0) \\ &= (A_0 \odot B_0) (\bar{A}_1 \bar{B}_1 + A_1 B_1) \\ &= (A_0 \odot B_0) (A_1 \odot B_1) \end{aligned}$$

Logic Diagram.